 


VERILOG 6:

DECODER DESIGN EXAMPLES

Decoder

- A decoder with i inputs and fully-populated outputs has 2^i outputs
- It is generally better to work with both the input and output as buses rather than individual signals
- Output is “one-hot”
 - One and only one output is high at a time
- Common uses:
 - Selection of a word within a memory
 - Selection of one module connected to a bus when many modules are connected (e.g., tri-state drivers)



3:8 Decoder

Example 1: Individual wires

- Example 1: A very manual approach à la EEC 180A methods
- Recall that a block with 8 outputs is really 8 distinct designs

```
// in[2:0] may be a wire, reg, or input
wire [7:0] out1;

// Individual wires
assign out1[0] = ~in[2] & ~in[1] & ~in[0];
assign out1[1] = ~in[2] & ~in[1] & in[0];
assign out1[2] = ~in[2] & in[1] & ~in[0];
assign out1[3] = ~in[2] & in[1] & in[0];
assign out1[4] = in[2] & ~in[1] & ~in[0];
assign out1[5] = in[2] & ~in[1] & in[0];
assign out1[6] = in[2] & in[1] & ~in[0];
assign out1[7] = in[2] & in[1] & in[0];
```

3:8 Decoder

Example 2a: case Statement

- Example 2a: Straightforward case statement
- In this and all following examples, *out* is an 8-bit bus

```
// in[2:0] may be a wire, reg, or input
reg [7:0] out2;

// Example 1: case statement
always @(in) begin
    case(in)
        3'b000: begin    out2=8'b00000001;    end
        3'b001: begin    out2=8'b00000010;    end
        3'b010: begin    out2=8'b00000100;    end
        3'b011: begin    out2=8'b00001000;    end
        3'b100: begin    out2=8'b00010000;    end
        3'b101: begin    out2=8'b00100000;    end
        3'b110: begin    out2=8'b01000000;    end
        3'b111: begin    out2=8'b10000000;    end
    endcase
end
```

3:8 Decoder

Example 2b: case Statement

- Example 2b: Straightforward case statement with three independent inputs rather than one 3-bit bus

```
// inputs a, b, c may be a wire, reg, or input
reg [7:0] out2;

// Example 1: case statement
always @(a or b or c) begin
    case({a,b,c})
        3'b000: begin    out2=8'b00000001;    end
        3'b001: begin    out2=8'b00000010;    end
        3'b010: begin    out2=8'b00000100;    end
        3'b011: begin    out2=8'b00001000;    end
        3'b100: begin    out2=8'b00010000;    end
        3'b101: begin    out2=8'b00100000;    end
        3'b110: begin    out2=8'b01000000;    end
        3'b111: begin    out2=8'b10000000;    end
    endcase
end
```

Decoder Test Environment

- These are independent blocks inside the test module

```
//----- Main test loop
// This block is executed once at the
// beginning of the simulation.
initial begin
    $write("Simulation beginning\n");
    #100;
    in = 3'b000; #100;
    in = 3'b001; #100;
    in = 3'b010; #100;
    in = 3'b011; #100;
    in = 3'b100; #100;
    in = 3'b101; #100;
    in = 3'b110; #100;
    in = 3'b111; #100;

    $stop;          // ends simulation
end
```

```
//----- Print statements
always @(in) begin
    #10; // gives a tiny delay after "in" changes
    $write("in = %b, out1 = %b\n", in, out1);
end
```

```
reg    [2:0] in;
reg    [7:0] out1;

// example decoder hardware
always @(in) begin
    case(in)
        3'b000: begin out1=8'b00000001; end
        ...
    endcase
end
```

```
Simulation beginning
in = 000, out1 = 00000001
in = 001, out1 = 00000010
in = 010, out1 = 00000100
in = 011, out1 = 00001000
in = 100, out1 = 00010000
in = 101, out1 = 00100000
in = 110, out1 = 01000000
in = 111, out1 = 10000000
```

3:8 Decoder

Example 3: Shift Left Operator

- Example 3: Treat the 8 outputs as a single reg bus

```
// in[2:0] may be a wire, reg, or input
reg [7:0] out3;

// Example 3: reg with <<
always @(in) begin
    out3 = 8'b0000_0001 << in;
end
```

3:8 Decoder

Example 4: Shift Left Operator

- Example 4: Treat the 8 outputs as a single wire bus

```
// in[2:0] may be a wire, reg, or input
wire [7:0] out4;

// Example 4: wire with <<
assign out4 = 8'b0000_0001 << in;
```


3:8 Decoder, Partially-Defined Output Cases; Example 5


- Example 5: Only 4 of the input combinations are defined: 000, 001, 100, 110
- Choose invalid inputs to have “x” output (trivial change to set outputs to zero instead)
- Could also implement by:
 - 1) setting default at beginning of always block
 - 2) setting default then using "if" statements
 - 3) many other options

```
reg [7:0] out5;

// Example 5: partially-defined outputs
always @(in) begin
    case(in)
        3'b000: begin    out5=8'b00000001;    end
        3'b001: begin    out5=8'b00000010;    end
        //
        //
        3'b100: begin    out5=8'b00010000;    end
        //
        3'b110: begin    out5=8'b01000000;    end
        //
        default:begin    out5=8'bxxxxxxxx;    end
    endcase
end
```

Decoder With Additional *invalid* Output Signal

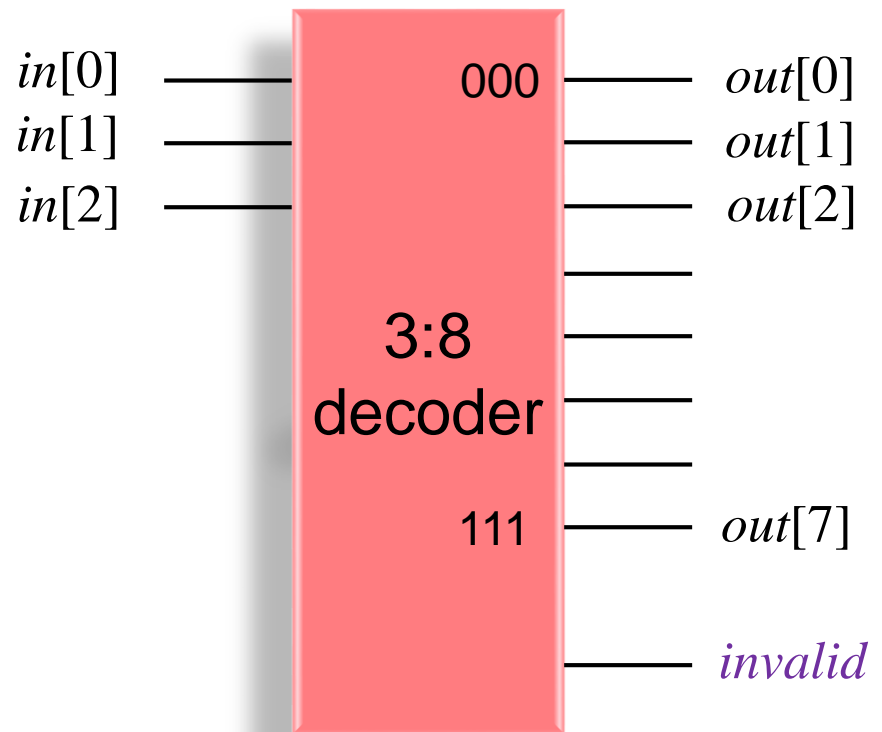- The next example is for a 3:8 decoder that has the same valid input combinations: 000, 001, 100, 110
- But in this example when the input does not have a valid value:
 - The eight main outputs must be all zeros
 - A new *invalid* output signal is set high



3:8 Decoder, *invalid* Output Example 6


- Example 6: Same as previous example except:
 - Undefined cases have zero output
 - *invalid* signal set when input equals a value for which the outputs are undefined

```
reg [7:0] out6;

// Example 6: invalid output signal
always @(in) begin
    invalid = 1'b0;
    case(in)
        3'b000: begin    out6=8'b00000001;    end
        3'b001: begin    out6=8'b00000010;    end
        //
        //
        3'b100: begin    out6=8'b00010000;    end
        //
        3'b110: begin    out6=8'b01000000;    end
        //
        default: begin
            out6      = 8'b0000_0000;
            invalid = 1'b1;
        end
    endcase
end
```

Decoder With Enabled Output

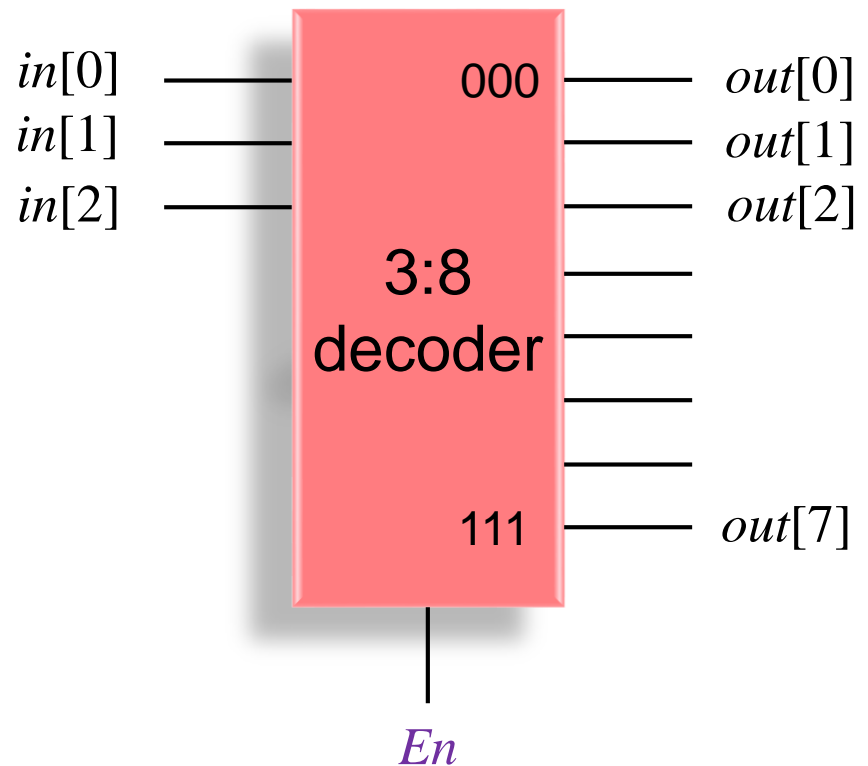- Decoders frequently have an *Enable* input which controls the overall state of the outputs
 - When input *En* is high, it functions as a normal decoder
 - When input *En* is low, all outputs are low



3:8 Decoder, Enabled Output Example 7

- Example 7: Enabled output:
 - When input En is high, it functions as a normal decoder
 - When input En is low, all outputs are low
- Many implementations are possible

```
reg [7:0] out7;  
  
// Example 7: Enabled output version 1  
always @(in) begin  
    // enabled, function like a normal encoder  
    if (En == 1'b1) begin  
        case(in)  
            3'b000: begin out7=8'b00000001; end  
            3'b001: begin out7=8'b00000010; end  
            3'b010: begin out7=8'b00000100; end  
            3'b011: begin out7=8'b00001000; end  
            3'b100: begin out7=8'b00010000; end  
            3'b101: begin out7=8'b00100000; end  
            3'b110: begin out7=8'b01000000; end  
            3'b111: begin out7=8'b10000000; end  
        endcase  
    end  
  
    // not enabled, set all outputs to zero  
    else begin  
        out7=8'b00000000;  
    end  
end  
end
```

3:8 Decoder, Enabled Output Example 8

- Example 8: Enabled output:
 - When input En is high, it functions as a normal decoder
 - When input En is low, all outputs are low
- Many implementations are possible

```
reg [7:0] out8;


// Example 8: Enabled output version 2
always @(in) begin
    // default. Initialize output as if not enabled.
    out8=8'b00000000;

    // if enabled, function like a normal encoder
    if (En == 1'b1) begin
        case(in)
            3'b000: begin out8=8'b00000001; end
            3'b001: begin out8=8'b00000010; end
            3'b010: begin out8=8'b00000100; end
            3'b011: begin out8=8'b00001000; end
            3'b100: begin out8=8'b00010000; end
            3'b101: begin out8=8'b00100000; end
            3'b110: begin out8=8'b01000000; end
            3'b111: begin out8=8'b10000000; end
        endcase
    end
end
end
```

Decoder “Manually” Designed


For Example: Memory Array Design

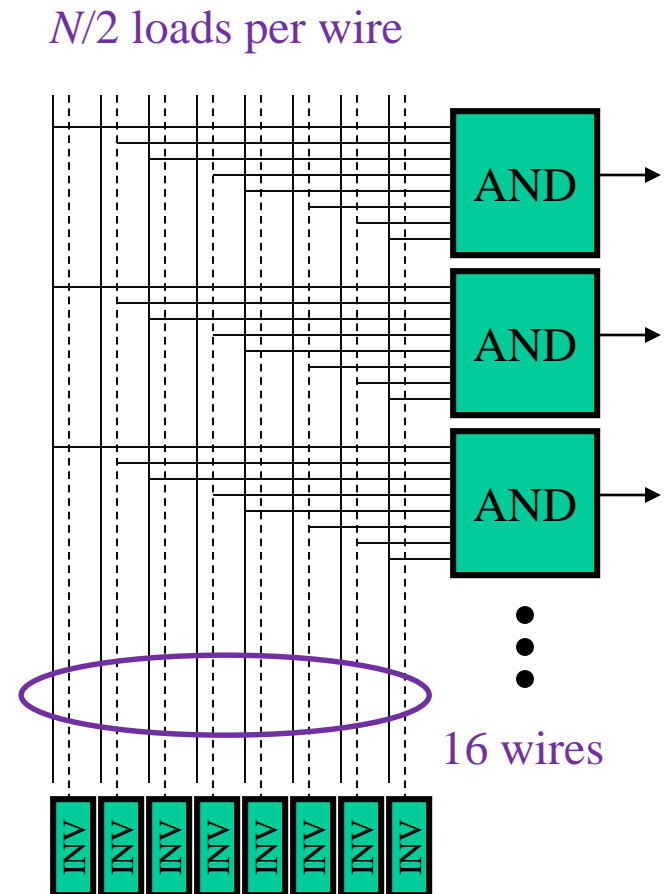- Example: 256-output (8 input bits)
 - Straightforward approach
 - Route 8 input wires plus inverted versions (16 wires) along array
 - Each word uses an 8-input AND gate
 - Each long wire has $N/2=128$ gate loads




Decoder Design

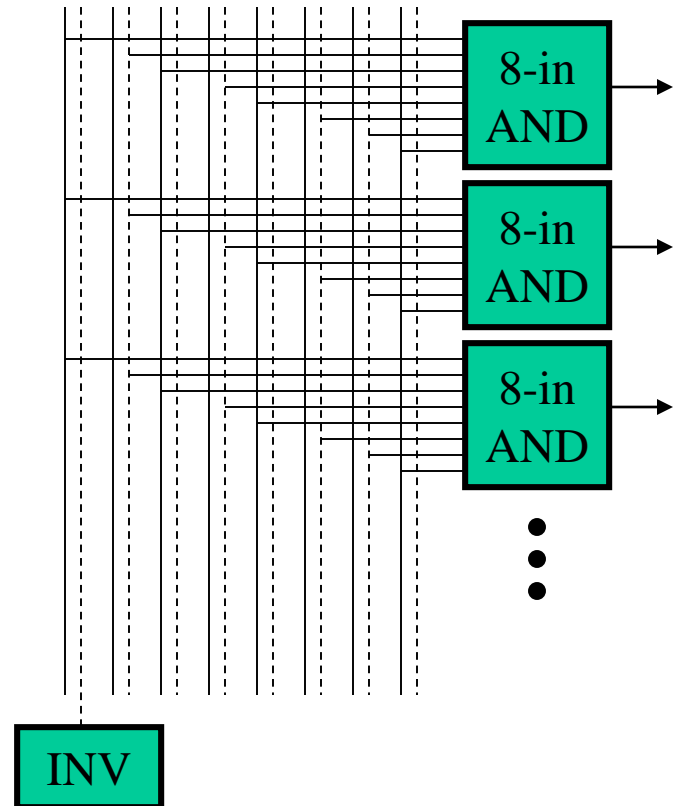- Critical path
 - INV + 8-input AND
 - Neglect assertion level because we'll have to add a number of inverters (buffers) anyway
 - Building an 8-input AND:
 - AND-AND (inefficient)
 - NAND-NOR (better)
 - Total critical path
 - INV + 4-input NAND + 2-input NOR, or
 - INV + 3-input NAND + 3-input NOR




Decoder Design Using Predecoding

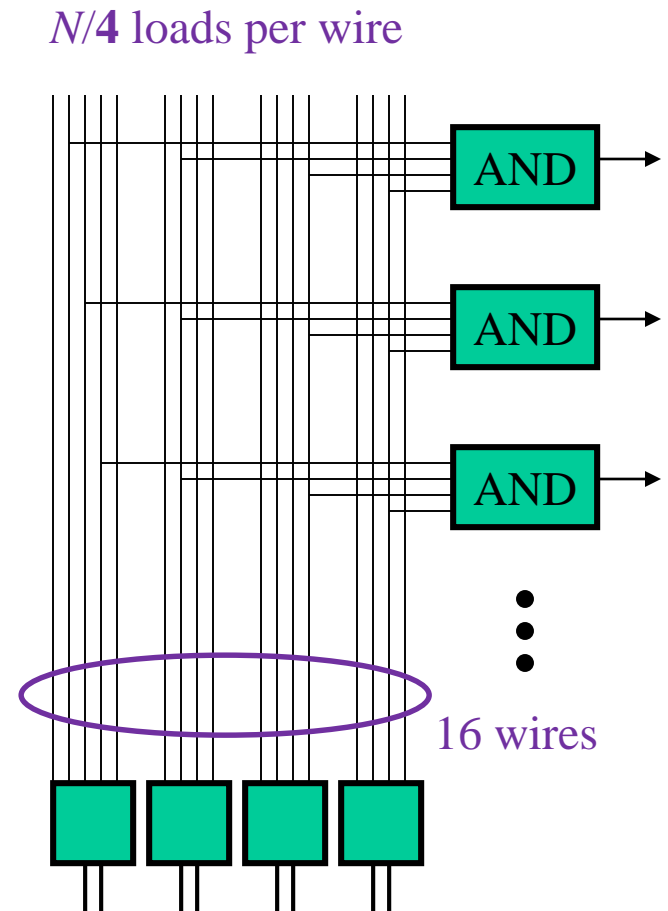- Example: 256-output (8 input bits) with predecode
 - Ex: take groups of 2 input bits
 - Four possibilities; activate one of four wires (use 2 INVs, 4 ANDs)
 - Wires along array: $2^2 * (8/2) = 4$ groups of 4 = 16 (same as non-predecoded)
 - Each output uses a 4-input AND gate (much faster)
 - Each long wire has $N/4=64$ gate loads (half of other approach!)
 - Predecoding works best with large decoders
 - May have less toggling, be faster



Decoder Design Using Predecoding

 - Critical path
 - Predecoder + 4-input AND
 - Neglect assertion level because we'll have to add a number of inverters (buffers) anyway
 - INV + 2-input AND + 4-input AND
 - May be able to use NANDs instead of ANDs



Decoder Design Using Predecoding

- Example: predecode groups of 3 address bits
 - Predecoding groups: $3 + 3 + 2$ for the same 8:256 decoder
 - Each 3-input predecode group has $2^3 = 8$ output wires
 - Each 3-input predecoded wire has $N/8$ loads
 - Total of $8 + 8 + 4 = 20$ predecoded wires
- Example: predecode groups of 4 address bits
 - Predecoding groups: $4 + 4$ for the same 8:256 decoder
 - Each predecode group has $2^4 = 16$ output wires
 - Each predecoded wire has $N/16$ loads
 - Total of $16 + 16 = 32$ predecoded wires