

April 8, 2021

Concurrency

Single-bit

wire reset;
reg start;

Multiple-bit

$[(\#bits - 1) : 0]$

wire [7:0] phase;
reg [31:0] a;
reg [7:0] b;
b = a [15:8];


↑
wire or reg
=

1101 = 9
8421
 $2^3 \ 2^2 \ 2^1 \ 2^0$
a[3:0]

```

module module abc (in1, in2, out);
    input in1;
    input in2;
    output out;

    //
    //
endmodule
    
```

 


x abc instance1 (x, y, z);


```

abc instance2 (           // use this
  .in1 (x),
  .in2 (y),
  .out (z) );

```

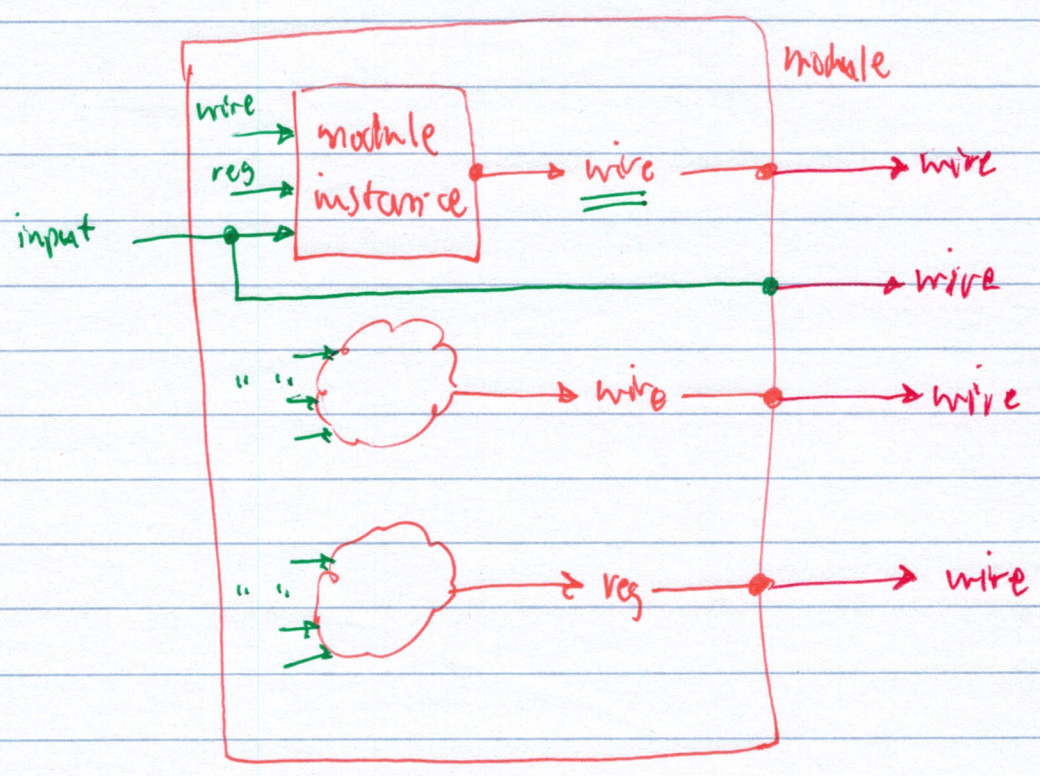


2) Wire, Assign

 

```
wire out;
```

```
assign out = a & b;
```

 


```
wire [4:0] sum;
```

```
assign sum = {c[3], c} + {d[3], d}; // sign extension
```

 3) reg, always

- more general
- if/then/else, case, for
- statements execute in order to specify a circuit
- always @ (sensitivity list) begin
statements
end

statements executed when a signal in sensitivity list changes



- v. 2001

```
always @(*) begin // incl. all inputs in sens. list
```

a
b → out

reg out;

always @ (a or b) begin
out = a & b;
end


initial begin
=====
end

executes once at beginning of simulation
* 1) Test bench
2) contents of a ROM


always begin
=====
end

executes repeatedly
needs delay inside

Ex: clock generator

 

Ex- 2: 1 mux

 

```

1) reg out
   always @ (a or b or s) begin
     if (s == 1'b0) begin
       out = a;
     end
     else begin
       out = b;
     end
   end
end


```

```

case (expr)
  value1: 'statement'
  value2: statement
  ==
  default: statement (optional)
end case


```

state = xx




 


case z
" ? " wildcard

case x - don't use

 

ab	out
00	1
01	1
10	1
11	0

   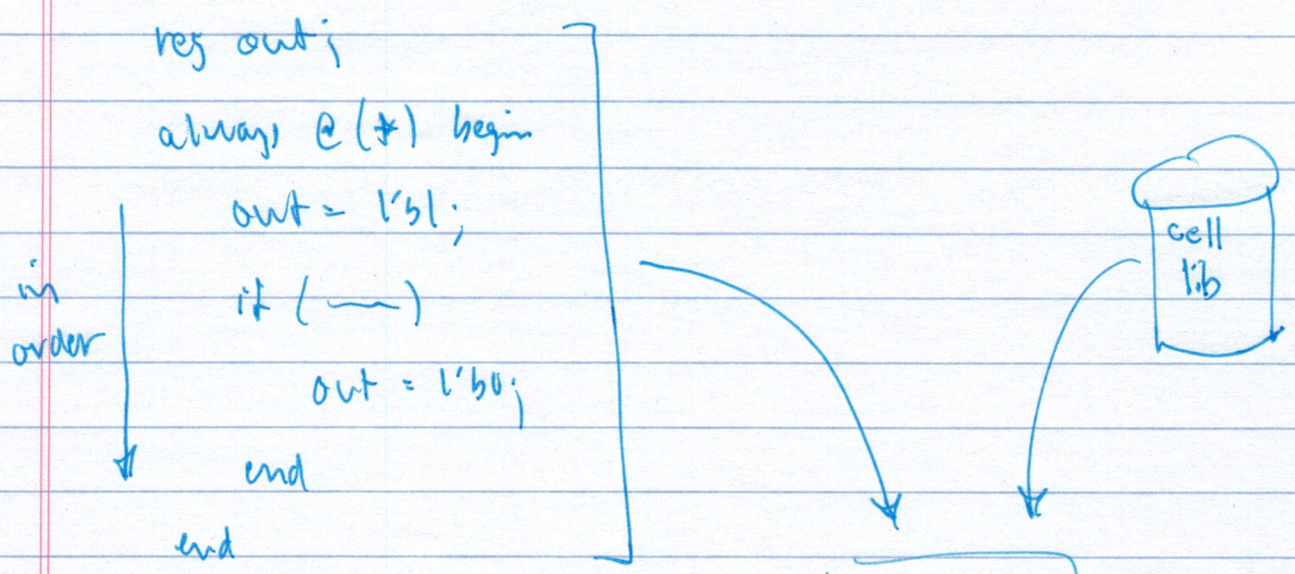

$d = \{c, v, x, b[A:z], y\}$