
 


April 22, 2021



1) Single-Bit Memories

 

2) Array

Non-blocking assignment

" <="

  

reg b, c;

always @ (posedge clk) begin


b <= a;

c <= b;

end

9 Rules for memories in LBO

 1) Use only FFs, not trans, latches or clockless latches



2) For comb. logic always blocks, always use blocking assignment "="

// OR

always @(*) begin

out = a | b;

end

a b $\Rightarrow$ out


3) For FF, always use non-blocking "<="

4) For LBO: Add #1 for clk-to-Q delay

always @ (posedge clk) begin

a <= #1 b;

Q <= #1 D;

 

5) Guideline

Do not include logic in a FF declaration

always @ (posedge clk) begin

a <= #1 out;

x <= #1 y;

~~if (reset == 1'b1) state == 5'h12) begin~~

~~end~~

end

6) Suggestion

// Block 1

// Comb. Logic

// FF


// Block 2

// ..


// ..

;

 1) a) Only a clock may connect to a FF clock input



 b) Clock may not connect to any node other than a FF clock input



c) There are a few exceptions - not in 180