



Clocks

May 4, 2021

Clocks pace the flow of data inside digital processors

Variations
"PVT"

  
- Process
- Supply Voltage
- Temperature
- Parasitics, ex. capacitance



- Data-dependent variations


$$1 \text{ OR } 1 = 1 \text{ faster}$$

$$1 \text{ OR } 0 = 1$$

 

We care
about shortest
path


→ t

 


Use FFs

Rules

 - 1) Only clk may connect to clk input of a FF




 - 2) clks may not connect to any node other than FF clk input




Exceptions:

- Clock generation circuit

 


- Clock gate

 

circuit design issues

180 system
gate $\Rightarrow$
 $\rightarrow$ circuit $\Rightarrow$


Critical Timing Relationships

 

Requirement 31 - Logic is not too slow (clock not too fast)

Ex: 1 GHz = 10^9 Hz

 
clock period = $1/10^9 = 10^{-9}$ sec = 1 nsec



$$t_{clk-to-Q} + t_{logic\ max} + t_{setup} \leq t_{cycle} \leq 1/freq$$

What if the relationship is violated?

- A) Design time
 - speed up logic

 

B) After chip is built

- reduce clk freq

i) Product

a) 4.0 GHz $\rightarrow$ 3.9 GHz $\checkmark$ ok

b) 60 fps $\rightarrow$ 59.9 fps $\times$ fail

ii) Research

6.0 GHz $\rightarrow$ 5.9 GHz $\checkmark$ ok

reg out,
case {a, b}

00: begin out = 1'b0; end

01: 0

10: 0

11: 1

end case

5'hFF

1 1 1 1 1

5'b11111

X	X	X	X
-8	4	2	1

1 0 0 0 = -8

0 1 1 1 = +7

1 1 1 1 = -1

X	X	X	X
8	4	2	1

0 0 0 0

1 0 0 1 = 9

0-9

XXXX

XXXX