

May 11,
2021

Variable-frequency clocking HW
Multi-frequency " "

Reason 1: to reduce power dissipation


$$\text{Active power for CMOS} = \alpha C V^2 f$$

α = activity

C = capacitance

V = V_{DD}


f = clock frequency

 

Reason 2: A sub-module requires a clock freq. that is different than the main clk frequency.


Ex: DDR4-3200 operates at 1.60 GHz
will need a clock at 660 MHz (or 0.80 GHz)

1) Build slower divided clocks using FFs

 

Never use this!


2) Use multiple - freq clocks

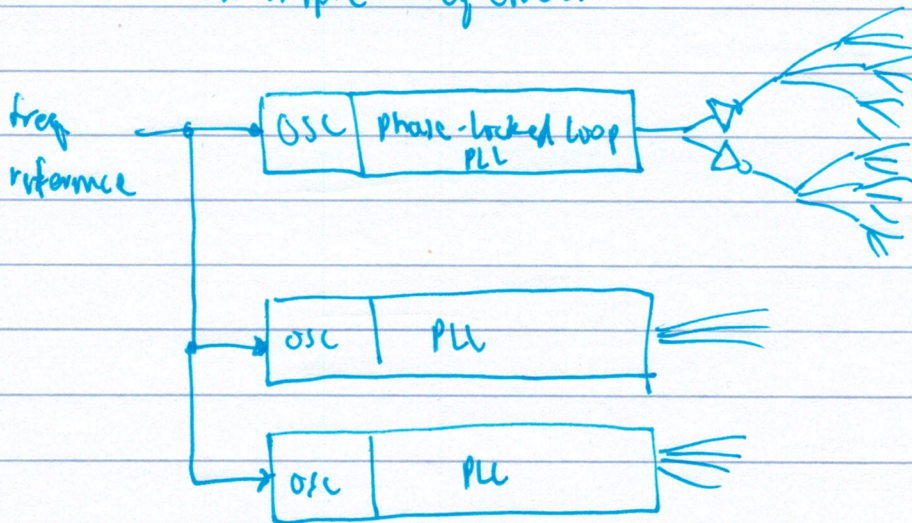

- How real systems are commonly built
- + Likely to save power in large systems
- Requires multiple independent clocking systems
- PLLs require significant power

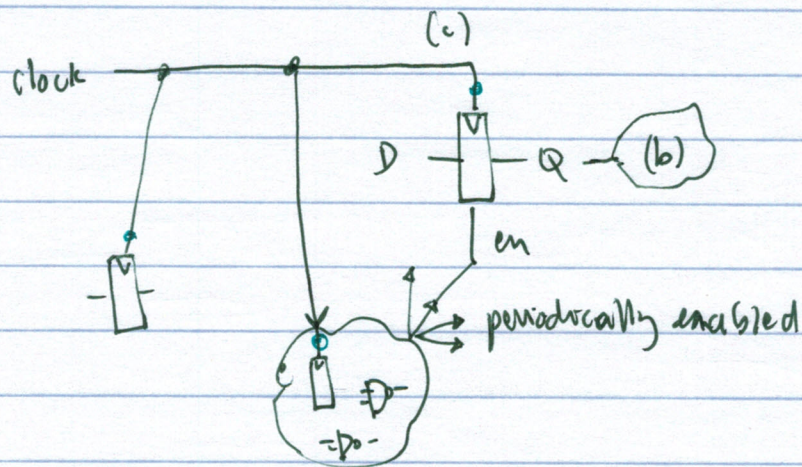3) Pseudo multi-rate

- Clock all logic with the highest clock rate clock
- Utilize counters that load registers, or route signals on only certain clock edges
- + Simplest and most robust
- Counters must be reset simultaneously
- Design in this way for 180




- possible issue for en signal if many FFs
 - delay of en fanout tree
 - en could be pipelined

- Effectiveness:

- Logical operations - same as if delay was reduced ✓
- Power reduction of logic - " " " ✓
- Power reduction of clock - no reduction

Example 1a - Divide freq/4


(e.g., 1 GHz, 250 MHz)

 

```
reg [1:0] count, count_c;
reg Q;
```


```
always @(*) begin
    count_c = count + 2'b01;
end
```

// 00 → 01 → 10 → 11 → 00 ^{wrap}

 

```
reg en_freq4;
always @(*) begin
    if (count == 2'b00) begin
        en_freq4 = 1'b1;
    end
    else begin
        en_freq4 = 1'b0;
    end
end
```

```
always @ (posedge clk) begin
    count <= #1 count_c;
    if (en_freq4 == 1'b1) begin
        Q <= #1 D;
        // more registers
    end
end
```

 


Ex 1b:

```

wire en_freq4;
assign en_freq4 = (count == 2'b00);
    
```

Ex 2: Imitate 1 Hz with 500 MHz clock

 

Divide by 500 million \rightarrow 29 bits \rightarrow 536 million

```

reg [28:0] count, count_c;
reg en_inc;
reg a;
    
```

always @ (*) begin

// default

```
count_c = count + 29'h0000_0001;
```

```
en_inc = 1'b0;
```



if (count == 29'h499_999_999) begin



```
count_c = 29'h0000_0000;
```

```
en_inc = 1'b1;
```

end

end

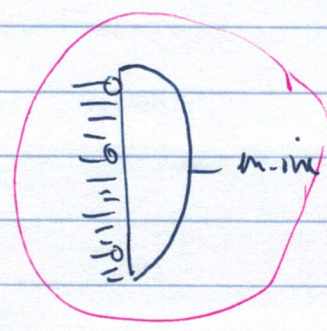 

 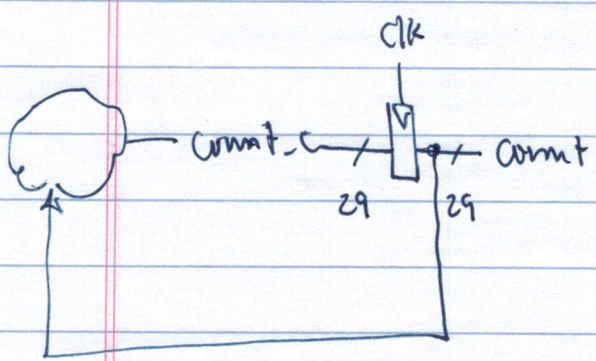

always @ (posedge clk) begin


count <= #1 count_c;

if (en_inc == 1'b1) begin

Q <= #1 D;

end

end

 

Next States
(a b)

(Moore)

Present State	00	01	10	11	output(s)
init					
a					
a0					
ab					
ab0					
aba					
aba0					