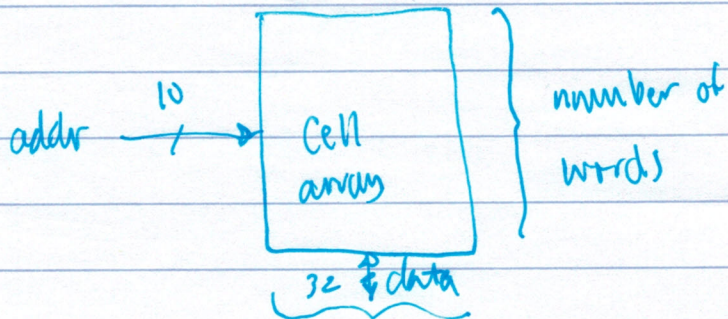


May 27,
2021


Memories III

1024 word x 32 bit
= 32Kbit




Total memory size = # words x # bits/word word width
 $= 2^{\text{addr_width}} \times \text{\#bits/word}$

Timing

 


Memory Write

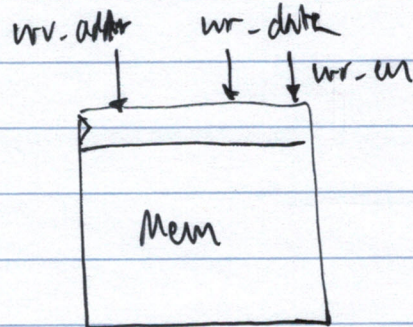


Read After Write hazard

RAW

 


Memory Reads

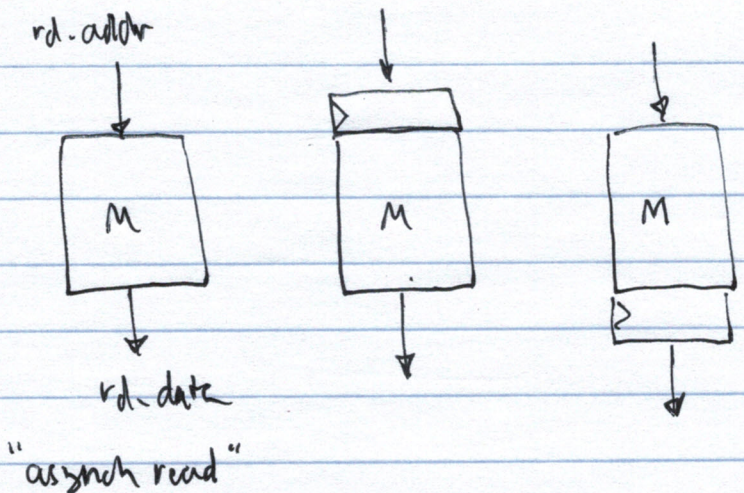



"same" external things


Simultaneous Rd + Wr

 - 1) Rd returns old data
- 2) Rd returns new data
- 3) Don't care / don't know
 - old
 - new
 - some of each



Style #2 - built from PEs

  


 

For max clk freq, a, b, c, d

should have ~ balanced delays



① Mem w/ async read

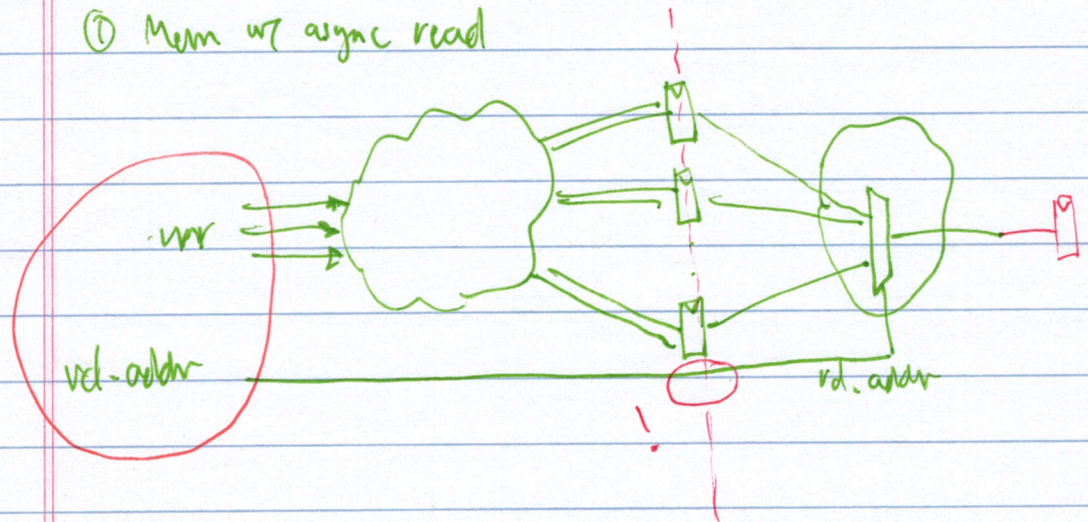

Not a valid pipeline block diagram

```

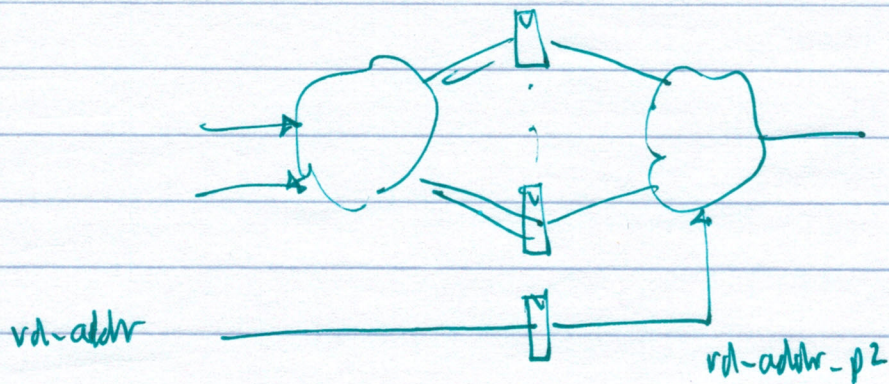 * {
  always @ (posedge clk) begin
    if (wr_en ...)
      mem[wr_addr] <= #1 wr_data;
  end
  rd_data = mem[rd_addr];
}
  
```



```

*
if (posedge clk) begin
    rd-addr-p2 <= #1 rd-addr;
end



```

```

assign rd-data = mem[rd-addr-p2];

```

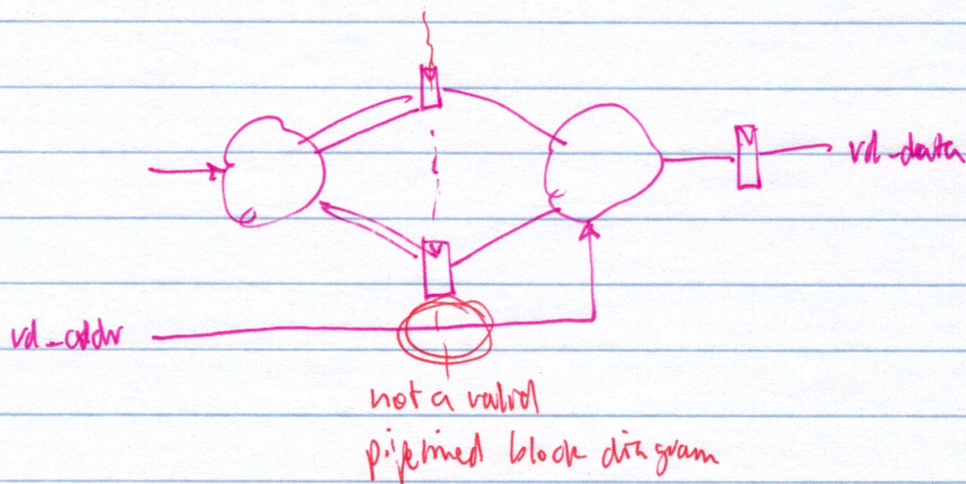 Simultaneous rd + wr to same address → rd gets new data




Simult. rd/wr
to same addr
→ rd gets
old data

```

*
if (posedge clk) begin
    rd-data <= #1 mem[rd-addr];
end

```

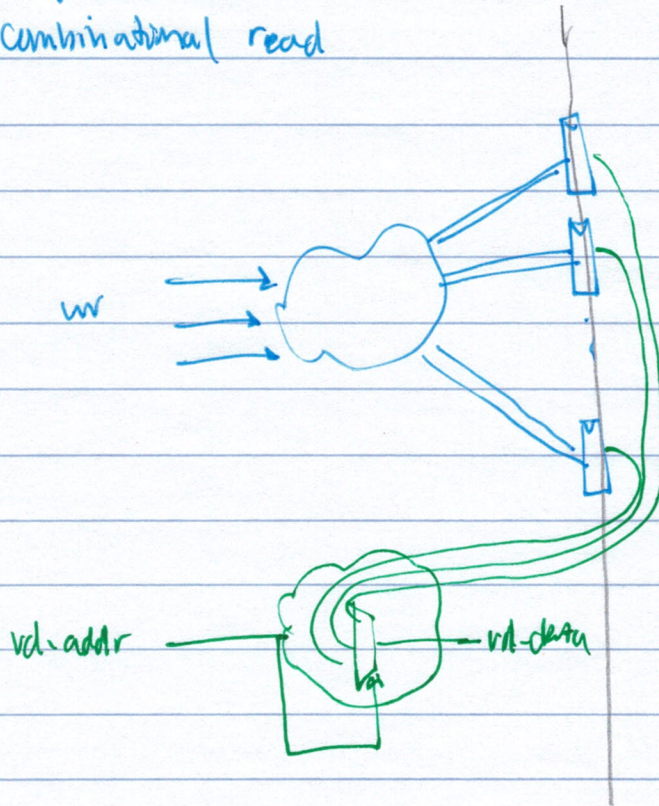Ex: "asynchronous" read
 combinational read



Simult. rd/wr to same addr → rd get old data

Read-Only Memories (ROMs)


Common solution: large case statement

always @ (addr) begin
 case (addr)

4'b0000: begin r = 8'b.....; i = 8'b.....;

end case

end

 

1) Israh. from std. cells

Efficiency of solution depends on randomness of data

- Generate case statements with a program
 - matlab

2) Block RAM (RAM)

- MQK - Altera FPGA

MQK Block RAMs on Altera FPGA chips