 


VARIABLE FREQUENCY CLOCKING HARDWARE

Variable-Frequency Clocking Hardware


- Many complex digital systems have components clocked at different frequencies
- Reason 1: to reduce power dissipation
 - The dominant “active” component of power is proportional to the clock frequency
 - If a module’s clock frequency can be reduced while maintaining acceptable performance, a reduced frequency will reduce the *active* power dissipation
- Reason 2: Because a sub-module requires a specific clock frequency that is different than the main system’s frequency.
 - For example, the DDR4-3200 synchronous DRAM memory interface has an I/O bus that operates at 1.60 GHz and so the module certainly requires a 1.60 GHz (actually probably 0.8 GHz) clock



Multi-rate Clocking Hardware

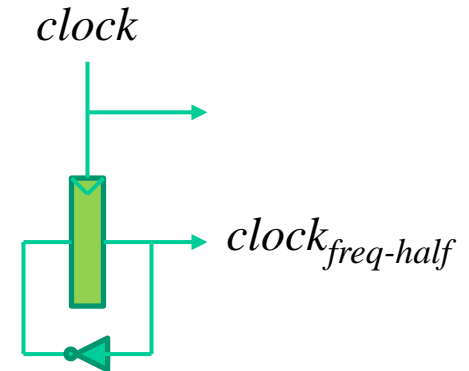
1) Build slower divided clocks with FFs

- Some FFs are clocked by the real *clock* signal, others are clocked by a delayed slower $clock_{freq-half}$ signal coming from a frequency divider. Significant clock skew \rightarrow potential for dead chip ☹
- Could risk your job security (moderate exaggeration)



 
2) Use multi-frequency clocks

- + May save significant power in large active circuits
- Requires a complete and independent clock tree for each frequency and possibly an independent phased-locked loop (PLL) for each
- Each PLL uses significant power




Multi-rate Clocking Hardware

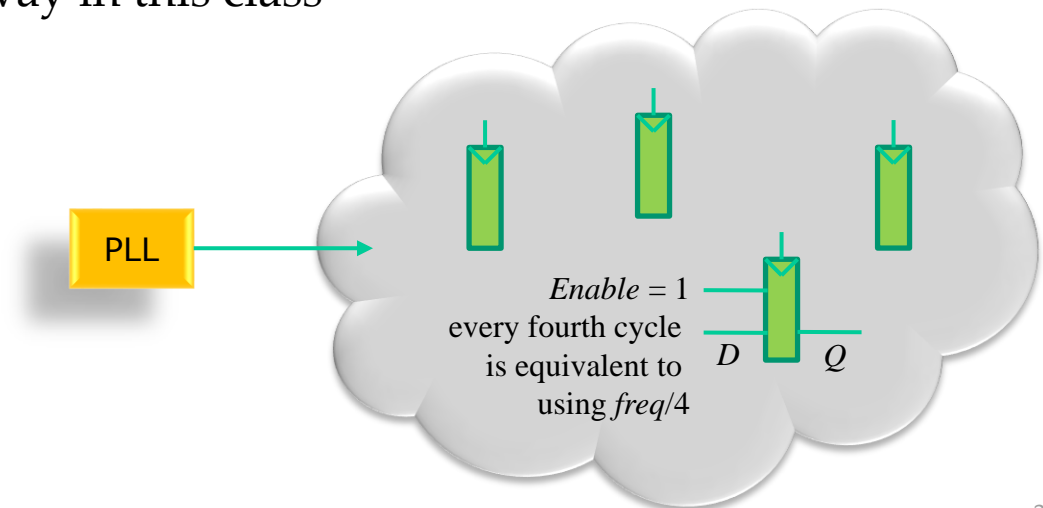- 3) Pseudo-multi-rate: Clock all logic with the highest-rate clock
- Utilize simple counters that load registers or route signals on only certain clock edges (for example, every fourth clock edge for $freq/4$).
 - + Definitely the simplest and most robust
 - Counters must be reset simultaneously and the *reset* signal must meet timing requirements at the highest frequency
 - Design in only this way in this class



Multi-rate Clocking Hardware

 - 3) Pseudo-multi-rate: Clock all logic with highest-rate clock
- Possible issue if there are a very large number of FFs requiring the same enable signal
 1. delay of the fanout tree reduces available cycle time
 2. the enable signal could be modestly pipelined
 - Effectiveness
 - + Logical operation—same as if frequency was reduced
 - + Power reduction of logic—same as if frequency was reduced
 - Power reduction of clock signal—none at all



Multi-rate Clocking Hardware

- Example 1a to imitate a clock frequency of $freq/4$

```
reg [1:0] count, count_c;           // two bits counts 00, 01, 10, 11, 00, ...
reg      Q;                         // assume D comes from elsewhere
always @(*) begin
    count_c = count + 2'b01;         // let the counter wrap 2'b11 → 2'b00
end
```


```
// en_freq4 will be high every 4th cycle
```

```
reg en_freq4;
always @(*) begin
    if (count == 2'b00) begin
        en_freq4 = 1'b1;
    end
    else begin
        en_freq4 = 1'b0;
    end
end
```

```
// breaking a guideline with "if" here
```

```
always @(posedge clk) begin
    count_c <= #1 count_c;
    if (en_freq4 == 1'b1) begin
        Q <= #1 D;
        state_c <= #1 state_c;
    end
end
```

```
end
```

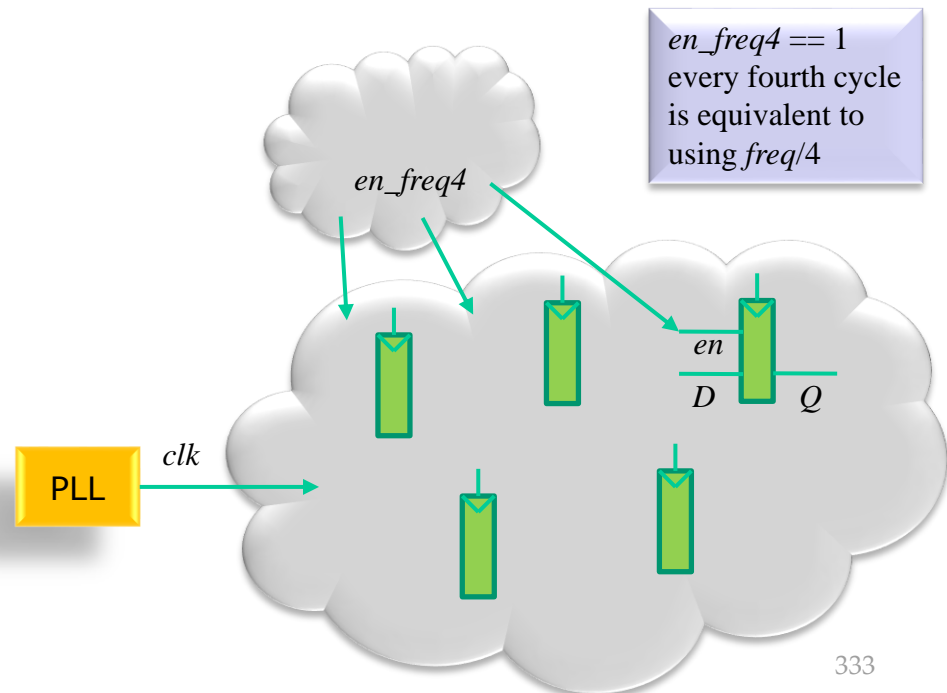


Multi-rate Clocking Hardware

- Example 1b to imitate a clock frequency of $freq/4$

```
reg [1:0] count, count_c;           // two bits counts 00, 01, 10, 11, 00, ...
reg      Q;                         // assume D comes from elsewhere
always @(*) begin
    count_c = count + 2'b01;        // let the counter wrap 2'b11 → 2'b00
end

wire en_freq4;                      // use a wire in this example
assign en_freq4 = (count == 2'b00); // code is compact but slightly less clear

 // breaking a guideline with "if" here
always @(posedge clk) begin
    count <= #1 count_c;
    if (en_freq4 == 1'b1) begin
        Q <= #1 D;
    end
end
end
```



Multi-rate Clocking Hardware

- Example 2 to imitate a clock toggling at 1 Hz, a with 500 MHz clock

```
reg [28:0] count, count_c;           // 29 bits counts up to 536 million
reg      en_increment;               // I use a reg in this example
reg      Q;                          // assume D comes from elsewhere
always @(*) begin
    // defaults
    count_c = count + 29'h0000_0001; // "count" is a flip-flop register
    en_increment = 1'b0;             // a combinational logic signal

    if (count == 29'd499_999_999) begin
        count_c = 29'h0000_0000;    // wrap counter back to zero
        en_increment = 1'b1;        // pulse FF enable signal high
    end
end

always @(posedge clk) begin
    count <= #1 count_c;
    if (en_increment == 1'b1) begin
        Q <= #1 D;
    end
end
```

