

7 BASIC DIAGRAMS


Basic Diagrams

1. Block diagram

- Just like it says; diagram of blocks (and inter-connections)

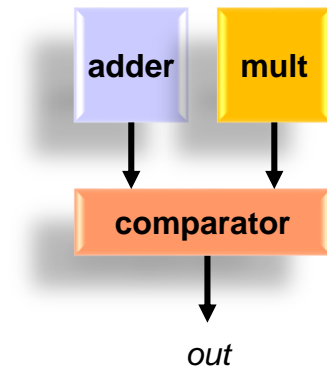2. Circuit diagram



- Although it may not require details to the transistor level or gate level (e.g., NAND or NOR), it should have more circuit-type detail if applicable
- Having said that, in some cases it may be the same as a block diagram



Basic Diagrams

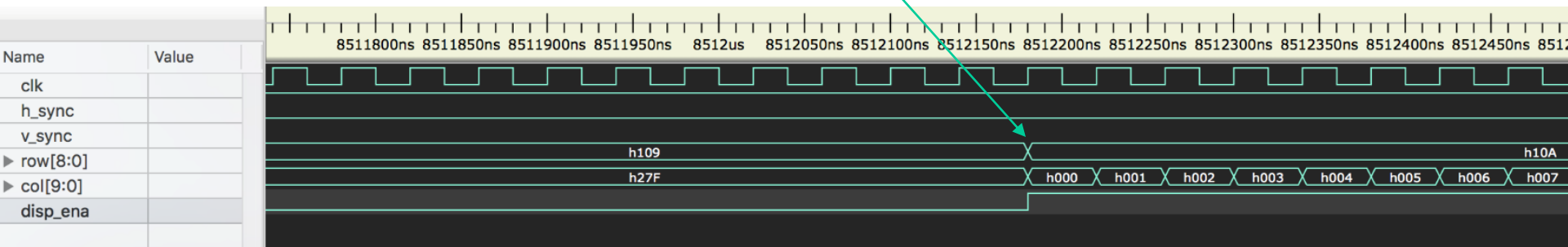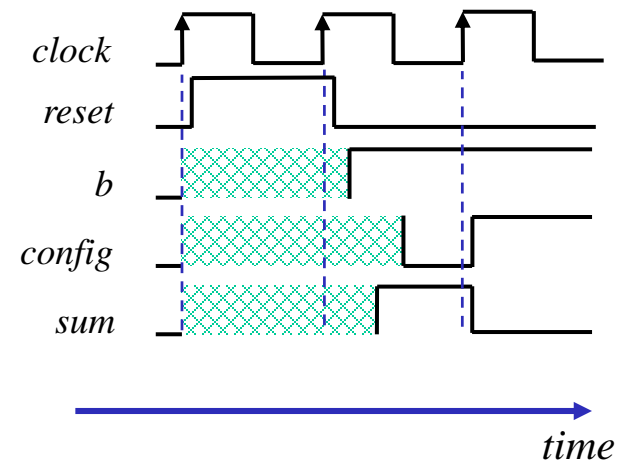3. Timing diagram


- Logic level (voltage) versus time
- As a rule, the *clock* is at the top. Draw a small arrow on each active edge. Draw a light vertical line aligned with each active clock edge.
- Several common waveform features:
 - Simple single-bit signal 0/1 values
 - Multi-bit bus
 - Transition location or region where a signal, or signal(s) within a bus, changes value



Basic Diagrams

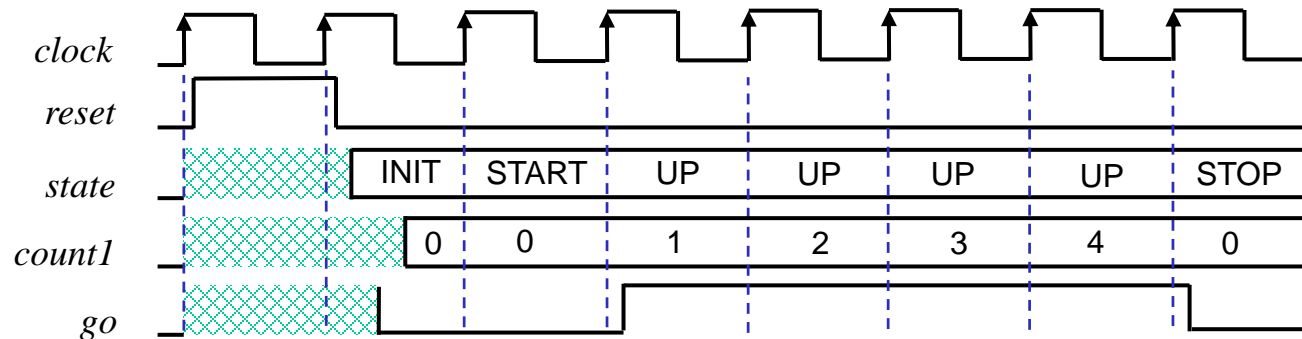
3. Timing Diagram continued

- Draw transitions of signals that come from a register a very short time after the active edge of the clock, not at the same time as the clock edge—this is for increased clarity however it also explicitly shows the “*clock-to-Q* delay”
- Timing diagrams may also show higher-level events such as state and counter values




Basic Diagrams

4. State Diagram

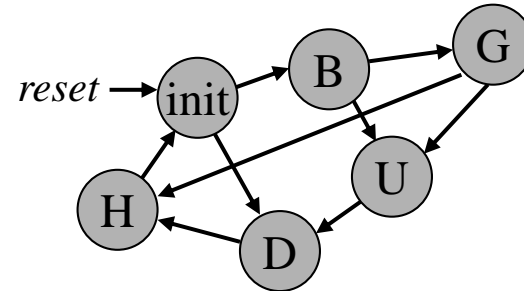


5. Arithmetic Dot Diagrams

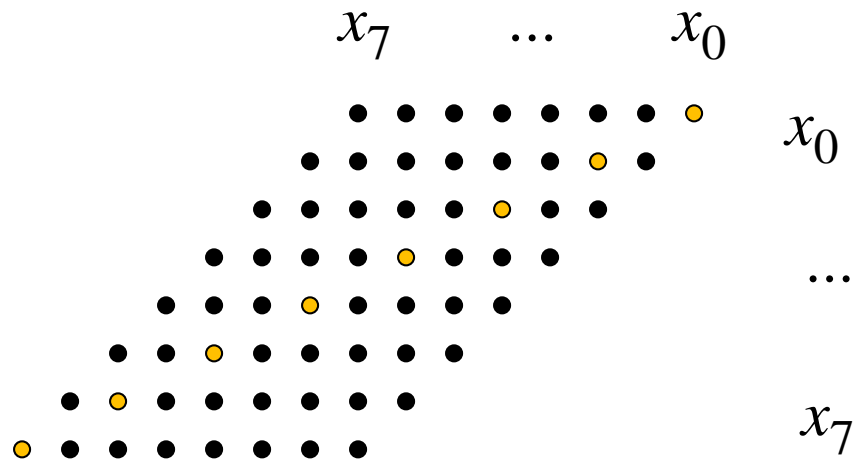

Basic Diagrams

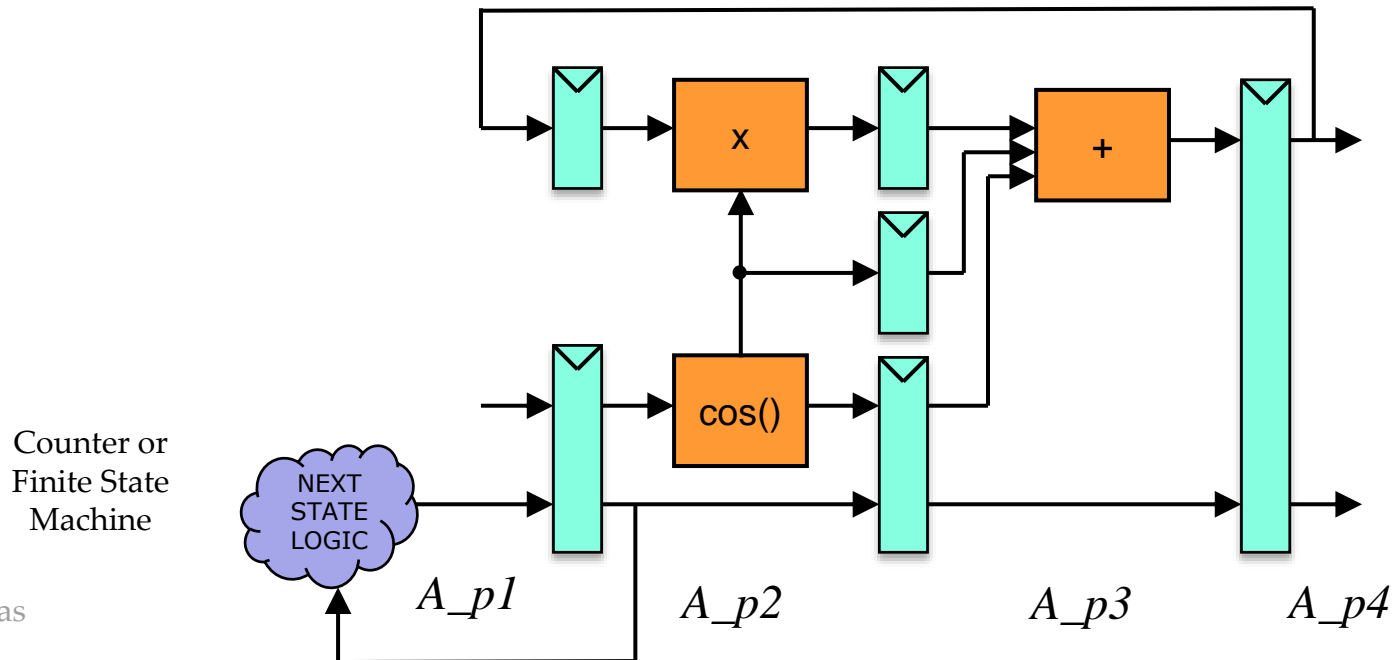6. Pipelined Block Diagram

- All registers are aligned with others in the same pipeline stage
- “Reverse-flowing” signals are generally not pipelined
- It is often advisable to include a pipeline-stage notation in each signal’s name



Basic Diagrams

7. Pipeline Diagram

- Useful for designing deeply-pipelined digital processors

