
 


ADDERS & SUBTRACTORS

Arithmetic Blocks

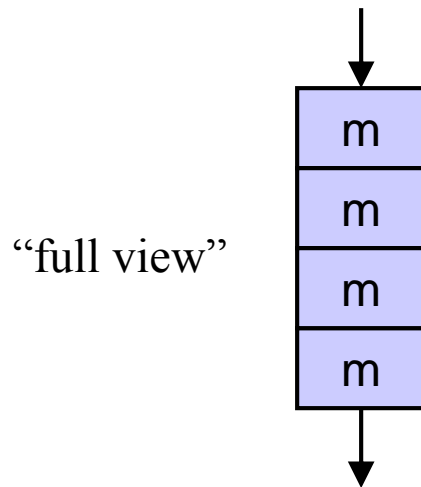- We'll first look at adder and multiplier
- Look at in “full” non-iterative view, but hardware may require smaller area and less performance so we can then “time-multiplex” a portion of the datapath





an iterative potentially
functionally-identical
implementation

Adders

- One of the most fundamental arithmetic units
- Signal Growth Rule:
width of *sum* = width of *input* + 1
 - for a 2-input adder
 - both inputs are of equal width
- Different styles produce faster or smaller circuits; many types are useful, not just the fastest ones
 - Ex: add two 3-bit numbers. Likely choose the simplest (slowest) architecture
 - Ex: 32-bit adder in critical path of a datapath. Likely choose the fastest architecture


Two Broad Classes of Adders

  - Carry-propagate adder (CPA)
 - What we think of as normal addition
 - Output is a single word
 - Carry must effectively propagate across the entire word
- Carry-save adder (sometimes CSA)
 - *Sum* is not in a “normal” single-word format
 - Output is in a redundant “carry-save” format
 - Output consists of 2+ words
 - Input consists of 3+ words




Full Adder

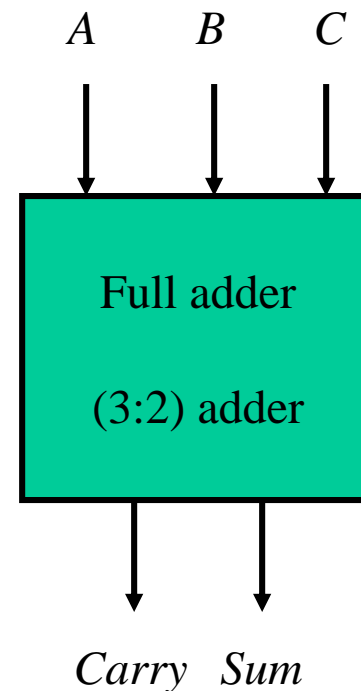- A fundamental adder building block
- Adds three bits of equal weight
- *Carry* has a $2\times$ higher-significance or positional weight than *Sum*



 
1) Ripple Carry Adder

- We can chain together or “bit slice” full adders to add two numbers
- Note the extra input in the LSB position



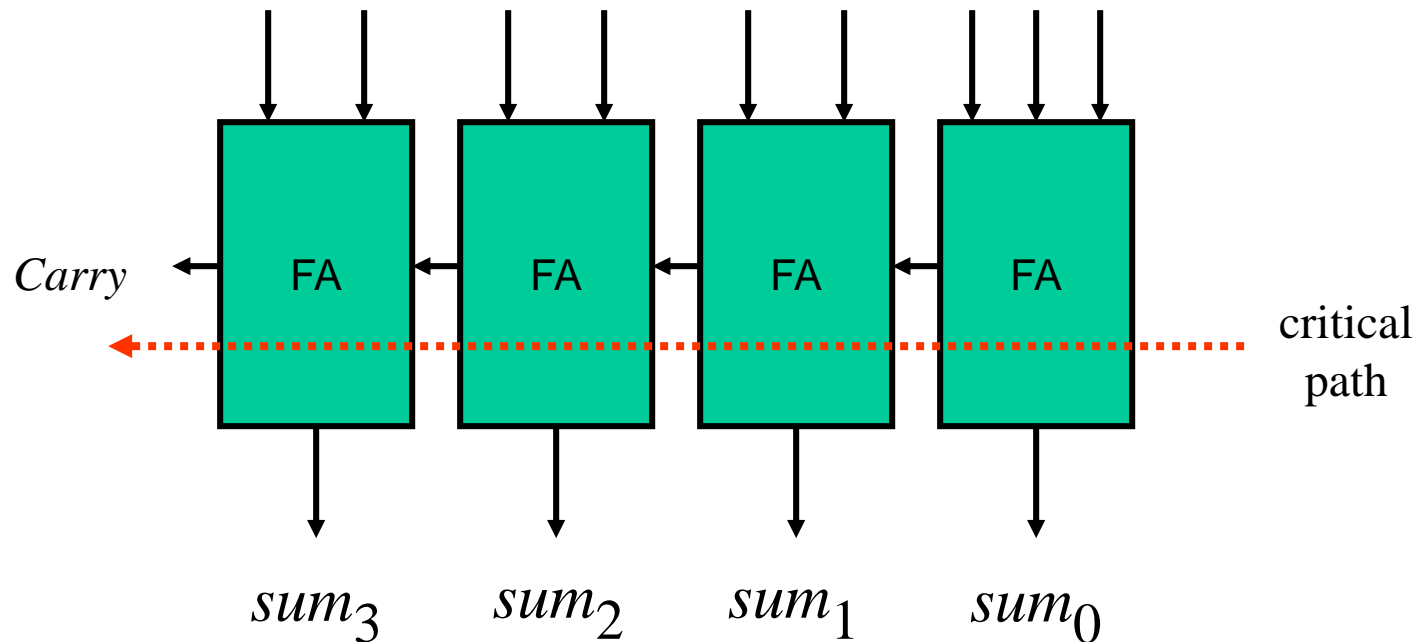1) Ripple Carry Adder

- The *carry ripples* through the chain of full adders



1) Ripple Carry Adder

- Simplest adder
- Smallest adder
- Slowest adder (for wide words)
 - However, for narrow word-widths, it can be fast!
- We can view most (all?) other CPAs as improved ripple-carry adders

Faster Adders

- The entire goal to make faster adders is to resolve the carry across the entire adder structure more quickly
- A few common faster CPAs:
 - 1) Carry Select
 - Speculatively add and select later
 - 2) Carry Lookahead
 - Look at how a carry propagates through a group of bits
 - 3) Conditional-sum (recursive carry select)
 - 4) Carry skip
 - 5) Other parallel prefix adders
 - Kogge-Stone, 1973
 - Brent-Kung, 1982
 - etc.

Subtraction

- Subtraction *requires* a signed number format
 - Ex: $2 - 3 = -1$
- 2's complement is the preferred format for fixed-point because subtraction with it is straightforward
- 2's complement subtraction is implemented with a slightly-modified normal adder
 - $A - B = A + (-B)$
 - Recall that for 2's complement numbers,
 $-B = (\sim B) + 1$
 - So now we have
 $A - B = A + (\sim B) + 1$
- Signal growth is the same as with addition

Subtraction

- It is typically easy to find a place to add a “1” in the LSB position

