 



## Critical Timing Relationships

If these are violated, the circuit will definitely fail under some circumstances.


Fundamental block of every clocked digital system:



 - FSM control, datapath, anything
- could also be latches, but we use FFs



 
- could be the same register for both sides



Requirement #1 : Logic is not too slow (clock not too fast)

Ex:- 1 GHz clock
 
$$\text{clock period} = \frac{1}{\text{freq}} = \frac{1}{10^9 \text{ Hz}} = 10^{-9} \text{ sec} = 1 \text{ nsec}$$



- There is one clock period for data to get from one register to the next one.

a) clock edge  $\rightarrow$  Q output

$$t_{\text{clk-to-Q}}$$

b) time for the slowest path  
through the comb. logic

$$t_{\text{logic max}}$$

c) time to arrive before the  
active clock edge

$$t_{\text{setup}}$$

$\therefore$  time circuit requires  $\leq$  time allowed, for correct operation


$$\boxed{t_{\text{clk-to-Q}} + t_{\text{logic max}} + t_{\text{setup}} \leq t_{\text{cycle}} \\ \leq \frac{1}{\text{freq}}}$$

What if the requirement is violated?

### A) Design time

- speed up logic

but...

 

### B) After chip is built

- only  $t_{cycle}$  is available

slow  $f_{clk} \rightarrow$  longer  $t_{cycle}$

i) product - maybe ok

1.9 GHz proc instead of 2.0 GHz ✓

59 frames per second vs. 60 fps ✗

ii) research - probably fine