

# FIXED-INPUT MULTS


# Fixed-input Multiplier

---

- This topic deals with a single multiply operation where one of the inputs is fixed—by this we mean one of the multiplier's inputs is known at the time of hardware design, will never change, and is therefore designed into the hardware
- Simplifications will generally place the fixed input onto the *multiplier* input rather than the *multiplicand* input

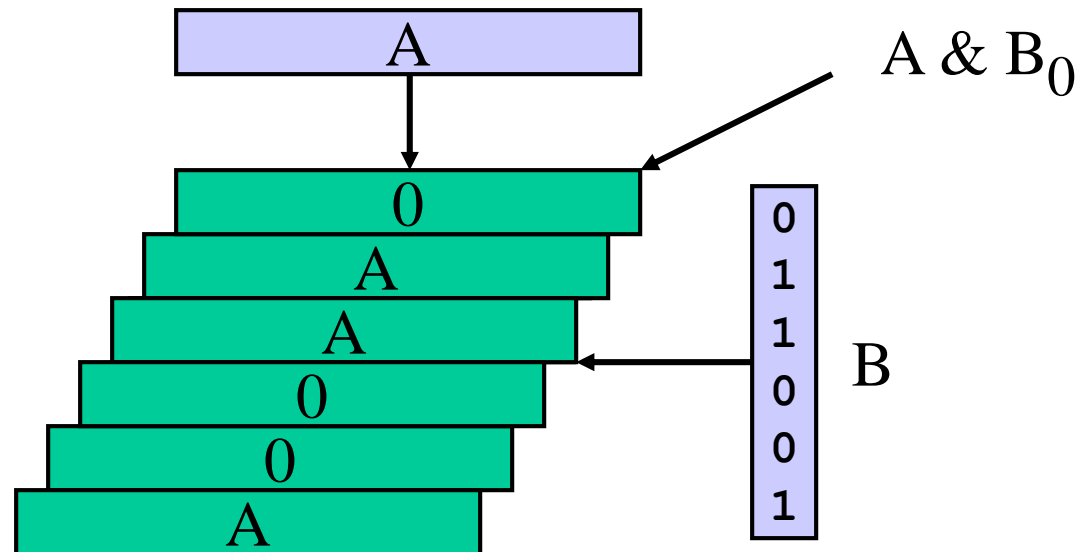
# Fixed-input Multiplier

- Sometimes, one input is fixed
  - So remove partial products that are always zero



 
# Fixed-input Multiplier

- Remove partial products that are always zero


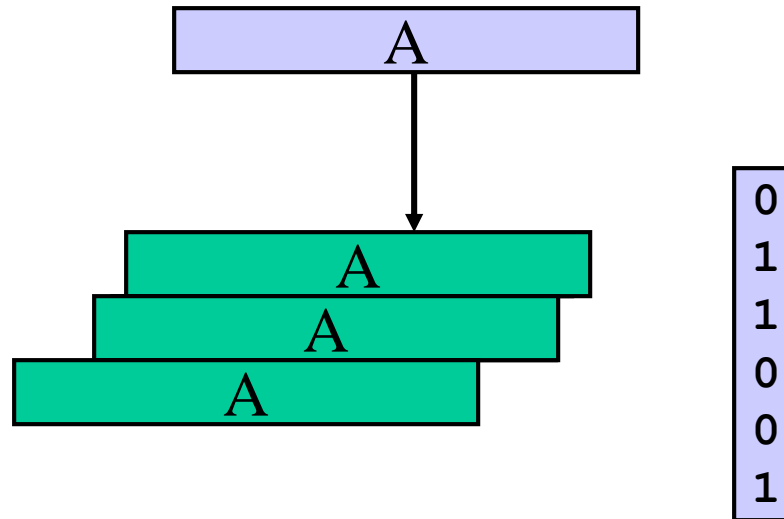
# Fixed-input Multiplier

- Reduce the overall size by half on average, and even more if you can pick the *multiplier* carefully



# Fixed-input Multiplier

---

- An efficient design would instantiate hardware for only the necessary (non-zero) partial products—the minimum number of power-of-2 numbers which add together to equal the fixed multiplier input
- Secondly, we look for cases when a negative partial product will simplify the overall circuit
- A very simple example: multiply by 3

$$\times 3 = (\times 2) + (\times 1)$$


# Multiply by 3

- Ex: multiply by 3

- $\times 3 = (\times 2) + (\times 1)$

- Verilog:

 
```
input [7:0] in;  
wire [9:0] product;
```




```
// multiply by 3  
assign product = {in[7], in[7], in}  
                + {in[7], in, 1'b0};
```
 
# Handling Negative Partial Products

- There are two ways to handle negative partial products; the dot diagram is different but both give the same result and eventually simplify to the same hardware
  - Multiply the *multiplicand*, then invert it (Ex: 6-bit *multiplicand*  $\times -8$ )



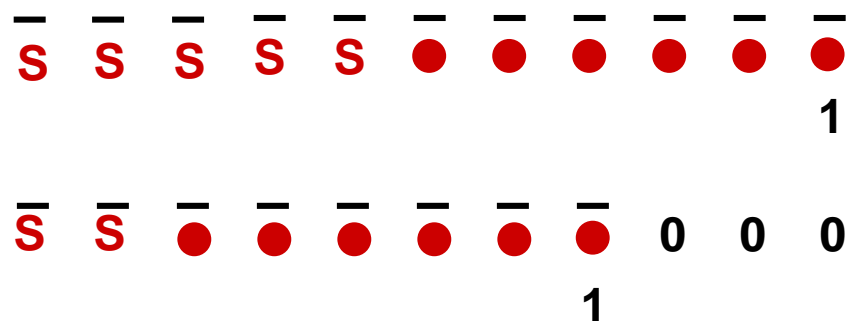- Invert the *multiplicand*, then multiply it






# Multiply by 56

- Ex: 8-bit 2's complement number multiplied by +56

- Three partial products
- $\times 56 = (\times 32) + (\times 16) + (\times 8)$
- Verilog:

```
input [7:0] in;  
wire [13:0] product;
```
 
```
// multiply by 56  
assign product =  
    {in[7], in[7], in[7], in, 3'b000}  
    + {in[7], in[7], in, 4'b0000}  
    + {in[7], in, 5'b00000};
```




# Multiply by 56 (better)

- Ex: 8-bit 2's complement number multiplied by +56 (better)
  - Implement with 2 partial products
  - $\times 56 = (\times 64) - (\times 8)$
  - Verilog:

```
input [7:0] in;  
wire [13:0] product;
```


```
// multiply by 56  
assign product =  
    {in, 6'b000000}  
    - {in[7], in[7], in[7], in, 3'b000};
```
 
```
// one way of many possible ways to write it  
assign product_same =  
    {in, 6'b000000}  
    + {~in[7], ~in[7], ~in[7], ~in, 3'b111};  
    + {14'b0000000000000001};
```


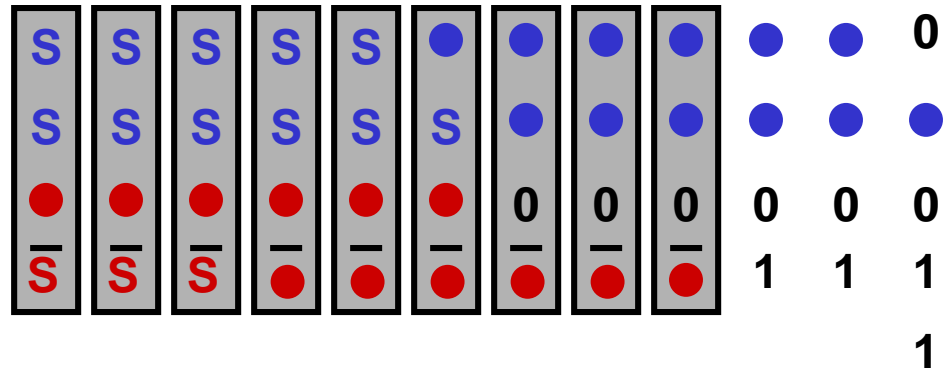
# Dot Diagram Example

- $out = X*3 + Y*56$ 
  - Inputs: 6-bit 2's complement
- Procedure:
  - Input range of  $X$  and  $Y$ :  $[-32, +31]$
  - Decompose  $x3 = x2 + x1$
  - Decompose  $x56 = x64 - x8$
  - Output range:  $[-32, +31] \times [59=3+56]$   
 $= [-1888, +1829]$
  - Output width: 12 bits,  $[-2048, +2047]$
  - Fill out dot diagram
    - $S$  = sign extension bit
    - invert bits when necessary
    - show zeros if dot alignment is not obvious



- OR -

