

EXAMPLE MULTIPLIER

Example 20 bit x 20 bit Multiplier

- 20 bit \times 20 bit signed 2's complement multiplier
- “Full” non-iterative datapath (one multiply per cycle)
- Four pipeline stages
 - Four cycles of latency
- “Booth-2” *multiplier* encoding
- Complex sign extension techniques eliminates sign extension bits with Booth-2 staggered partial products

Example 20 bit x 20 bit Multiplier

- Full output is $20 + 20 = 40$ bits
 - Will need to round down to 20 bits later
 - Choose to keep a 24-bit output for later calculations
 - The motivation can be illustrated with a base-10 example
 - The lowest 4 digits of the product have little meaning

$$\begin{array}{r} 0.5213 \\ \times 0.8392 \\ \hline 0.43747496 \end{array}$$

- In this example multiplier, the partial product array is truncated, and the output is rounded to keep the mean of the rounding error equal to zero. This array truncation results in a 27% reduction of partial product array hardware. Although the savings are substantial, this method is generally not recommended due to greatly increased difficulty in writing a matching golden reference, and increased irregularity in the hardware.

Guideline #1 for Placing Carry-Save Adders

- Each “dot” that exists at the end of a pipeline stage must be registered (one high-power large-area clock-requiring flip-flop)
 - Of course constant “1”s can be placed anywhere and are never registered
 - There is no such thing as a “0” in a dot diagram
- Therefore, the best design will minimize the number of dots in each stage by placing as many full adders (eliminates one dot) and 4:2 adders (eliminates two dots)

Guideline #2 for Placing Carry-Save Adders

- Each pipeline stage requires a large number of flip-flops
- Each pipeline stage adds one cycle of latency to the datapath
 - This often causes a penalty at a higher level of the architecture. In some cases the penalty is significant, in some cases it is negligible.
- Therefore, place carry-save adders to minimize the number of pipeline stages

Example 20 bit x 20 bit Multiplier

- Notation for upcoming dot diagrams:

`.` = input_bit, can be either a 0 or 1

`,` = NOT(.)

`0` = always zero

`1` = always one

`S` = the partial product sign bit

`E` = bit to clear out sign_extension bits



`e` = NOT(E)

`-` = carry_out bit from (4,2) or (3,2) adder in adjacent column to the right

`x` = throw this bit away


Example 20 bit x 20 bit Multiplier

- Booth-encoded partial product array

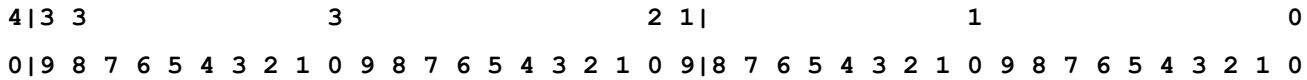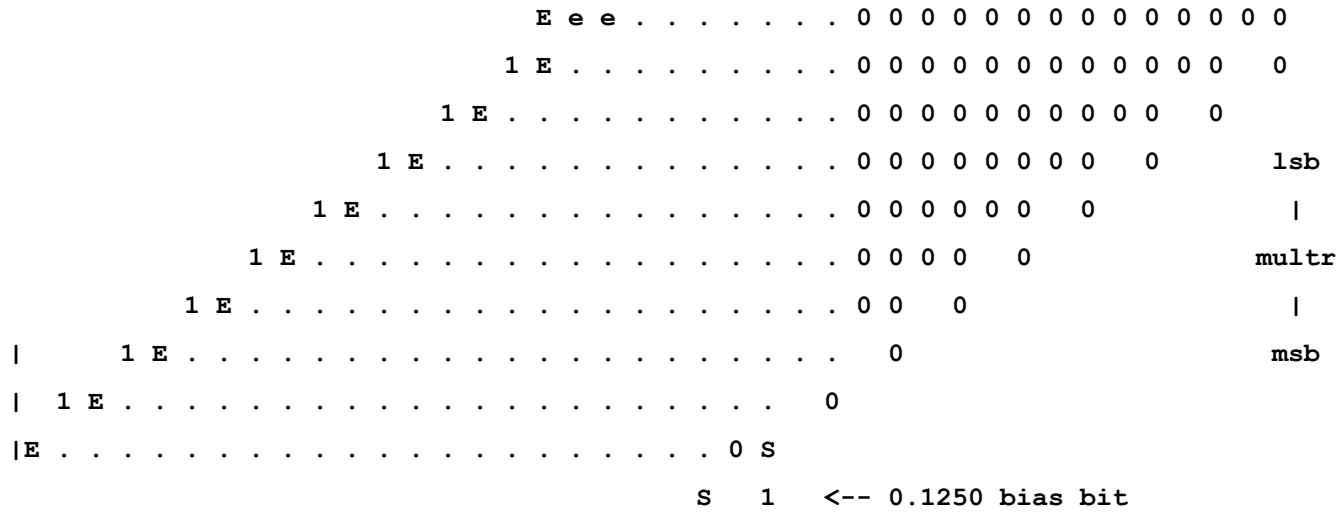


Example 20 bit x 20 bit Multiplier

- After one level of adders

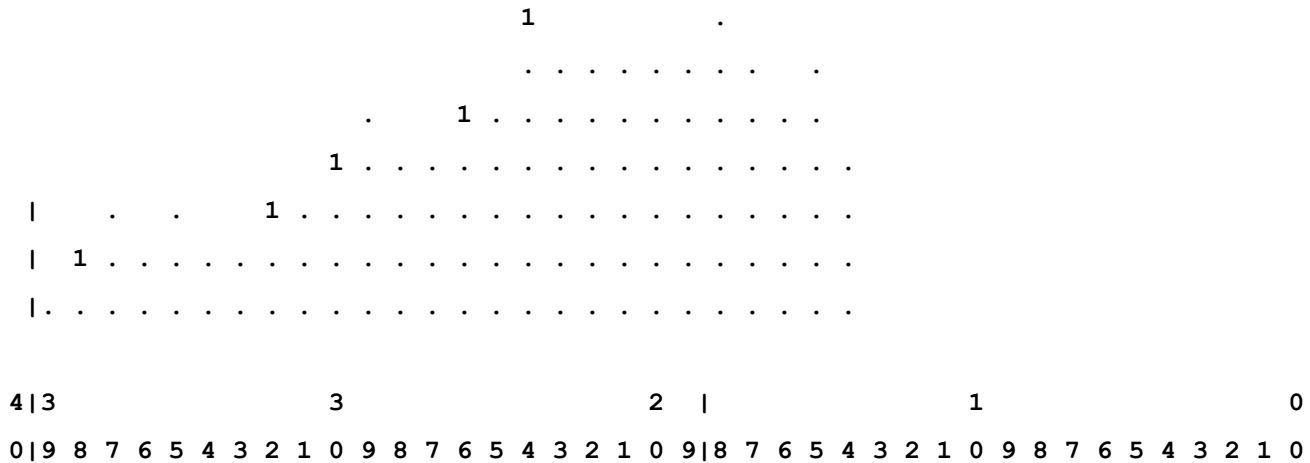


Example 20 bit x 20 bit Multiplier

- Another pass of 3:2 and 4:2 adders

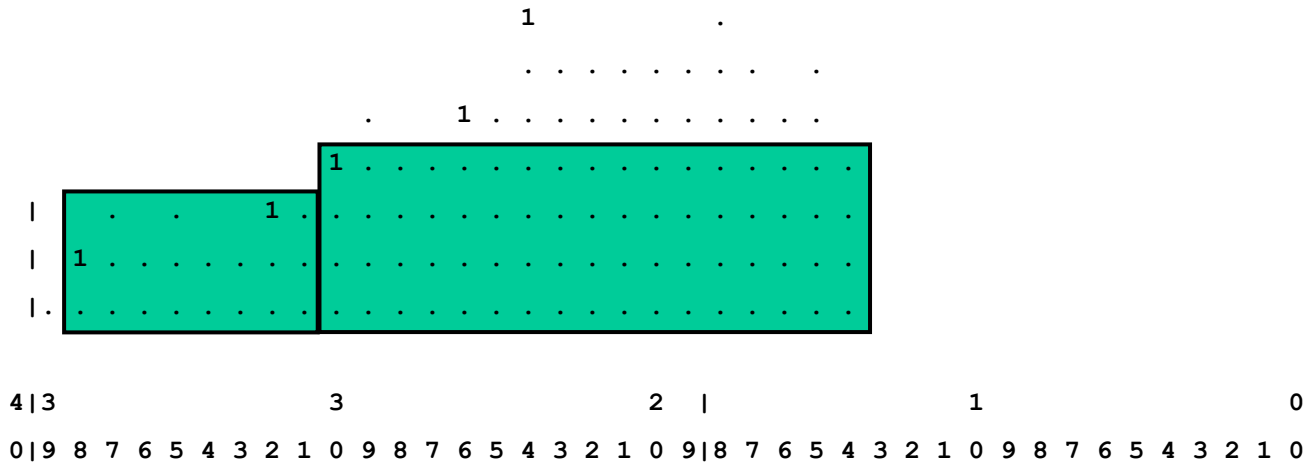


Example 20 bit x 20 bit Multiplier

- After two levels of adders

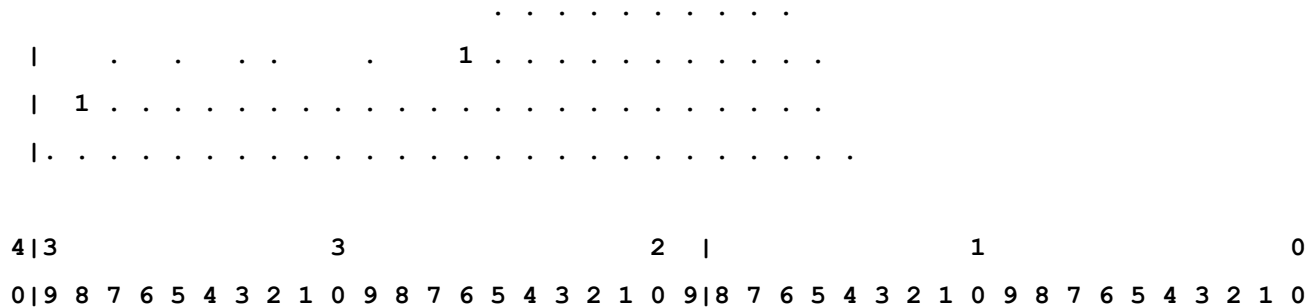

Example 20 bit x 20 bit Multiplier

- Another pass of 3:2 and 4:2 adders

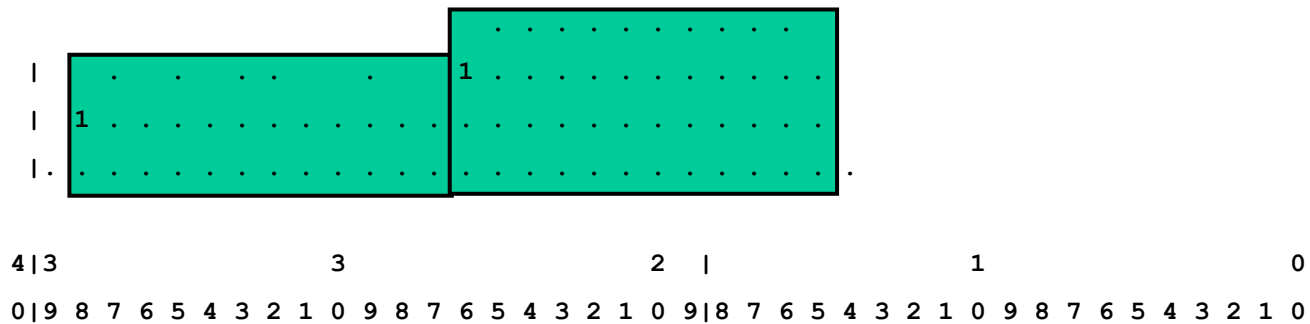

Example 20 bit x 20 bit Multiplier

- After three levels of adders, it's ready for a carry-propagate adder!

```

| . . . . .
| . . . . . x
                                0 1
4|3          3          2 |          1          0
0|9 8 7 6 5 4 3 2 1 0 9 8 7 6 5 4 3 2 1 0 9|8 7 6 5 4 3 2 1 0 9 8 7 6 5 4 3 2 1 0

```

Die Photo

