

HARDWARE MULTIPLIERS

Multipliers

- Multipliers are widely used in digital signal processing, generally more so than in general-purpose workloads
- Common multiplier types
 - *Unsigned × Unsigned*
Also useful for sign-magnitude format numbers
 - *Signed 2's complement × Signed 2's complement*
- Hardware is typically built in a manner broadly similar to how you would do it with paper and pencil
- The naming convention is somewhat unfortunate:

$$\begin{array}{r} \text{multiplier} \\ \times \text{multiplicand} \\ \hline \text{product} \end{array}$$

Example Unsigned Multiplier

- Example: 4-bit unsigned *multiplicand* “ a ” times 4-bit *multiplier* “ b ”
- $p_{xy} = a_x \times b_y$
 $= a_x \text{ AND } b_y$

| | | a_3 | | a_2 | | a_1 | | a_0 | | |
|----------|----------|----------|----------|----------|----------|----------|--|-------|--|------------------|
| | | \times | b_3 | b_2 | b_1 | b_0 | | | | |
| | | | p_{30} | p_{20} | p_{10} | p_{00} | | | | $\leftarrow b_0$ |
| | | p_{31} | p_{21} | p_{11} | p_{01} | 0 | | | | $\leftarrow b_1$ |
| p_{32} | | p_{22} | p_{12} | p_{02} | 0 | 0 | | | | $\leftarrow b_2$ |
| p_{33} | p_{23} | p_{13} | p_{03} | 0 | 0 | 0 | | | | $\leftarrow b_3$ |

Example 2's Complement Multiplier


- Example: 4-bit signed 2's complement *multiplicand* " a " times 4-bit *multiplier* " b "
- s = partial product sign extension bits
- $p_{xy} = a_x \times b_y$
 $= a_x \text{ AND } b_y$

| | | | | a_3 | a_2 | a_1 | a_0 | |
|-----|---------------------|---------------------|---------------------|---------------------|----------|----------|----------|------------------|
| | | | \times | b_3 | b_2 | b_1 | b_0 | |
| s | s | s | s | p_{30} | p_{20} | p_{10} | p_{00} | $\leftarrow b_0$ |
| s | s | s | p_{31} | p_{21} | p_{11} | p_{01} | 0 | $\leftarrow b_1$ |
| s | s | p_{32} | p_{22} | p_{12} | p_{02} | 0 | 0 | $\leftarrow b_2$ |
| s | $\overline{p_{33}}$ | $\overline{p_{23}}$ | $\overline{p_{13}}$ | $\overline{p_{03}}$ | 0 | 0 | 0 | $\leftarrow b_3$ |

1

3 Main Steps in Every Multiplier

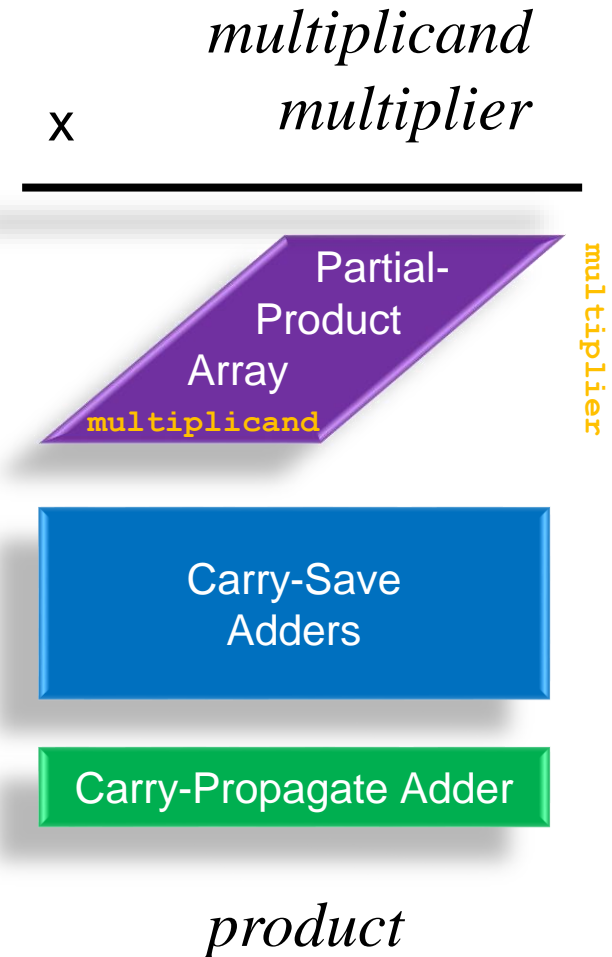
- 1) Generation of partial products
- 2) Reduction or “compression” of the partial product array (normally using carry-save addition) into a two-word product
 - Linear array addition
 - Tree addition (Wallace tree)
- 3) Final adder: Carry-propagate adder (CPA)
 - Converts the product in carry-save form into a single word form
 - Any style of CPA is fine though we probably favor faster ones
 - The CPA may be omitted if a better overall design results if the product is used in carry-save form



Straight-forward Partial Product Generation

- This is the simplest method to generate partial products
- Hardware looks at one bit of the *multiplier* (Y_i) at a time
- Partial products are copies of the *multiplicand* AND'd by bits of the *multiplier*
- Number of bits in the *multiplier*
= Number of partial products
= Number of terms/words/rows that must be added

| Y_i | Partial product |
|-------|--------------------------------|
| 0 | 0 |
| 1 | $+x (= \textit{multiplicand})$ |

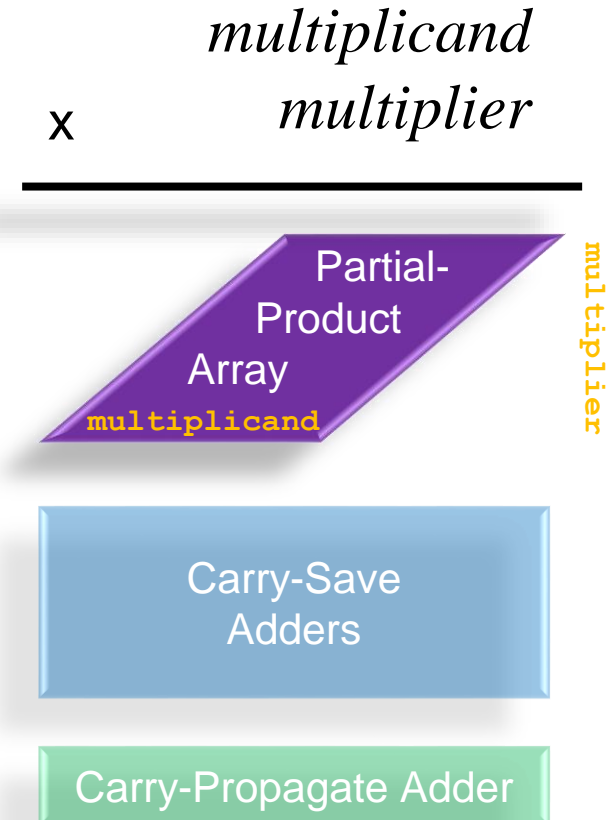

Straight-forward Partial Product Generation

- There are only two possible partial product results
- Two reasonable hardware solutions are:
 - a row of 2:1 muxes with zeros on one input
 - a row of AND gates (this should be more efficient)

$+x$

multiplicand


0

0

| Y_i | Partial product |
|-------|--------------------------------|
| 0 | 0 |
| 1 | $+x (= \textit{multiplicand})$ |


Example unsigned 4-bit × 4-bit multiplication

 - Example: 4-bit unsigned *multiplicand* “a” 1100 times 4-bit *multiplier* “b” 1010
- $1100 \times 1010 = 12 \times 10 = 120$
- $1100 \times 1010 = (12 \times 8) + (12 \times 0) + (12 \times 2) + (12 \times 0) = 120$
- $1111000 = 64 + 32 + 16 + 8 = 120$ 😊



Example 2's complement 4-bit × 4-bit multiplication

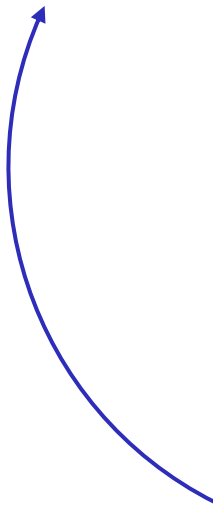- Example: 4-bit signed 2's complement *multiplicand* "a" 1100 times 4-bit *multiplier* "b" 1011
- $1100 \times 1011 = -4 \times -5 = +20$
- $1100 \times 1011 = (-4 \times -8) + (-4 \times 0) + (-4 \times 2) + (-4 \times 1) = +20$
- $00010100 = 16 + 4 = +20$ 😊



| | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|---|---|---|-----|
| | | | | | 1 | 1 | 0 | 0 | |
| | | | | × | 1 | 0 | 1 | 1 | |
| | | | | | <hr/> | | | | |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | ← 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | ← 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | ← 0 |
| <hr/> | <hr/> | <hr/> | <hr/> | <hr/> | <hr/> | 0 | 0 | 0 | ← 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | |
| <hr/> | | | | | | | | | |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | | |