

10 pts

MT 1 Soln

E100

F '15

1. a) A filter has a transfer function  $H_1(j\omega) = \frac{-j2\omega}{(2+j\omega)}$ . What is the phase of this transfer function [ or the angle( $H_1$ ) ] at  $\omega = 2$  rad/s ?

Phase or angle = \_\_\_\_\_

$$\begin{aligned}\text{angle } H_1 &= \text{angle } (-j2 \times 2) - \text{angle } (2+j2) \\ &= -90^\circ - \tan^{-1} \frac{2}{2} = -90^\circ - 45^\circ \\ &= -135^\circ\end{aligned}$$

- b) At what frequency  $\omega$  does the amplitude (or magnitude) of  $H_1$  equal -6 dB ?

$\omega =$  \_\_\_\_\_

$$-6 \text{ dB} = 20 \log |H_1| \Rightarrow |H_1| = \frac{1}{2}$$

$$\frac{1}{2} = \left| \frac{-j2\omega}{2+j\omega} \right| =$$

$$= \frac{2\omega}{\sqrt{2^2 + \omega^2}}$$

square:  $\left(\frac{1}{2}\right)^2 = \frac{4\omega^2}{4 + \omega^2}$

$$\Rightarrow \frac{1}{4}(4 + \omega^2) = 1 + \frac{\omega^2}{4} = 4\omega^2 \Rightarrow \omega = 0.52 \frac{\text{r}}{\text{s}}$$

1 (con't):


c) What type of filter is  $H_1(j\omega) = \frac{-j2\omega}{(2+j\omega)}$  ? Check one box:

- ☐ a low-pass filter.
- ☒ a high-pass filter.
- ☐ a bandpass filter.
- ☐ none of the above.

6 pts

2) What are the magnitude and phase of the complex number  $-1 + j4$  ?

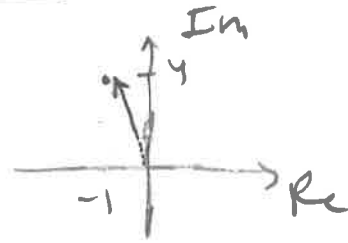a) magnitude or amplitude = \_\_\_\_\_ (not in dB)



$$|-1 + j4| = \sqrt{1^2 + 4^2} = \sqrt{17} = 4.1$$

b) Phase or angle = \_\_\_\_\_

$$\phi = \tan^{-1} \frac{4}{1} = 76^\circ$$

$$\theta = 180^\circ - 76^\circ = 104^\circ$$



3: For the signal  $v(t) = (0.8 \text{ V})\cos(1000t)$  :  $V(t) \rightarrow 0.8 \text{ V}_p$

a) What is the peak-to-peak voltage of this waveform? \_\_\_\_\_

$$2(0.8 \text{ V}) = 1.6 \text{ V}_{p-p}$$


b) What is the rms voltage for this waveform? \_\_\_\_\_

$$r_{ms} = \frac{0.8 \text{ V}}{\sqrt{2}} = 0.566 \text{ V}$$

6 pts

4. Find the transfer function  $H(j\omega) = V_o(j\omega)/V_{in}(j\omega)$  for the circuit below. (The answer should be in the form of a ratio of two complex expressions like 'a + jb', where a and/or b may be a function of  $\omega$ .)

$H(j\omega) =$  \_\_\_\_\_

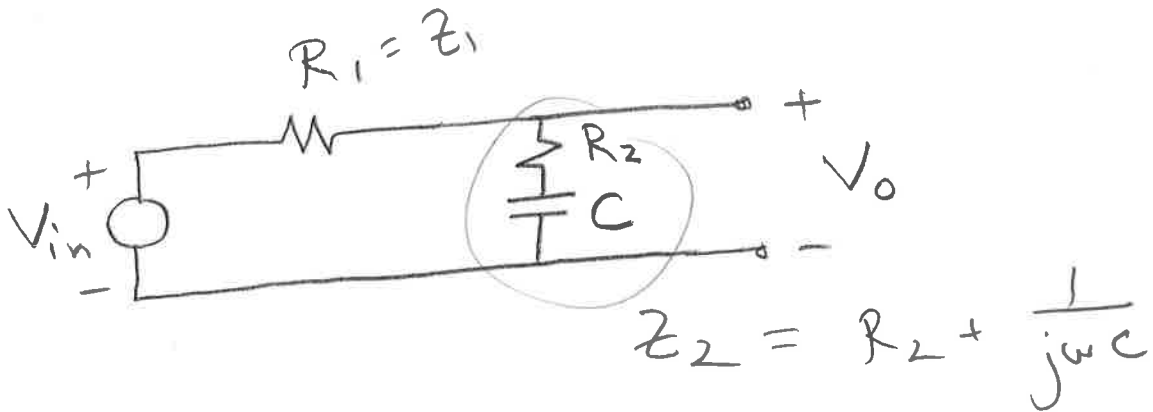

$$\begin{aligned} \frac{V_o}{V_{in}} &= \frac{Z_2}{Z_1 + Z_2} \\ &= \frac{R_2 + \frac{1}{j\omega C}}{R_1 + R_2 + \frac{1}{j\omega C}} \quad \begin{matrix} \nearrow j\omega C \\ \nearrow j\omega C \end{matrix} \\ &= \frac{j\omega R_2 C + 1}{(R_1 + R_2)j\omega C + 1} \end{aligned}$$

9 pts


5. A function generator in our lab has generated a voltage signal  $v(t)$ . That signal is shown below, as it appears on an oscilloscope in our lab. This voltage can be expressed in the form :

$$v(t) = A + B\sin(2\pi ft)$$

What are A, B and f ?

NOTE: Scope settings are: 1 V / division on the vertical scale and 0.5 ms / division on the horizontal scale. Ground = 0 V is marked on the left.
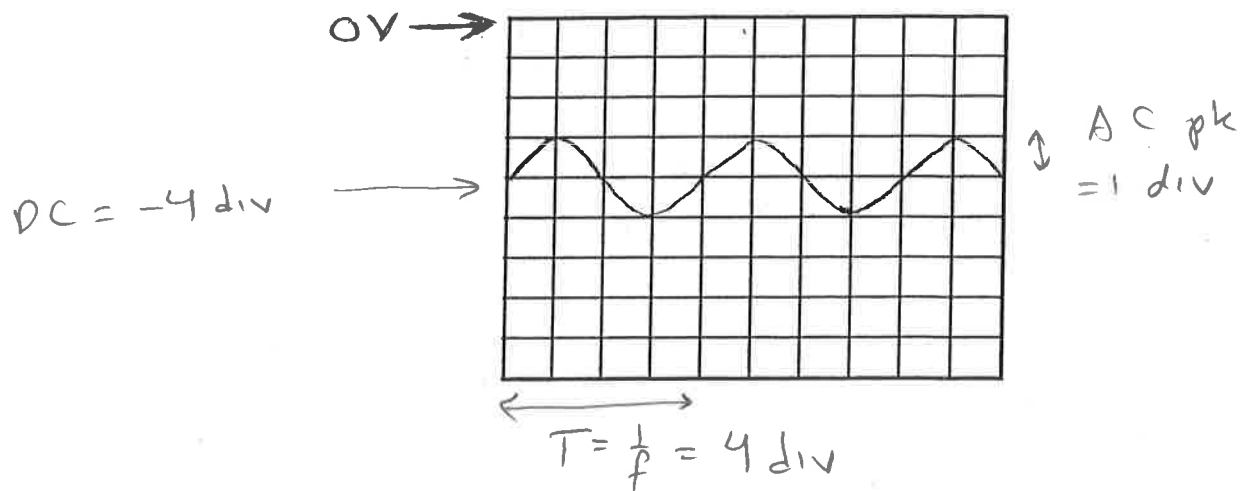
$$A = \underline{-4 \text{ V}} \quad B = \underline{1 \text{ V}} \quad f = \underline{500 \text{ Hz}}$$




$$T = \frac{1}{f} = 4 \text{ div} \times 0.5 \text{ ms/div} = 2 \text{ ms} \Rightarrow f = \frac{1}{T} = 500 \text{ Hz}$$

$$A = DC = -4 \text{ div} \times 1 \text{ V/div} = -4 \text{ V}$$

$$B = \text{pk AC} = 1 \text{ div} \times 1 \text{ V/div} = 1 \text{ V}$$

9 pts

6. a) Draw the approximate Bode magnitude (or amplitude) plot [  $|H|$  in dB vs.  $\omega$  on a log scale ] for the transfer function  $H(s) = \frac{s+10}{s}$ . (Set  $s = j\omega$ .) (A Bode plot using only straight-line segments is acceptable here.)

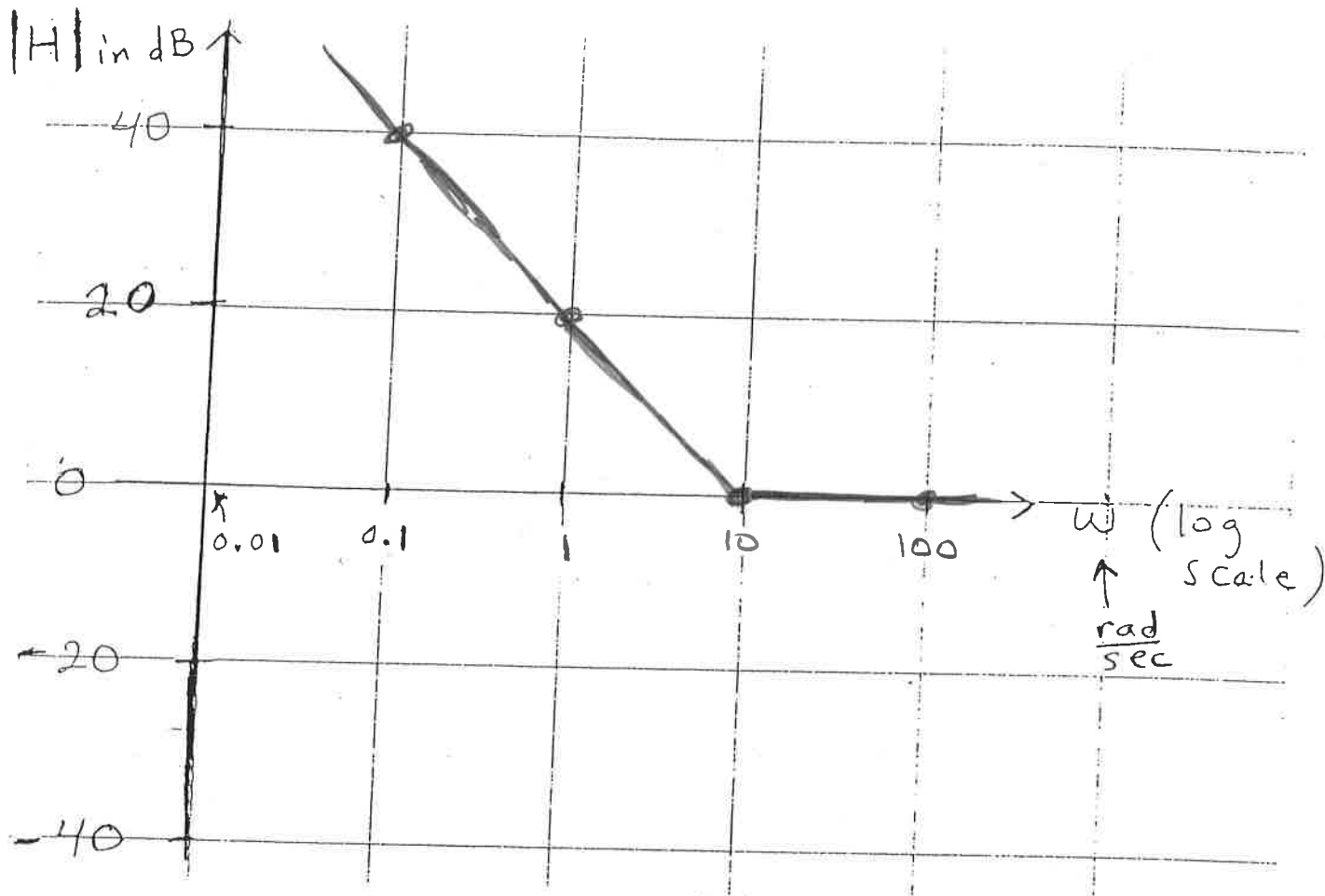

$$H(j\omega) = \frac{10(1 + j\frac{\omega}{10})}{j\omega}$$

$$\begin{aligned} \rightarrow 20 \log |H| &= 20 \log 10 + 20 \log |1 + j\frac{\omega}{10}| \\ &\quad - 20 \log \omega \end{aligned}$$

Blank page

①

$$20 \log 10$$

20dB

$\omega$

②

$$20 \log \left| 1 + j \frac{\omega}{10} \right|$$

20dB

0dB

10

20dB/dec

$\omega$

③

$$-20 \log \omega$$

20dB

-20dB

0.1

1

10

100

$\omega$




9 pts

6 (continued)

$$\frac{10(\frac{s}{10} + 1)}{s}$$

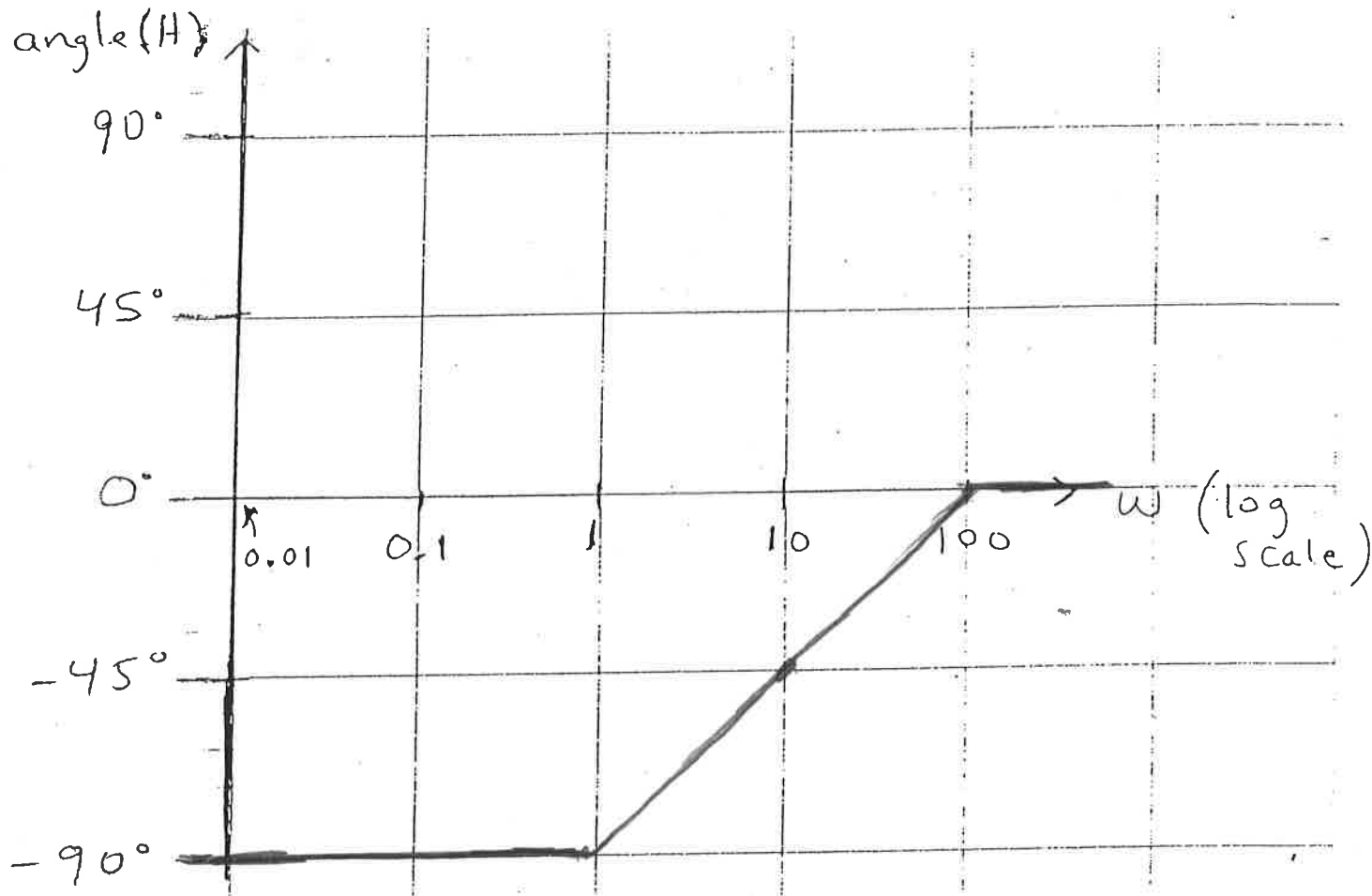b) Draw the approximate Bode phase (or angle) plot [ angle(H) vs.  $\omega$  on a log scale ] for the transfer function  $H(s) = \frac{s+10}{s}$ . (Set  $s = j\omega$ .) (A Bode plot using only straight-line segments is acceptable here.)



$$\text{angle } H = \text{angle } 1.0 + \text{angle}\left(1 + j\frac{\omega}{10}\right) - \text{angle}(j\omega)$$


$$= 0^\circ + \text{tan}^{-1} \frac{\omega}{10} - 90^\circ$$

↑


ignore

Blank page

(A)

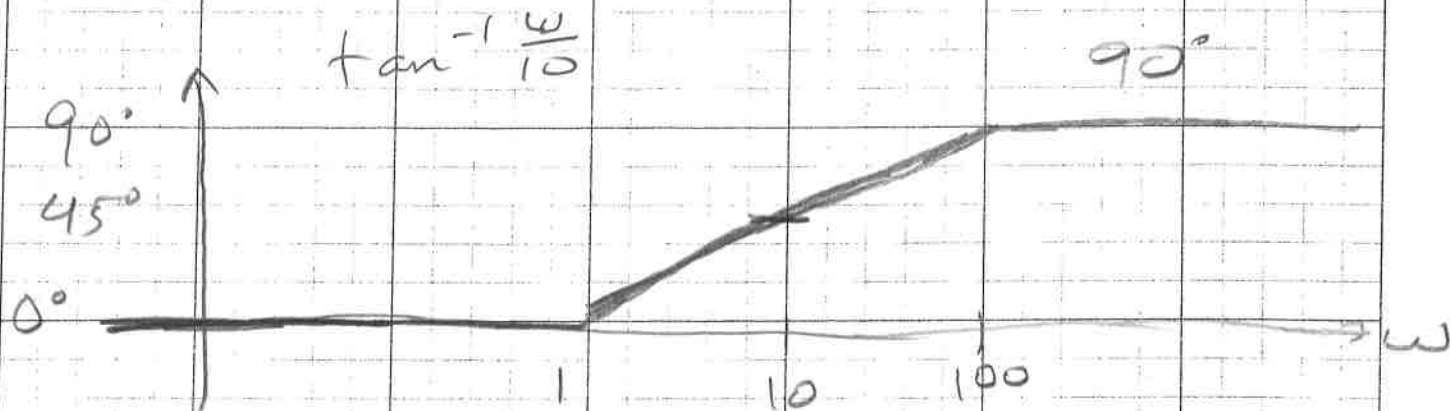

(B)

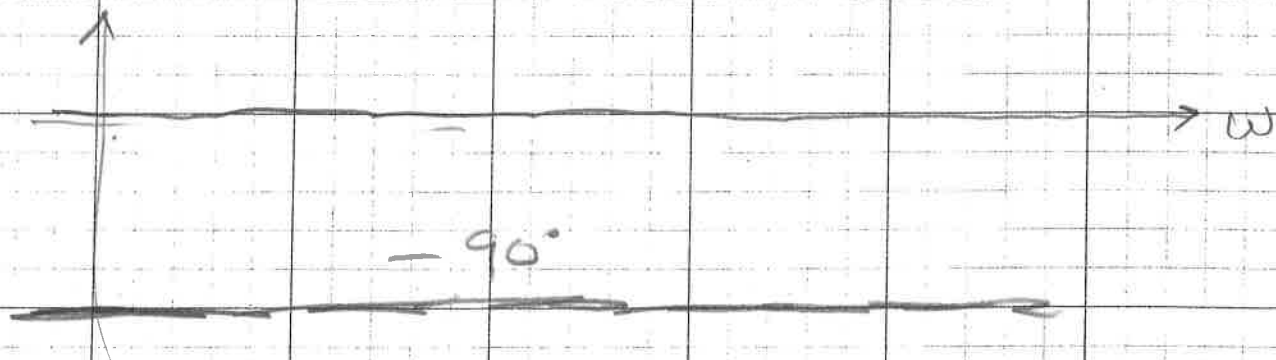


(8 pts)

7. In the circuits below, assume the op amp is ideal.

- a) For the circuit below, what is  $V_o / V_{in}$ ? [Write an expression that is a function of  $L$ ,  $R$  and  $\omega$ .]


$V_o / V_{in} =$  \_\_\_\_\_

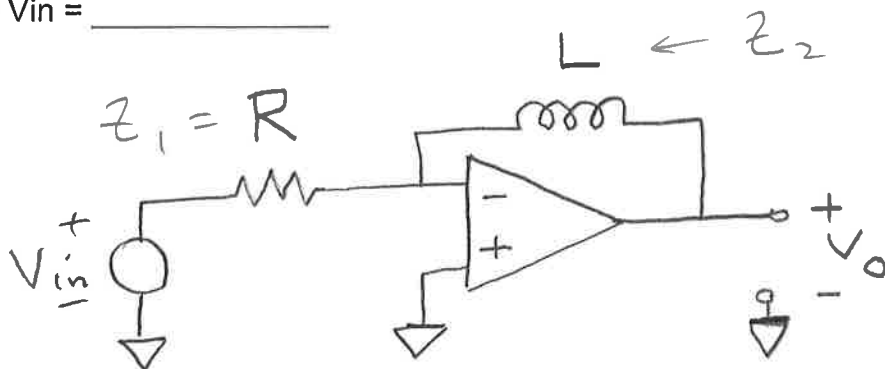

$$\frac{V_o}{V_{in}} = - \frac{z_2}{z_1} = - \frac{j\omega L}{R}$$

- b) For the circuit below, what is the output voltage,  $V_o$ ? (The current source and voltage source are DC sources.)

$V_o =$  \_\_\_\_\_

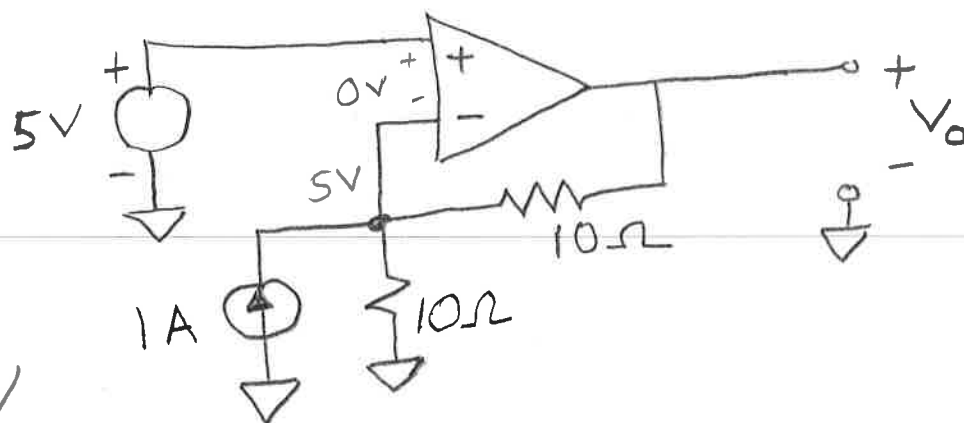

$$V_e = 0V$$

$$\Rightarrow V_+ = 5V$$

$$\text{KCL at } v_- : 1A = \frac{5V}{10\Omega} + \frac{5V - V_o}{10\Omega}$$

$$\Rightarrow \underline{V_o = 0V}$$