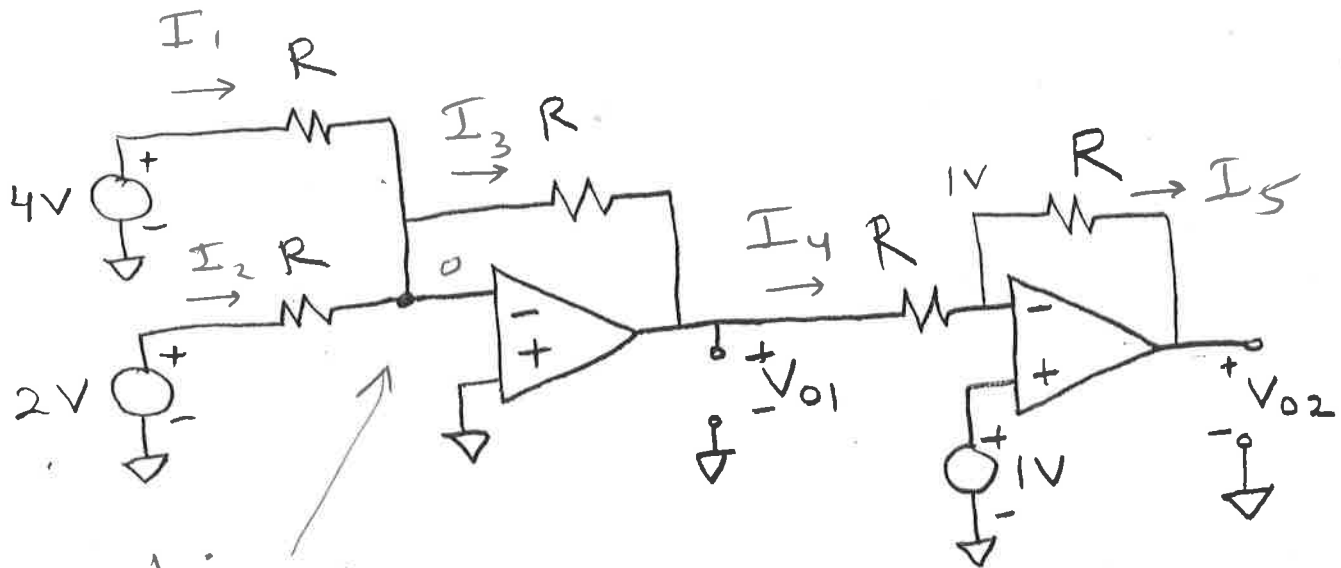


1. For the circuit below, what are the opamp output voltages, V_{O1} and V_{O2} ? (note: the voltage sources are generating DC voltages.) Assume the op amp is ideal.

$V_{O1} =$ _____

$V_{O2} =$ _____



op amp 1:

$$I_1 + I_2 = I_3$$

$$\frac{4-0}{R} + \frac{2-0}{R} = \frac{0-V_{O1}}{R}$$

$$\Rightarrow 4 + 2 = -V_{O1} \Rightarrow \underline{V_{O1} = -6V}$$

op amp 2:

$$\frac{V_{O1}-1}{R} = I_4 = I_5 = \frac{1-V_{O2}}{R}$$


$$\Rightarrow -6-1 = 1-V_{O2}$$

$$\underline{V_{O2} = 8V}$$

2. What is the s-domain transfer function $H(s) = V_o/V_{in}$ for the circuit below?

Assume the op amps are ideal. (Your answer should be in the form $N(s)/D(s)$, where $N(s)$ and $D(s)$ are polynomials in s .)

$H(s) =$ _____

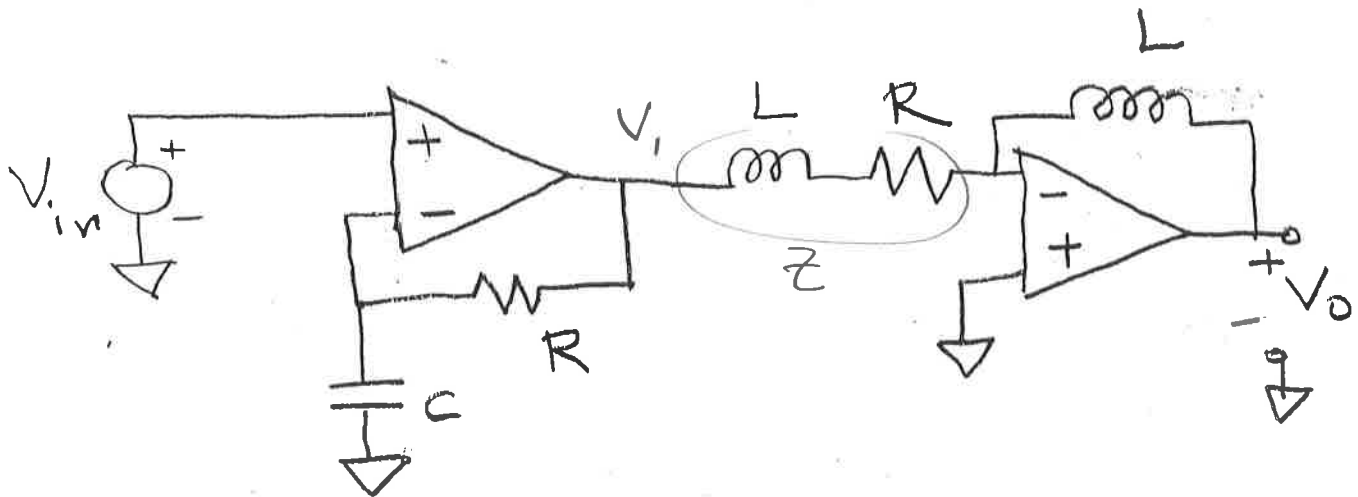

$$\frac{V_1}{V_{in}} = 1 + \frac{R}{\frac{1}{sC}} = 1 + sRC$$

$$\frac{V_o}{V_1} = - \frac{sL}{Z} = - \frac{sL}{R + sL}$$


$$\frac{V_o}{V_{in}} = \frac{V_o}{V_1} \cdot \frac{V_1}{V_{in}} = - \frac{sL}{R + sL} (1 + sRC)$$

$$= - \frac{sL + s^2 LRC}{R + sL}$$

3. The circuit below uses an opamp that is NOT ideal. Assume that the op amp has a finite gain-bandwidth product (or unity-gain frequency) but is otherwise ideal. The opamp has a gain-bandwidth product of 100 MHz.

In the feedback circuit shown below, what value of R_2 will give a circuit with a bandwidth of 1 MHz?

$R_2 =$ _____

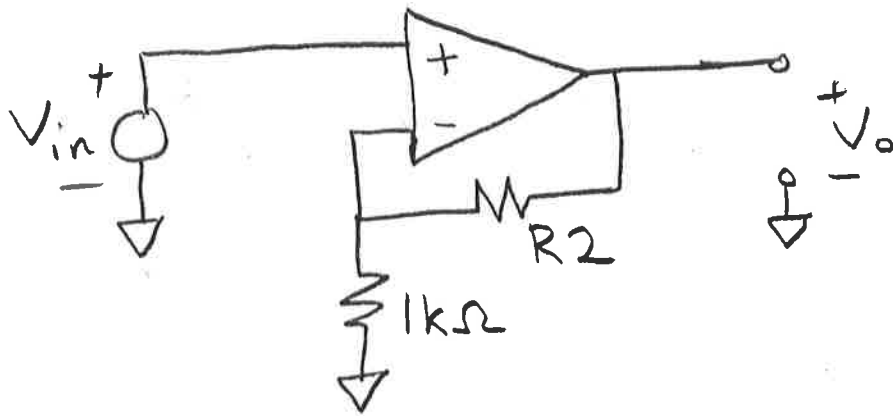

$$\text{gain} \times \text{bw} = 100 \text{ MHz}$$

$$\Rightarrow \text{gain} \times 1 \text{ MHz} = 100 \text{ MHz}$$

$$\text{so want gain} = 100$$

$$\text{gain} = 1 + \frac{R_2}{1k\Omega} = 100$$

$$R_2 = 99k\Omega$$

4. a) Convert the decimal number 29 (or 29_{10}) to a 6-bit 2's complement binary number.

Binary number = _____

base 10	$\div 2$	Quot.	Remainder
29	$29/2$	14	1
14	$14/2$	7	0
7	$7/2$	3	1
3	$3/2$	1	1
1	$1/2$	0	1

unsigned = 11101

2's comp = 011101

b) Convert the 2's complement binary number 01110.01 to a base 10 number.

Base 10 number = _____

$$\begin{array}{c} 01110.01 \\ \downarrow \quad \searrow \quad \searrow \quad \searrow \\ \Rightarrow 2^3 + 2^2 + 2^1 + 2^{-2} \end{array}$$

$$8 + 4 + 2 + \frac{1}{4}$$

$$\underline{14.25}$$

c) Convert the decimal number -37 (or -37_{10}) to a 2's complement binary number with 7 bits.

Binary number = _____

base 10	$\div 2$	Quot	Remaind.	
37	$37/2$	18	1	
18	$18/2$	9	0	
9	$9/2$	4	1	
4	$4/2$	2	0	
2	$2/2$	1	0	
1	$1/2$	0	1	

$37 \Rightarrow$ unsigned = 100101

2's comp = 0100101

-37 is 2's comp of 0100101

1's comp = 1011010
+1

\Rightarrow 1011011 = -37_{10}

5. a) What is the sum of the 2's complement binary numbers $i=01001$ and $k=11101$? Give the sum in binary form (base 2).

$i+k$ (in 2's-complement binary) = 000110

sign extend →

$$\begin{array}{r}
 001001 \\
 + 11101 \\
 \hline
 000110
 \end{array}$$

ignore

b) Compute the difference ($n - m$) of the 2's-complement binary numbers $n = 00111$ and $m = 01001$

$n - m$ (in 2's-complement binary) = _____

$-m = 2's \text{ comp. of } m: m = 01001$

1's comp = 10110
+ 1

$-m = 10111$

sign extend
↓

$n: 000111$

$-m + 110111$

111110 = $n - m$

6. What is the standard Sum of Products (that is, a sum of minterms) expression for the logic function described by the truth table below?

F = _____

A	B	F
0	0	1
0	1	0
1	0	1
1	1	1

minterm where row has F=1

$\overline{A}\overline{B}$

$A\overline{B}$


$A B$

$$F = \overline{A}\overline{B} + A\overline{B} + A B$$

7. For the logic circuits below, fill in the values for the output F in the truth table.

a)

A	B	F
0	0	0
0	1	1
1	0	0
1	1	1

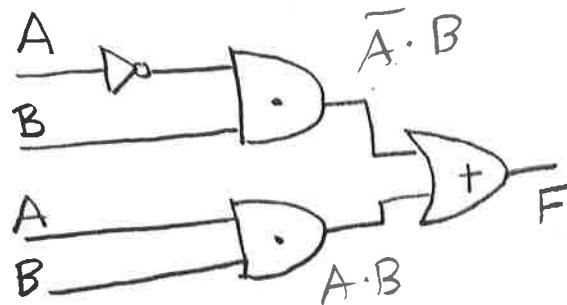


$$F = \bar{A} \cdot B + A \cdot B$$

b)

$$\overline{A \cdot B} \cdot (B + C)$$

A	B	C	F	$\overline{A \cdot B}$	$B + C$
0	0	0	0	1	0
0	0	1	1	1	1
0	1	0	1	1	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	0	1
1	1	1	0	0	1

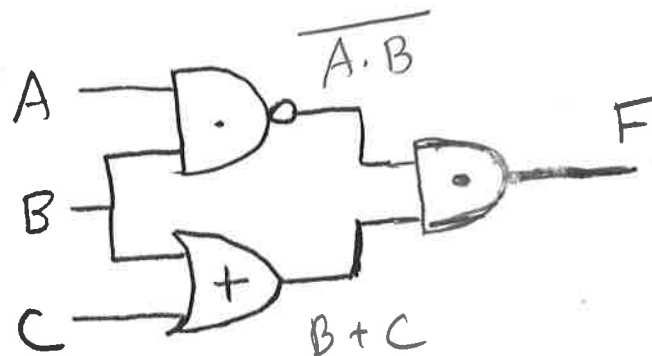

8. Draw a circuit consisting of AND, OR and INVERT logic gates that implements the function below. The inputs to the circuit are A, B and C.

$$F = \overline{A}\overline{B} + AC$$

