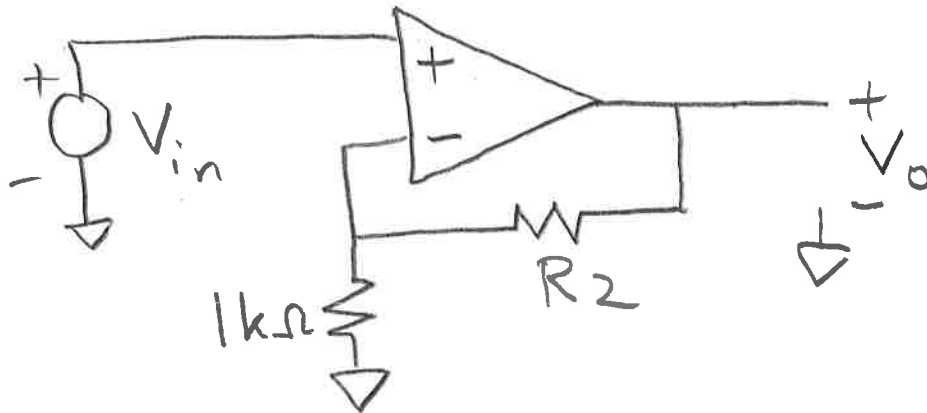


1. a) Select R_2 in the circuit below to give a voltage gain $V_o/V_{in} = 40$.

$R_2 =$ _____



$$\frac{V_o}{V_{in}} = 1 + \frac{R_2}{1k\Omega} = 40$$

$$\frac{R_2}{1k\Omega} = 39 \Rightarrow R_2 = 39k\Omega$$

- b) For the feedback circuit shown above, assume you are using a 741 opamp as in the lab. The 741 opamp has a finite gain-bandwidth product. Assume that the bandwidth (or cutoff frequency) of the circuit in part (a) is 25 kHz when the voltage gain = 40. If you change R_2 to DOUBLE the voltage gain to 80, the bandwidth (or cutoff frequency) of the circuit will


- ☐ increase.
☒ decrease.
☐ not change.

$$\text{gain} \times \text{bw} = \text{constant}$$

$$\text{gain} \uparrow \Rightarrow \text{bw} \downarrow$$

2. Find the s-domain transfer function $H(s) = V_o/V_{in}$ for the circuit below. (Your answer should be in the form $H(s) = N(s)/D(s)$, where $N(s)$ and $D(s)$ are polynomials in 's'.)

$H(s) =$ _____

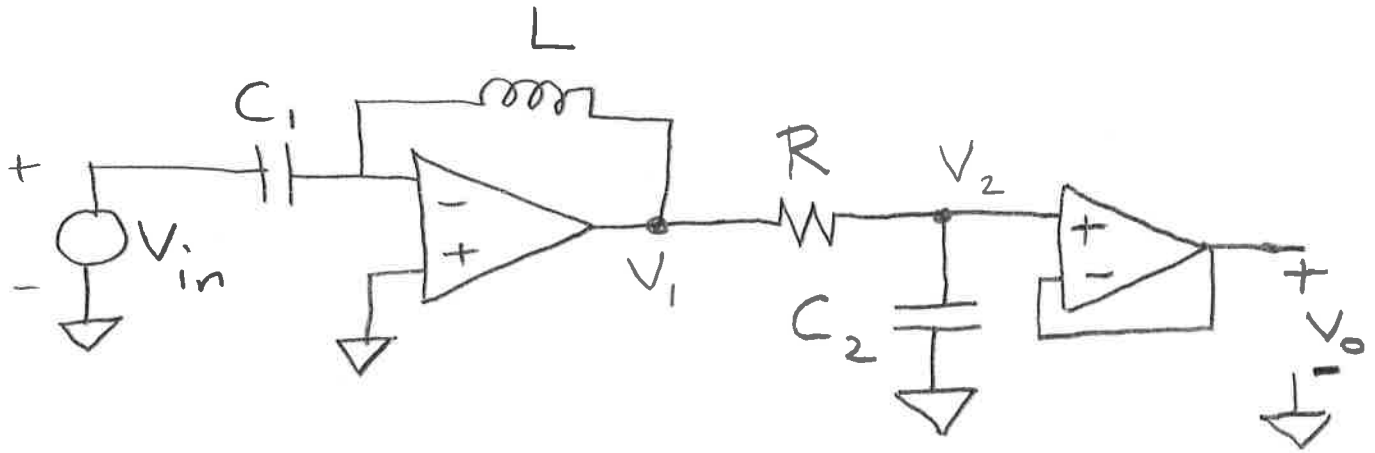

$$\frac{V_1}{V_{in}} = - \frac{sL}{\frac{1}{sC_1}} = -s^2 LC_1$$

$$\frac{V_2}{V_1} = \frac{\frac{1}{sC_2}}{R + \frac{1}{sC_2}} = \frac{1}{sRC_2 + 1}$$

$$\frac{V_o}{V_2} = 1$$

$$\begin{aligned} \Rightarrow \frac{V_o}{V_{in}} &= \frac{V_o}{V_2} \cdot \frac{V_2}{V_1} \cdot \frac{V_1}{V_{in}} = 1 \cdot \frac{1}{sRC_2 + 1} \cdot (-s^2 LC_1) \\ &= - \frac{s^2 LC_1}{sRC_2 + 1} \end{aligned}$$

3. a) Convert the decimal number 22 (or 22_{10}) to a 6-bit binary number.

Binary number = 010110

#	$\div 2$	remainder
22	11	0 = LSB
11	5	1
5	2	1
2	1	0
1	0	1

unsigned = 10110

add sign:

010110

$2^3 \quad 2^1 \quad 2^{-2}$
↓ ↓ ↓

b) Convert the binary number 01010.01 to a base 10 number.

Base 10 number = 10.25

$$1 \cdot 2^3 + 1 \cdot 2^1 + 1 \cdot 2^{-2} = 8 + 2 + 0.25$$

$$= \boxed{10.25}$$

4. a) What is the sum of the 2's complement binary numbers 001101 and 001001. Give the sum in binary form (base 2).

Sum (in base 2) = 0010110


$$\begin{array}{r}
 \swarrow \text{sign extend} \\
 001101 \\
 + 001001 \\
 \hline
 0010110 \leftarrow \text{Sum}
 \end{array}$$

b) What is the 2's-complement of the binary number 00101?

2's-complement = 11011

$$\begin{array}{r}
 00101 \\
 11010 \leftarrow 1's \text{ compl.} \\
 + 1 \\
 \hline
 11011 \leftarrow 2's \text{ compl.}
 \end{array}$$

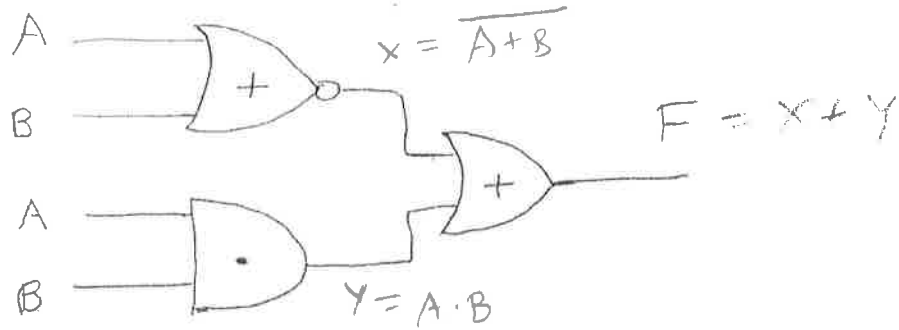5. For the logic circuit below, fill in the values for the output F in the truth table.



A	B	$X + Y$ = F	X	Y
0	0	1	1	0
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1

↑
Answer


6. Write a Sum of Products (a sum of minterms) expression for the logic function described by the truth table below.

$$F = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C$$

A	B	C	F	minterm
0	0	0	0	
0	0	1	1	$\bar{A}\bar{B}C$
0	1	0	0	
0	1	1	1	$\bar{A}BC$
1	0	0	0	
1	0	1	1	$A\bar{B}C$
1	1	0	0	
1	1	1	0	

7. For the logic function below, draw a logic circuit that implements that logic function, using AND, OR and INVERT gates.

$$F = A \cdot B + \bar{B} \cdot C$$

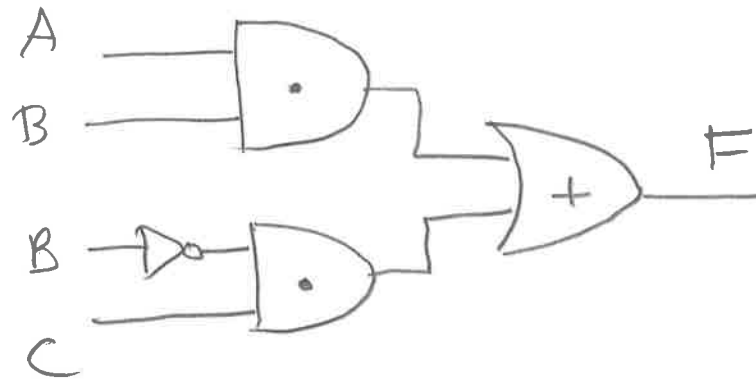

8. Compute the difference $n - m$ of the binary numbers $n = 1011$ and $m = 0011$.
Give the answer in binary form (in 2's complement form).

$$n - m = \underline{11000}$$

add $-m$ to n . $-m = 2$'s compl. of m

$$m = 0011 \Rightarrow \begin{array}{r} 1100 \\ + 1 \\ \hline 1101 \end{array} \begin{array}{l} = 1's \text{ compl.} \\ \\ = -m \end{array}$$

sign extend

$$\begin{array}{r} \swarrow 111 \\ 11011 \quad n \\ + 11101 \quad -m \\ \hline *11000 \end{array}$$



ignore carry
on left