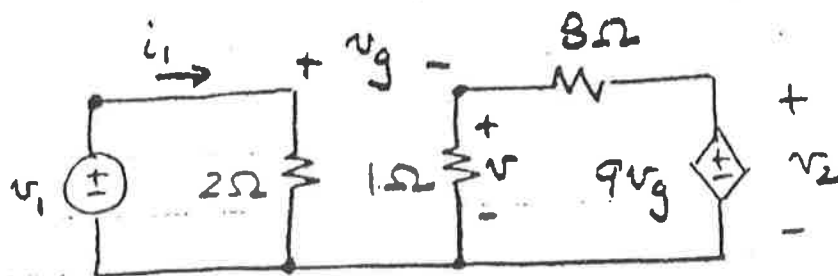


1.47



(a) By KVL, $v_1 = 2i_1$

$$\therefore R_{eq} = \frac{v_1}{i_1} = \underline{\underline{2\Omega}}$$


(b) By voltage division, $v = \frac{1}{1+8} (9v_g) = \underline{\underline{v_g}}$

(c) By KVL, $v_1 = v_g + v = v_g + v_g = 2v_g$

$$\therefore v_g = \frac{1}{2} v_1$$

Thus, $v_2 = 9v_g = 9\left(\frac{1}{2}v_1\right) = \frac{9}{2}v_1 = \underline{\underline{4.5v_1}}$

2.6

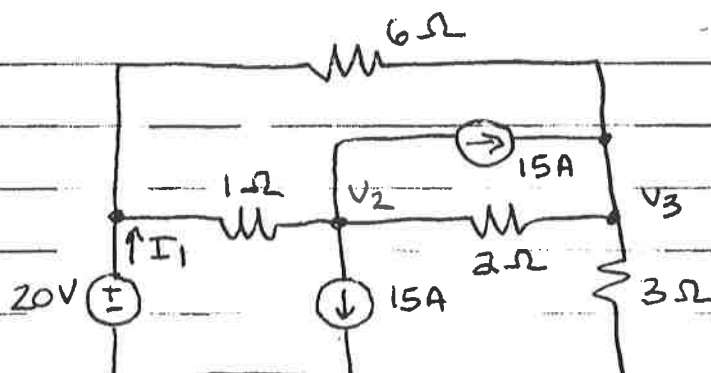

$$V_1 = 20 \text{ volts}$$

$$\text{Node } V_1 : I_1 = \frac{20 - V_2}{1} + \frac{20 - V_3}{6}$$

$$\text{Node } V_2 : \frac{V_2 - 20}{1} + 30 + \frac{V_2 - V_3}{2} = 0$$

$$\text{Node } V_3 : \frac{V_3 - V_2}{2} + \frac{V_3}{3} - 15 + \frac{V_3 - 20}{6} = 0$$


Rewrite

$$\begin{bmatrix} 1 & 1 & \frac{1}{6} \\ 0 & 1.5 & -\frac{1}{2} \\ 0 & -\frac{1}{2} & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \frac{70}{3} \\ -10 \\ \frac{55}{3} \end{bmatrix}$$

$$V_2 = \frac{\begin{vmatrix} 1 & \frac{70}{3} & \frac{1}{6} \\ 0 & -10 & -\frac{1}{2} \\ 0 & \frac{55}{3} & 1 \end{vmatrix}}{\begin{vmatrix} 1 & 1 & \frac{1}{6} \\ 0 & 1.5 & -\frac{1}{2} \\ 0 & -\frac{1}{2} & 1 \end{vmatrix}} = \frac{-10 - \left(\frac{55}{3}\right)\left(-\frac{1}{2}\right)}{1.5 - \left(-\frac{1}{2}\right)\left(-\frac{1}{2}\right)} = -\frac{2}{3} \text{ volts}$$

$$V_3 = \frac{\begin{vmatrix} 1 & 1 & \frac{70}{3} \\ 0 & 1.5 & -10 \\ 0 & -\frac{1}{2} & \frac{55}{3} \end{vmatrix}}{1.5 - \frac{1}{4}} = \frac{\frac{3}{2} \frac{55}{3} - \left(-\frac{1}{2}\right)(-10)}{\frac{5}{4}} = 18 \text{ volts}$$

2.11

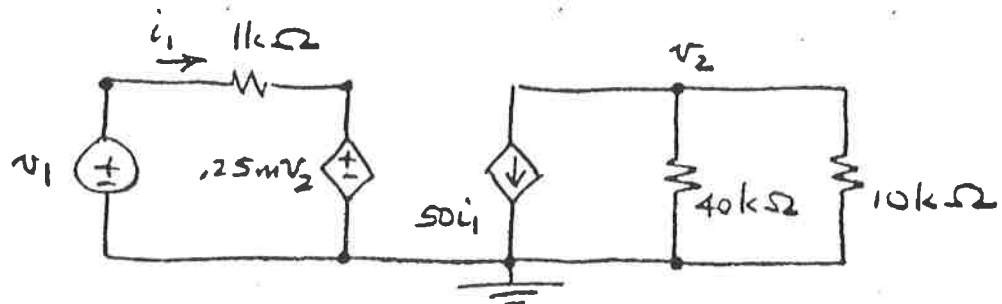

(a)

By Ohm's law, $i_1 = \frac{v_1 - 0.25mV_2}{1k}$

By KCL at node v_2 ,

$$50i_1 + \frac{v_2}{40k} + \frac{v_2}{10k} = 0$$

$$50 \frac{v_1 - 0.25mV_2}{1k} + \frac{v_2}{40k} + \frac{v_2}{10k} = 0$$

$$2k(v_1 - 0.25mV_2) + v_2 + 4v_2 = 0$$

$$2kV_1 - 0.5V_2 + v_2 + 4v_2 = 0$$

$$2kV_1 + 4.5V_2 = 0$$

$$4.5V_2 = -2kV_1$$


$$\frac{V_2}{V_1} = \frac{-2k}{4.5} = \underline{\underline{-444}}$$

(b) From above,

$$i_1 = \frac{v_1 - 0.25m\left(\frac{-2k}{4.5}v_1\right)}{1k}$$

$$i_1 = \frac{v_1 + \frac{0.5}{4.5}v_1}{1k} = \frac{5}{4.5k}v_1$$
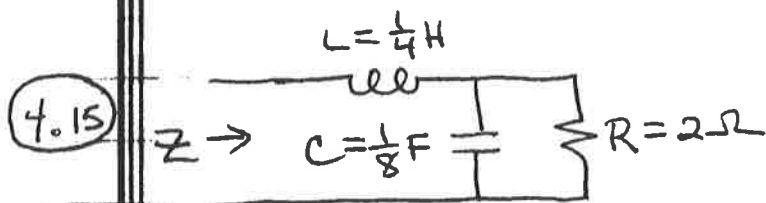
$$\therefore R_{in} = \frac{v_1}{i_1} = \frac{4.5k}{5} = \underline{\underline{900\Omega}}$$



$$Z = j\omega L + \frac{R \left(\frac{1}{j\omega C} \right)}{R + \frac{1}{j\omega C}} = j\omega L + \frac{R}{(1 + j\omega CR)} \cdot \frac{(1 - j\omega CR)}{(1 - j\omega CR)}$$

$$= j\omega L + \frac{R - j\omega CR^2}{1 + \omega^2 C^2 R^2} = \frac{j\omega L + j\omega^3 LC^2 R^2 + R - j\omega CR^2}{1 + \omega^2 C^2 R^2}$$

$$= \frac{R + j\omega (L + \omega^2 LC^2 R^2 - CR^2)}{1 + \omega^2 C^2 R^2}$$

$$= \frac{2 + j\omega \left(\frac{1}{4} + \omega^2 \frac{1}{4} \left(\frac{1}{8} \right)^2 2^2 - \frac{1}{8} 2^2 \right)}{1 + \omega^2 \left(\frac{1}{8} \right)^2 2^2}$$

$$= \frac{2 + j\omega \left(-\frac{1}{4} + \frac{\omega^2}{64} \right)}{1 + \omega^2 \left(\frac{1}{8} \right)^2 2^2}$$


$$= \frac{2 + \frac{j\omega}{4} \left(-1 + \frac{\omega^2}{16} \right)}{1 + \frac{\omega^2}{16}}$$

$$= \frac{2 + \frac{j\omega}{4} \left(\frac{\omega^2 - 16}{16} \right)}{\frac{\omega^2 + 16}{16}}$$

$$= \frac{32 + \frac{j\omega}{4} (\omega^2 - 16)}{\omega^2 + 16}$$

$$= \frac{32}{\omega^2 + 16} + \frac{j\omega (\omega^2 - 16)}{4 (\omega^2 + 16)}$$

(4.18)

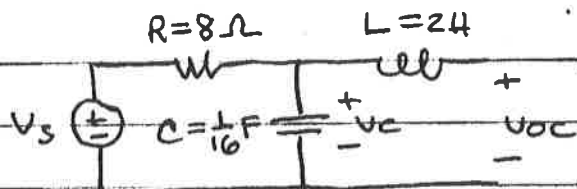Find V_{oc} 

$V_{oc} = V_c$ because the current in L is zero


$$\frac{V_{oc}}{V_s} = \frac{V_c}{V_s} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega CR}$$

Since $V_s(t) = 4 \cos(2t - 60^\circ) V$, $\omega = 2 \frac{r}{s}$

$$\frac{V_{oc}}{V_s} = \frac{1}{1 + j(2)\frac{1}{16}(8)} = \frac{1}{1 + j1} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$V_{oc} = \frac{1}{\sqrt{2}} \angle -45^\circ V_s$$


$$V_{oc} = \frac{1}{\sqrt{2}} \angle -45^\circ (4 \angle -60^\circ) = \boxed{2\sqrt{2} \angle -105^\circ}$$

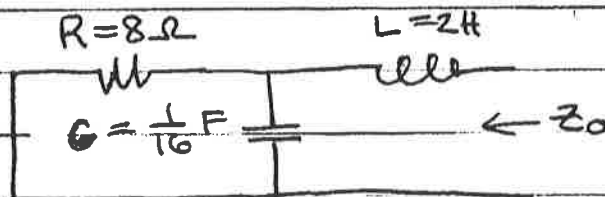Find Z_o 

$$Z_o = j\omega L + \frac{R \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R + j\omega(L + \omega^2 LC^2 R^2 - CR^2)}{1 + \omega^2 C^2 R^2} \quad \text{From Prob. 4.15}$$

$$= \frac{8 + j(2)(2 + 4 \cdot 2 \cdot \frac{1}{256} \cdot 64 - \frac{1}{16} \cdot 64)}{1 + 4 \frac{1}{256} \cdot 64}$$

$$= \frac{8 + j(2)(2 + 2 - 4)}{1 + 1} = \boxed{4 \Omega}$$

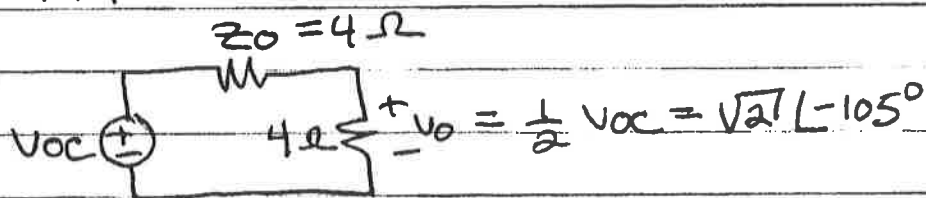Find $V_o(t)$ 

$$\text{so } \boxed{V_o(t) = \sqrt{2} \cos(2t - 105^\circ) \text{ volts}}$$