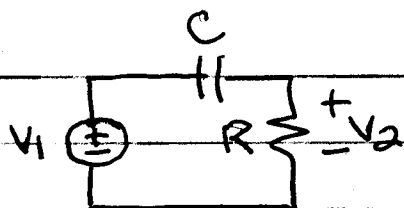



5.1




$$\frac{V_2}{V_1} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega CR}{1 + j\omega CR}$$

$$\begin{aligned} \text{ang} \left(\frac{V_2}{V_1} \right) &= \text{ang}(j\omega CR) - \text{ang}(1 + j\omega CR) \\ &= 90^\circ - \arctan(\omega CR) \end{aligned}$$

ω	$\text{ang} \left(\frac{V_2}{V_1} \right)$
0	90°
$\frac{1}{RC}$	$90^\circ - \arctan(1) = 90^\circ - 45^\circ = 45^\circ$
$\frac{2}{RC}$	$90^\circ - \arctan(2) = 90^\circ - 63^\circ = 27^\circ$
$\frac{3}{RC}$	$90^\circ - \arctan(3) = 90^\circ - 72^\circ = 18^\circ$
$\frac{4}{RC}$	$90^\circ - \arctan(4) = 90^\circ - 76^\circ = 14^\circ$
∞	0°

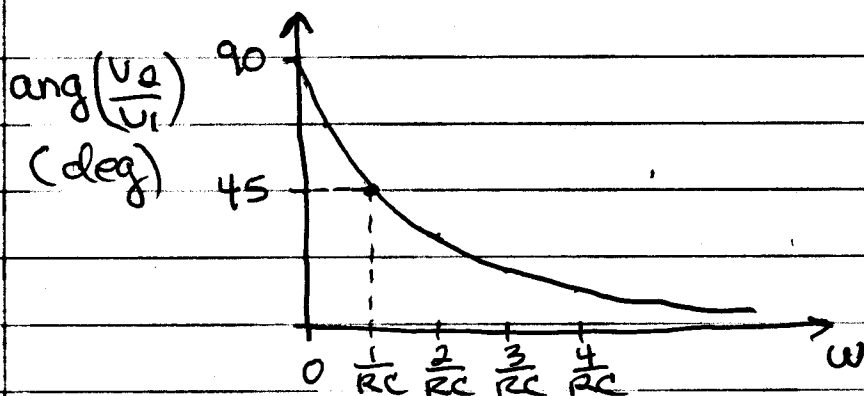

5.5

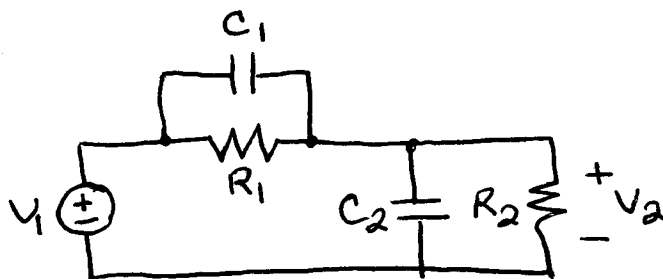

$$\frac{V_2}{V_1} = \frac{Z_2}{Z_1 + Z_2} \quad \text{where } Z_1 = \frac{R_1 \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} = \frac{R_1}{1 + j\omega C_1 R_1}$$



$$Z_2 = \frac{R_2 \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{1 + j\omega C_2 R_2}$$

$$\frac{V_2}{V_1} = \frac{\frac{R_2}{1 + j\omega C_2 R_2}}{\frac{R_1}{1 + j\omega C_1 R_1} + \frac{R_2}{1 + j\omega C_2 R_2}}$$

$$\frac{V_2}{V_1} = \frac{\frac{R_2}{1 + j\omega C_2 R_2}}{\frac{R_1(1 + j\omega C_2 R_2) + R_2(1 + j\omega C_1 R_1)}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_2)}} = \frac{R_2(1 + j\omega C_1 R_1)}{R_1 + R_2 + j\omega R_1 R_2 (C_1 + C_2)}$$

$$= \frac{R_2(1 + j\omega C_1 R_1)}{(R_1 + R_2) \left[1 + j\omega \frac{R_1 R_2}{R_1 + R_2} (C_1 + C_2) \right]} \quad \begin{matrix} R_1 = R_2 = R \\ C_1 = C_2 = C \end{matrix}$$
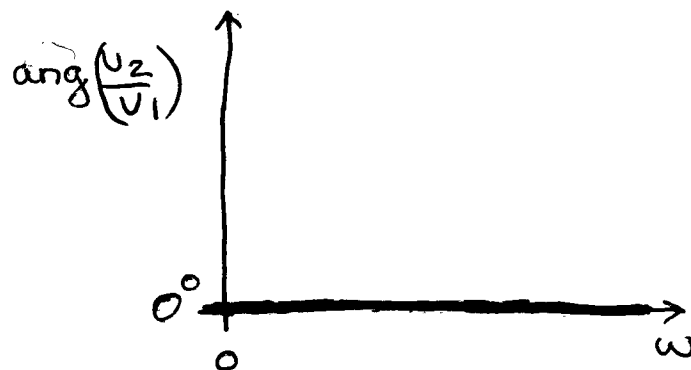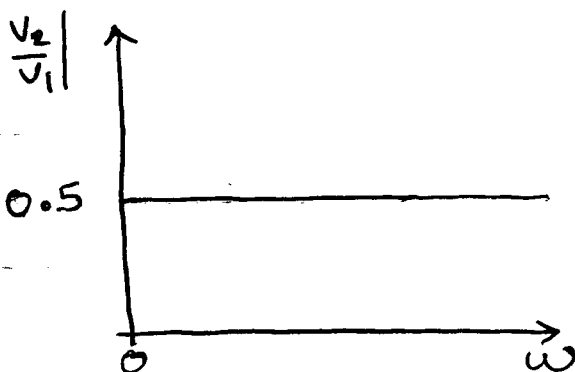
$$\frac{R}{2R} \frac{(1 + j\omega CR)}{\left[1 + j\omega \frac{R^2}{2R} (2C) \right]} = \frac{1}{2} \frac{(1 + j\omega CR)}{(1 + j\omega CR)} = \frac{1}{2}$$



5.11


$$H(j\omega) = \frac{a}{a + j\omega} = \frac{1}{1 + j\frac{\omega}{a}} \quad \text{where } a > 0$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{a}\right)^2}} \quad \text{ang}[H(j\omega)] = -\tan^{-1}\left(\frac{\omega}{a}\right)$$

For small ω , $|H(j\omega)| \approx 1 \rightarrow 20\log_{10}|H(j\omega)| \approx 0\text{dB}$

For large ω , $|H(j\omega)| \approx \frac{1}{\omega/a} = \frac{a}{\omega}$

$$\rightarrow 20\log_{10}|H(j\omega)| = 20\log_{10}\left(\frac{a}{\omega}\right) = -20\log_{10}\left(\frac{\omega}{a}\right)$$

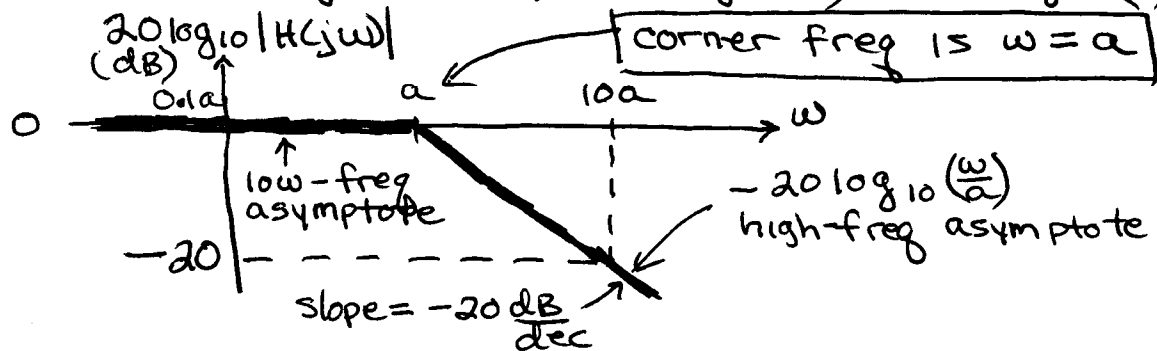


$$\text{ang}[H(j\omega)] = -\tan^{-1}\left(\frac{\omega}{a}\right)$$

For small ω , $\text{ang}[H(j\omega)] \approx 0^\circ$

For $\omega = a$, $\text{ang}[H(j\omega)] = -\tan^{-1}(1) = -45^\circ$

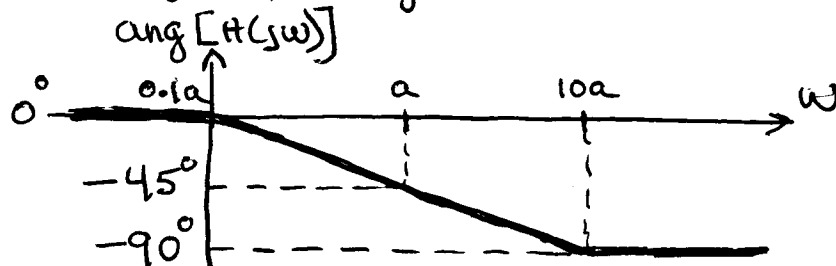
For large ω , $\text{ang}[H(j\omega)] \approx -90^\circ$




This is a low-pass filter.

5.13

$$H_1(j\omega) = \frac{1}{1+j\omega} \rightarrow |H_1(j\omega)| = \frac{1}{\sqrt{1+\omega^2}} \quad \text{ang}[H_1(j\omega)] = -\tan^{-1}(\omega)$$

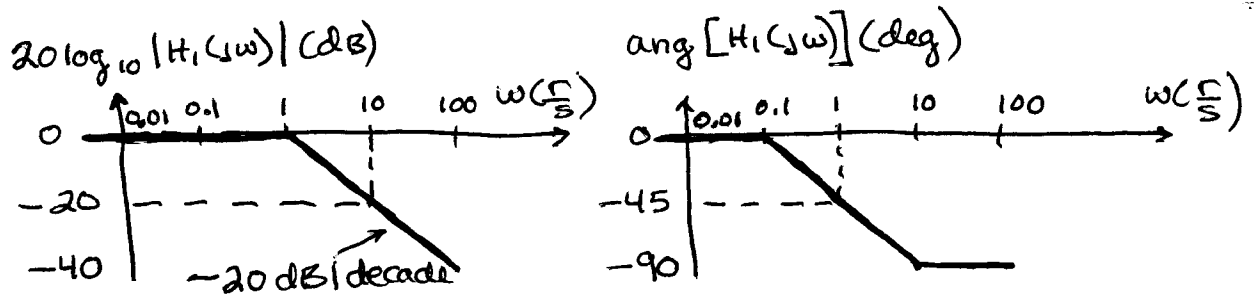

$$H_2(j\omega) = \frac{1}{1+j\omega(10)} \rightarrow |H_2(j\omega)| = \frac{1}{\sqrt{1+100\omega^2}} \quad \text{ang}[H_2(j\omega)] = -\tan^{-1}(10\omega)$$

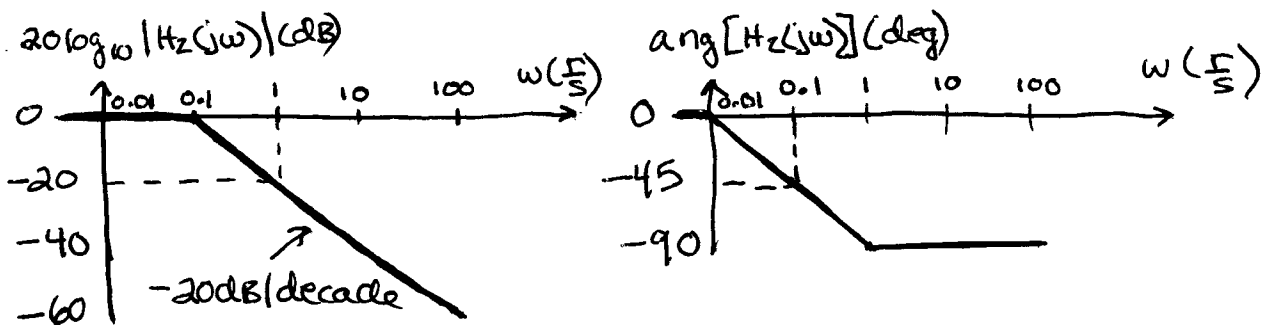

Adding the plots gives:

