


1890 Midterm Sol'n

F'09

1: a) Find the small-signal output resistance R_{out} for the amplifier shown below. Assume all the transistors are forward-active with $I_{C1} = I_{C2} = 1 \text{ mA}$.

$R_{out} = 26 \Omega$

7 pts

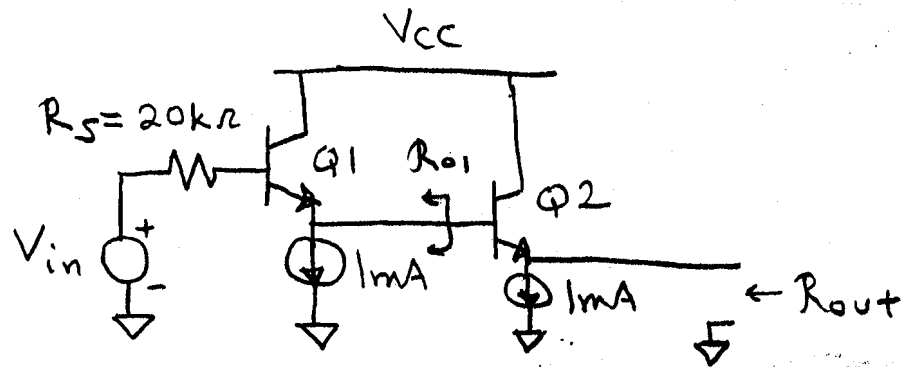

$$R_{out} = \frac{r_{\pi 2} + R_{O1}}{\beta + 1} = \frac{5.2k + 124}{201} = 26 \Omega$$

$$R_{O1} = \frac{r_{\pi 1} + R_S}{\beta + 1} = \frac{5.2k + 20k}{201} = 124 \Omega$$

$$r_{\pi 1} = r_{\pi 2} = \frac{\beta V_T}{I_C} = 5.2k \Omega$$

4 pts

b) How does the small-signal output resistance R_{out} change in each case:

i) if R_S decreases: (circle one) $\Rightarrow R_{O1} \downarrow \Rightarrow R_{out} \downarrow$

R_{out} decreases

R_{out} increases

R_{out} doesn't change

ii) if I_{C1} and I_{C2} both increase to 2 mA: (circle one) $\Rightarrow r_{\pi} \downarrow \Rightarrow R_{out} \downarrow$

R_{out} decreases


R_{out} increases

R_{out} doesn't change

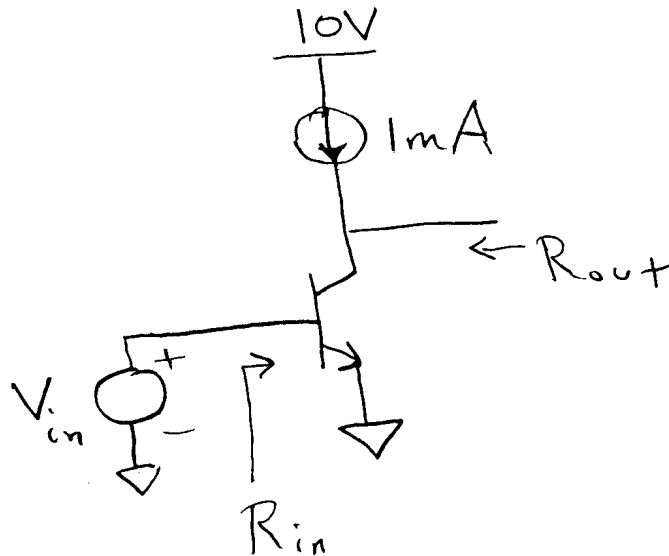2. In the circuit below, R_{in} and R_{out} have been measured in the lab: $R_{in} = 4k$ ohms and $R_{out} = 112k$ ohms. Assuming the transistor is forward active and the DC collector current is 1 mA:

What is β for this transistor? $\beta = \underline{154}$

What is V_A for this transistor? $V_A = \underline{112V}$



$$R_{in} = r_{\pi} = \frac{\beta V_T}{I_c} = \frac{\beta (26mV)}{1mA}$$

" $4k\Omega$

$$\Rightarrow \beta = 154$$

$$R_{out} = r_o = \frac{V_A}{I_c} = \frac{V_A}{1mA}$$

" $112k\Omega$


$$\Rightarrow V_A = 112V$$

3. a) A current source is shown below. All transistors are identical. Assume Q2 is forward active (its collector connects to other circuitry that is not shown). Find the value of I_0 in the model shown.

$$I_0 = \underline{1.36 \text{ mA}}$$

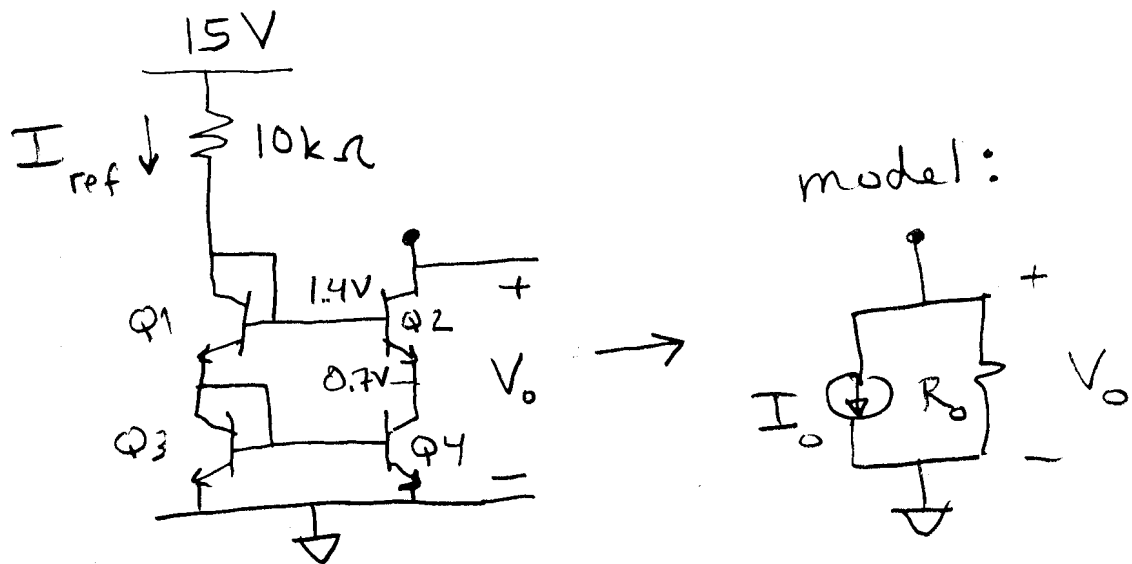b) What is the minimum value of the voltage at the collector of Q2 (V_O) for which Q2 remains forward active?

$$V_{O(\min)} = \underline{0.8 \text{ V}}$$



a) Q3-Q4 = current mirror

$$\Rightarrow I_{C3} = I_{C4} = I_{C2} = I_0 \text{ (ignoring } r_o)$$

$$\begin{aligned} I_{C3} = I_{ref} &= \frac{15\text{V} - 2V_{BE}}{10\text{k}\Omega} \\ &\approx \frac{15\text{V} - 2(0.7\text{V})}{10\text{k}\Omega} \\ &= 1.36\text{mA} \end{aligned}$$


$$\begin{aligned} b) \quad V_E(Q2) &= V_{BE1} + V_{BE3} - V_{BE2} \approx 0.7\text{V} \\ V_{O(\min)} &\approx 0.7\text{V} + V_{CE\text{SAT}}(Q2) = 0.8\text{V} \end{aligned}$$

12 pts


4. Find the DM and CM gains for the differential amplifier below. Assume all transistors are forward active; Q1 and Q2 are identical; and $I_{C1}(D.C.) = I_{C2}(D.C.) = 1 \text{ mA}$. FOR THIS PROBLEM ONLY, ignore the transistor's output resistance (that is, take $V_A = \infty$).

a) What is the Differential Mode (DM) gain? $V_{od}/V_{id} = \underline{-7.5}$

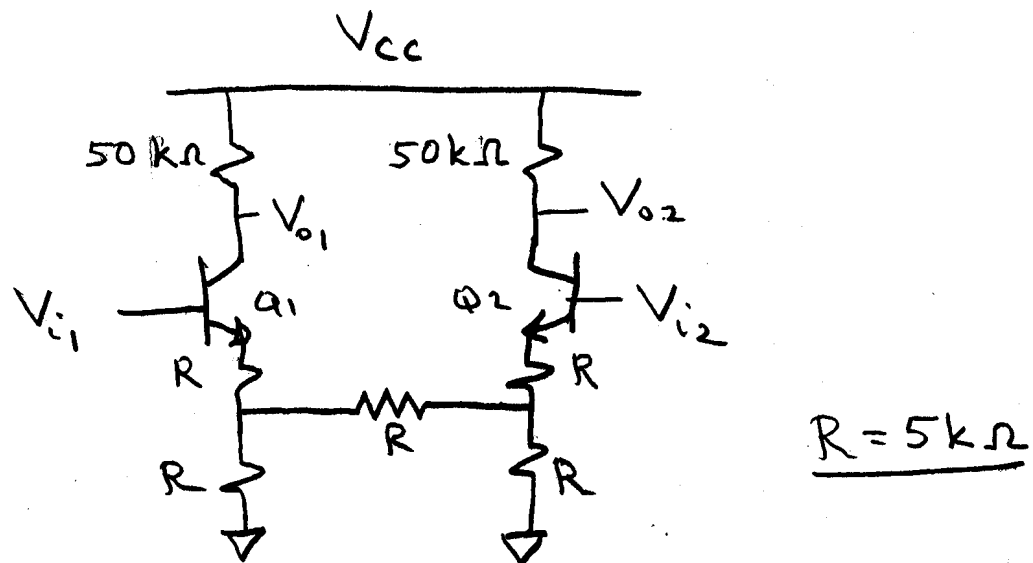b) What is the Common Mode (CM) gain? $V_{oc}/V_{ic} = \underline{-5}$




DM $\frac{1}{2}$ ckt :

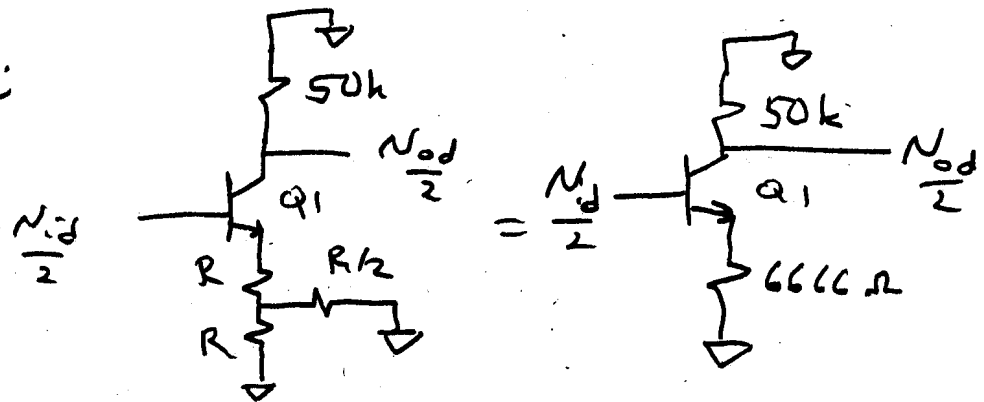

$$\begin{aligned} \frac{N_{od}}{N_{id}} &= a_{DM} \approx -G_{m1}(50k) = \frac{-g_{m1}}{1 + g_{m1} \cdot 6666} \cdot (50k) \approx \\ &= -\frac{\frac{1}{26}}{1 + \frac{6666}{26}} 50k = -7.5 \end{aligned}$$

Extra work space for Problem 4.

cm $\frac{1}{2}$ ckt

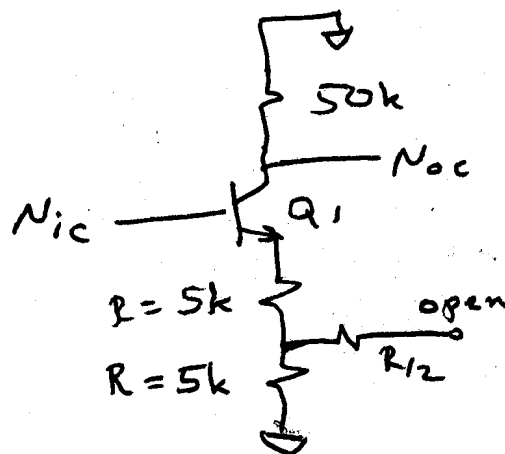


$$a_{cm} = \frac{N_{oc}}{N_{ic}} = -G_{m1}(50k) = \frac{-g_{m1}}{1+g_{m1}(10k)}(50k)$$

$$= -5$$

5. A class A output stage is shown below.

a) What is the positive output swing limit? $V_{out(max)} = \underline{9.9V}$

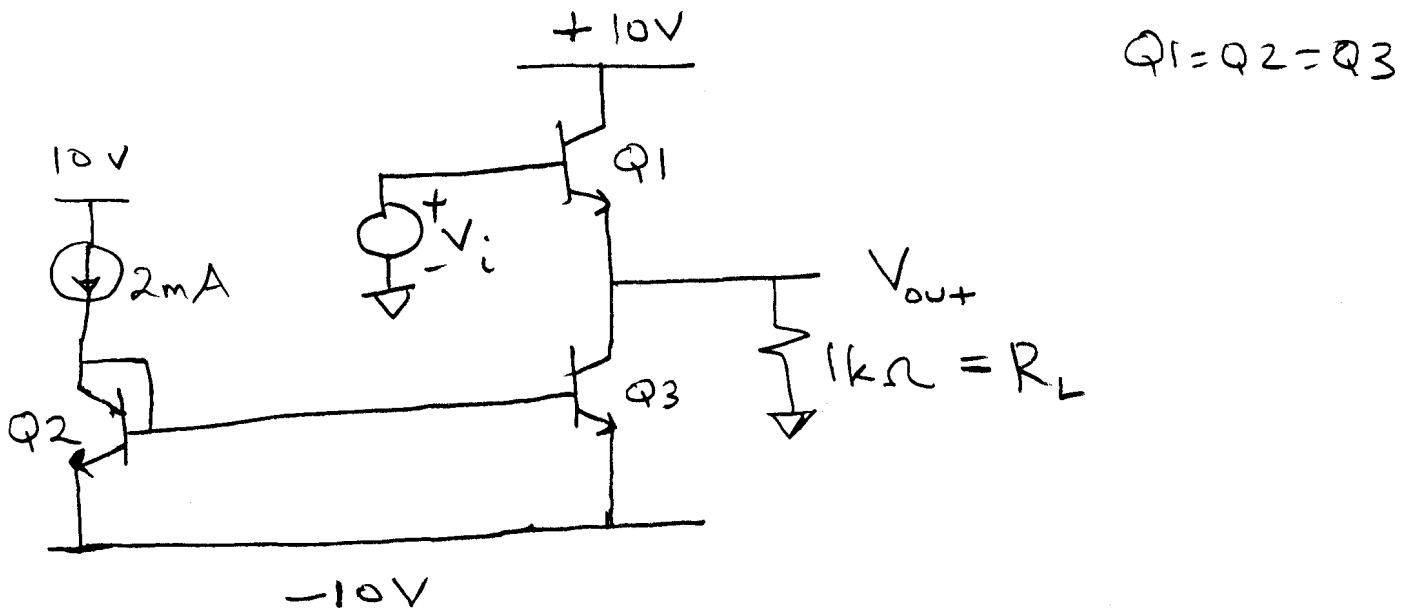b) What is the negative output swing limit? $V_{out(min)} = \underline{-2.0V}$



$Q2 - Q3 = \text{current mirror} \Rightarrow I_{C3} = 2\text{mA}$


a) $V_o(max) = 10V - V_{CE(sat)}(Q1) = 9.9V$

b) $V_o(min) = \max\left(\underbrace{-10V + V_{CE(sat)}(Q3)}_{-9.9V}, \underbrace{-I_{C3}R_L}_{-2V}\right)$

$\rightarrow V_o(min) = -2V$

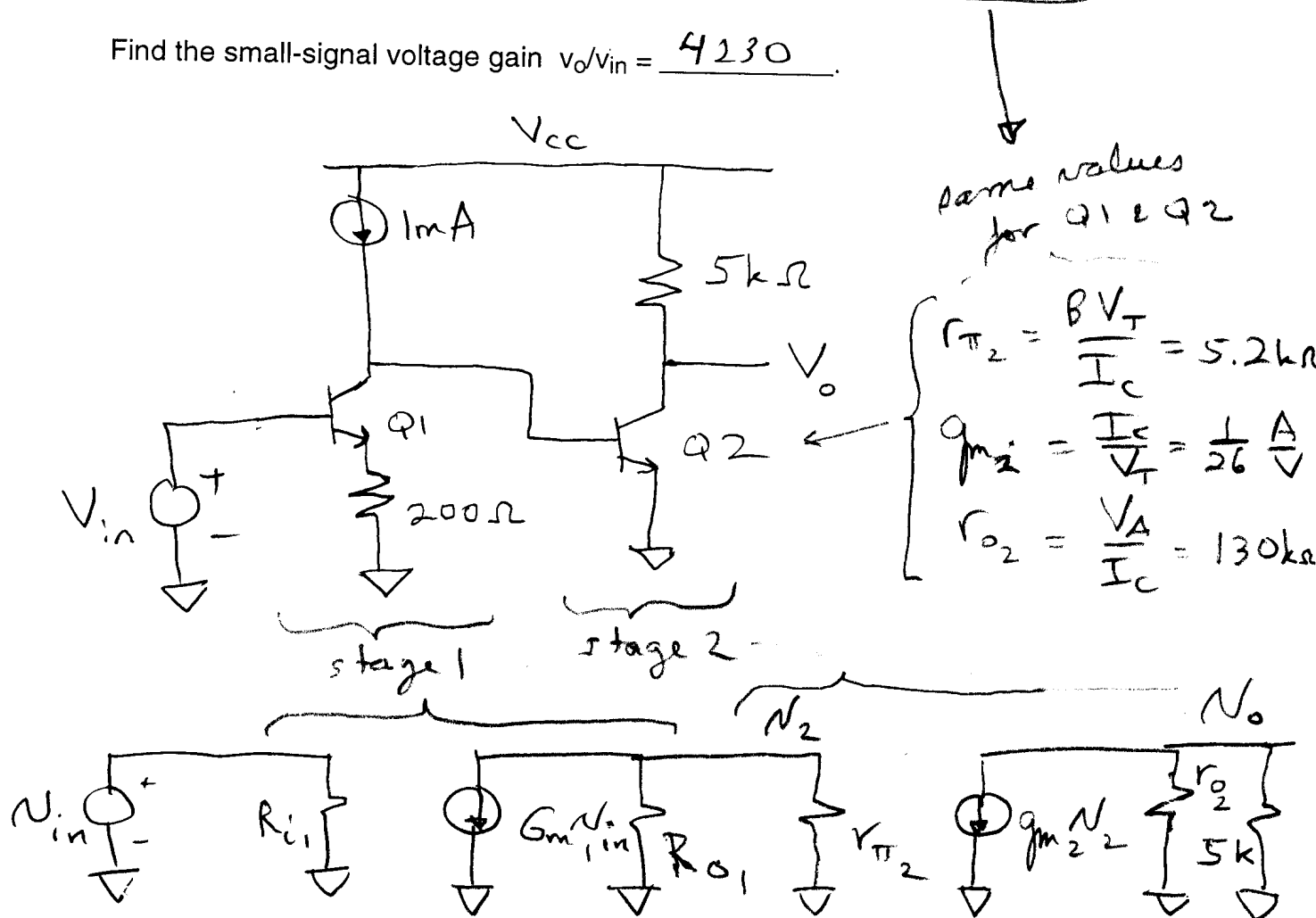6. A two-transistor amplifier is shown below. For simplicity, the DC sources are not shown. Assume all transistors are forward active with $I_{C1} = I_{C2} = 1 \text{ mA}$.

Find the small-signal voltage gain $v_o/v_{in} = \underline{4230}$.



$$N_2 = -G_{m1} N_{in} (R_{o1} \parallel r_{\pi 2})$$

$$N_o = -g_{m2} (r_{o2} \parallel 5 \text{ k}\Omega)$$

$$G_{m1} = \frac{g_{m1}}{1 + g_{m1}(200 \Omega)} = 4.4 \frac{\text{mA}}{\text{V}}$$

$$R_{o1} \approx r_{o1} (1 + g_{m1}(200 \Omega)) = 1.1 \text{ M}\Omega$$

$$\begin{aligned} \text{So } N_o &= +g_{m2} (r_{o2} \parallel 5 \text{ k}\Omega) G_{m1} (R_{o1} \parallel r_{\pi 2}) = \\ &= \left(\frac{1}{26} \frac{\text{mA}}{\text{V}} \right) (130 \text{ k}\Omega \parallel 5 \text{ k}\Omega) \left(4.4 \frac{\text{mA}}{\text{V}} \right) (1.1 \text{ M}\Omega \parallel 5 \text{ k}\Omega) \approx 4230 \end{aligned}$$