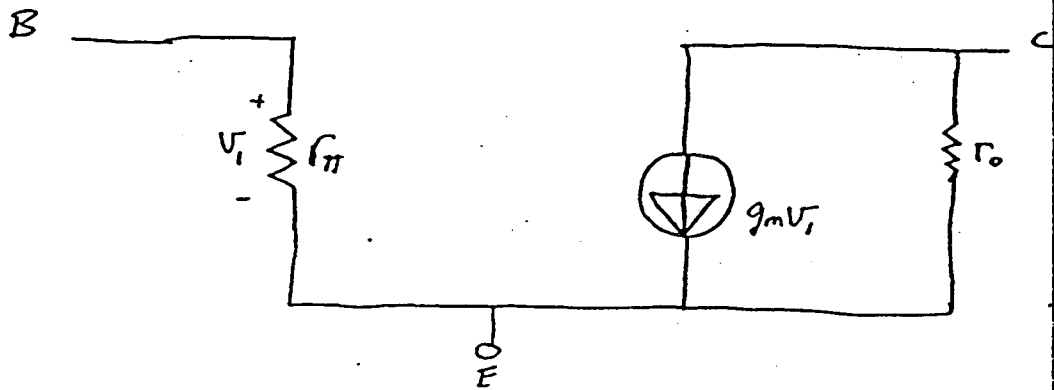


EEC 114
HW #2

1) SMALL SIGNAL MODEL Neglecting r_b, r_c, r_{ex}




where $r_{\pi} = \beta / g_m \approx \frac{200}{g_m}$ (Assuming $\beta_o \approx 200$)

$r_o = \frac{1}{\lambda g_m} \approx \frac{5 \times 10^3}{g_m}$ (From fig 2.23 $\lambda = 2 \times 10^{-4}$)

$g_m = \frac{I_c}{V_T}$

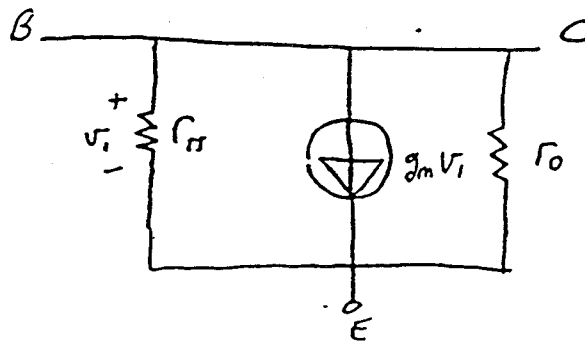
NOW WHEN CONNECTING THE BASE TO THE COLLECTOR:



IT SHOULD BE NOTED THAT THE VOLTAGE CONTROLLED CURRENT SOURCE IS CONTROLLED BY A VOLTAGE ACROSS ITS OWN TERMINALS. IT CAN THEN BE REPLACED BY A RESISTOR OF VALUE $1/g_m$. (NOTE: $I_{\text{current source}} = g_m V_i \rightarrow$)

Then $g_m = \frac{I_{\text{current source}}}{V_i}$ or $\frac{1}{g_m} = \frac{V_i}{I_{\text{current source}}} = \text{RESISTANCE!!}$

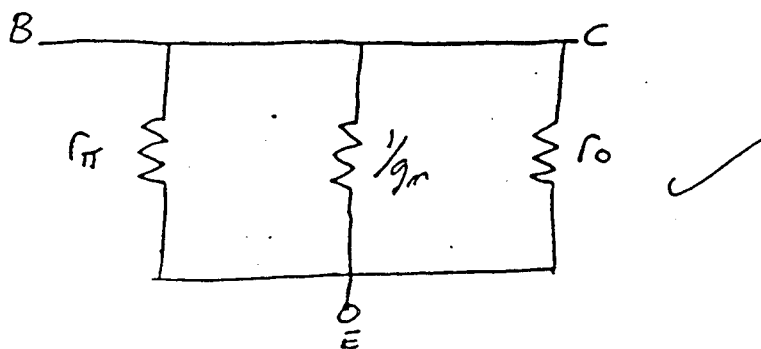SO NOW THE CIRCUIT LOOKS LIKE THE ONE BELOW:



NOW AS MENTIONED BEFORE: $r_{\pi} = \beta/g_m \approx \frac{200}{g_m}$


$r_o = \frac{1}{\lambda g_m} \approx \frac{5000}{g_m}$ ✓

Well, the EQUIVALENT RESISTANCE OF THE CIRCUIT IS $r_{\pi} \parallel r_o \parallel \frac{1}{g_m} = r_{\pi} \parallel (r_o \parallel \frac{1}{g_m})$


$$r_o \parallel \frac{1}{g_m} = \frac{\frac{5000}{g_m} \cdot \frac{1}{g_m}}{\frac{5000}{g_m} + \frac{1}{g_m}} = \frac{5000/\cancel{g_m^2}}{\frac{5001}{g_m}} = \frac{5000}{5001 g_m} \approx \frac{1}{g_m}. \text{ This is TRUE}$$

SINCE $r_o \gg \frac{1}{g_m}$. THE SAME IS TRUE FOR r_{π} , SINCE $r_{\pi} \gg \frac{1}{g_m}$

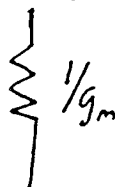THE EQUIVALENT RESISTANCE OF THE CIRCUIT CAN IGNORE r_{π} AND r_o . OUR CIRCUIT BECOMES



2a) IF $R_2 = 100R_1$

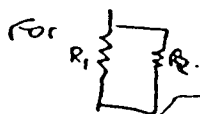

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{100R_1^2}{101R_1} = \frac{100}{101} R_1 \leftarrow \text{ACTUAL} \quad \text{APPROX} \Rightarrow R_1$$

$$\text{ERROR} = \frac{|\text{Actual} - \text{Approx}|}{\text{Actual}} = \frac{\left| \frac{100}{101} R_1 - R_1 \right|}{\frac{100}{101} R_1} = \frac{R_1/101}{\frac{100R_1}{101}} = \frac{1}{100} = \boxed{.01 = 1\%}$$

2 b) $R_2 = 10R_1$... CALCULATE ERROR IF $R_1 || R_2 \approx R_1$

Well ACTUAL VALUE IS $\frac{R_2 R_1}{R_2 + R_1} = \frac{10R_1^2}{11R_1} = \frac{10}{11} R_1$

So ERROR = $\frac{\left| \frac{10}{11} R_1 - R_1 \right|}{\frac{10}{11} R_1} = \frac{\frac{1}{11} R_1}{\frac{10}{11} R_1} = \frac{1}{10} = \boxed{.1 \text{ or } 10\%}$

2 c) $R_2 = R_1$ CALCULATE ERROR IF $R_1 || R_2 \approx R_1$

Well ACTUAL VALUE IS $\frac{R_1 R_2}{R_1 + R_2} = \frac{R_1^2}{2R_1} = \frac{1}{2} R_1$

So ERROR = $\frac{\left| \frac{1}{2} R_1 - R_1 \right|}{\frac{1}{2} R_1} = \frac{\frac{1}{2} R_1}{\frac{1}{2} R_1} = \boxed{1 \text{ or } 100\%}$

3) $L = 200 \mu$
 $W = 5 \mu$

$$R = \frac{L}{W} R_{\square}$$

For emitter diffused: $R_{\square} = 5 \Omega/\square$

So $R = \frac{200 \mu}{5 \mu} 5 = \underline{200 \Omega}$

For BASE Diffused: $R_{\square} = 100 \Omega/\square$

$R = \frac{200 \mu}{5 \mu} 100 \Omega = \underline{4 K\Omega}$

For pinch resistor = $R_{\square} = 5 K\Omega/\square$


$R = \frac{200 \mu}{5 \mu} \times 5 K\Omega = \underline{200 K\Omega}$

4) Find R_{in} , g_m , R_o of the CE Amplifier

IF $R_c = 20k\Omega$

$I_C = 250\mu A$

Assume $r_b = 0$.

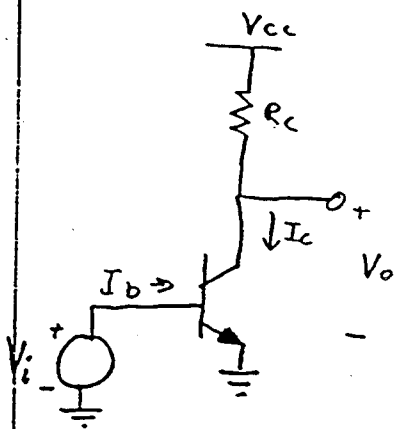

$$G_m = g_m = \frac{I_C}{V_T} = \frac{250\mu A}{26mV} = \underline{9.62mA/V}$$

USING FIG 2.30:

$\beta_o = 200$

$$R_{in} = r_{\pi} = \frac{\beta_o}{g_m} = \frac{200}{9.62mA/V} = \underline{20.8k\Omega}$$

$$R_o = r_o \parallel R_c \quad r_o = \frac{1}{\lambda g_m} = \frac{1}{(2 \times 10^{-4})(9.62mA/V)} = 519.7k\Omega$$

$\rightarrow 2 \times 10^{-4}$ (From Fig 2.30)

$$R_o = \frac{(519.7k)(20.8k)}{(20.8k) + (519.7k)} \approx \underline{20k}$$


5) Find R_{in} , G_m , R_o

$I_C = 250\mu A$

$R_c = 10k\Omega$

Neglect r_b, r_o

From Fig. 2.30,
 $\beta_o = 200$

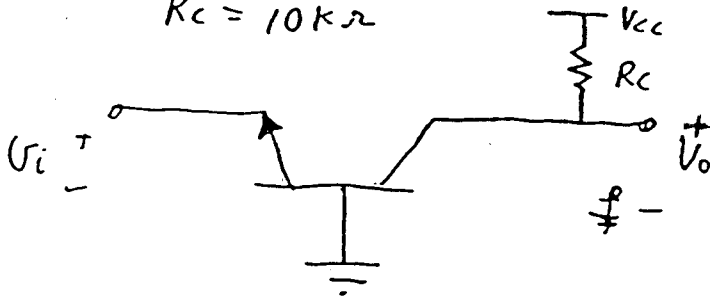


Now $G_m = g_m = \frac{250\mu A}{26mV} = \underline{9.62mA/V}$

$$R_{in} = \frac{\alpha_o}{g_m} = \frac{\beta_o / (\beta_o + 1)}{g_m} = \frac{200}{(201) 9.62mA/V} = \underline{103\Omega}$$

5 (cont)

$$R_{out} = R_c = 10k\Omega$$

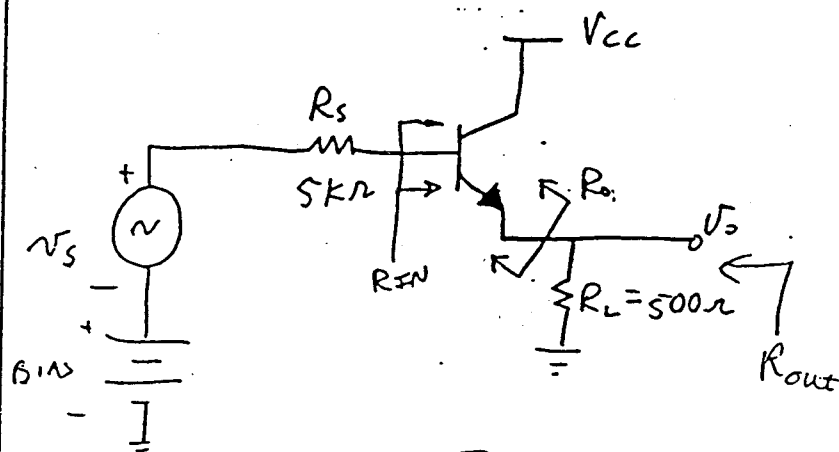6. Find R_{in} , V_o/V_s (VOLTAGE Gain), R_o for the Common Collector Amplifier



$$I_C = 1mA$$

$$\beta_o = 200$$

$$g_m = \frac{I_C}{V_T} = \frac{1mA}{26mV} = \underline{38.5mA/V}$$

$$r_{\pi} = \frac{\beta_o}{g_m} = \frac{200}{38.5mA/V} = \underline{5.2k\Omega}$$

$$R_{in} = r_{\pi} + (1 + \beta_o)R_E = 5.2k\Omega + (201)(500)$$

$$= \underline{\underline{105.7k\Omega}}$$

$$\frac{V_o}{V_s} = \frac{1}{1 + \frac{r_{\pi} + R_s}{(\beta_o + 1)R_E}} = \frac{1}{1 + \frac{(5.2k) + 5k}{(201)500}} = \underline{\underline{.908}}$$

$$R_o = \frac{R_s + r_{\pi}}{1 + \beta_o} = \frac{5.2k + 5k}{201} = 50.7\Omega$$

- Including R_L

$$R_{out} = R_o \parallel R_L = \frac{(50.7)(500)}{50.7 + 500} = \underline{\underline{46.1\Omega}}$$