

- 1) Determine the dc collector currents in Q_1 & Q_2 and then R_{in} and A_v for The Warlington emitter follower shown below. Neglect r_{π} & r_o . Assume $V_{BE(on)} = 0.7V$.

large signal analysis

$$V_I = 5V$$

$$V_{E1} = V_I - 0.7 = 4.3V$$

$$V_{E2} = V_{E1} - 0.7 = 3.6V$$

$$I_{S0} = \frac{3.6V}{50\Omega} = 72mA$$

$$I_{Ik} = \frac{(4.3 - 3.6)V}{1k\Omega} = 700\mu A$$

$$I_{E2} = I_{S0} - I_{Ik} = 72mA - 700\mu A = 71.3mA$$

$$I_{B2} = \frac{I_{E2}}{\beta + 1} = \frac{71.3mA}{201} = 354.7\mu A$$

$$I_{C2} = I_{E2} - I_{B2} = 71.3mA - 354.7\mu A = 70.95mA$$

$$I_{E1} = I_{Ik} + I_{B2} = 700\mu A + 354.7\mu A = 1.05mA$$

$$I_{B1} = \frac{I_{E1}}{\beta + 1} = \frac{1.05mA}{201} = 5.22\mu A$$

$$I_{C1} = I_{E1} - I_{B1} = 1.05mA - 5.22\mu A = 1.04mA$$


you can see that $I_{C2} \approx I_{E2}$, $I_{C1} \approx I_{E1}$

$\Rightarrow$ could have assumed I_B 's = 0 for I_C calculations.

however I_{B2} was significant in calculating I_{E1} !

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{1.04mA}{26mV} = 40mS \quad g_{m2} = \frac{70.95mA}{26mV} = 2.73S$$
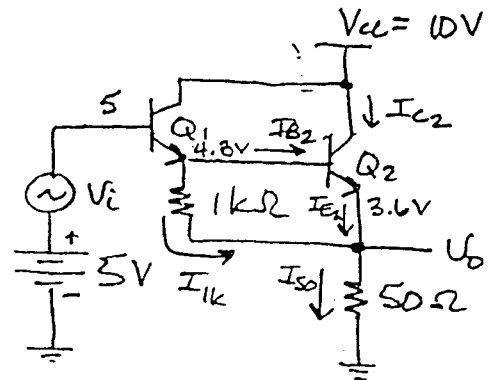
$$r_{\pi1} = \frac{\beta}{g_{m1}} = \frac{200}{40mS} = 5k\Omega \quad r_{\pi2} = \frac{200}{2.73S} = 73.3\Omega$$



1 cont'd)

Small Signal analysis

exact analysis:

$$\underline{R_{in}}: V_T = V_{\pi_1} + V_{\pi_2} + V_o \quad (1)$$

$$V_o = 50 i_o = 50 (i_1 + g_{m2} V_{\pi_2})$$

$$V_{\pi_2} = i_1 R'$$

$$V_{\pi_1} = i_T r_{\pi_1}$$

substitute these into eqn (1)

$$V_T = \underbrace{i_T r_{\pi_1}}_{V_{\pi_1}} + \underbrace{i_1 R'}_{V_{\pi_2}} + \underbrace{50 i_1 + 50 g_{m2} i_1 R'}_{V_o}$$

need to get i_1 in terms of i_T

$$i_1 = (\beta + 1) i_T$$

$$\begin{aligned} \Rightarrow V_T &= i_T r_{\pi_1} + i_T (\beta + 1) R' + i_T (\beta + 1) 50 + i_T (\beta + 1) 50 g_{m2} R' \\ &= i_T [r_{\pi_1} + (\beta + 1) R' + (\beta + 1) 50 + (\beta + 1) 50 g_{m2} R'] \end{aligned}$$


$$\boxed{R_{in} = \frac{V_T}{i_T} = r_{\pi_1} + (\beta + 1) R' + (\beta + 1) 50 + (\beta + 1) 50 g_{m2} R'}$$

from large signal analysis, plug in values

$$R_{in} = 5k\Omega + (201)68.3 + (201)50 + (201)(50)(2.73)(68.3)$$

$$\boxed{R_{in} = 1.9 M\Omega}$$

→
next page

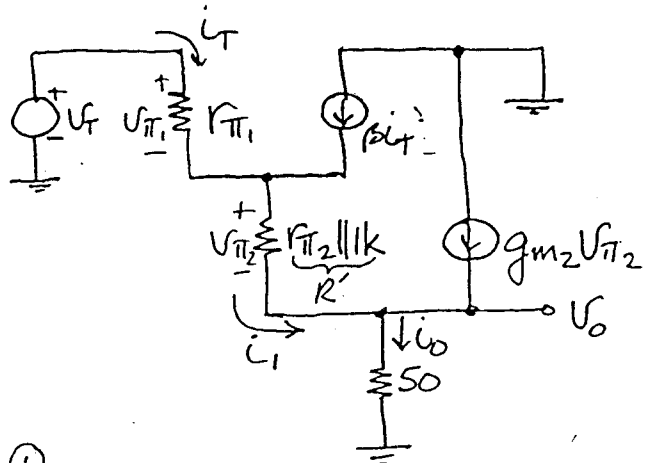

1. cont'd)

A_v : looking at the same ckt:

$$v_T = v_{\pi_1} + v_{\pi_2} + v_o \quad (1)$$

$$v_o = (i_1 + g_{m2} v_{\pi_2}) 50 = 50 i_1 + 50 g_{m2} v_{\pi_2}$$

$$i_1 = \frac{v_{\pi_2}}{R'}$$

$$\Rightarrow v_o = 50 \frac{v_{\pi_2}}{R'} + 50 g_{m2} v_{\pi_2}$$

$$= 50 v_{\pi_2} \left[\frac{1}{R'} + g_{m2} \right]$$

Solving for v_{π_2} :

$$\Rightarrow v_{\pi_2} = \frac{v_o}{50 \left(\frac{1}{R'} + g_{m2} \right)} \quad (2)$$

plugging into (1):

$$\Rightarrow v_T = v_{\pi_1} + \frac{v_o}{50 \left(\frac{1}{R'} + g_{m2} \right)} + v_o$$

need to get v_{π_1} in terms of v_o

$$i_T + \beta i_T = i_1 = \frac{v_{\pi_2}}{R'} \Rightarrow (\beta + 1) i_T = \frac{v_{\pi_2}}{R'}$$

$$\Rightarrow (\beta + 1) \frac{v_{\pi_1}}{r_{\pi_1}} = \frac{v_{\pi_2}}{R'}$$

$$v_{\pi_1} = \frac{v_{\pi_2} r_{\pi_1}}{R' (\beta + 1)} \xrightarrow{\text{sub eqn (2)}} \frac{v_o r_{\pi_1}}{R' (\beta + 1) 50 \left(\frac{1}{R'} + g_{m2} \right)}$$

plug into eqn (1):

$$v_T = v_o \left[\frac{r_{\pi_1}}{R' (\beta + 1) 50 \left(\frac{1}{R'} + g_{m2} \right)} + \frac{1}{50 \left(\frac{1}{R'} + g_{m2} \right)} + 1 \right]$$


$$A_v = \frac{v_o}{v_T} = \frac{1}{\left[\frac{r_{\pi_1}}{R' (\beta + 1) 50 \left(\frac{1}{R'} + g_{m2} \right)} + \frac{1}{50 \left(\frac{1}{R'} + g_{m2} \right)} + 1 \right]}$$

$$A_v = \frac{1}{\frac{5k}{(683)(201)(50) \left(\frac{1}{68} + 2.73 \right)} + \frac{1}{50 \left(\frac{1}{68} + 2.73 \right)} + 1} \approx 0.990 = A_v$$

contd)

Approximate analysis :

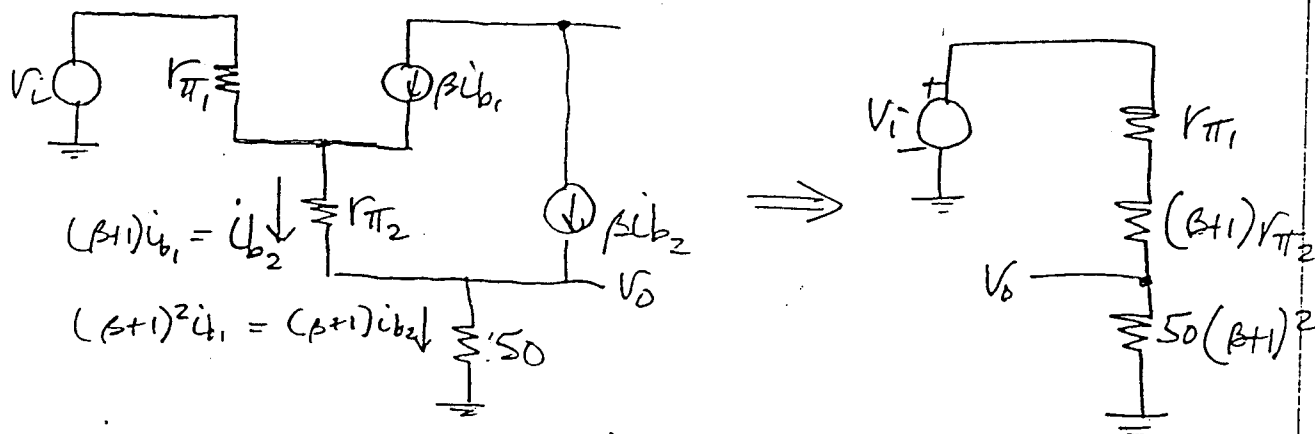if we assume that $R' = r_{\pi 2} \parallel 1k \approx r_{\pi 2}$
then the analysis is much easier.



without the $1k\Omega$ resistor, the current across $r_{\pi 2}$ is i_{b2} and is the only current between the emitter of Q_1 and the emitter of Q_2 .
So, Impedance reflection can be used, twice! (as shown above)

R_{in} $R_{in} = r_{\pi 1} + (\beta+1)r_{\pi 2} + 50(\beta+1)^2$
 $= 5k\Omega + (201)(73.3) + 50(201)^2$
 $\Rightarrow \boxed{R_{in} = 2.04 M\Omega}$

A_v : this is just a voltage divider!

$$V_o = \frac{50(\beta+1)^2}{50(\beta+1)^2 + (\beta+1)r_{\pi 2} + r_{\pi 1}} V_i$$

$$A_v = \frac{50(\beta+1)^2}{50(\beta+1)^2 + (\beta+1)r_{\pi 2} + r_{\pi 1}} = \frac{50(\beta+1)^2}{R_{in}}$$

$$= \frac{50(201)^2}{2.04 M\Omega} \Rightarrow \boxed{A_v = 0.990}$$

2. Assume All XSTRs identical

$$I_{C1} = I_{C2} = I_S \left\{ e^{V_{BE1}/V_T} \right\} \left(1 + \frac{V_{CE1}}{V_A} \right)$$

$$\Rightarrow I_S e^{V_{BE1}/V_T} = \frac{I_{C1}}{\left(1 + \frac{V_{CE1}}{V_A} \right)}$$

$$\therefore I_{C3} = I_{C1} \frac{\left(1 + \frac{V_0}{V_A} \right)}{\left(1 + \frac{V_{CE1}}{V_A} \right)}$$

$$I_R = I_{C1} + I_{C2} = \frac{15 - 0.72}{10K\Omega} = 1.4mA$$

$$\therefore I_{C1} = 0.72mA$$

$$\therefore I_0 = 3I_{C3} = 3I_{C1} \left(\frac{1 + V_0/V_A}{1 + V_{CE1}/V_A} \right) = 2.15mA \left(\frac{V_A + V_0}{V_A + 0.7V} \right)$$

$$V_A = 130V -$$

V_0	$I_0 (mA)$
1	2.15
5	2.22
30	2.63


For $R_0 \Rightarrow$

$$I_C = I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$r_o = \left[\frac{\partial I_C}{\partial V_{CE}} \right]^{-1} = \left[I_S e^{V_{BE}/V_T} \left(\frac{1}{V_A} \right) \right]^{-1} \quad \frac{V_A}{I_{C0}} = \frac{V_A}{I_C |_{V_{CE}=0}}$$

$$\therefore R_0 = r_{o3} \parallel r_{o4} \parallel r_{o5} = \frac{r_{o3}}{3} = \frac{1}{3} \frac{V_A}{I_{C0}} = \frac{1}{3} \frac{130V}{0.72mA} = \boxed{60.6K\Omega}$$

3)

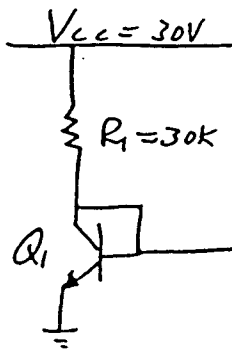

HSPICE:

V_o	I_o	R_o
1 Volt	4.9915 μA	86.96 M Ω
5 Volts	5.0354 μA	95.24 M Ω
30 Volts	5.2668 μA	125 M Ω

$$I_R = \frac{V_{CC} - V_{BE}}{R_1} = \frac{30 - 1.7}{30} = .977 \text{ mA}$$

$$V_{BE1} = V_{BE2} + I_o R_2 \quad I_o R_2 = V_T \ln \frac{I_{C1}}{I_o} \approx V_T \ln \frac{I_R}{I_o}$$

$$R_2 = \frac{V_T}{I_o} \ln \frac{I_R}{I_o} = \frac{26}{5} \ln \frac{.977 \text{ mA}}{5 \mu A}$$

$$= 27.4 \text{ k}$$

R_o is that of a CEWO with $\frac{1}{g_{m1}} \parallel 30 \text{ k}\Omega$ as R_s :

$$R_o \approx r_{o2} \left(1 + g_{m2} R_2 \frac{r_{\pi 2}}{r_{\pi 2} + R_{s2} + R_2} \right)$$

$$V_{o2} = \frac{130 \text{ V}}{5 \mu A} = 26 \text{ M}\Omega$$

$$r_{\pi 2} = \frac{(200)(26 \text{ mV})}{5 \mu A} = 1.04 \text{ M}\Omega$$

$$g_{m2} = \frac{5 \mu A}{26 \text{ mV}} = 0.192 \text{ mS}$$

$$R_o \approx (26 \text{ M}\Omega) \left(1 + (.192 \text{ mS})(27.4 \text{ k}) \frac{1040 \text{ k}}{1040 \text{ k} + 27.4 \text{ k}} \right)$$

$$R_o = 159.5 \text{ M}\Omega$$

Using formula in book for Widlar Source yields a similar result of $R_o = 159 \text{ M}\Omega$

$$4) \quad I_{ref} = \frac{15 - 1.7}{20 \text{ k}} = .72 \text{ mA}$$

$$I_o R_2 = V_T \ln \frac{I_{C1}}{I_o} \approx V_T \ln \frac{I_{ref}}{I_o}$$

$$I_o \approx 10.9 \mu A$$


$$I_o = 26 \times 10^{-3} \ln \frac{.72 \text{ mA}}{I_o}$$

↳ Iterate

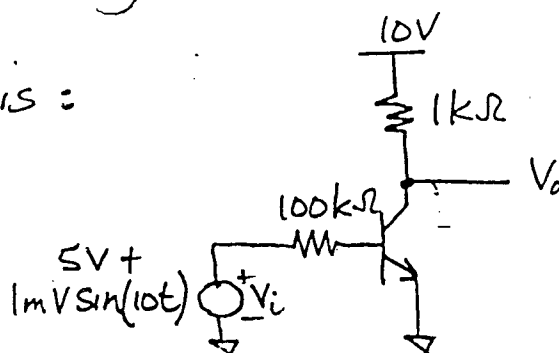5) Find V_o of the following CE circuit


from load line analysis:

$$\left. \begin{aligned} I_B &= 44 \mu A \\ I_C &= 4.6 \text{ mA} \\ V_{CE} &= 5.25 \text{ V} \end{aligned} \right\} \text{ see graphs}$$



$$V_o = V_{CE} + v_o = 5.25 \text{ V} + v_o$$

small signal analysis:

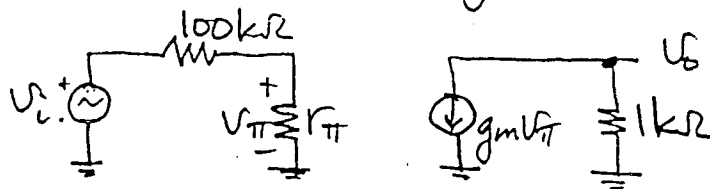

$$v_o = (-g_m v_{\pi})(1k\Omega)$$

$$v_{\pi} = \left(\frac{r_{\pi}}{100k\Omega + r_{\pi}} \right) v_i$$

$$v_o = -g_m(1k\Omega) \left(\frac{r_{\pi}}{100k\Omega + r_{\pi}} \right) v_i$$

$$g_m = \frac{I_C}{V_T} = \frac{4.6 \text{ mA}}{26 \text{ mV}} = 176.9 \text{ mS}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{102.5}{176.9 \text{ mS}} = 579.35 \Omega$$


$$v_i = 1 \text{ mV} \sin(10t) \leftarrow \text{given}$$

plugging in:

$$v_o = -(176.9 \text{ mS})(1k\Omega) \left(\frac{579.35 \Omega}{100k\Omega + 579.35 \Omega} \right) (1 \text{ mV} \sin(10t))$$

$$v_o = -1.02 \text{ mV} \sin(10t)$$
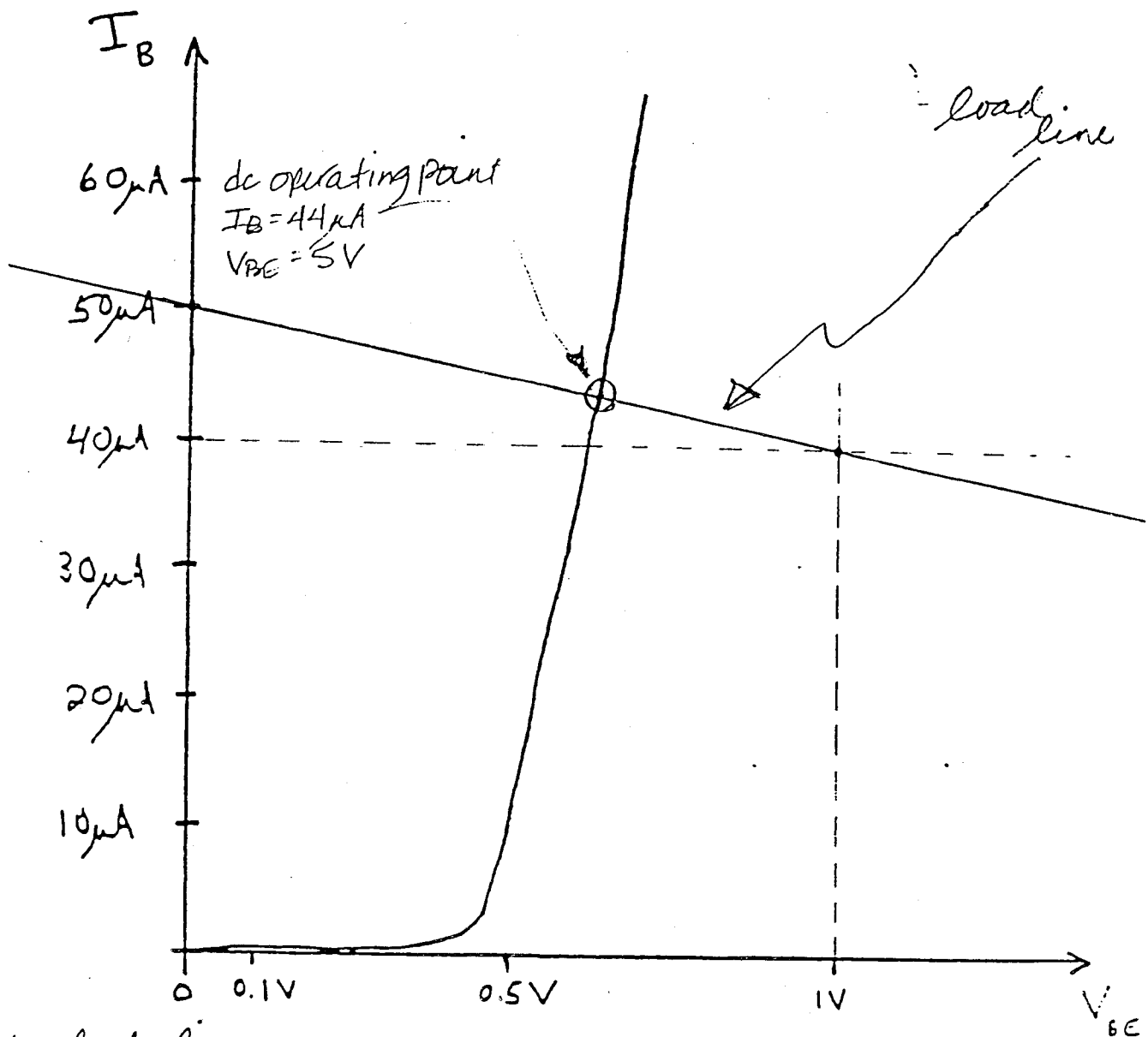
$$V_o = 5.25 \text{ V} - 1.02 \text{ mV} \sin(10t)$$



- V_{BE} load line :

- $V_{100k} - V_{BE} = 0$

- $(100k\Omega)I_B - V_{BE} = 0$

$$= \frac{5V - V_{BE}}{100k\Omega} = 50\mu A - 10\mu V_{BE}$$


load line

Super Impose on graph above

$V_{open\ ckt} \Rightarrow I_B = 0 ; V_{oc} = 5V$

$I_{short\ ckt} \Rightarrow V_{BE} = 0, I_{sc} = 50\mu A$

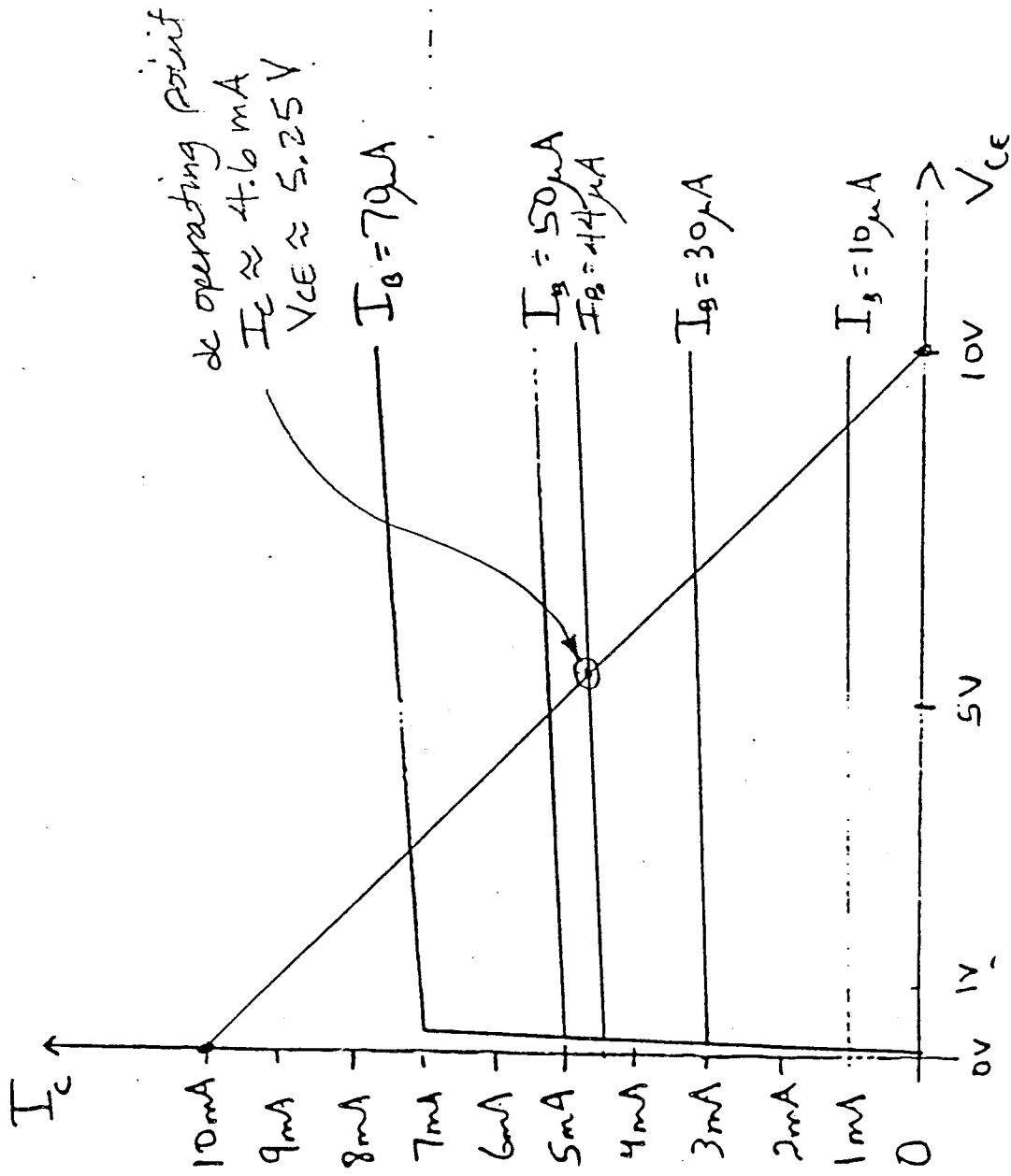draw in $I_B = 44\mu A$ curve on next graph.



$I_C - V_{CE} \text{ load line} :$

$$I_C = \frac{V_{CE} - V_0}{R_C} = \frac{10\text{V} - V_0}{1\text{k}\Omega}$$


$$V_0 = V_{CE} \rightarrow I_C = 10\text{mA} - 1\text{m} V_{CE}$$

Load line
 superimpose on graph

$$\beta = \frac{\Delta I_C}{\Delta I_B} \approx \frac{2.05}{20 \mu\text{A}}$$

$$\beta_F \approx 102.5$$

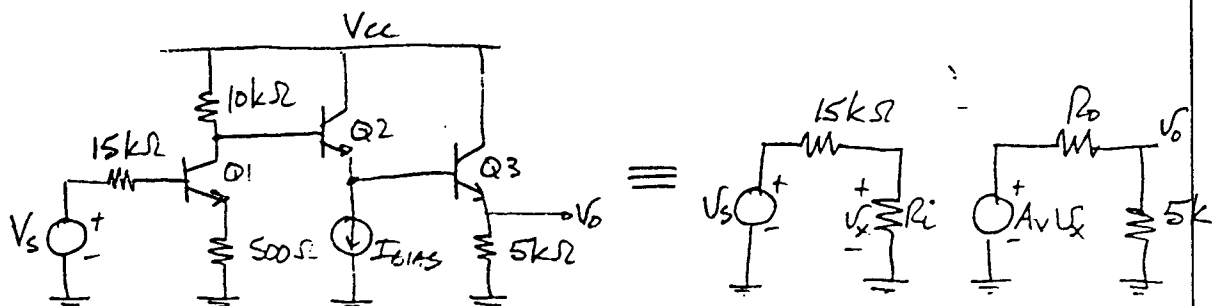- 6) For the circuit below, find the elements R_i , R_o , A_v in the model. Assume DC biasing sets $I_{C1} = I_{C2} = I_{C3}$ and all xtrs are in F.A.R.



large signal analysis

assume $I_{C1} = I_{C2} = I_{C3} = I_{Bias} = 1\text{mA}$


$$g_{m1} = g_{m2} = g_{m3} = \frac{I_C}{V_T} = \frac{1\text{mA}}{26\text{mV}} = \underline{38.5\text{mS}}$$

$$r_{\pi 1} = r_{\pi 2} = r_{\pi 3} = \frac{\beta}{g_m} = \frac{200}{38.5\text{mS}} = \underline{5.2\text{k}\Omega}$$

$$r_{o1} = r_{o2} = r_{o3} = \frac{V_A}{I_C} = \frac{130\text{V}}{1\text{mA}} = \underline{130\text{k}\Omega}$$

small signal analysis

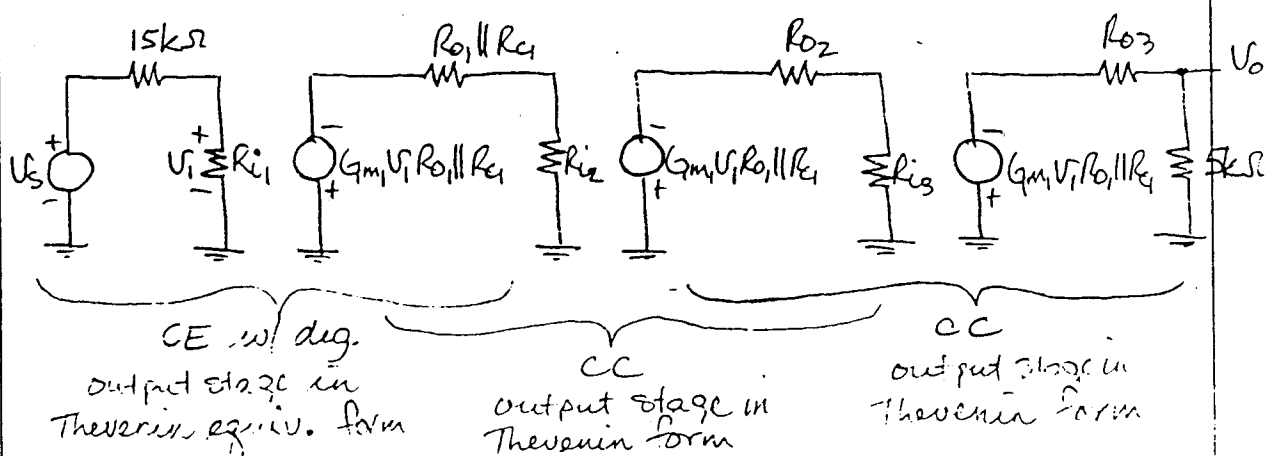using the "single transistor" handout, represent the circuit as 3 single transistors in cascade:



6 cont'd)

from small signal model on previous page:

$$\begin{aligned} R_{in} &= R_{i1} = R_{in}(CE \text{ w/ deg}) \\ &= r_{\pi 1}(1 + g_{m1}R_E) \leftarrow \text{neglecting } r_b \\ &= (5.2k)(1 + [38.5mV][500\Omega]) \end{aligned}$$

$$\Rightarrow R_{in} = 105.3k\Omega$$

$$R_{o3} = R_{out}(CC) = \frac{r_{\pi 3} + R_{s3}}{\beta + 1}$$

$$R_{s3} = R_{o2} = R_{out}(CC) = \frac{r_{\pi 2} + R_{s2}}{\beta + 1}$$

$$\begin{aligned} R_{o1} &= R_{out}(CE \text{ w/ deg}) = R_o \left(1 + g_{m1}R_E \frac{r_{\pi 1}}{r_{\pi 1} + R_{s1} + R_E} \right) \\ &= (130k\Omega) \left(1 + (38.5m)(500) \left(\frac{5.2k}{5.2k + 15k + 500} \right) \right) \end{aligned}$$

$$= 758.65k\Omega \Rightarrow R_{s2} = R_{o1} \parallel R_{c1} \approx 9.9k\Omega$$

$$\begin{aligned} \Rightarrow R_{s3} &= \frac{r_{\pi 2} + R_{s2}}{\beta + 1} = \frac{5.2k + 9.9k\Omega}{201} \\ &= 75\Omega \end{aligned}$$

$$\begin{aligned} \Rightarrow R_{o3} &= \frac{r_{\pi 3} + R_{s3}}{\beta + 1} = \frac{5.2k + 75\Omega}{201} \\ &= 26\Omega \end{aligned}$$

$$\Rightarrow R_o = R_{o3} = 26\Omega$$

6 cont'd.)

$$A_v = \frac{V_o}{V_i} = \frac{V_o}{V_1} \cdot \frac{V_1}{V_s}$$

$$V_o = -G_{m1} V_1 R_{o1} \parallel R_{c1} \left(\frac{5k\Omega}{R_{o3} + 5k\Omega} \right)$$

$$\frac{V_o}{V_1} = -G_{m1} R_{o1} \parallel R_{c1} \left(\frac{5k\Omega}{R_{o3} + 5k\Omega} \right)$$

$$G_{m1} = G_m(\text{CE w/ deg.}) = \frac{g_{m1}}{1 + g_{m1} R_E}$$

$$= \frac{38.5 \text{ mS}}{1 + (38.5 \text{ mS})(500\Omega)}$$

$$= 1.9 \text{ mS}$$

$$\Rightarrow \left. \frac{V_o}{V_1} \right|_{R_L = \infty} = (-1.9 \text{ mS})(758.6k\Omega \parallel 10k\Omega)$$

$$= -18.59$$

$$V_1 = \frac{R_{i1}}{R_{i1} + 15k\Omega} V_s \Rightarrow \frac{V_1}{V_s} = \frac{R_{i1}}{R_{i1} + 15k\Omega}$$

$$\Rightarrow \frac{V_1}{V_s} = \frac{105.3k\Omega}{105.3k\Omega + 15k\Omega} = 0.875$$

$$\Rightarrow A_v = \frac{V_o}{V_s} = \frac{V_o}{V_1} \cdot \frac{V_1}{V_s} = (-18.59)(0.875)$$

$$\boxed{A_v = -16.3} \quad (A_{vs} = \left. \frac{V_o}{V_s} \right|_{R_L = \infty})$$

final model

