


EEC PS#4 Solution

- 1) Find Diff. mode gain, Common mode gain, differential mode input resistance, Common mode input resistance, Find CMRR.

$$I_{EE} = 20 \mu A \quad R_C = 100 K\Omega$$

Neglect C_o, r_{μ}, r_b
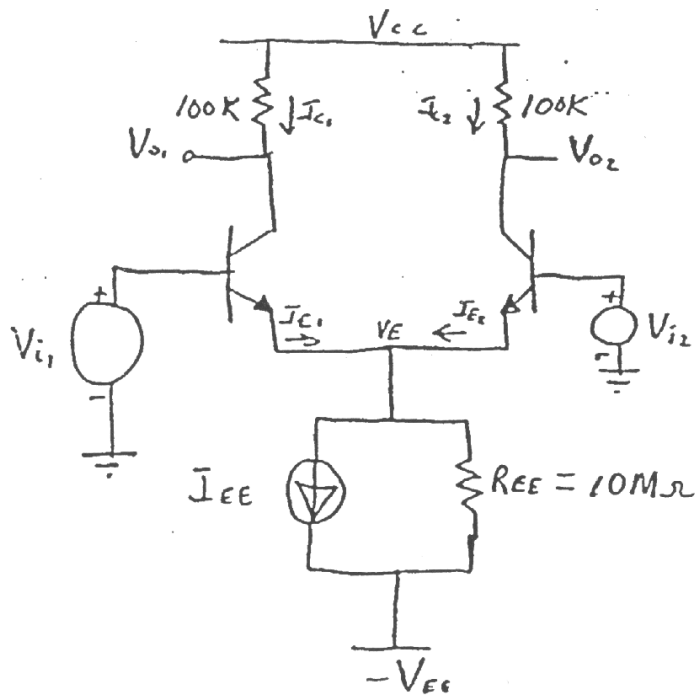
$$R_{EE} = 10 M\Omega \quad V_{EE} = V_{CC} = 5V$$



D.C. CALCULATIONS

Assume $V_E = 0V$ Because of SYMMETRY $I_{EE} = 20 \mu A + \frac{5V}{10 M\Omega} = 20.5 \mu A \approx 20 \mu A$

$$\therefore I_{C1} = I_{C2} = 10 \mu A$$

$$g_m = \frac{10 \mu A}{26 mV} = 385 \mu A/V$$

1
Cont.)

Differential Mode Gain

$$A_{dm} = -g_m R_c = \underline{-38.5}$$

Common Mode gain

$$A_{cm} = \frac{-g_m R_c}{1 + 2g_m R_{EE}(1 + \frac{1}{\beta_o})} = \frac{-38.5}{1 + (38.5 \times 10^{-3})(2)(10^7)(1 + \frac{1}{200})} = \underline{-4.97 \times 10^{-3}}$$

$\beta_o = 200$

Differential Mode Input Resistance

$$R_{id} = 2r_{\pi} = \frac{2\beta_o}{g_m} = \frac{400}{38.5 \times 10^{-3}} = \underline{1.04 M\Omega}$$

Common Mode Input Resistance


$$\begin{aligned} R_{ic} &= r_{\pi} + 2R_{EE}(1 + \beta_o) = 520K + 2(10 M\Omega)(1 + 200) \\ &= 520K + 4,020 M\Omega \\ &\approx \underline{4.020 \times 10^9 \Omega} \end{aligned}$$

CMRR

$$\begin{aligned} CMRR &= 1 + 2g_m R_{EE}(1 + \frac{1}{\beta_o}) \\ &= 1 + 2(38.5 \times 10^{-3})10^7(1 + \frac{1}{200}) \\ &= \underline{7.73 \times 10^3} \end{aligned}$$

2)

Looking at the half ckt

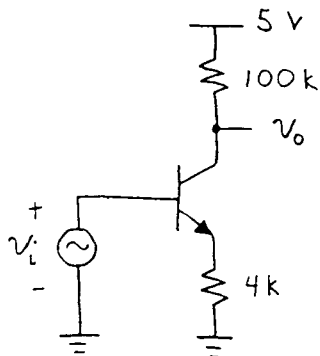 $\Rightarrow$ CE w/ degeneration


$$A_{dm} = \frac{-g_m}{1 + g_m R_E} R_C$$

$$= \frac{-0.385 \text{ mA/V}}{1 + (0.385 \text{ mA/V})(4 \text{ k})} [100 \text{ k}]$$

$$A_{dm} \approx -15$$

$$g_{m1} = g_{m2} = \frac{10 \mu\text{A}}{26 \text{ mV}} = 0.385 \text{ mA/V}$$

For Common mode ckt

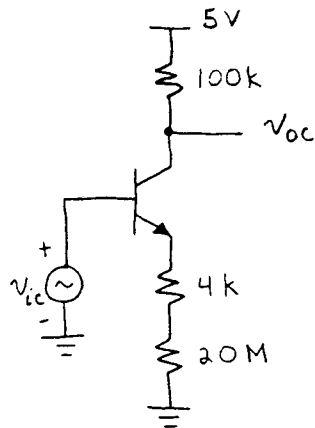

$$\Rightarrow A_{cm} = \frac{-g_m}{1 + g_m R_E} [100 \text{ k}]$$

$$= \frac{-0.385 \text{ mA/V}}{1 + (0.385 \text{ mA/V})(20 \text{ M})} 100 \text{ k}$$

$$A_{cm} = -0.005$$

$$\Rightarrow \text{CMRR} = \frac{A_{dm}}{A_{cm}} = 3000 = 69 \text{ dB}$$


$$\Rightarrow R_{id} = 2(r_{\pi} + (\beta + 1)4 \text{ k})$$

$$= 2.12 \text{ M}\Omega$$

$$\Rightarrow R_{ic} = r_{\pi} + (\beta + 1)(20 \text{ M} + 4 \text{ k})$$


$$= 4.02 \times 10^9 \Omega$$

3.

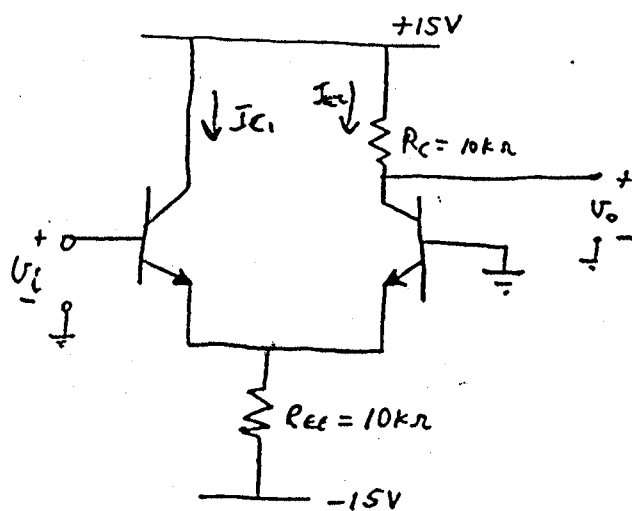 R_{in}, A_v, R_o 

Resistor has no effect!!

(r_n called r_e by some)

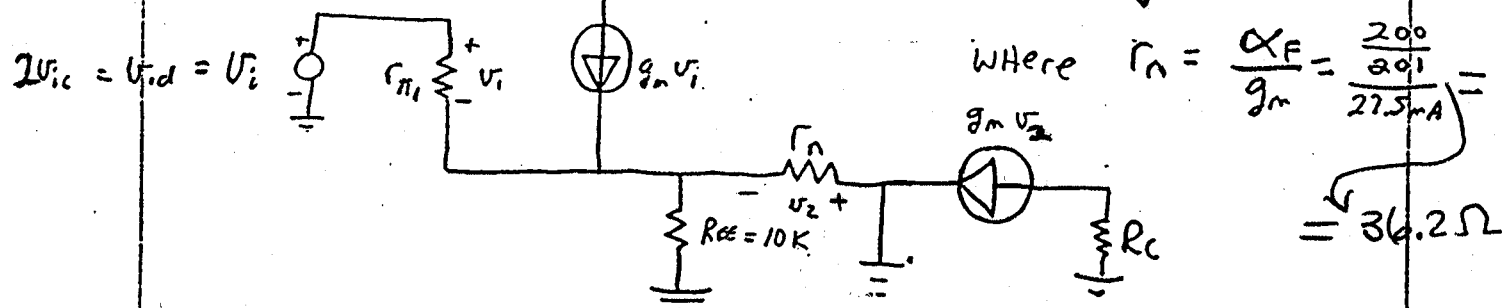

Where $r_n = \frac{\alpha_F}{g_m} = \frac{\frac{200}{201}}{27.5 \text{ mA/V}} = 36.2 \Omega$

D.C. ANALYSIS $-(I_{E1} + I_{E2}) = \frac{15V - 0.7V}{10K} = 1.43 \text{ mA} = \frac{I_{T1}}{2}$

$I_{C1} = I_{C2} = \frac{I_{E1}}{2} = \frac{1.43 \text{ mA}}{2} = 0.715 \text{ mA}$

$g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.715 \text{ mA}}{26 \text{ mV}} = 27.5 \text{ mA/V} = g_{m2}$ since $I_{C1} = I_{C2}$

$\beta_0 = 200$ From model data in Chap 2.

$r_{\pi 1} = r_{\pi 2} = \frac{200}{27.5 \text{ mA/V}} = 7.273 \text{ k}\Omega$

SO $R_{in} = r_{\pi 1} + (\beta + 1)(R_{EE} \parallel r_n)$

$= 7.273 \text{ k}\Omega + (201)(10 \text{ k}\Omega \parallel 36.2 \Omega)$

$R_{in} = 14.53 \text{ k}\Omega$

3.

Cont

 $R_{out} = R_c \parallel \text{current source}$

$$R_{out} = R_c = \underline{10k\Omega}$$

$$V_{out} = V_{o2} = -\frac{V_{od}}{2} + V_{oc} \triangleq -A_{dm} \frac{V_{id}}{2} + A_{cm} V_{ic} = -\frac{A_{dm}}{2} (V_i) + A_{cm} \left(\frac{V_i}{2}\right)$$


$$\text{BUT } A_{dm} = g_m R_c = (27.5 \text{ mA/V})(10k) = \underline{-275}$$

$$A_{cm} = \frac{-g_m R_c}{1 + 2g_m R_E (1 + \frac{1}{\beta_o})} = \frac{-275}{1 + 550(1 + \frac{1}{200})} = \underline{-.4966}$$

$$V_o = \frac{275}{2} (V_i) - \frac{.4966}{2} V_i$$

$$\frac{V_o}{V_i} = \underline{137.25}$$

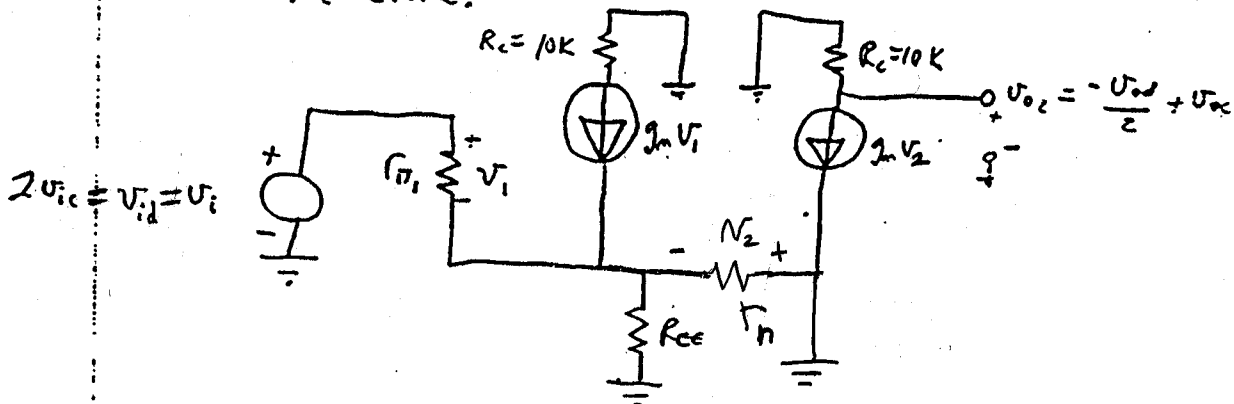Now IF we put a Resistor R_c the analysis is just the same.




$$R_{in} = r_{\pi 1} + (\beta_{11})(R_{EE} \parallel r_{\pi})$$

$$= \underline{1453k\Omega}$$

$$R_{out} \approx R_c = \underline{10k\Omega}$$

$$A_v = \frac{-A_{dm}}{2} + \frac{A_{cm}}{2} = \frac{275}{2} - \frac{.4966}{2} = \underline{137.25}$$

3. (b) TO ANALYZE AS A CC-CB REPAIRS

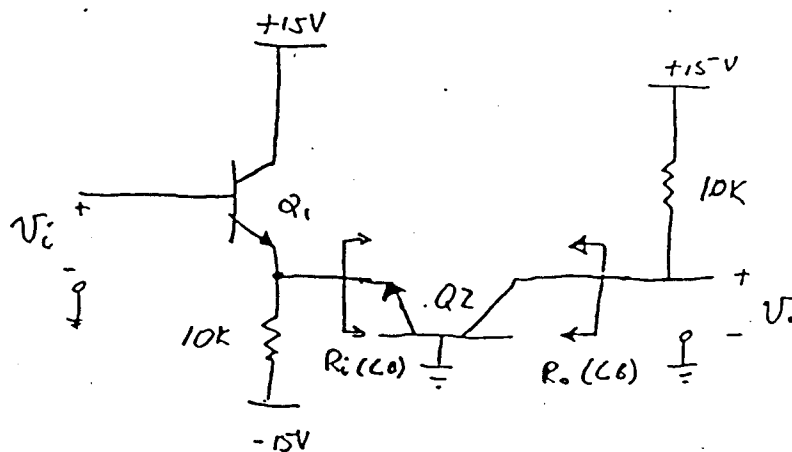

NOW: Q_1 C.C. Q_2 C.B.

$$R_{IN_TOTAL} = R_i(C.C. Q_1) = \overbrace{r_{\pi_1} + (\beta+1)(10K \parallel R_i(C.B.))}^{\text{USE HANDOUT}}$$


$$\text{BUT } R_i(C.B.) \approx \frac{1}{g_{m2}}$$

$$g_{m1} = g_{m2} = \frac{.71mA}{26mV} = \underline{\underline{27.3mA/V}}$$

$$r_{\pi_1} = \frac{200}{g_{m1}} = \frac{200}{27.3mA/V} = \underline{\underline{7.324K}}$$

$$R_{IN_TOTAL} = 7.324K + (201)(10K \parallel 36.6\Omega) \\ = \underline{\underline{14.69K}}$$
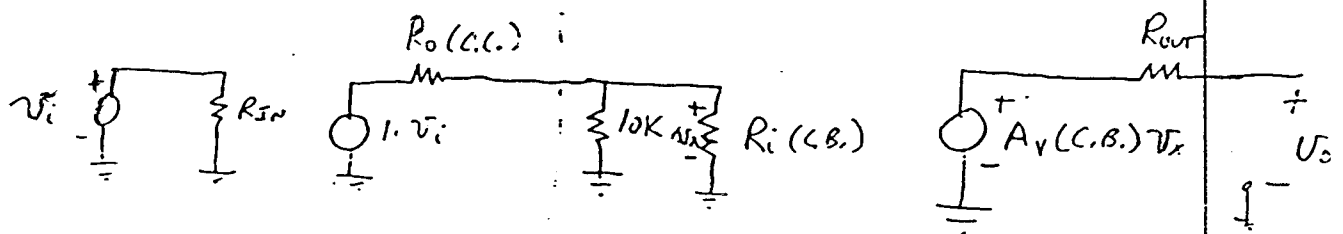
$$R_{out} = R_o(C.B.) \parallel 10K\Omega \approx 10K\Omega$$



$$V_o = A_v(C.B.) V_x = \left[1 \cdot V_i \cdot \frac{R_i(C.C.) \parallel 10K}{R_o(C.C.) \parallel R_i(C.B.) \parallel 10K\Omega} \right] A_v(C.B.)$$

$$V_o \approx g_{m2} 10k \cdot \left[V_i \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} \right] = g_{m2} 10k \frac{V_i}{2} = 136 V_i$$

$$\text{So } \frac{V_o}{V_{in}} = 136$$

SPICE COMPARISON

	CC-CB			diff pair		
	$R_L[\Omega]$	$R_O[\Omega]$	$A_v[V/V]$	$R_L[\Omega]$	$R_O[\Omega]$	$A_v[V/V]$
SPICE	14.58k	10k	136.7	14.58k	10k	136.7
calculated	14.69k	10k	136	14.53k	10k	137.25

***** SPICE 2G.5 (

) *****21:16:17*****

**** OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG

CC-CB

**** BIPOLAR JUNCTION TRANSISTORS

	Q1	Q2
MODEL	XTER	XTER
IB	3.54E-06	3.54E-06
IC	7.08E-04	7.08E-04
VBE	0.765	0.765
VBC	-15.000	-7.918
VCE	15.765	8.683
BETADC	200.001	200.000
GM	2.74E-02	2.74E-02
RPI	7.30E+03	7.30E+03
RX	0.00E+00	0.00E+00
RO	1.00E+12	1.00E+12
CPI	0.00E+00	0.00E+00
CMU	0.00E+00	0.00E+00
CBX	0.00E+00	0.00E+00
CCS	0.00E+00	0.00E+00
BETAAC	200.000	200.000
FT	4.36E+17	4.36E+17

**** SMALL-SIGNAL CHARACTERISTICS

V(6)/VIN	=	1.3670+02
INPUT RESISTANCE AT VIN	=	1.4580+04
OUTPUT RESISTANCE AT V(6)	=	1.0000+04

JOB CONCLUDED

CPU	TIME ELAPSED	PAGE FAULTS	DIRECT I/O	BUFFERED I/O
0: 0: 0.58	0: 0: 1.61	36	7	1


4 Recall from Lecture #1 that the linear approximation holds only for $v_{be} \ll V_T$ (all quadratic or higher-order terms in v_{be}/V_T were neglected). The approximation is accurate to within 50% for $v_{be} < V_T$. $\therefore$ Find maximum input values V_A and V_B such that small-signal $v_{be} < V_T$

→ Differential Mode (determine V_A):

Neglect r_b, r_μ, r_o :

By inspection,
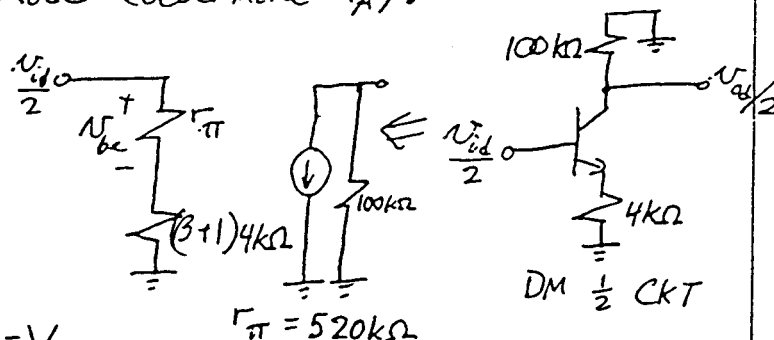
$$v_{be} = \frac{r_\pi}{r_\pi + (\beta+1)(4k)} \frac{v_{id}}{2}$$



Set $v_{be} = V_T$ for $v_{id} = V_A$

$$v_{id} \Big|_{v_{be}=V_T} = V_A = \frac{(2)(V_T)(r_\pi + (\beta+1)4k)}{r_\pi} = 132.4 \text{ mV} \Rightarrow V_A = 132 \text{ mV} = 0.132 \text{ V}$$

for $V_T = 26 \text{ mV}$

- Answer -

$$V_A = 132 \text{ mV} = 0.132 \text{ V}$$

Maximum Differential Input

→ Common Mode (determine V_B)


Neglect $4k\Omega$ compared to $20M\Omega$:

$$v_{be} = \frac{r_\pi}{r_\pi + (\beta+1)(20M\Omega)} v_{ic}$$

Set $v_{be} = V_T$ to find $v_{ic} = V_B$

$$v_{ic} \Big|_{v_{be}=V_T} = V_B = \frac{(V_T)(r_\pi + (\beta+1)20M\Omega)}{r_\pi}$$
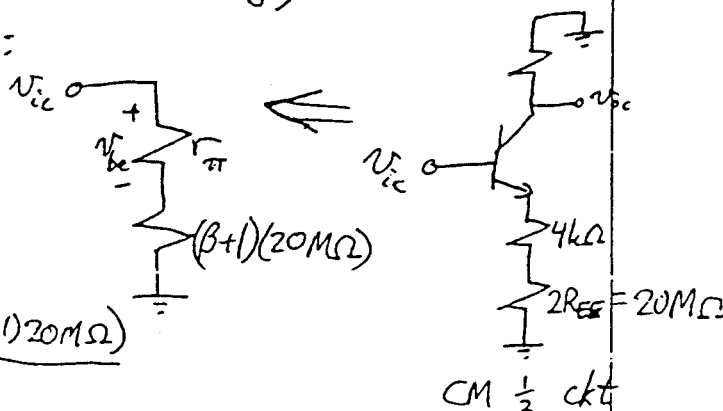
$$= \frac{(26 \text{ mV})(520k + 4020M\Omega)}{520k} = 201 \text{ V} \text{ for } \beta=200, V_T=26 \text{ mV}$$




$$V_B = 201 \text{ V}$$

- Answer -

Maximum CM Input
for ss. linearity

Note that other factors (e.g. entering sat., supplies and breakdowns) will prevent the circuit from violating this CM linearity limit (V_B).

5.

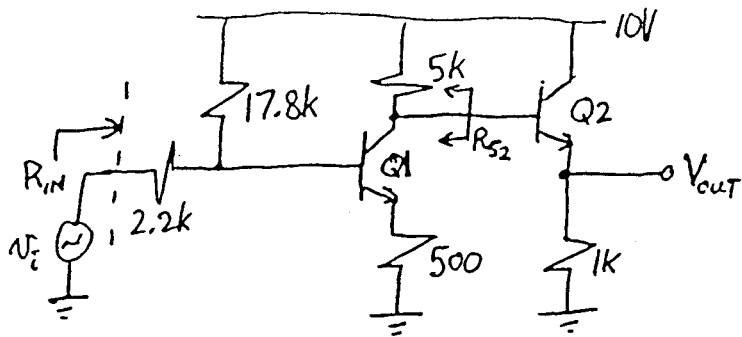

Neglecting base current in Q1, the DC Base Voltage of Q1 is

$$V_{B1} = \frac{2.2k}{2.2k + 17.8k} (10V) = 1.1V$$

KVL $V_{B1} - V_{BE1} - (I_{E1})(500\Omega) = 0$

$$V_{BE1} \approx 1.1V - (I_{C1})(500\Omega) \quad \text{for } I_C \approx I_E$$

Neglecting Early Effect $\rightarrow V_{BE1} = V_T \ln \frac{I_{C1}}{I_{S1}} = 1.1V - (I_{C1})(0.5k\Omega)$ $I_S = 5 \times 10^{-15} A$ from fig 2.23

$$(0.026V) \ln \frac{I_{C1}}{5 \times 10^{-12} \text{ mA}} = 1.1V - I_{C1}(0.5k\Omega) \quad \leftarrow \text{Iterate to find } I_{C1}$$

$$I_{C1} = 0.855 \text{ mA} = 855 \mu A \quad \boxed{\text{HSPICE: } I_{C1} = 848 \mu A}$$

Note that $V_{BE1} = 0.7V$ was NOT used to determine I_{C1} because the 500 ohm only has about 0.4 V across it, and a 100 mV discrepancy in V_{BE} is significant (in this case, $V_{BE} = 0.67V$).

Note also that at $\beta = 200$, $I_{B1} \approx 4.3 \mu A \ll \frac{10V}{20k\Omega} = 500 \mu A$, so the voltage divider approximation for V_{B1} is good!

$$I_{C1} = 855 \mu A \rightarrow g_{m1} = \frac{855 \mu A}{26 \text{ mV}} = 32.9 \text{ mS} \rightarrow r_{\pi 1} = \frac{200}{32.9 \text{ mS}} = 6.08 \text{ k}\Omega$$

$$V_{B2} = V_{C1} = 10V - (5k\Omega)(855 \mu A) = 5.73V \quad r_{o1} = \frac{130V}{855 \mu A} = 152 \text{ k}\Omega$$

$$\therefore V_{out} \approx V_{B2} - 0.7V \approx 5.0 \text{ VDC} \quad \boxed{\text{HSPICE: } I_{C2} = 4.9 \text{ mA}}$$

$$I_{C2} \approx \frac{V_{out}}{1k\Omega} = 5.0 \text{ mA} \rightarrow g_{m2} = \frac{5.0 \text{ mA}}{26 \text{ mV}} = 192 \text{ mS} \rightarrow r_{\pi 2} = \frac{200}{192 \text{ mS}} = 1.04 \text{ k}\Omega$$

$$r_{o2} = \frac{130V}{5 \text{ mA}} = 26 \text{ k}\Omega$$

For CEWD, plus by inspection of above diagram:

$$R_{in} = 2.2k\Omega + (17.8k\Omega) \parallel (r_{\pi 1} + (\beta + 1)R_E)$$

$$= 2.2k + (17.8k) \parallel (6.08k + (201)(500\Omega)) = 17.5k\Omega$$

$$\Rightarrow \boxed{R_{in} = 17.5k\Omega}$$

- Answer -

$$\boxed{\text{HSPICE } R_{in} = 17.47k\Omega}$$

R_{out} is that for a CC stage (see Handout)

$$R_{out} = (1k\Omega) \parallel (R_{o2}) \quad R_{o2} \approx \frac{1}{g_{m2}} + \frac{R_{s2}}{\beta+1} \quad \text{where } R_s \text{ is that looking back into the CEWD}$$


$$\begin{aligned} R_{o1}' = R_{s2} &= 5k\Omega \parallel R_{o1} \approx (5k\Omega) \parallel \left[r_{o1} (1 + g_{m1} R_{E1} \frac{r_{\pi1}}{r_{\pi1} + R_{s1} + R_{E1}}) \right] \\ &= 5k\Omega \parallel \left[(152k\Omega) (1 + (32.9mV)(0.5k\Omega) \frac{6.08k\Omega}{6.08k + 0.5k + 2.2k \parallel 17.8k}) \right] \\ &= 5k\Omega \parallel 1.93M\Omega \approx 5k\Omega \end{aligned}$$

$$R_{out} = (1k\Omega) \parallel \left(\frac{1}{192mV} + \frac{5k\Omega}{201} \right) = 1k\Omega \parallel 30.1\Omega$$

$$R_{out} \approx 29\Omega \quad \text{-Answer-}$$

$$\text{HSPICE } R_{out} = 31.5\Omega$$

For A_v :

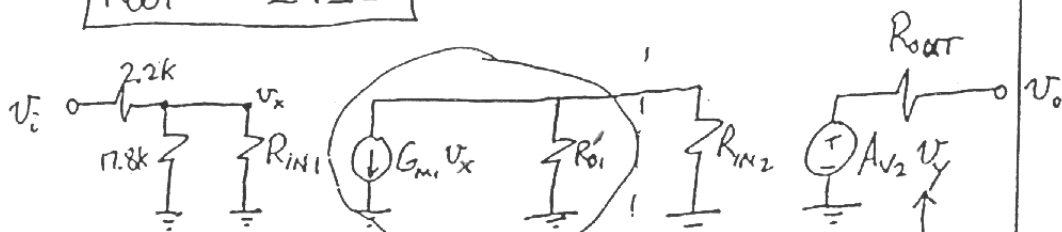

V_y is defined after Thevenizing input to CEWD

From Single Xstr Handout:

$$R_{in1} = r_{\pi1} + (\beta+1)R_{E1} = 106.6k\Omega$$

$$G_{m1} \approx \frac{g_{m1}}{1 + g_{m1}R_{E1}} = \frac{32.9mV}{1 + (32.9mV)(0.5k\Omega)} = 1.89mV$$

$$R_{in2} = r_{\pi2} + (\beta+1)(R_{L2} \parallel R_{o2}) = 1.04k\Omega + (201)(1k\Omega \parallel 26k\Omega) = 195k\Omega$$

$$A_v = \left(\frac{R_{in1} \parallel 17.8k}{R_{in1} \parallel 17.8k + 2.2k} \right) (G_{m1} R_{o1}') (A_{v2})$$

$$A_{v2} \approx \frac{R_{L2}}{R_{L2} + R_{o2}} = \frac{1k\Omega}{1k\Omega + 30.1\Omega} = 0.971$$

$$A_v = \left(\frac{106.6k \parallel 17.8k}{106.6k \parallel 17.8k + 2.2k} \right) (-1.89mV)(5k\Omega)(0.971)$$

$$A_v = -8.00 \quad \text{-Answer-}$$

$$\text{HSPICE } A_v = -7.96 \text{ at } 1kHz$$

6) Compute $V_o(t)$ for the circuit below. Use $\frac{1}{2}$ ckt analysis technique. Assume all xtrs are FAR wthd $I_C = 1\text{mA}$

$$V_{i1} = 4\text{mV} \sin 10t$$


$$V_{i2} = 6\text{mV} \sin 10t$$

$$\begin{aligned} V_{id} &= V_{i1} - V_{i2} \\ &= -2\text{mV} \sin 10t \end{aligned}$$

$$\begin{aligned} V_{ic} &= \frac{V_{i1} + V_{i2}}{2} \\ &= 5\text{mV} \sin 10t \end{aligned}$$

the dotted line in the ckt is the line of symmetry. Can use $\frac{1}{2}$ ckt analysis.
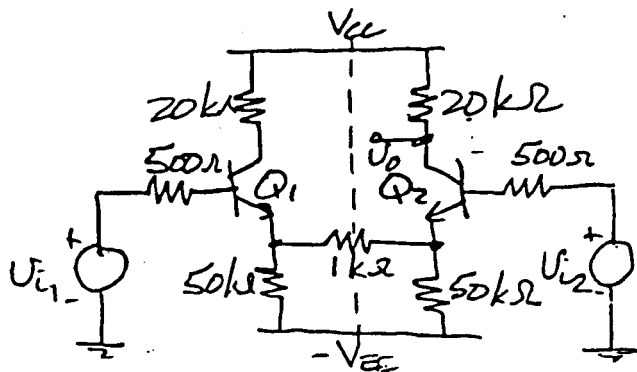
$$\begin{aligned} V_o(t) &= -\frac{V_{od}}{2} + V_{oc} \\ &= -A_{dm} \frac{V_{id}}{2} + A_{cm} V_{ic} \end{aligned}$$



$$I_C = 1\text{mA}$$

$$g_{m1} = g_{m2} = \frac{I_C}{V_T} = \frac{1\text{mA}}{26\text{mV}}$$


$$= 38.5\text{mS}$$

$$\begin{aligned} r_{\pi 1} = r_{\pi 2} &= \frac{\beta}{g_m} = \frac{200}{38.5\text{mS}} \\ &= 5.2\text{k}\Omega \end{aligned}$$

$$\begin{aligned} r_{o1} = r_{o2} &= \frac{V_A}{I_C} = \frac{130\text{V}}{1\text{mA}} \\ &= 130\text{k}\Omega \end{aligned}$$

DM $\frac{1}{2}$ ckt analysis

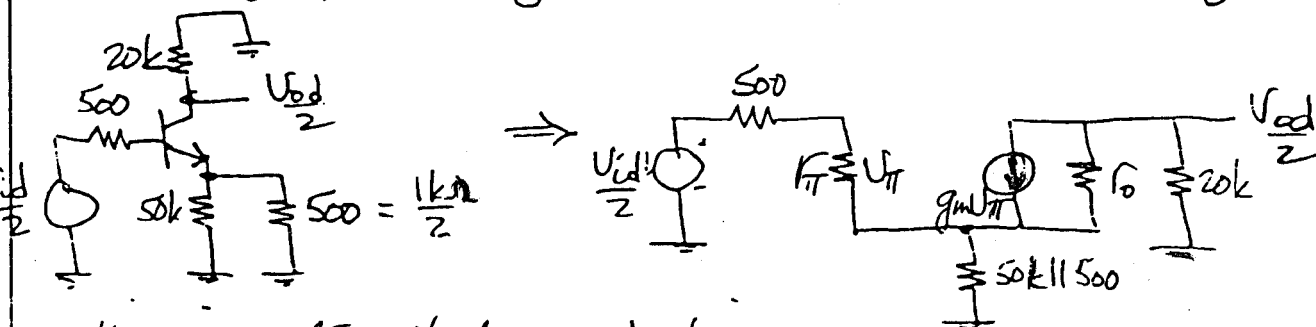axis of symmetry is small signal vertical gnd.



this is CE w/ degeneration

$$\begin{aligned} \Rightarrow A_{dm} &= A(\text{CE w/ deg}) = -\left(\frac{R_{id}}{R_{id} + R_s}\right) G_m R_{od} \parallel R_c \\ &\approx -\left(\frac{R_{id}}{R_{id} + R_s}\right) G_m R_c \end{aligned}$$

cont'd)

$$R_{id} = 2R_i(\text{CE w/ deg}) = r_{\pi} + (\beta+1)R_E \quad \leftarrow 50k \parallel 500$$

$$= (5.2k + (201)495)2$$

$$= 209 \text{ k}\Omega$$

$$G_m = \frac{g_m}{1 + g_m R_E} = \frac{38.5 \text{ mS}}{1 + (38.5 \text{ mS})(495\Omega)} = 1.92 \text{ mS}$$


$$A_{dm} = - \left(\frac{209 \text{ k}\Omega}{209 \text{ k}\Omega + 500\Omega} \right) (1.92 \text{ mS}) (20 \text{ k}\Omega)$$

$$A_{dm} = -38.4$$

cm $\frac{1}{2}$ ckt analysis

line of symmetry is open ckt for OSS analysis. ($I=0$)

again this looks like CE w/ degeneration

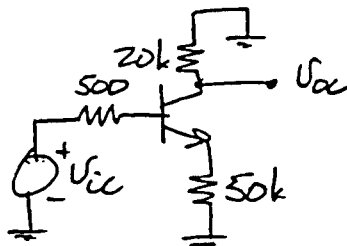

$$A_{cm} = - \left(\frac{R_{ic}}{R_s + R_{ic}} \right) G_m R_c$$

$$R_{ic} = R_i(\text{CE w/ degen}) = r_{\pi} + (\beta+1)R_E$$

$$= 5.2k + (201)(50k)$$

$$= 10 \text{ M}\Omega$$

$$\frac{R_{ic}}{R_s + R_{ic}} \approx 1$$

$$G_m = \frac{g_m}{1 + g_m R_E} = \frac{38.5 \text{ mS}}{1 + (38.5 \text{ mS})(50k)}$$

$$= 19.99 \times 10^{-6} \text{ S}$$

$$A_{cm} = - (19.99 \times 10^{-6})(20k) \Rightarrow A_{cm} = -0.4$$

$$V_o(t) = - \frac{(-38.4)(-2 \text{ mV} \sin 10t)}{2} + (-.4)(5 \text{ mV} \sin 10t)$$

$$V_o(t) = -40.4 \text{ mV} \sin 10t \text{ V}$$