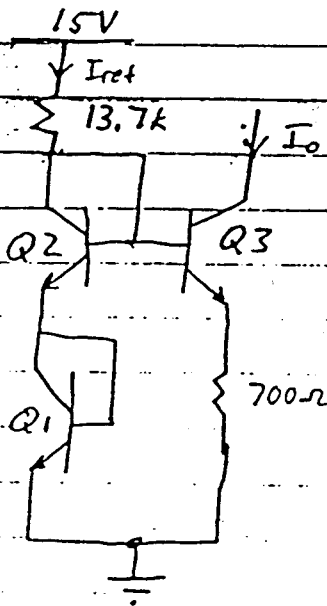


PS#5 HW SOLUTIONS 114

1) DETERMINE OUTPUT CURRENT AND OUTPUT RESISTANCE OF THE Ckt Below

Assume $I_S = 5 \times 10^{-15}$
 $\beta = 200$
 $V_A = 130V$ } Fig 2.30



$$I_{ref} = \frac{15V - 1.4V}{13.7k\Omega} = 0.993mA$$

$$V_{CE1} + V_{CE2} \approx V_{CE3} + I_O(700\Omega)$$

$$V_T \ln \frac{I_{ref}}{I_S} + V_T \ln \frac{I_{ref}}{I_S} = V_T \ln \frac{I_O}{I_S} + I_O(700\Omega)$$

$$V_T \ln \frac{I_{ref}^2}{I_S^2} = V_T \ln \frac{I_O}{I_S} + I_O(700)$$

$$V_T \ln \frac{I_{ref}^2}{I_S I_O} = I_O(700)$$

$$SO I_O = \frac{V_T}{700} \ln \left(\frac{I_{ref}^2}{I_S I_O} \right) = \frac{.026}{700} \ln \left(\frac{.993 \times 10^{-3}}{5 \times 10^{-15} I_O} \right)^2$$

$$I_O = \frac{.026}{700} \ln \left(\frac{1.972 \times 10^{-8}}{I_O} \right)$$


TRIAL & ERROR $\Rightarrow I_O \approx .97mA$

$$R_o = R_{o, CE \text{ w/ } d_{e3}} \approx r_{o3} \left(1 + g_{m3} R_E \frac{r_{\pi3}}{r_{\pi3} + R_{S3} + R_E} \right)$$

$$= \frac{130V}{0.97mA} \cdot \left(1 + \frac{0.97mA}{26mV} \cdot (700\Omega) \cdot \frac{5.4k}{5.4k + 52 + 700} \right) \approx \underline{\underline{3.2M\Omega}}$$

$$R_{S3} = \left(\frac{1}{g_{m2}} + \frac{1}{g_{m1}} \right) \parallel 13.7k\Omega = (2) \left(\frac{26mV}{0.993mA} \right) \parallel 13.7k\Omega \approx 52\Omega$$

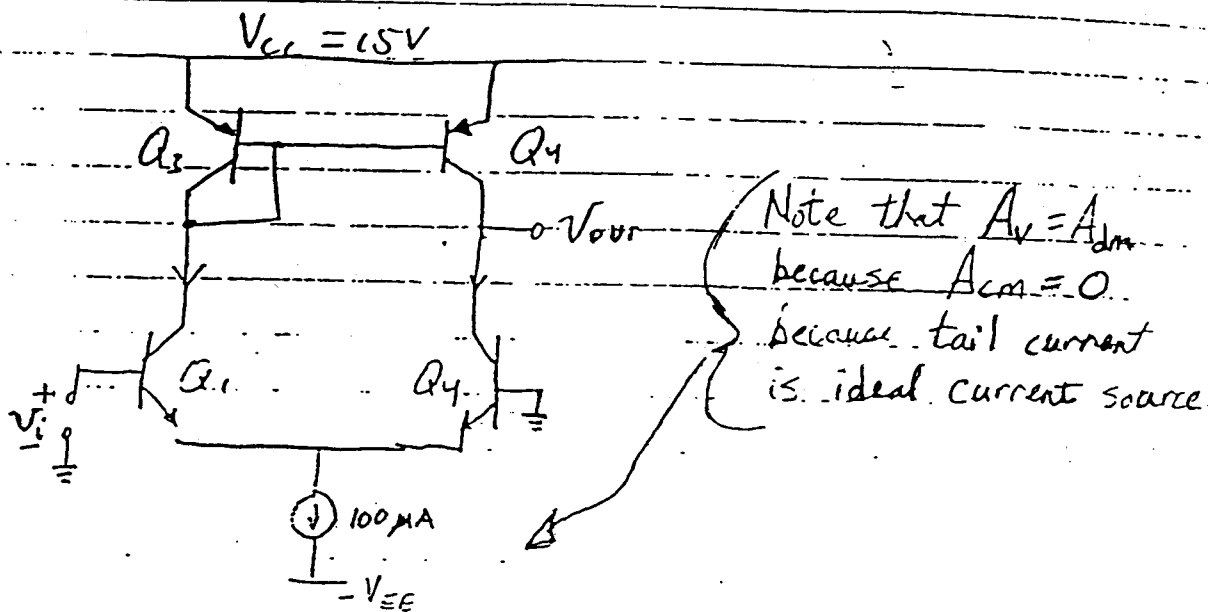2) Determine the UNLOADED VOLTAGE GAIN AND OUTPUT RESISTANCE for the CIRCUIT:



$$I_1 \approx I_2 \approx 50 \mu A$$

$$R_{out} = r_{opnp} \parallel r_{onpn}$$

$$r_{opnp} = \frac{V_A}{I_C} = \frac{50V}{50\mu A} = 1 \text{ MEG}$$

$$r_{onpn} = \frac{130V}{50\mu A} = 2.6 \text{ M}\Omega$$

$$R_{out} = 1 \text{ MEG} \parallel 2.6 \text{ MEG} = 722 \text{ K}\Omega$$

- Answer -

$$G_m = g_m$$

$$A_v = g_m R_{out} = \frac{50\mu A}{0.025} (722 \text{ K})$$

$$A_v = 1388$$

- Answer -

Alternatively, $A_v = \frac{1}{r_{opnp} + r_{onpn}}$

$$A_v = 1429$$

- Answer -

simple bjt model (44V)

$$\text{HSPICE : } A_v = 1456$$


The discrepancy between these two values for A_v is due to roundoff error between the values for η and V_A given in Figures 2.30 and 2.37.

3


To solve this, we must go back to the single xstr. models used to solve the active load w/o degeneration case

⇒ Now Q4 is no longer a CE xstr. ($G_m = g_m, R_o = r_o$), but a CEWD!

⇒ Use single xstr. handout for CEWD

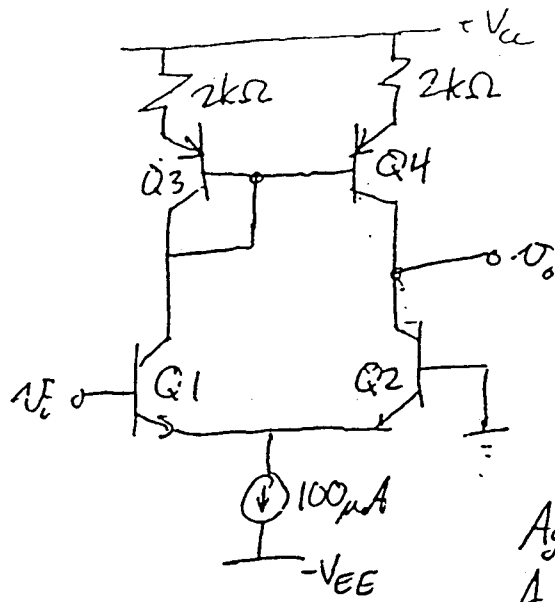

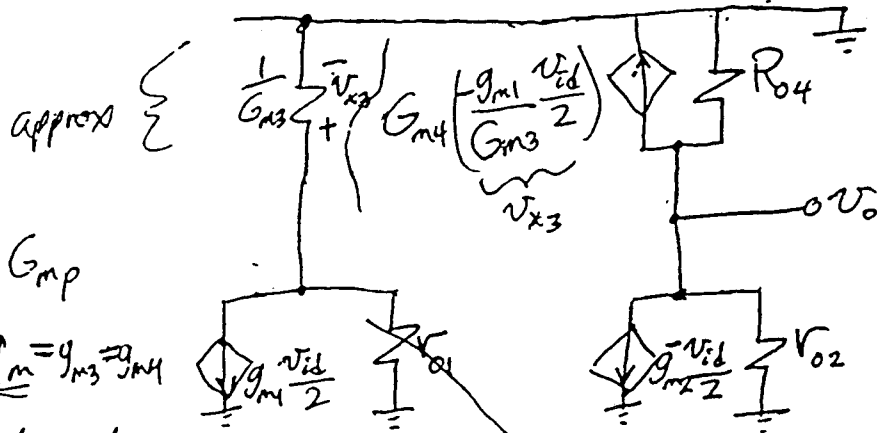Again,
 $A_{cm} = 0$
 $\Rightarrow A_v = A_{dm}$



Since

$$G_{m3} = G_{m4} = G_{mp}$$


$$g_{m1} = g_{m2} = \underline{g_m} = g_{m3} = g_{m4}$$

The output side reduces to:

neglect compared to $\frac{1}{G_{m3}} = 2.56k$

$$g_m = \frac{50 \mu A}{26 mV} = 1.92 mS$$
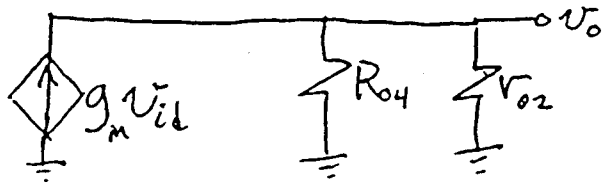
$$r_{o2} = r_{o_{npn}} = \frac{130V}{50 \mu A} = 2.6 M\Omega$$



$$R_{o4} \approx r_{o_{pnp}} \left(1 + g_m R_E \frac{r_{\pi 4}}{r_{\pi 4} + R_{S4} + R_E} \right) \text{ where } r_{o_{pnp}} = 1 M\Omega, R_E = 2 k\Omega, r_{\pi 4} = 26 k\Omega$$

$$= (1 M\Omega) \left[1 + (1.92 mS)(2 k\Omega) \left(\frac{26 k\Omega}{26 k\Omega + 2.52 k\Omega + 2 k\Omega} \right) \right]$$

$$R_{S4} = \left(\frac{1}{g_m} + 2 k\Omega \right) \parallel r_{o1} \approx 2.52 k\Omega$$

$$= \underline{4.28 M\Omega}$$

$$\therefore R_{out} = R_{o4} \parallel r_{o2} = 4.28 M\Omega \parallel 2.6 M\Omega \Rightarrow \boxed{R_{out} = 1.62 M\Omega}$$

$$A_v = A_{dm} = g_m (R_{o4} \parallel r_{o2}) = (1.92 mS)(1.62 M\Omega) \Rightarrow \boxed{A_v = 3110}$$

(continued)

-Answer-
 -Answer

Alternate Method

You may have noticed in the solution that the only thing that changed from problem #2 is the R_{out} of the active load.

i.e. $r_{opp} \rightarrow (R_{out})_{CEWD}$

This shows an alternate and much simpler method:

Method #2.


Notice that the pnp mirror IS a mirror, i.e. the current on the left is repeated on the right (since emitter resistors are matched also). This works for ac as well as dc currents

∴ if Q1 produces small signal output current $(g_m \frac{v_{id}}{2})$, then

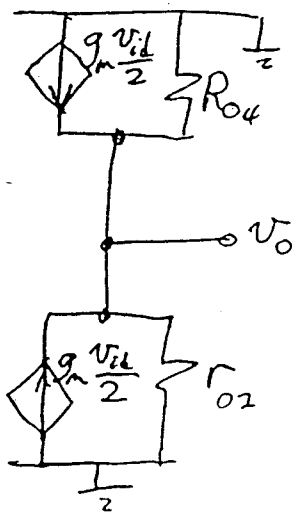Q4 must mirror approximately $g_m \frac{v_{id}}{2}$.

∴ only R_{out} changes for Q4; the dependent current generator remains the same!*

* R_{o4} must still be calculated as before using $(R_o)_{CEWD}$.




4)

$$(a) I_R = \frac{V_{CC} - V_{BE3}}{R_3} = \frac{15 - 0.7}{5K} = 2.86 \text{ mA}$$


Thus, $I_Q = 2.86 \text{ mA}$

$$I_Q R_L = 2.86 (2) = 5.72 \text{ V}$$

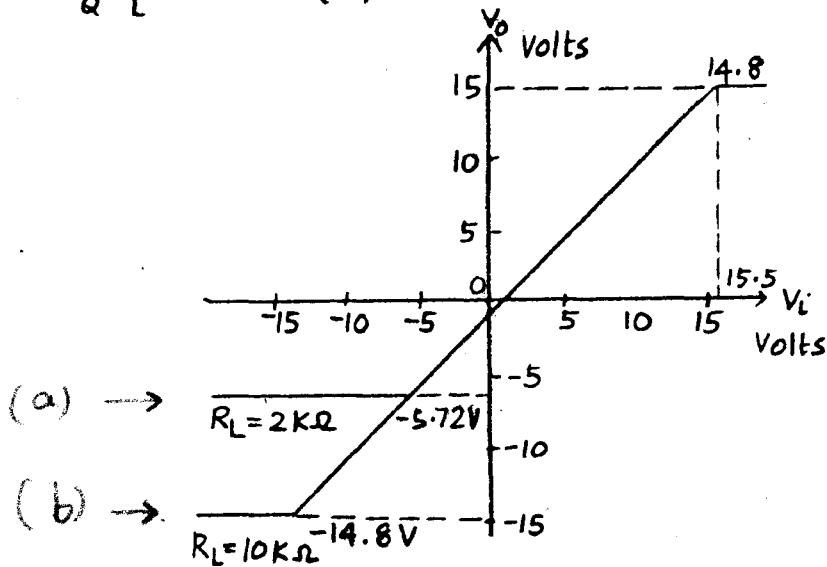

$$(b) I_Q R_L = 2.86 \times 10 = 28.6 \text{ V}$$

Thus, the lower limit on V_o is $(-V_{CC} + |V_{CE,sat}|)$
 \parallel
 -14.8 V

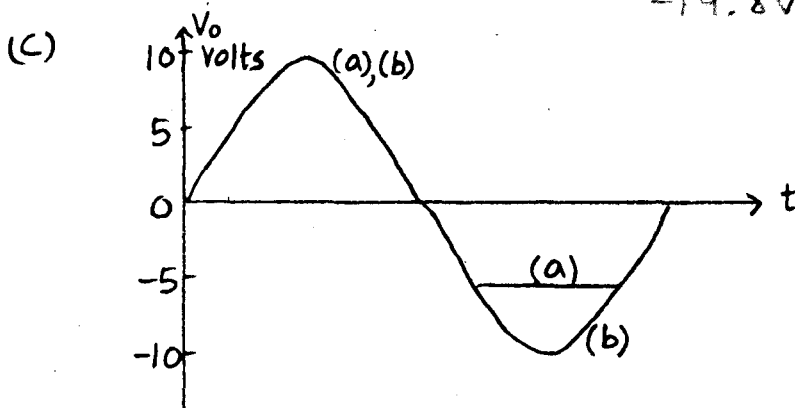

(a): output clips
 at -5.72 V

(b): no clipping