

- 1) determine output current as a function of input voltage. assume transistor is FAR


the op amp is given to be ideal. so we can immediately say:

$$\text{virtual short} \Rightarrow V_1 = V_2 = V_{in}$$

$$\Rightarrow V_R = V_{in} \Rightarrow I_O = \frac{V_R}{R} \Rightarrow \boxed{I_O \approx \frac{V_{in}}{R}}$$

actually $I_C = \alpha I_E$


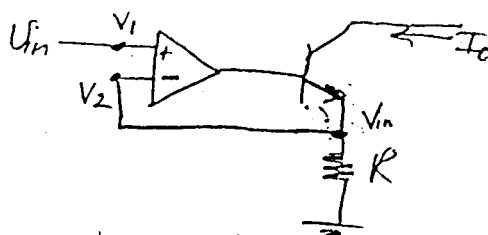
$$\Rightarrow \boxed{I_O = \frac{\alpha V_{in}}{R}}$$



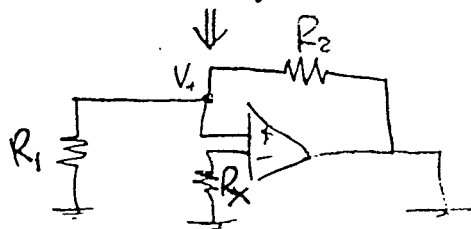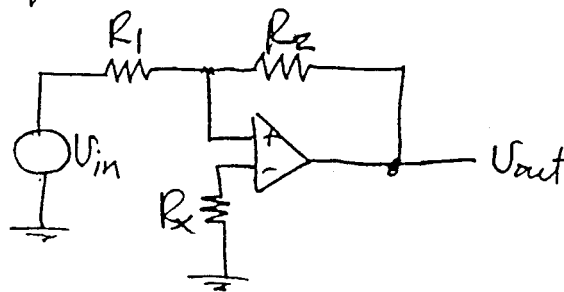
- 2) In the circuit below, determine the correct value of R_x so that the output voltage is zero when the input voltage is zero. Assume finite input bias current, but zero input offset current and voltage.

want $V_o = 0$ when $V_{in} = 0$

redraw the circuit with output & input shorted to zero.



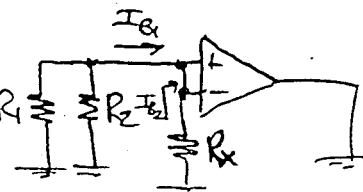R_2 & R_1 go between V_+ & ground $\Rightarrow$



because of the high gain of the amplifier, we can assume a virtual short between input terminals: $V_+ = V_-$

$$V_+ = -I_{B1}(R_1 \parallel R_2), \quad V_- = -I_{B2}R_x$$

$$\text{since } V_+ = V_- \quad I_{B1}(R_1 \parallel R_2) = I_{B2}R_x$$


$$\text{given that } I_{B1} = I_{B2} \quad (\text{offset current} = 0) \Rightarrow \boxed{R_x = R_1 \parallel R_2}$$

3)

(a) find the DC operating currents.

(1) find current of current source

since $\beta = 200$, it is fairly safe to assume all I_B 's = 0.

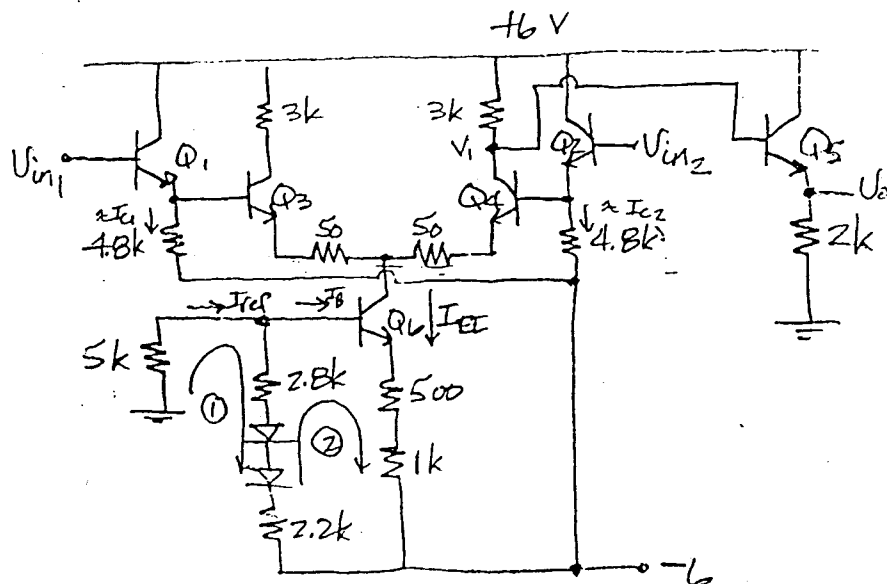KVL @ ①:

$$-I_{ref} \cdot 5.0k - I_{ref} \cdot 2.8k - 1.4 - I_{ref} \cdot 2.2k - (-6) = 0$$

$$I_{ref}(-5k - 2.8k - 2.2k) = -6 + 1.4 = -4.6$$

$$I_{ref}(10k) = -4.6 \Rightarrow \underline{I_{ref} = 460 \mu A}$$

KVL @ ②:

$$I_{ref} \cdot 2.2k + 1.4 + I_{ref} \cdot 2.8k - V_{BE6} - 500 \cdot I_{EE} - 1k \cdot I_{EE} = 0$$

$$5k \cdot I_{ref} - V_{BE6} + 1.4 = 1.5k I_{EE}$$

$$\frac{(5k \times 460 \mu) + 1.4 - V_T \ln \frac{I_{EE}}{I_S}}{1.5k} = I_{EE}$$

$$2.47m - 17.33 \mu \ln \left(\frac{I_{EE}}{5 \times 10^{-15}} \right) = I_{EE}$$

by trial & error

$$1^{st} \text{ guess: } \underline{I_{EE} = 2mA}$$

wow, I got it on the 1st try! All my EE experience has paid off!

(2) current through collectors of diff pair

$$\underline{I_{C3} = I_{C4} \approx \frac{I_{EE}}{2} = 1mA} \quad (\text{matched transistors})$$

(3) current through collector of Q5

$$V_B \text{ of } Q5 = V_{CC} - I_{C4} R_C = 6 - (1mA)(3k\Omega) = 3V$$

$$V_{E5} = 3.0V - 0.7V = 2.3V$$

$$\underline{I_{E5} = \frac{2.3V}{2k\Omega} \Rightarrow I_{E5} = 1.15mA}$$

3 cont'd)

(4) I_{E1} & I_{E2}

assume $V_{B1} = V_{B2} = 0$.

$$V_{E1} = V_{E2} = -0.7V$$



$$\underline{I_{E1} = I_{E2} \approx \frac{0 - (-0.7)}{4.8k} = 1.1mA}$$

(b) find R_{id} , R_o , $A = \frac{U_o}{U_{id}}$


new circuit

this circuit is $\approx$ symmetric $\Rightarrow$ use half circuit analysis

1st find gain of diff pair and then the gain of CC output stage and multiply together.

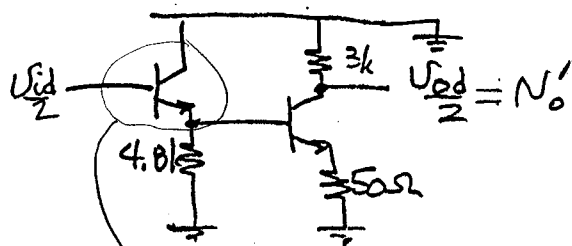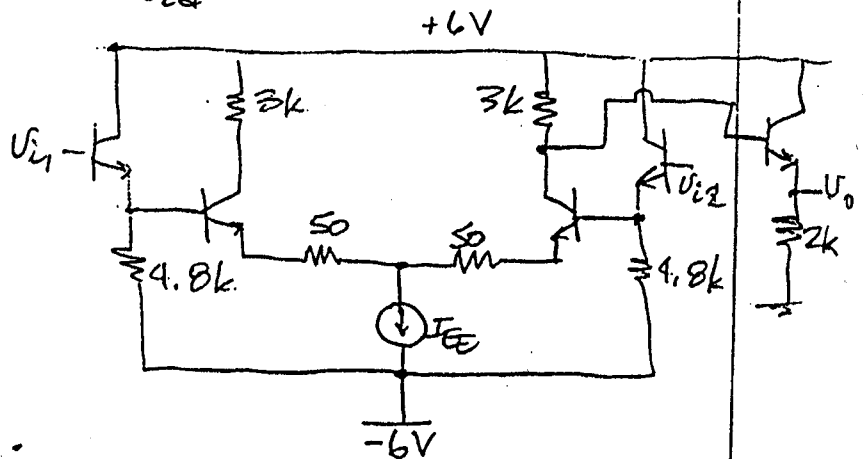DM $\frac{1}{2}$ ckt w/o Q5 (C.C. buffer):

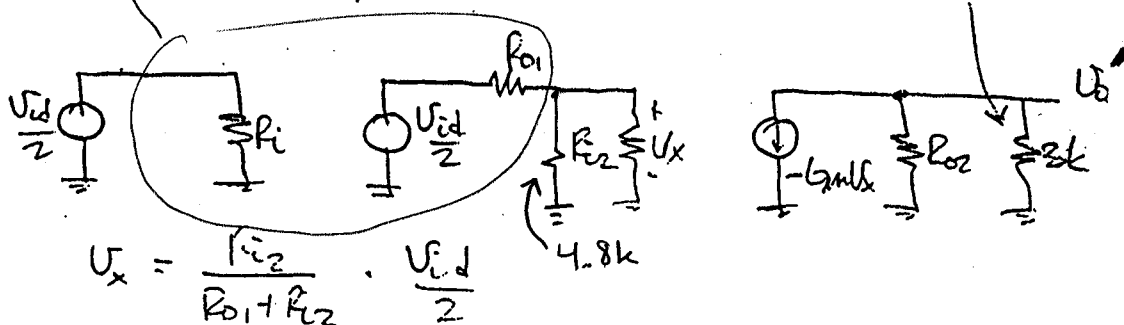CC, CE w/ deg
 R_i of CC_3 is very large
 $\Rightarrow R_i \parallel 3k \approx 3k$



$$U_x = \frac{R_{i2}}{R_{o1} + R_{i2}} \cdot \frac{U_{id}}{2}$$

$$R_{i2} = R_i (CE w/ deg) = r_{\pi 3} + (\beta + 1)R_{E3} = 5.2k + (201)(50)$$

$$\underline{R_{i2} = 15.2k\Omega}$$

$$R_{o1} = R_o(CC) = \frac{r_{\pi}}{\beta + 1} (R_s = 0) = \frac{4.72k}{201} = 23\Omega$$

$$\Rightarrow U_x = \frac{4.8k \parallel 15.2k}{4.8k \parallel 15.2k + 23} \cdot \frac{U_{id}}{2} \Rightarrow U_x \approx \frac{U_{id}}{2}$$

3 cont'd)

4/4 P.4

$$V_o' = -G_m V_x (R_{o2} \parallel 3k) \Rightarrow \frac{V_o'}{V_{id}/2} = -G_m (R_{o2} \parallel 3k)$$

$$R_{o2} = f_o(\text{CE w/deg}) \approx r_o (1 + g_m R_E) \quad \left[\begin{array}{l} \text{ignore } R_s \text{ \& } R_E \\ \text{since } r_{\pi} \gg R_s + R_E \end{array} \right]$$

$$g_{m3} = \frac{I_{E3}}{V_T} = \frac{1\text{mA}}{26\text{mV}} = 38.5\text{mS}$$

$$\Rightarrow R_{o2} = \frac{120}{1\text{mA}} (1 + (38.5\text{m})(50)) = 380\text{k}\Omega$$

$$\Rightarrow R_{o2} \parallel 3k \approx 3k\Omega$$

$$G_m = \frac{g_m}{1 + g_m R_E} = \frac{38.5\text{m}}{1 + (38.5\text{m})(50)} = 13.2\text{mS}$$

$$\frac{V_o'}{V_{id}/2} = -(13.2\text{mS})(3k\Omega) = -39$$

$$A_{cc} = 1 \cdot \left(\frac{R_L}{R_L + R_{o3}} \right) \Rightarrow R_{o3} = \frac{r_{\pi3} + R_{s3}}{\beta + 1} = \left(\frac{220 \left(\frac{2k\Omega}{1.15\text{m}} \right) + 3k}{201} \right) = 37\Omega$$

$$A_{cc} = 1 \cdot \left(\frac{2k}{2k + 37} \right) \approx 1$$

$$\Rightarrow \left| \frac{V_o}{V_{in}} \right| \approx \frac{1}{2} \cdot \frac{V_o'}{V_{id}/2} = (-39)^{\frac{1}{2}} = -19.5\text{A}$$

$$R_{out} = R_{o3}(\text{w/out load}) \approx 37\Omega = R_{out}$$

$$R_{id} = \frac{V_{id}}{i_{b1}} \approx [r_{\pi} + (\beta + 1)R_E] \times 2$$

$$R_E = 4.8k \parallel R_{i2} = 4.8k \parallel 15.2k = 3.64k\Omega$$

$$R_{id} = [4.7k\Omega + (201)3.64k\Omega] \times 2$$

$$R_{id} = 736k\Omega \times 2 = 1.47\text{M}\Omega$$