

1

(a) Transistor parameters are:

$$r_{\pi} = \frac{\beta_o}{g_m} = 200 \times 52 = 10.4 \text{ k}\Omega$$

$$\tau_T = \frac{1}{2\pi f_T} = 318 \text{ ps}$$

$$C_{\pi} + C_{\mu} = g_m \tau_T = \frac{1}{52} \times 318 = 6.12 \text{ pF}$$

$$\therefore C_{\pi} = 6.1 - 0.3 = 5.8 \text{ pF}$$

$$\begin{aligned} C_M &= (1 + g_m R_L) C_{\mu} \\ &= \left(1 + \frac{3000}{52}\right) \times 0.3 = 17.6 \text{ pF} \end{aligned}$$

In (7.12)

$$\begin{aligned} f_{-3\text{dB}} &= \frac{1}{2\pi} \frac{5000 + 300 + 10400}{(5000 + 300) \times 10400} \frac{10^{12}}{5.8 + 17.6} \\ &= 1.94 \text{ MHz} \end{aligned}$$

(b) From (7.27)

$$P_2 = - \left(\frac{1}{R_L C_{\mu}} + \frac{1}{R C_{\pi}} + \frac{1}{R_L C_{\pi}} + \omega_T \right)$$

$$\begin{aligned} R &= (R_S + r_b) \parallel r_{\pi} \\ &= 5300 \parallel 10400 = 3511 \Omega \end{aligned}$$

$$\begin{aligned} \therefore P_2 &= - \left(\frac{10^{12}}{3000 \times 0.3} + \frac{10^{12}}{3511 \times 5.8} + \frac{10^{12}}{3000 \times 5.8} \right. \\ &\quad \left. + 2\pi \times 500 \times 10^6 \right) \\ &= -43.6 \times 10^8 \text{ rad/sec} \\ &= -693 \text{ MHz} \end{aligned}$$

#2

$$C_{\pi} + C_u = \frac{g_m}{2\pi f_T} = \frac{1}{2\pi \times 26 \times 500 \times 10^6}$$

$$= 12.2 \text{ pF at } I_C = 1 \text{ mA}$$

$$\therefore C_{\pi} = 11.8 \text{ pF}$$

$$r_{\pi} = \frac{\beta}{g_m} = 2.6 \text{ k}\Omega, r_o = \infty$$

(a) For each circuit

$$\frac{v_o}{v_i} = - \frac{r_{\pi}}{r_{\pi} + R_s} g_m R_L$$

$$= - \frac{2.6}{2.6 + 5} \frac{3000}{26} = -39.5$$

(b) Common Emitter

$$R_{\pi 0} = r_{\pi} \parallel R_s = 2.6 \parallel 5 = 1.71 \text{ k}\Omega$$

$$R_{u0} = R_{\pi 0} + R_L + g_m R_L R_{\pi 0}$$

$$= 1.71 + 3 + \frac{3000}{26} \times 1.71$$

$$= 202 \text{ k}\Omega$$

$$C_{\pi} R_{\pi 0} = 11.8 \times 1.71 = 20.2 \text{ ns}$$

$$C_u R_{u0} = 0.4 \times 202 = 80.8 \text{ ns}$$

$$C_{cs} R_L = 1 \times 3 = 3 \text{ ns}$$

$$\therefore \Sigma T_o = 20.2 + 80.8 + 3 = 104 \text{ ns}$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \Sigma T_o} = 1.53 \text{ MHz}$$

Cascode

$$C_{\pi 1} R_{\pi 01} = 20.2 \text{ ns}$$

$$R_{u01} = R_{\pi 01} + R_{L1} + g_{m1} R_{L1} R_{\pi 01}$$

$$R_{L1} = \frac{1}{g_{m2}} = 26 \Omega$$

$$\therefore R_{u01} = 1.71 + 0.026 + \frac{1}{26} \times 26 \times 1.71$$

$$= 3.45 \text{ k}\Omega$$

$$\therefore C_{u1} R_{u01} = 0.4 \times 3.45 = 1.38 \text{ ns}$$

$$C_{cs1} R_{L1} = 1 \times 0.026 = 0.026 \text{ ns}$$

$$R_{\pi 02} = \frac{1}{g_{m2}} = 26 \Omega$$

$$\therefore C_{\pi 2} R_{\pi 02} = 11.8 \times 0.026 = 0.31 \text{ ns}$$


$$(C_{u2} + C_{cs2}) R_{L2} = 1.4 \times 3 = 4.2 \text{ ns}$$

$$\therefore \Sigma T_o = 20.2 + 1.38 + 0.31 + 4.2 = 26.1 \text{ ns}$$

$$\therefore f_{-3dB} = 6.1 \text{ MHz}$$

This is 4 times higher than the common-emitter stage. because Miller effect in Q_1 is eliminated.

#3

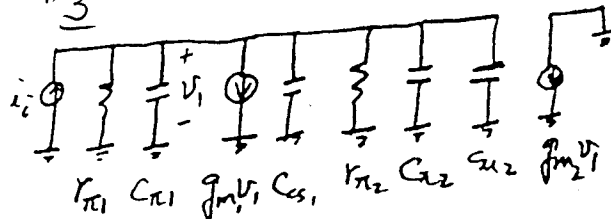

$$v_i = i_i (r_{\pi 1} \parallel \frac{1}{g_{m1}} \parallel r_{\pi 2})$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = 200 \times 26 = 5.2 \text{ k}\Omega$$

$$\frac{1}{g_{m1}} = 26 \Omega$$

$$r_{\pi 2} = \frac{\beta}{g_{m2}} = 200 \times \frac{26}{4} = 1.3 \text{ k}\Omega$$

$$\therefore v_i = i_i \times 25.37 \Omega$$

$$i_o = g_{m2} v_i = \frac{4}{26} v_i$$

$$\therefore \frac{i_o}{i_i} = \frac{4}{26} \times 25.37 = 3.90$$

$$\text{For } Q_1, C_b = \tau_F g_{m1}$$

$$= 0.2 \times \frac{1}{26} \times 10^9 = 7.7 \text{ pF}$$

$$\therefore C_{\pi 1} = 8.7 \text{ pF}$$

$$\text{For } Q_2, C_b = 0.2 \times \frac{4}{26} \times 10^9 = 30.8 \text{ pF}$$

$$\therefore C_{\pi 2} = 34.8 \text{ pF}$$

Total shunt C

$$= C_{\pi 1} + C_{cs1} + C_{\pi 2} + C_{u2}$$

$$= 8.7 + 1 + 34.8 + 0.8 = 45.3 \text{ pF}$$

$$r_{\pi 1} \parallel \frac{1}{g_{m1}} \parallel r_{\pi 2} = 25.4 \Omega$$

$$\therefore \text{Time constant} = 45.3 \times 25.4 = 1.15 \text{ ns}$$

$$\therefore f_{-3dB} = 138 \text{ MHz}$$


$$4. a) \frac{N_a}{N_{in}} = - \frac{Z_F}{1k\Omega} = - \frac{\frac{200k\Omega}{1 + s(200k)(500p)}}{1k\Omega}$$

$$= -200 \cdot \frac{1}{1 + \frac{s}{10k}}$$

$$b) \frac{N_{out}}{N_{in}} = \frac{N_a}{N_{in}} \cdot \frac{10k}{10k + \frac{1}{s \cdot 1\mu}} = \frac{\frac{s}{100}}{1 + \frac{s}{100}} \cdot \frac{N_a}{N_{in}}$$

$$= -200 \frac{\frac{s}{100}}{\left(1 + \frac{s}{10k}\right)\left(1 + \frac{s}{100}\right)}$$
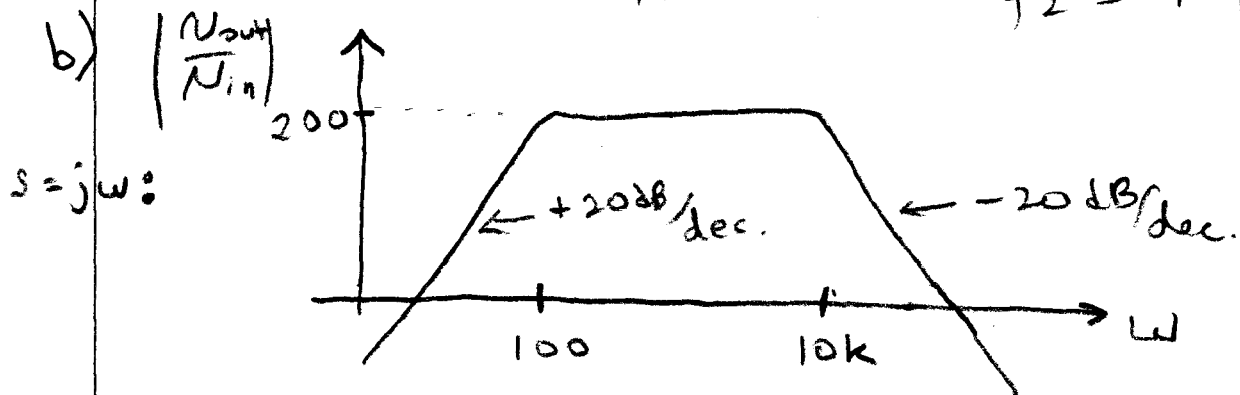
$$z = DC = 0 \quad p_1 = -100 \quad p_2 = -10k$$



$$c) \text{ Now } 1k\Omega \rightarrow Z = 1k\Omega + \frac{1}{s(25\mu)}$$

$$\frac{N_a}{N_{in}} = - \frac{\frac{200k}{1 + s(200k)(500p)}}{1k + \frac{1}{s(25\mu)}} \cdot \frac{\frac{s}{100}}{1 + \frac{s}{100}}$$

$$= -200 \cdot \left(\frac{1}{1 + \frac{s}{10k}} \right) \cdot \left(\frac{\frac{s}{40}}{1 + \frac{s}{40}} \right) \left(\frac{\frac{s}{100}}{1 + \frac{s}{100}} \right)$$

$$\text{two zeros @ } z=0 \quad p_1 = -40 \quad p_2 = -100 \quad p_3 = -10k$$