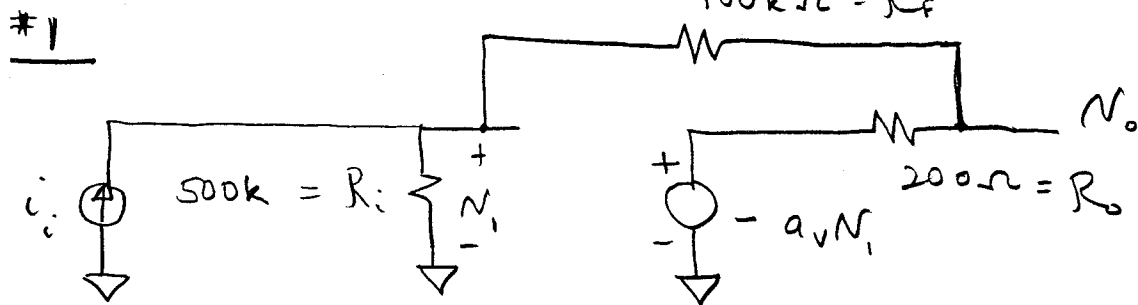




- if $a_v \rightarrow \infty$ (causing $RR \rightarrow \infty$); then $N_i \rightarrow 0$ (ideal op amp) and $N_o = -100k\Omega \cdot i_i$

$$\Rightarrow A_\infty = -100k\Omega$$

$$d = \left. \frac{N_o}{i_i} \right|_{a_v=0} = \frac{R_i}{R_i + R_F + R_o} \cdot R_o = \underline{167\Omega}$$

$$RR = a_v \cdot \frac{R_i}{R_i + R_o + R_F} = \underline{\underline{62.5k}}$$

$$A_{cl} = A_\infty \frac{RR}{1+RR} + \frac{d}{1+RR} \cong A_\infty = \underline{\underline{-100k\Omega}}$$

$$R_{in}(C.L.) = R_{in}(a=0) \cdot \frac{1+RR(\text{in shorted})}{1+RR(\text{in open})}$$

$$R_{in}(a=0) = R_i \parallel (R_F + R_o) = 83.5k\Omega$$

$$RR(\text{in shorted}) = 0 \quad (\because N_1 = 0)$$

$$RR(\text{in open}) = RR \text{ above} = 62.5k$$

$$\Rightarrow R_{in}(C.L.) = 83.5k\Omega \cdot \frac{1+0}{1+62.5k} = \underline{\underline{1.3\Omega}}$$


(quite a drop !)

$$R_{out}(C.L.) = R_{out}(a=0) \cdot \frac{1+RR(\text{out shorted})}{1+RR(\text{out open})}$$

$$= (200\Omega \parallel 600k\Omega) \cdot \frac{1+0}{1+62.5k} = \underline{\underline{3.2m\Omega}}$$
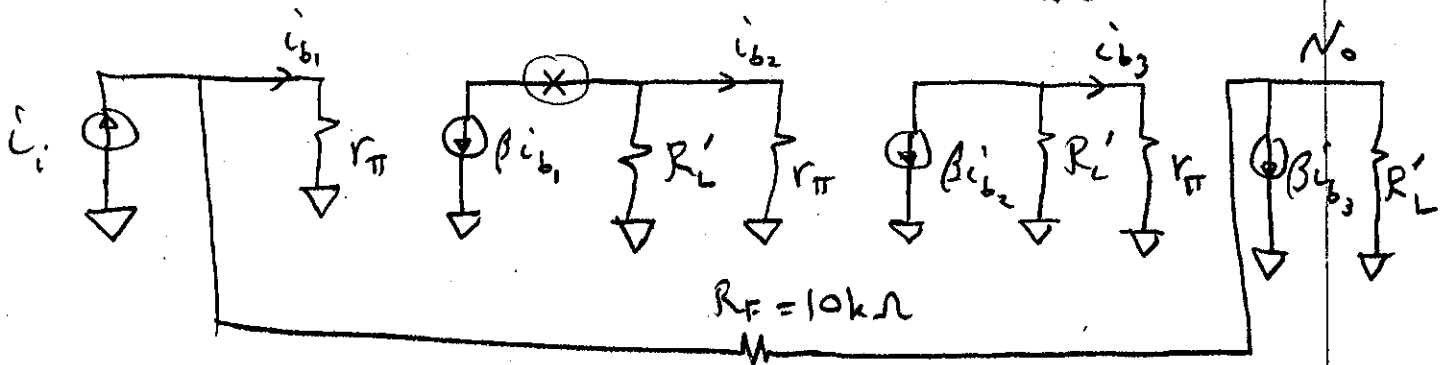
#2 Each Xdr has $r_o = \frac{50V}{1mA} = 50k\Omega$, $r_{\pi} = 5.2k\Omega$

$$R_L' = 5k \parallel 50k\Omega = 4.55k\Omega$$



- if $\beta \rightarrow \infty$, $R_R \rightarrow \infty$. $\beta \rightarrow \infty \Rightarrow i_{b1} = 0$


So all i_i flows thru R_F giving $N_o = -R_F i_i$

$$\therefore A_{\infty} = -R_F = -10k\Omega$$

- R_R (any βi_b source) = $R_R(\beta i_{b1}) = ?$

break at x, inject i_t to right of

break, measure $i_r \Rightarrow R_R = -\frac{i_r}{i_t} \Big|_{i_i=0}$

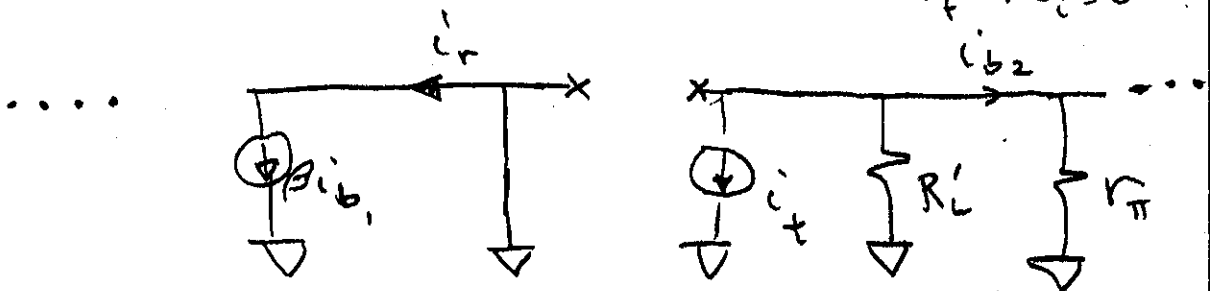

$$i_{b2} = - \frac{R_L'}{r_{\pi} + R_L'} \cdot i_+$$

$$i_{b3} = -\beta i_{b2} \cdot \frac{R_L'}{r_{\pi} + R_L'}$$

$$i_{b1} = -\beta i_{b3} \cdot \frac{R_L'}{r_{\pi} + R_F + R_L'}$$

$$i_r = +\beta i_{b1} = -\beta^3 \left(\frac{R_L'}{r_{\pi} + R_L'} \right)^2 \cdot \frac{R_L'}{r_{\pi} + R_F + R_L'} i_+$$

$$\Rightarrow RR = - \frac{i_r}{i_+} = \underline{\underline{401k}}$$

$$d = \left. \frac{V_o}{i_i} \right|_{\beta=0} = \frac{r_{\pi}}{r_{\pi} + R_F + R_L'} \cdot R_L' = 1.2k\Omega$$

$$A_{CL} = A_{\infty} \cdot \frac{RR}{1+RR} + \frac{d}{1+RR} \approx -10k\Omega$$

$$R_{in}(C.L.) \approx R_{in}(\beta=0) \cdot \frac{1+RR(\text{in shorted})}{1+RR(\text{in open})}$$


$$= r_{\pi} \parallel (R_F + R_L') \cdot \frac{1+0}{1+401k} = 9.5m\Omega$$

$$R_{out}(C.L.) = R_{out}(\beta=0) \cdot \frac{1 + RR(\text{out shorted})}{1 + RR(\text{out open})}$$

$$= \underbrace{R'_L \parallel (R_F + r_\pi)}_{3.5k\Omega} \cdot \frac{1 + 0}{1 + 401k}$$

$$= \underline{\underline{8.7m\Omega}}$$

#3.

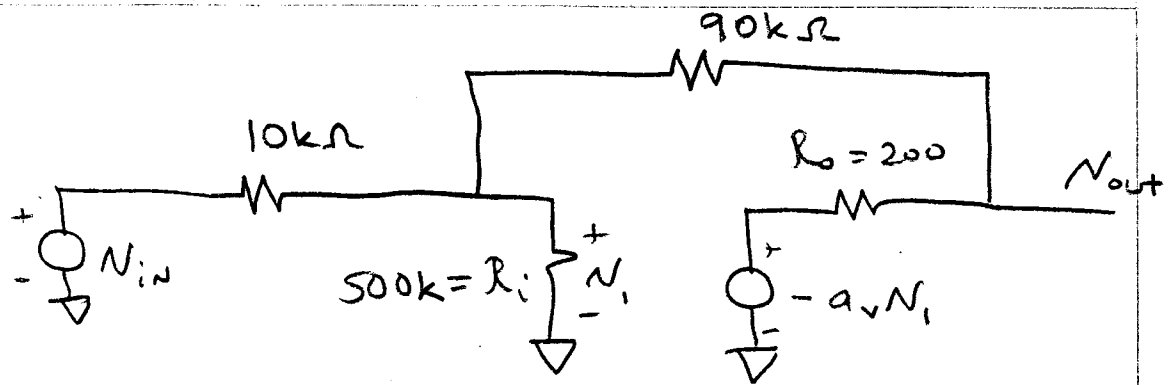

if $a_v \rightarrow \infty$, (ideal op amp) $\Rightarrow A_{\infty} = -\frac{90k}{10k} = -9$

$$d = \left. \frac{V_o}{V_{in}} \right|_{a=0} = \frac{R_i \parallel (90k + R_o)}{10k + R_i \parallel (90k + R_o)} \cdot \frac{R_o}{90k + R_o} = 2 \times 10^{-3}$$

$$RR = a_v \cdot \frac{10k \parallel 500k}{10k \parallel 500k + 90k + 200} = \underline{\underline{7350}}$$

$$A_u = -9 \cdot \frac{RR}{1+RR} + \frac{2 \times 10^{-3}}{1+RR} \approx \underline{\underline{-9}}$$

$$R_{in} = R_{in}(a=0) \cdot \frac{1+RR(\text{in short})}{1+RR(\text{in open})}$$

$$R_{in}(a=0) = 10k\Omega + R_i \parallel (90k\Omega + R_o) = 86.4k\Omega$$

$$RR(\text{in short}) = a_v \cdot \frac{10k \parallel R_i}{10k \parallel R_i + 90k + R_o} = 7350$$

$$RR(\text{in open}) = a_v \cdot \frac{R_i}{R_i + 90k + R_o} = 63,500$$

$$\therefore R_{in}(CL) = 86.4k\Omega \cdot \frac{1 + 7350}{1 + 63500} = \underline{\underline{10.0k\Omega}}$$

[not surprising, since the virtual ground forces $V_i \approx 0V \Rightarrow R_{in} \approx 10k\Omega$]

• To find R_{out} , set indep. source $V_{in} = 0$.

$$R_{out}(a_v=0) = 200\Omega \parallel [90k + 10k \parallel 500k]\Omega \approx 200\Omega$$

$$RR(\text{out shorted}) = 0 \quad (\text{if } V_{out} = 0; V_i = 0 \Rightarrow RR = 0)$$



$$RR(\text{out open}) = RR(\text{in shorted}) = 7350 \text{ (see last page)}$$

$$\therefore R_{out}(CL) = 200 \cdot \frac{1 + 0}{1 + 7350} \approx 0.027\Omega$$

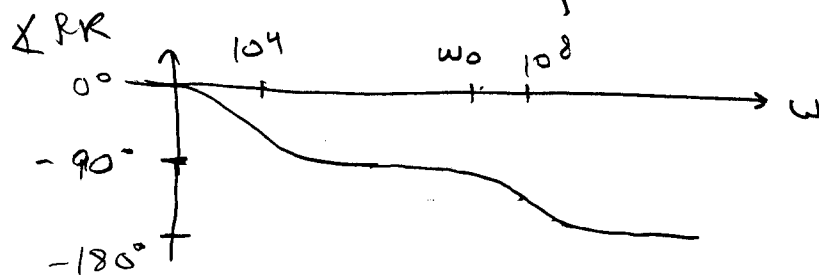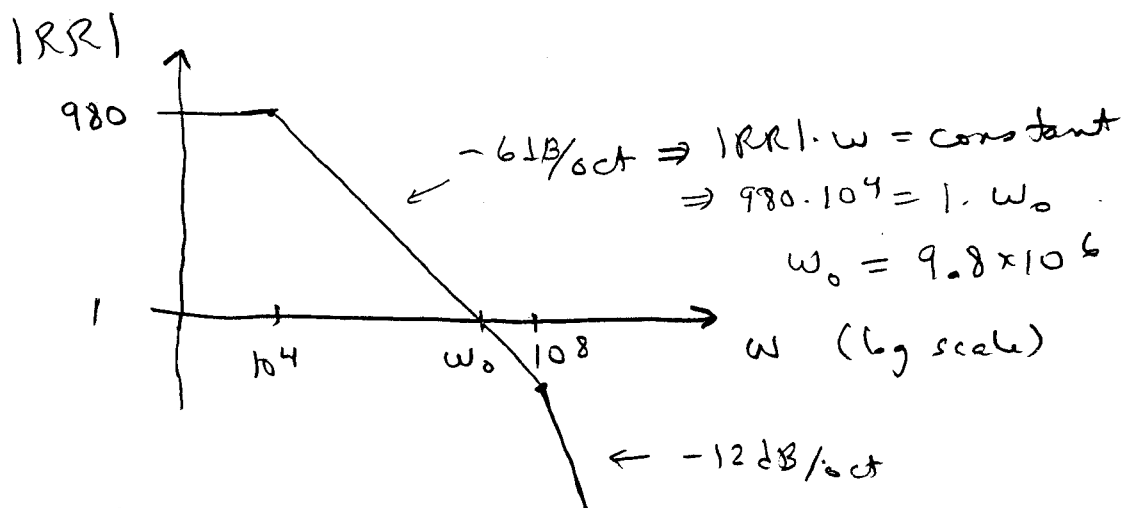4.a) RR is same as in #3 w/ new $a_v(s)$:

$$RR = a_v(s) \cdot \frac{10k \parallel 500k}{10k \parallel 500k + 90k + 200}$$

$$= \frac{980}{\left(1 + \frac{s}{10^4}\right) \left(1 + \frac{s}{10^8}\right)}$$



$$\begin{aligned} |RR(\omega_0)| &= 1 \\ \angle RR(\omega_0) &= \angle 980 - \angle \left(1 + \frac{j\omega_0}{10^4}\right) - \angle \left(1 + \frac{j\omega_0}{10^8}\right) \\ &\approx 0 - 90^\circ - \tan^{-1}\left(\frac{9.8 \times 10^6}{10^8}\right) \\ &= -95.6^\circ \end{aligned}$$


$$PM = 180^\circ + (-95.6^\circ) = 84.4^\circ \leftarrow \text{circuit is stable w/ large PM.}$$

4 b) now $RR = a_v(s) \cdot \frac{\frac{1}{sC} \parallel 500k}{\frac{1}{sC} \parallel 500k + 90k + 200}$

$$= a_v(s) \cdot \frac{500k\Omega}{590.2k\Omega + (90.2k\Omega)C_s(500k\Omega)}$$

$$= a_v(s) \cdot \frac{0.847}{1 + (76.4k\Omega)(C)s} \quad C = 1\mu F$$
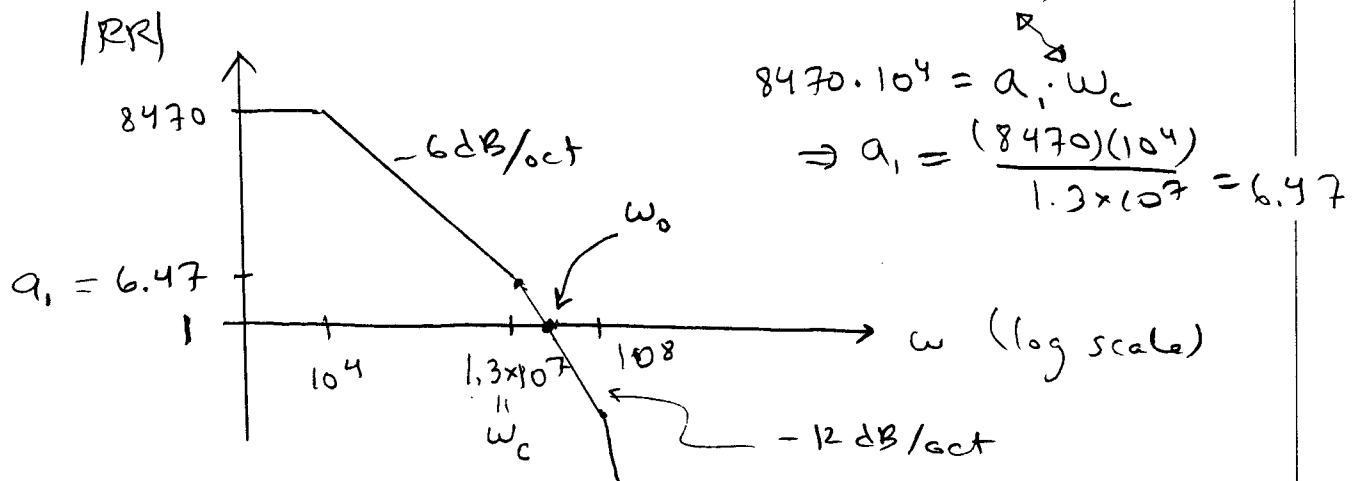
$$= \frac{8.47 \times 10^3}{\left(1 + \frac{s}{10^4}\right)\left(1 + \frac{s}{10^8}\right)\left(1 + \frac{s}{1.3 \times 10^7}\right)}$$



$$-12 \text{ dB/oct} \Rightarrow |RR| \cdot \omega^2 = \text{constant}$$

$$\Rightarrow a_1 \cdot \omega_c^2 = 1 \cdot \omega_0^2 \Rightarrow \omega_0 = \sqrt{(6.47)(1.3 \times 10^7)^2} = 3.31 \times 10^7$$

$$|RR(\omega_0)| = 1$$

$$\angle RR(\omega_0) = \angle 8.47 \times 10^3 - \angle \left(1 + \frac{j\omega_0}{10^4}\right) - \angle \left(1 + \frac{j\omega_0}{10^8}\right) - \angle \left(1 + \frac{j\omega_0}{1.3 \times 10^7}\right)$$

$$= 0 - 90^\circ - 18.3^\circ - 68.6^\circ = -176.9^\circ$$

$$PM = 180 + \angle RR(\omega_0) = 3.1^\circ \quad \text{barely stable (PM is unacceptable!)}$$

5. a) $\omega_{-3dB} \approx \omega_0$ $\omega_0 = \text{freq where}$
 $|RR(\omega_0)| = 1$


On plot of $|RR|$ for #4a):

$$\omega_0 = 9.8 \times 10^6 \frac{\text{rad}}{\text{s}}$$

$$\text{So } \omega_{-3dB} \approx 9.8 \text{ M } \frac{\text{rad}}{\text{s}}$$

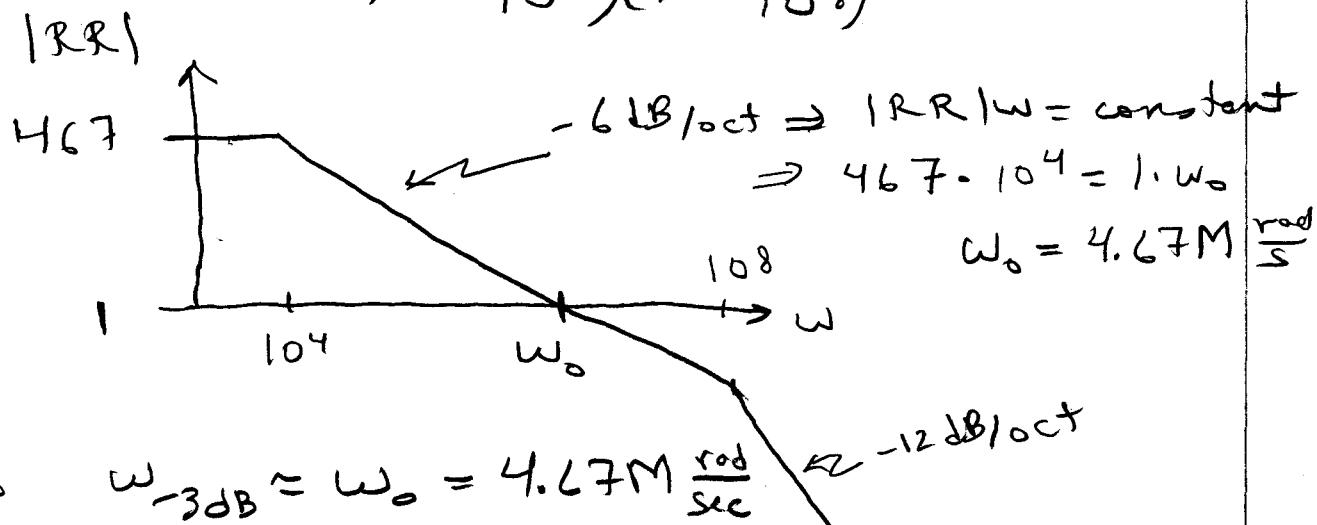b) now $RR = a_v(s) \cdot \frac{10k \parallel 500k}{10k \parallel 500k + 200k + 200}$

$$= \frac{467}{(1 + \frac{s}{10^4})(1 + \frac{s}{10^8})}$$



so $\omega_{-3dB} \approx \omega_0 = 4.67 \text{ M } \frac{\text{rad}}{\text{sec}}$

c) a) $|DC \text{ gain}| = 9$ $BW = 9.8 \text{ M } \frac{\text{rad}}{\text{sec}}$

b) $|DC \text{ gain}| = 20$ $BW = 4.67 \frac{\text{rad}}{\text{sec}}$

as $|gain| \uparrow$, $BW \downarrow$