
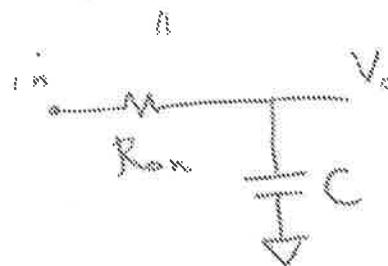


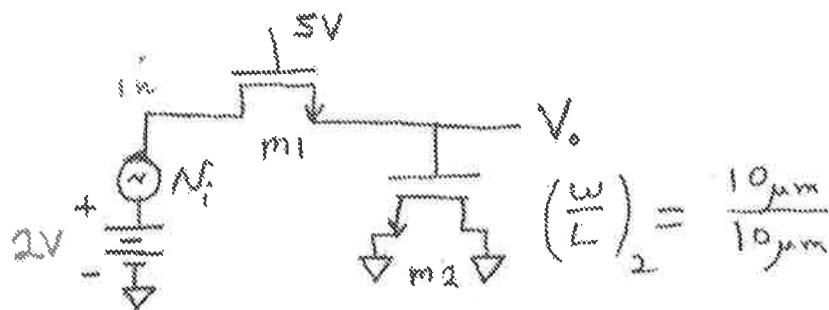1. A first-order RC filter that uses only MOS transistors is shown below. Assume that the AC input signal is small compared to the DC input bias voltage. What W/L ratio is needed for M1 to give a -3 dB frequency of 10 MHz? Ignore all junction and overlap capacitances.



$$C = C_{gs}(m_2) = C_{ox} \cdot W \cdot L = 3.5 \text{ fF}/\mu\text{m}^2 \times 10\mu\text{m} \times 10\mu\text{m}$$

$$= 350 \text{ fF}$$

m1 transist:

$$R_{m1} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_T)} = \frac{1}{130 \frac{fA}{V^2} \left(\frac{W}{L}\right) [5 - 2 - 1]} \approx$$


$$= \frac{2778 \Omega}{\frac{W}{L}}$$

want  $\frac{1}{2\pi f_m C} = 10 \text{ MHz} \Rightarrow R_m = 45.5 \text{ k}\Omega$

$$\Rightarrow \frac{W}{L} = 0.061$$

(c)

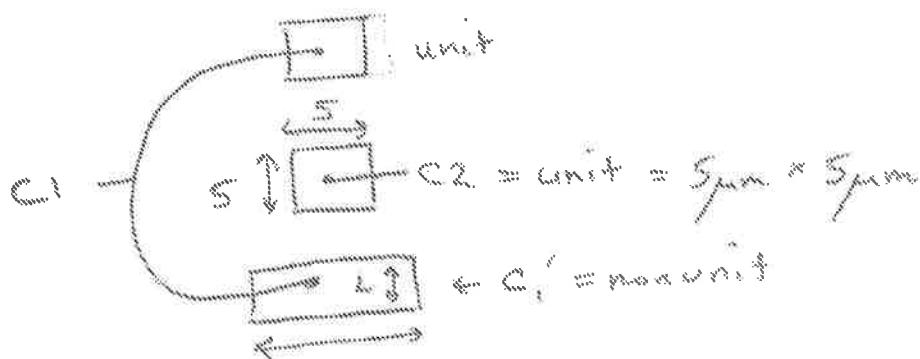2. Two capacitors  $C_1$  and  $C_2$  are needed with a very accurately defined ratio of  $C_1/C_2 = 2.6$ , with the constraint that the maximum area that can be used for  $C_2$  is  $25 \mu\text{m}^2$ . Draw a top view of the layout of the two capacitors. Show the dimensions of the capacitors on your drawing.



$C_2 = \text{biggest unit cap possible} = 5\mu\text{m} \times 5\mu\text{m}$

$$C_1 = \text{1 unit} + 1 \text{ non-unit}$$

$$C_1 = \text{non-unit} : \text{area} = w \cdot L = 1.6 (25 \mu\text{m}^2) = 40 \mu\text{m}^2$$


$$\therefore \frac{\text{per area } (C_1)}{\text{area}} = \frac{\text{per area } (\text{unit})}{\text{area}}$$

$$\frac{w}{25 \mu\text{m}} = \frac{1.6}{25} \Rightarrow w + L = \frac{1.6}{25} (40) \cdot \frac{1}{2} = 16 \mu\text{m}$$

$$w + L = w + \frac{40}{w} = 16 \Rightarrow w = 12.9 \mu\text{m}$$

$$\frac{40}{w} = 3.1 \mu\text{m}$$

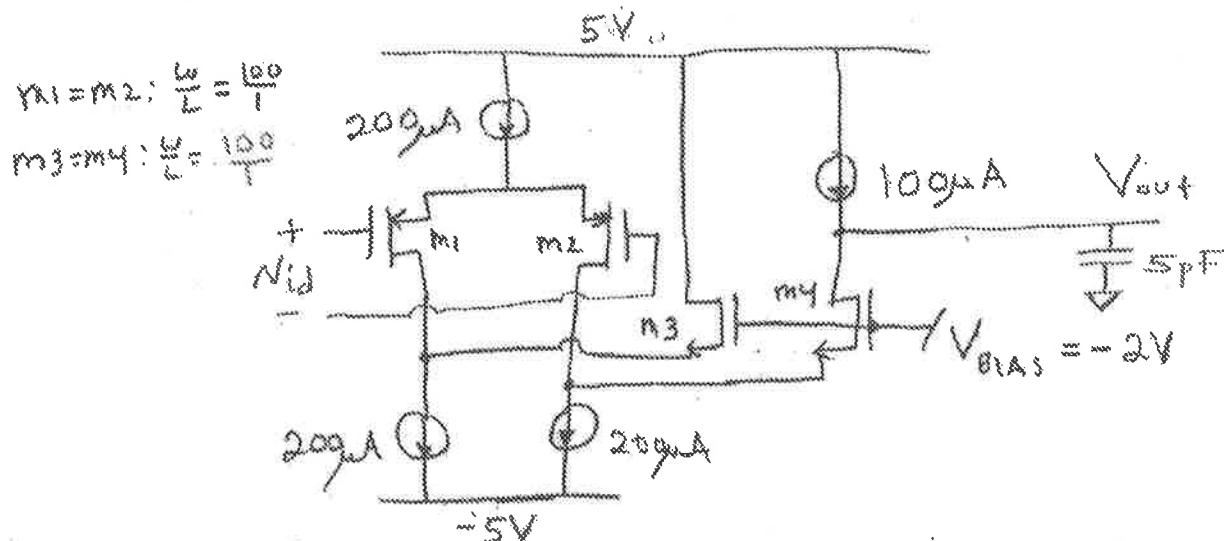3. For the op amp shown below, assume DC biasing places the transistors in the saturation region. (NOTE: This op amp is slightly different than the standard folded-cascode op amp.)



(5)

a) What is the low-frequency gain?  $V_{out}/V_{in} =$  \_\_\_\_\_

$$A_v = \pm g_m R_{out} = \pm \left(100 \frac{\mu A}{V}\right) (450 \text{ m}\Omega) = \underline{522 \frac{V}{V}}$$

$$f_{pz} \approx \sqrt{2 \left( 60 \frac{\mu A}{V} \right) (100) (100 \mu A)} = 1100 \frac{Hz}{V}$$

$$I_{out} \approx I_{c4} \left( 1 + g_m R_{o2} \right) = 100 \left[ 1 + \left( 100 \frac{\mu A}{V} \right) (1 \text{ m}\Omega) \right] = 950 \text{ mA}$$

$$R_{o4} = \frac{1}{0.02 \cdot 100 \mu A} = 500 \Omega$$

$$g_m = \sqrt{2 \left( 100 \frac{\mu A}{V} \right) (100) (100 \mu A)} = 1900 \frac{\mu A}{V}$$

$$R_{o2} = \frac{1}{0.01 \cdot 100 \mu A} = 1 \text{ m}\Omega$$

(7)

b) What is the positive output slew rate?  $SR^+ =$  \_\_\_\_\_

$$\frac{dV_o}{dt} = \frac{100 \mu A}{50 \text{ pF}} = 2.0 \times 10^6 \frac{V}{s}$$

- ③ c) What is the dominant pole for this op amp?  $p_1 =$
- 

$$p_1 = \frac{-1}{f_{\text{low}} C_L} = \frac{-1}{(950 \mu\text{V})(5 \text{ pF})} = -210 \frac{\text{rad}}{\text{s}}$$

- ③ d) Estimate the frequency at which the magnitude of the voltage gain falls to one. Ignore the nondominant poles for this calculation. (This is the GBW.)  $f_u = \underline{17.5 \text{ MHz}}$

$$|A_{v_s}| \cdot |j_{11}| = 1 \cdot \omega_u$$

$$(522k)(210 \frac{\text{rad}}{\text{s}}) = \omega_u = 110 \text{ rad/s}$$

$$\approx 2\pi f_u$$


- ③ e) Estimate the negative output swing limit.

Negative output swing limit = \_\_\_\_\_

Can swing down until m4 goes triode  
(when  $V_{ce}(m4) = V_T \approx 1V$ )

$$\hat{V}_{o^-} = -2V - V_{ce}(m4) \approx -2V - 1V = \underline{\underline{-3V}}$$

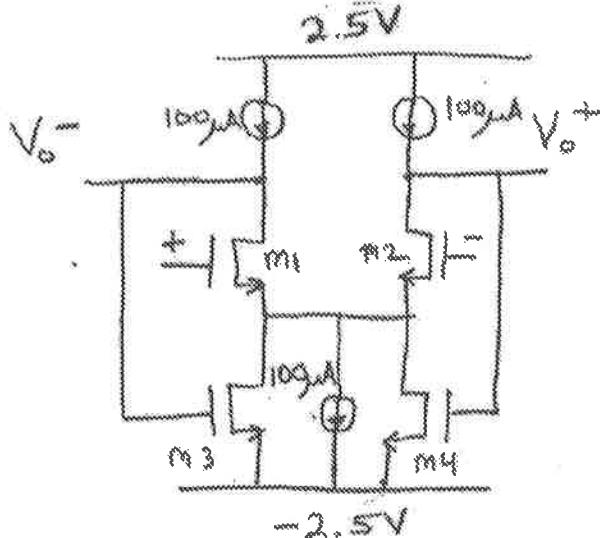4. A fully differential one-stage op amp with common-mode feedback is shown. The common-mode feedback is provided by M3 and M4. Assume all transistors are saturated, and assume  $M_1 = M_2$ ,  $M_3 = M_4$ .



$$m_1 = m_2 : \frac{W}{L} = 100$$

$$m_3 = m_4$$

(4)

- a) What should  $W/L$  be for M3 and M4 so that the common-mode output voltage is 0V?

$$W/L = \underline{\underline{_____}}$$

$$\underline{\underline{V_{DS}}}$$

$$\text{want } I_{D3} = I_{D4} = 50 \mu A = \frac{1}{2} \left( 180 \frac{\mu A}{V^2} \right) \frac{W}{L} \left( 0 - (-2.5V) - 1V \right)^2$$

$$\underline{\underline{\frac{W}{L} = 0.25}}$$

(4)

- b) What is the differential-mode (DM) voltage gain?

$$V_{out}/V_{in,d} = \underline{\underline{_____}}$$

$$A_V = g_m f_T = \sqrt{2(180 \frac{\mu A}{V^2})(10^8)(100 \mu A)} \times \frac{1}{0.82V^{-1} \cdot 100 \mu A}$$

$$= \underline{\underline{150}}$$

(4)

- c) For this op amp, estimate the lower limit of the common-mode input voltage.

Lower CM input limit = \_\_\_\_\_

Find when  $M_3$  goes triode:

$$V_{in}^-(CM) = -2.5V + V_{DSAT}(m_3) + V_{GS}(m_1)$$


$$= -2.5V + \sqrt{\frac{2I_{D3}}{\mu_{max} L_3}} + \left( V_{T^-} + \sqrt{\frac{2I_{D1}}{\mu_{max} L_1}} \right)$$

$$= -2.5V + 0.49V + (1V + 0.11)V$$

$$\approx 0.1V$$

- ④ 5. a) Find the frequency at which the magnitude of the return ratio equals 1 for the circuit below.

$$\omega_x = \text{Frequency where } |RR| = 1 : \quad g_m/C; C = 2\text{pF}$$

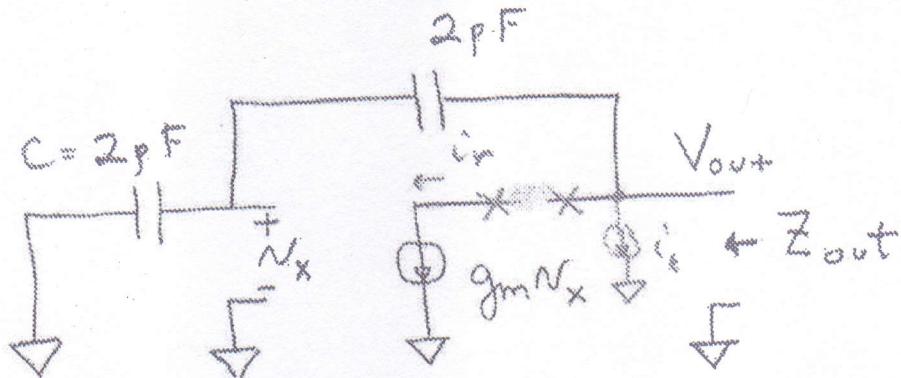

$$\left. \begin{aligned} N_x &= -\frac{1}{j\omega C} i_t \\ i_r &= g_m N_x \end{aligned} \right\} i_r = -\frac{g_m}{j\omega C} i_t$$

$$RR = -\frac{i_r}{i_t} = \frac{g_m}{j\omega C}$$

$$|RR| = 1 = \frac{g_m}{\omega C}$$

$$\omega = \frac{g_m}{C}$$

$$C = 2\text{pF}$$

5 (continued)

- b) Use Blackman's impedance formula to compute the magnitude of the output impedance at the frequency computed in part

(a).

$$|Z_{out}| = \frac{\sqrt{2}}{g_m}$$

$$\text{at } g_m = 0 : Z_{out} \leftrightarrow 1_{pF} = (2pF)(2pF)$$

$$RR(\text{out shorted}) = 0$$

$$RR(\text{out open}) = \frac{g_m}{j\omega C} = \frac{1}{j} = -j \quad @ \omega_u'$$

$$Z_{out}(\omega_u') = \frac{j\omega_u'(1_{pF})}{1-j} (1+0)$$

$$|Z_{out}(\omega_u')| = \frac{1}{\omega_u'(1_{pF})} \left| \frac{1}{1-j} \right|$$

$$= \frac{1}{\frac{g_m}{C} (1_{pF})} \cdot \frac{1}{\sqrt{2}} =$$

$$= \frac{2}{g_m} \cdot \frac{1}{\sqrt{2}} = \frac{\sqrt{2}}{g_m}$$

$$C = 2pF$$