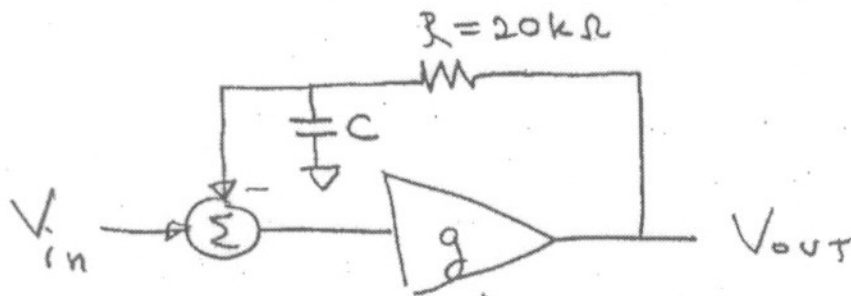


## HW #2


1. A gain stage with feedback to keep the output offset voltage low is shown below.



$g$  ranges from 1 to 100.

- a) What value of  $C$  will give a pole magnitude  $\leq 2\pi(30\text{kHz})$  over the entire gain range?
- b) What is the range of output offset voltage if the offset voltage at  $V_{in}$  is  $0.1\text{V}$ ?

2.

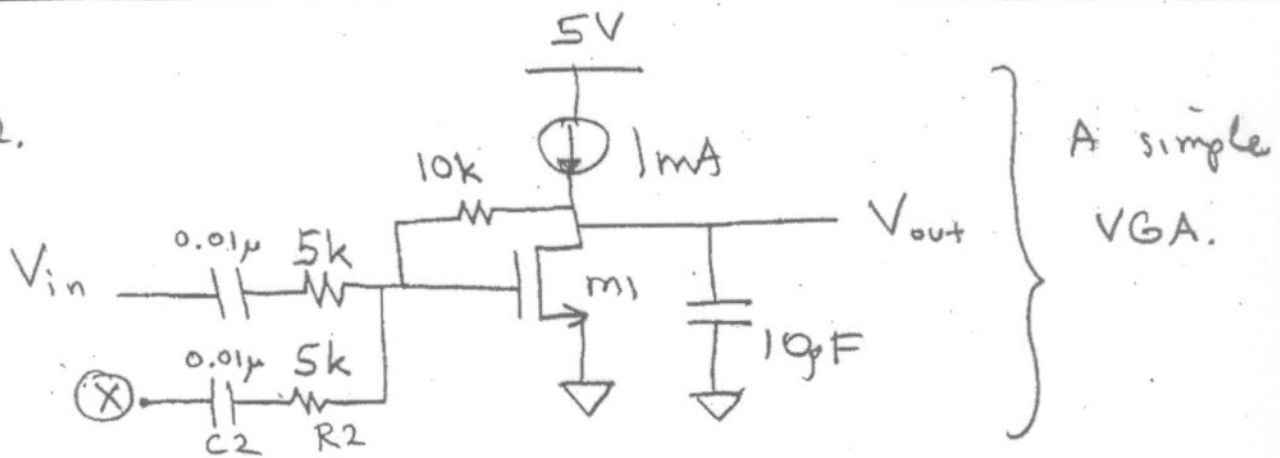

A simple  
VGA.

$m1: W=200\mu\text{m} \quad L=0.5\mu\text{m}$

$AS=AD=100(\mu\text{m})^2 \quad PS=PD=20\mu\text{m}$

a) With (X) connected to  $V_{in}$ , use HSPICE to find the gain and upper  $f_{-3dB}$  for this circuit.

b) Remove  $R2$  &  $C2$  and repeat a).


Why does  $f_{-3dB}$  change?

c) Simulate the circuit again, with (X) connected to  $\downarrow$ . How does  $f_{-3dB}$  compare with a) & b)? Explain.

Use the mos models in the file:

`~hurst/215/mos_models`



or on the 215 web page.

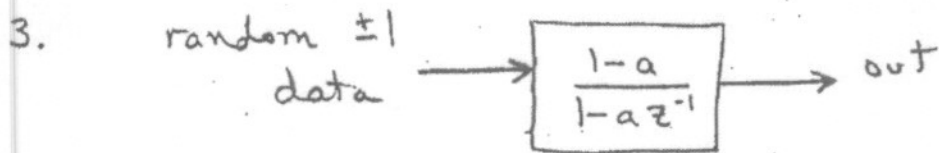


Let  $a = 0.2$

Simulate this equivalent discrete-time channel for a large number of bits ( $\sim 1000$ ) to find the range of high outputs and the range of low outputs.

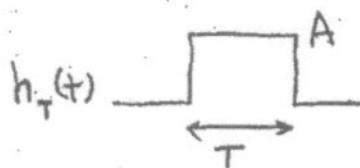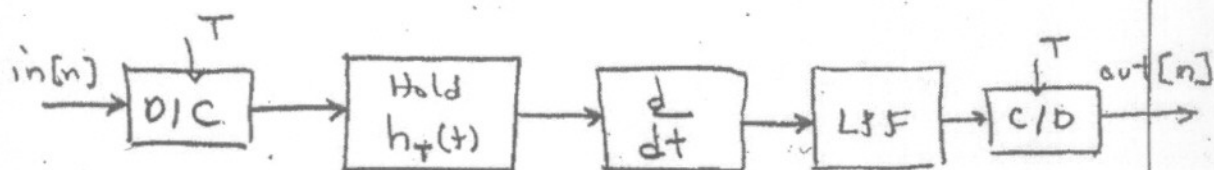4. Find the equivalent discrete-time channel  $G(z)$  for the following:





$$LPF(s) = \frac{1}{1+sT_1}$$

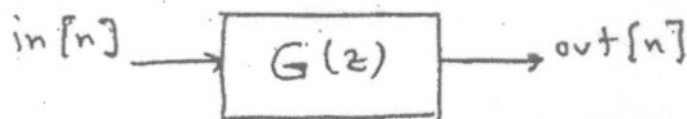


(hint: let  $in[n] = \delta[n]$ , then  $out[n] = g[n]$ .  
 $g[n] \leftrightarrow G(z)$ .)

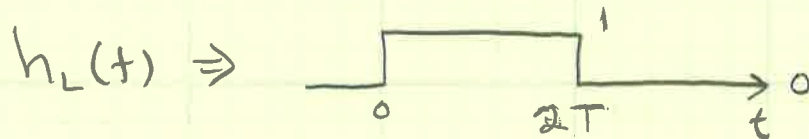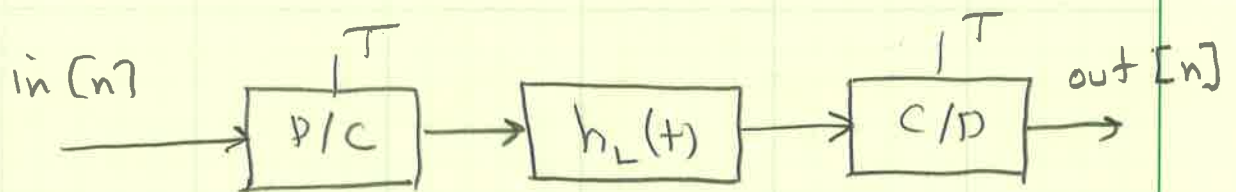5. Find the equivalent discrete-time model  $G(z)$  for the following:



$$h_L(t) = \begin{cases} 1 & 0 \leq t < 2T \\ 0 & \text{else} \end{cases}$$

6.

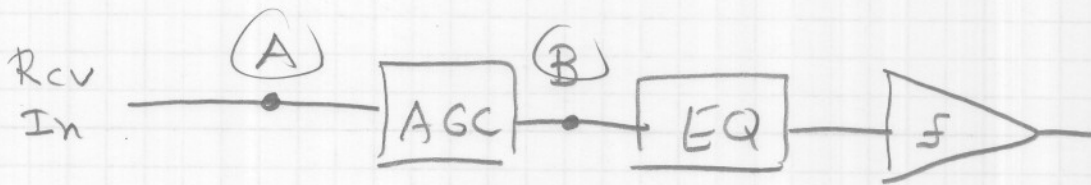

Assume the  $\frac{\text{peak}}{\text{rms}}$  ratio of the Rcv In signal is 5 ( $\approx 14 \text{ dB}$ ) and

the range of Rcv In is 24 dB

$$(24 \text{ dB} = 20 \log \left[ \frac{(\text{largest Rcv In})_{\text{rms}}}{(\text{smallest Rcv In})_{\text{rms}}} \right]).$$

If the SQNR required is  $\geq 22 \text{ dB}$ :

a) How many bits are needed if an

ADC is placed at (A), before the AGC?

Assume  $\text{Rcv In}(\text{peak}) = \text{ADC full scale}$ .

b) How many bits are needed if

an ADC is placed at (B)? Assume

the AGC is ideal, and

the peak at (B) = ADC full scale.

for any Rcv In signal.