

EEC 116 Lecture #10: Memories

**Rajeevan Amirtharajah
University of California, Davis**

**Jeff Parkhurst
Intel Corporation**

Announcements

- **Work on Lab 5 this week**
- **Quiz 3 Monday**
- **Midterms back at end of class**

Outline

- **Finish: Interconnect**
- **Memories: Rabaey 12.1-12.2 (Kang & Leblebici, 10.1-10.6)**

Memory and Performance Trend I

- **Memory is becoming a key factor in the performance of a computer**
- **1st generation computers had just system memory**
 - Very slow DRAM
 - As microprocessors got faster, the bottleneck in performance was data access
- **2nd generation computers added cache memory**
 - This provided faster access to small localized memory that was being read or written
 - Memory placed on front side bus (off-chip)
 - Performance increased
 - As processors got faster memory access again became the bottleneck

Memory and Performance Trend II

- **3rd generation computers added on chip cache**
 - These caches started out 16K and were termed level 1 cache
 - Soon we had level 1 and level 2 cache
 - Currently we have three levels of cache on chip that run at processor frequency, then access main memory if data can't be found in any of these caches
 - Moving to stacking memory die on top of processor

Types of Memory I

- **ROM: read-only memory**
 - Non-volatile – mask programmed
- **RWM: read-write memory (RAM, random access memory)**
 - SRAM: static memory
 - Data is stored as the state of a bistable circuit
 - State is retained without refresh as long as power is supplied
 - DRAM: dynamic memory
 - Data is stored as a charge on a capacitor
 - State leaks away, refresh is required

Types of Memory II


- **NVRWM: non-volatile read-write memory (also called NVRAM, non-volatile random access memory)**
 - Flash (EEPROM): ROM at low voltages, writable at high voltages (Electrically Erasable Programmable Read-Only Memory)
 - EPROM: ROM, but erasable with UV light (falling out of common usage)

Memory Usage in Computers

- **DRAM Memory**
 - Main memory storage. Used for data and programs
- **SRAM Memory**
 - Faster than DRAM, however, uses more transistors
 - Used to be used for external cache
 - Variant used in internal cache (on chip cache)
- **FLASH Memory and ROM**
 - Used for BIOS data storage in PCs
 - Also used to store pictures, MP3 files for digital cameras and MP3 players – eventually for hard disk

Basic Memory Array Structure

 
- **Memory cells arranged in a rectangular array**
- **Rows correspond to data words**
 - Accessed through a row decoder
- **Columns to individual bits**
 - Selected through a column mux
- **Bit voltage amplified by sense amplifier**



Memory Circuit Operation

- **Wordlines (WL) control row (word) access**
 - Usually control gates of pass transistors
- **Bitlines (BL) route column data (individual bits)**
 - Bitlines usually precharged high (like dynamic logic)
 - Memory cells discharge bitline depending on stored data (bitline left high if cell stores 1, bitline discharged if cell stores 0)
 - Bitline swings usually small (10s – 100s of mV) and must be amplified by sense amplifiers
 - Synchronous or asynchronous timing can be used
- **Memory cells store data value**
 - Static vs. dynamic, single or multiple bits, etc.

DRAM

 


- **Smaller cell size (1 transistor or 1T cell)**
 - Reason for inexpensive memory in computers
 - Tradeoff of area (memory density) vs. speed and complexity (refreshing)


DRAM Issues

- **Must be periodically refreshed**
 - Reads are destructive (modify voltage stored on capacitor)
 - Every read followed by a refresh of the bit (write back of read value)
- **No static power dissipation**
- **Output voltage is charge sharing result of storage capacitor and bitline capacitance**
 - More complex sense amplifiers
 - Higher noise susceptibility
- **Requires different CMOS process than high performance logic**
 - Not compatible with cache in microprocessors


3T DRAM Cell

 

 - Early DRAM technology
- Gate cap of M1 stores bit
- Nondestructive reads
- Storage node voltage $< V_{DD}$
 - Compensate with boosted wordline




Advanced DRAM Process

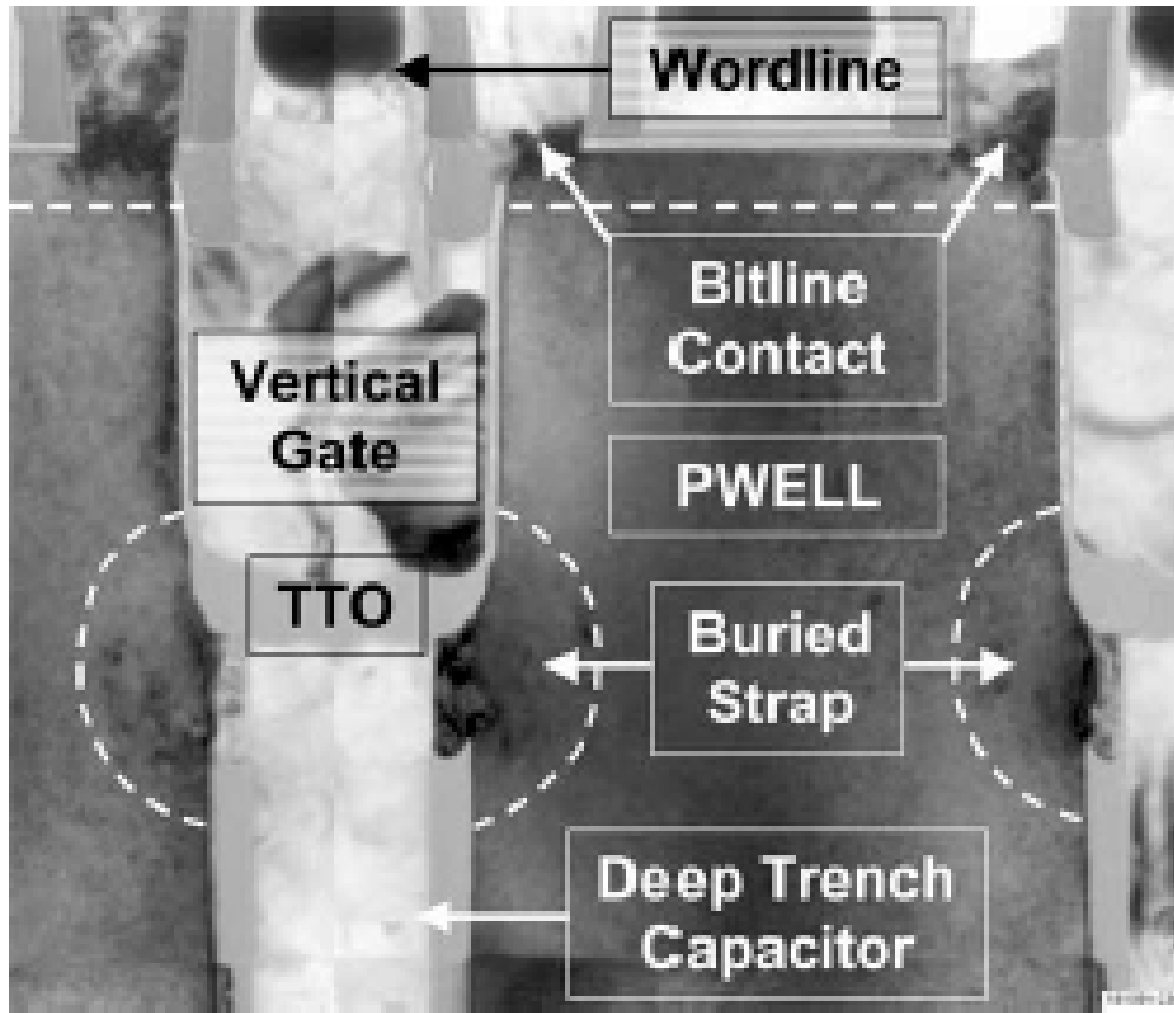


- **Vertical transistor, trench capacitor (Beintner, JSSC 04)**

ROM

 - **Dotted lines refer to either set at '1' or '0'**
 - PROM: Replace dotted lines with fuses
- **Small cell size (1T cell)**
- **Not necessary to refresh**
- **No static power dissipation**
- **Output voltage is set by WL duration**




SRAM Cell

 

- **Cross-coupled inverters: bistable element**
- **Density is important in memories**
 - Single NMOS pass transistor used for reading/writing
 - Transistor sizes should take up minimum area
- **Faster than DRAM since typically fewer cells**
- **No refresh required (nondestructive reads)**

SRAM Design: Read "0"

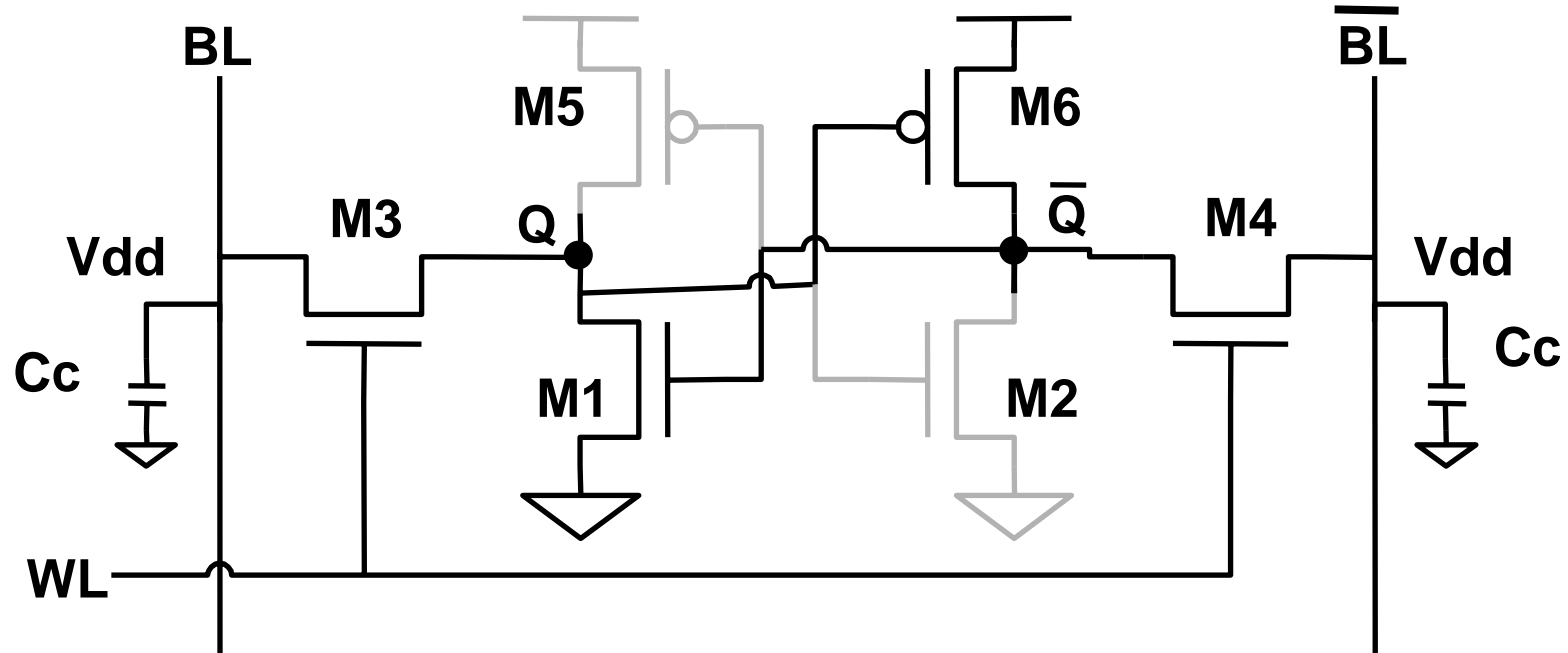

- Prior to read operation, voltage at node $Q = 0V$ and $\bar{Q} = V_{dd}$, bit lines precharged to V_{dd}
- Transistors $M3$ and $M4$ are turned on by word line (WL) select circuitry

SRAM Design: Read “0”

- **Transistors M3 and M4 are turned on by WL line select circuitry**
 - $C_c = V_{dd}$ to start...capacitance discharges through M1.
 - Need to make sure the ratio between M1 and M3 does not allow Q to go above V_{tn} .
 - Otherwise node \bar{Q} accidentally discharged
 - Conservative since there will also be charge sharing at that node as well between small internal node capacitance and large bitline capacitance
 - Sense amp detects that node Q was a stored 0 due to the minor drop of voltage on the bitline

SRAM Design: Read “0”

- **Data must not be destroyed when bitline voltage different than storage node**
 - V_Q must not exceed the threshold of the inverter (assumed to be $V_{DD}/2$), more conservative to keep it below V_{TN}


- **Assume V_{BL} initially remains at V_{DD} : M3 in saturation, M1 in linear**

$$\frac{k_{n,3}}{2} (V_{DD} - V_Q - V_{TN})^2 = \frac{k_{n,1}}{2} (2(V_{DD} - V_{TN})V_Q - V_Q^2)$$

$$\frac{k_{n,3}}{k_{n,1}} = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_1} < \frac{2(V_{DD} - 1.5V_{TN})V_{TN}}{(V_{DD} - 2V_{TN})^2}$$


**Guarantee $V_Q < V_{TN}$,
plug into I_D equations:
 $I_{D3} < I_{D1}$ at $V_Q = V_{TN}$**

SRAM Design: Write "0" (1st Analysis)

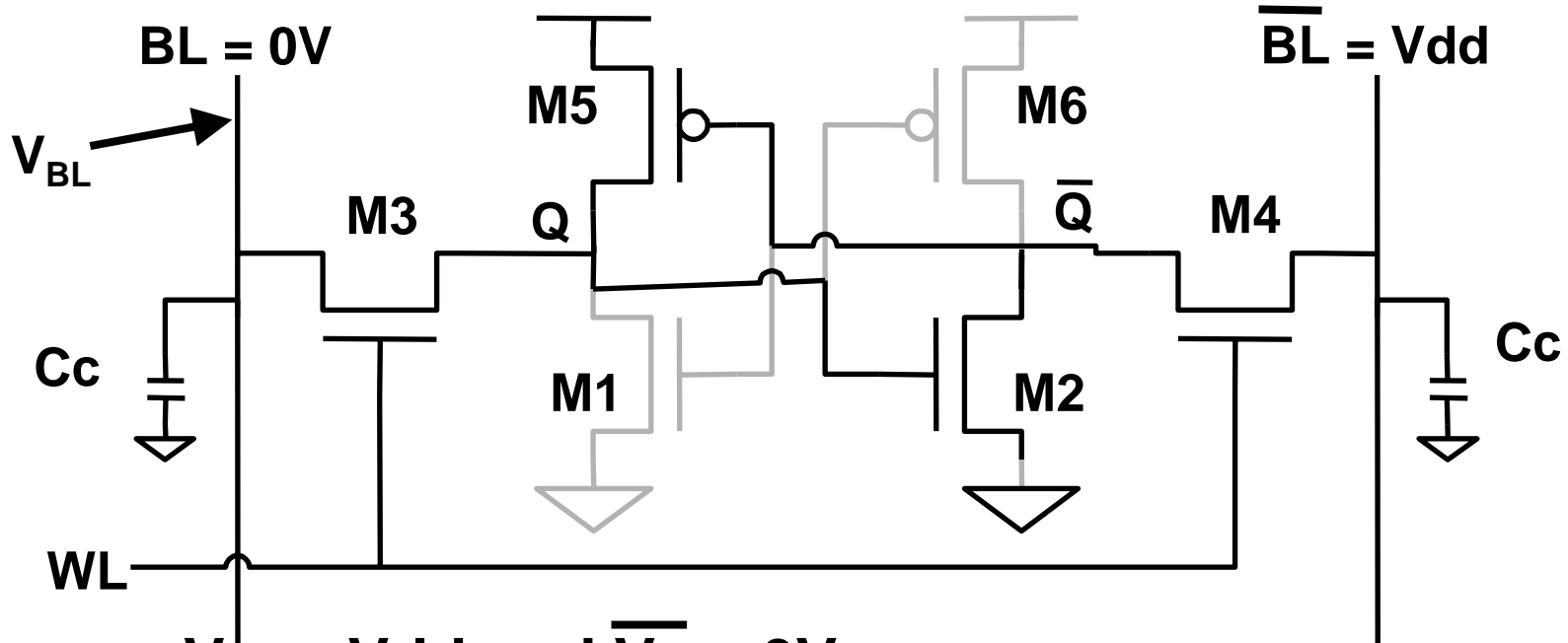

- Assume $V_Q = V_{DD}$ and $\overline{V}_Q = 0V$
- Data must be forced into the cell
 - V_Q must fall below the threshold of the inverter to turn M2 off.
 - This allows \overline{V}_Q to go high enough to go above the V_t of M1
 - This discharges node Q and stores a 0
- Assume V_{BL} remains at 0V: M3 linear, M5 linear ($V_Q = V_{DD}/2$)


SRAM Design: Write "0" (1st Analysis)

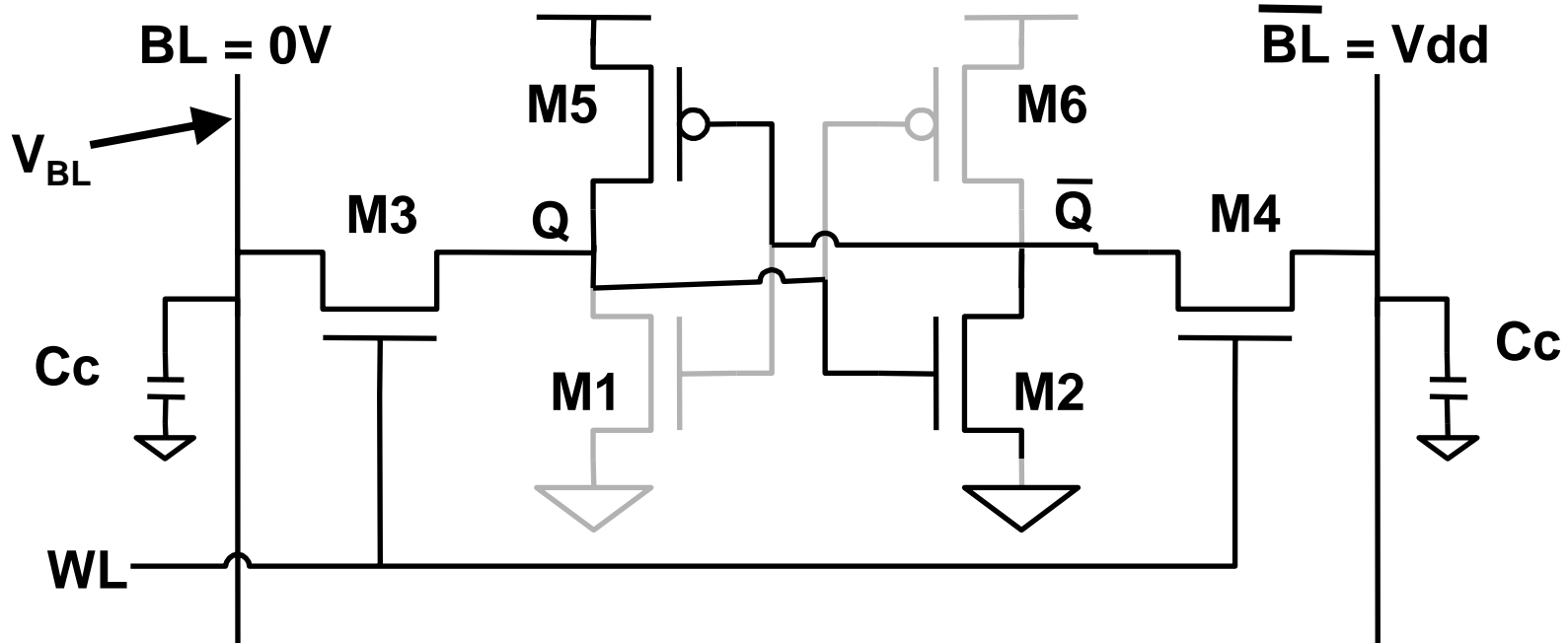

- **Conditions for this to happen: requires M5 to M3 ratio to be relatively small ($V_{DS} = V_Q = V_{DD}/2$)**

$$\frac{k_{p,5}}{2} \left((V_{DD} - |V_{TP}|) V_{DD} - \frac{V_{DD}^2}{4} \right) = \frac{k_{n,3}}{2} \left((V_{DD} - V_{TN}) V_{DD} - \frac{V_{DD}^2}{4} \right)$$


SRAM Design: Write "0" (1st Analysis)

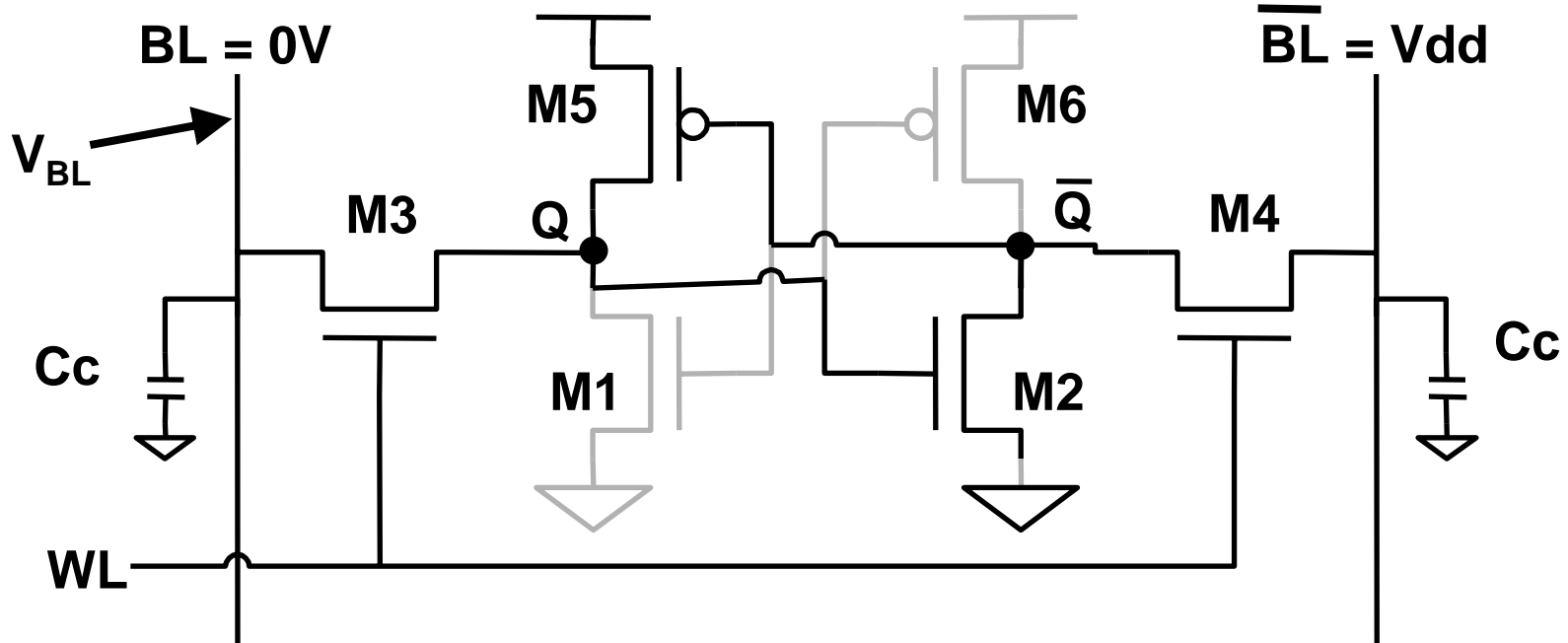

- Required sizing (size M5 below mobility ratio):


$$\frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_3} < \frac{k'_n \left((V_{DD} - V_{TN})V_{DD} - \frac{V_{DD}^2}{4} \right)}{k'_p \left((V_{DD} - |V_{TP}|)V_{DD} - \frac{V_{DD}^2}{4} \right)} = \frac{k'_n}{k'_p} \quad \text{If } V_{TN} = |V_{TP}|$$

SRAM Design: Write "0" (2nd Analysis)

 

- Assume $V_Q = V_{dd}$ and $\overline{V}_Q = 0V$
- Data must be forced into the cell
 - V_Q must fall below the threshold of the NMOS (turns M2 off).
 - This allows \overline{V}_Q to go high enough to go above the V_t of M1
 - This discharges node Q and stores a 0
- Assume V_{BL} remains at 0V: M5 sat., M3 linear ($V_Q = V_{TN}$)


SRAM Design: Write "0" (2nd Analysis)

 

- **Desired current conditions, want $V_Q < V_{TN}$ (M3 lin., M5 sat.):**

$$\frac{k_{n,3}}{2} \left(2(V_{DD} - V_{TN})V_{TN} - V_{TN}^2 \right) = \frac{k_{p,5}}{2} \left(0 - V_{DD} - V_{TP} \right)^2$$

SRAM Design: Write "0" (2nd Analysis)

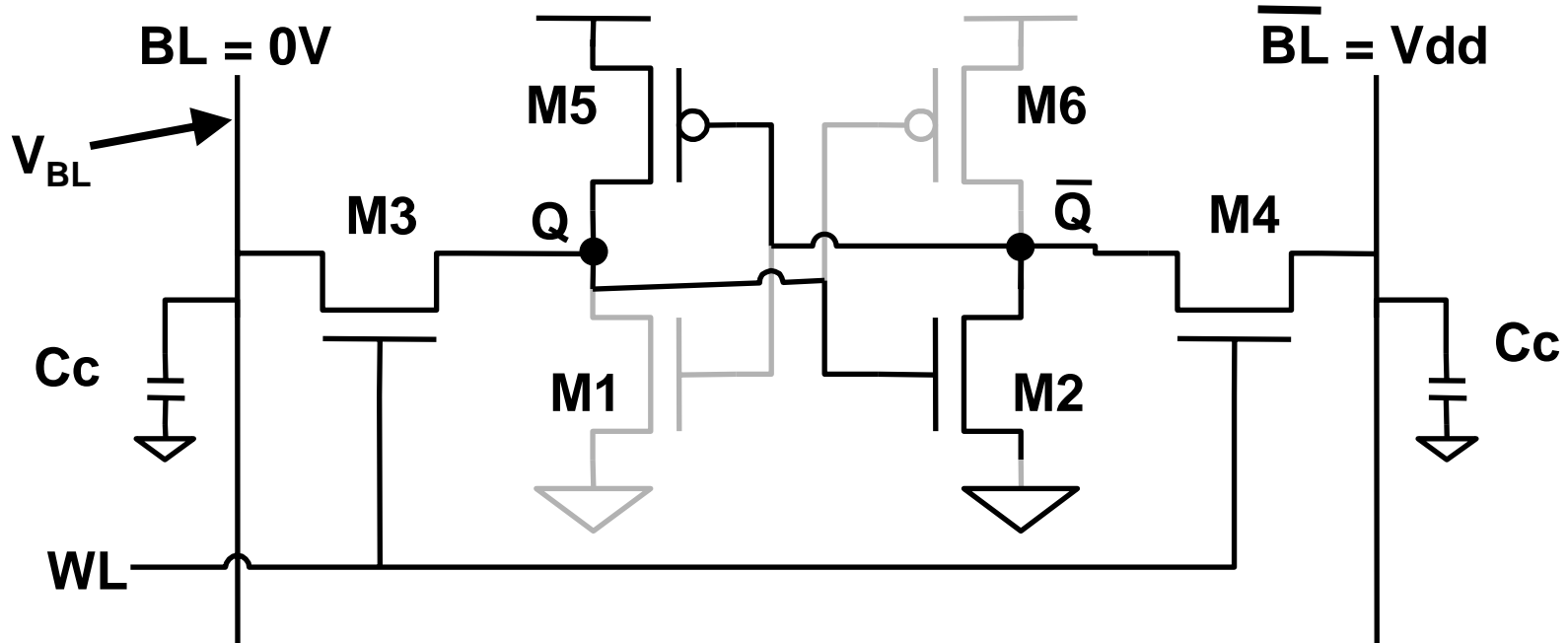


- Required sizing (make M5 relatively weaker than 1st case):

$$\frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_3} < \frac{k'_n}{k'_p} \frac{2(V_{DD} - 1.5V_{TN})V_{TN}}{(V_{DD} + V_{TP})^2}$$

SRAM Static Noise Margins

 
- **SRAM cell stability and writability quantitatively specified by static noise margin (SNM)**
 - Dependent on mode of operation (Hold, Read, or Write)



- **Hypothetical noise sources added to inverter inputs**
- **SNM corresponds to largest noise disturbances which won't disrupt cell operation**
- **SNM can be determined graphically by *butterfly plot***

Hold Static Noise Margin


Hold SNM Half Circuit

 

- Plot two mirrored V_{in}/V_{out} curves
- SNM = side of largest inscribed square


Hold SNM Butterfly Plot

Hold Static Noise Margin

 


Read Static Noise Margin

Read SNM Half Circuit

 


- **Diode-connected access NMOS simulates precharged bitline**

Read SNM Butterfly Plot

 


Write Static Noise Margin

Write 0 SNM Half Circuit

 

Write SNM Butterfly Plot

Write Static Noise Margin

 


- Always-on ground-connected access NMOS simulates bitline driven low, use Read Ckt for Write 1

Memory Peripherals

- **Memory core (memory cells) largely determined by technological considerations**
 - Emphasizes reduced area, sacrifices speed, reliability
 - Peripheral circuits can recover some of the lost performance
- **Address Decoders**
 - Row Decoders: one-hot decoding for word lines
 - Column Decoders: 2^L -to-1 multiplexers for bit lines
- **I/O Buffers and Drivers**
- **Sense Amplifiers**
- **Memory Timing and Control**

 Flash Memory Transistor With Floating Gate



- **Threshold voltage of device adjusted by placing charge on floating gate**

Flash Memory Operation

- **Two threshold voltages correspond to two states (1 bit)**
 - Bitline is precharged high before a read
 - Low V_T state, when wordline (control gate) is high the bitline is discharged and a “0” is read
 - High V_T state, the wordline (control gate) can’t go high enough to turn on transistor, bitline stays high and a “1” is read
- **Writing a “1”:** electrons are accelerated by a high field until they accumulate on the floating gate, raising V_T
- **Writing a “0”:** electrons driven off floating gate by a reverse gate-source bias through Fowler-Nordheim tunneling, lowering V_T

Next Topics: Low Power Circuits and Limits

- **Low power design principles and circuit techniques**
 - Voltage scaling, activity factor reduction, clock gating, leakage reduction
- **Implementation strategies**
 - Full Custom
 - ASIC (synthesis plus place & route)
 - Gate Array
- **Design for manufacturability**