

# **EEC 116 Lecture #5: CMOS Logic**

**Rajeevan Amirtharajah      Bevan Baas**  
**University of California, Davis**  
**Jeff Parkhurst**  
**Intel Corporation**

# Announcements

---


- **Quiz 1 today!**
- **Lab 2 reports due this week**
- **Lab 3 this week**
- **HW 2 due this Wednesday at 4 PM in box, Kemper 2131**

# Outline

---

- **Review: CMOS Inverter Transient Characteristics**
- **Review: Inverter Power Consumption**
- **Combinational MOS Logic Circuits: Rabaey 6.1-6.2 (Kang & Leblebici, 7.1-7.4)**
- **Combinational MOS Logic Transient Response**
  - AC Characteristics, Switch Model

# Review: CMOS Inverter VTC

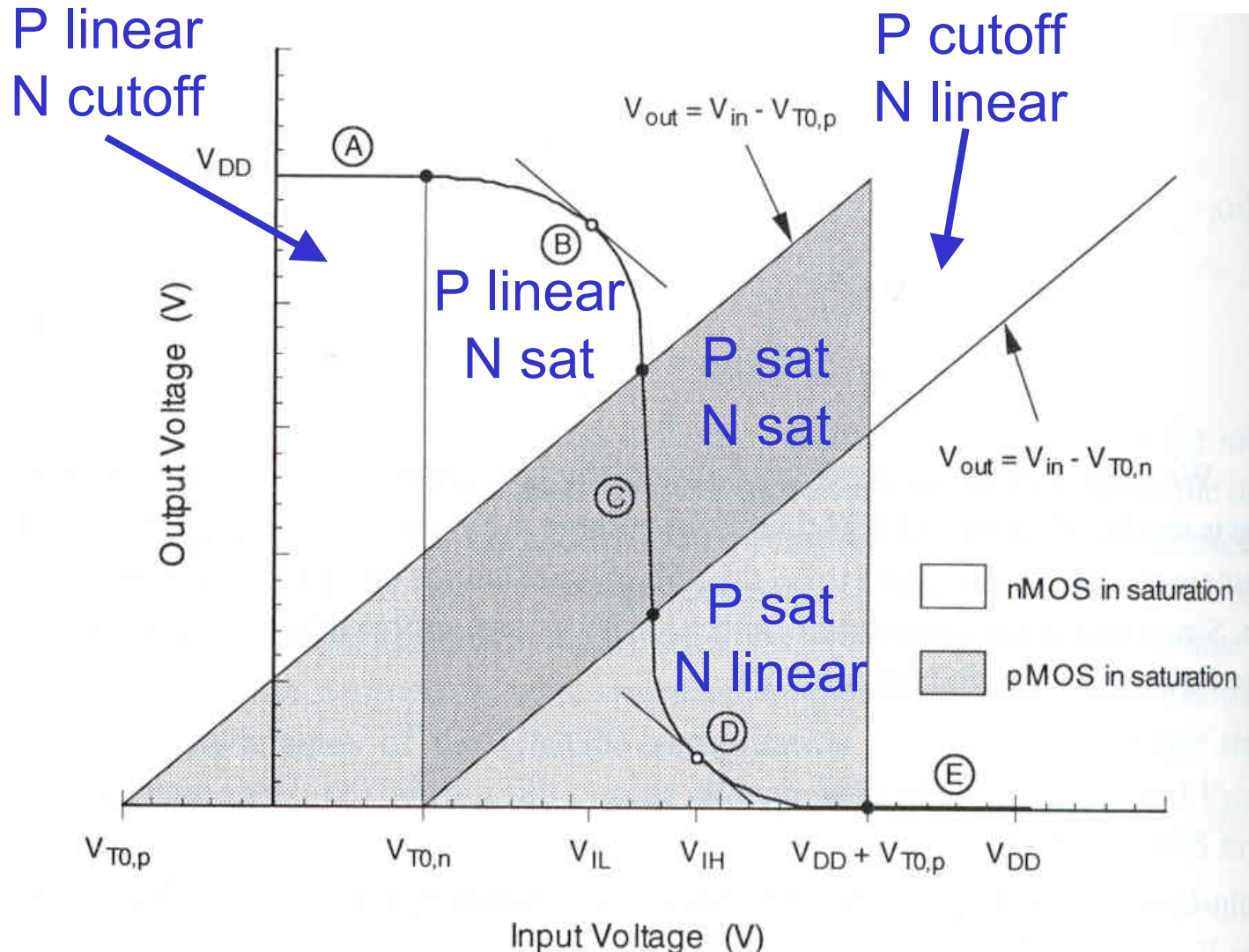

# Review: Logic Circuit Delay

---

- For CMOS (or almost all logic circuit families), only one fundamental equation necessary to determine delay:

$$I = C \frac{dV}{dt}$$

- Consider the discretized version:  $I = C \frac{\Delta V}{\Delta t}$

- Rewrite to solve for delay:  $\Delta t = C \frac{\Delta V}{I}$

- Only three ways to make faster logic:  $\downarrow C, \downarrow \Delta V, \uparrow I$

# Review: Inverter Delays

- **High-to-low and low-to-high transitions (exact):**

$$t_{PHL} = \frac{C_L}{k_n (V_{OH} - V_{T0,n})} \left[ \frac{2V_{T0,n}}{V_{OH} - V_{T0,n}} + \ln \left( \frac{4(V_{OH} - V_{T0,n})}{V_{OH} + V_{OL}} - 1 \right) \right]$$

$$t_{PLH} = \frac{C_L}{k_p (V_{OH} - V_{OL} - |V_{T0,p}|)} \left[ \frac{2|V_{T0,p}|}{V_{OH} - V_{OL} - |V_{T0,p}|} + \ln \left( \frac{4(V_{OH} - V_{OL} - |V_{T0,p}|)}{V_{OH} + V_{OL}} - 1 \right) \right]$$

- **Similar exact method to find rise and fall times**
- **Note: to balance rise and fall delays (assuming  $V_{OH} = V_{DD}$ ,  $V_{OL} = 0V$ , and  $V_{T0,n} = V_{T0,p}$ ) requires**

$$\frac{k_p}{k_n} = 1 \quad \left( \frac{W}{L} \right)_p / \left( \frac{W}{L} \right)_n = \frac{\mu_n}{\mu_p} \approx 2.5$$

# Review: Inverter Power Consumption


---

- **Static power consumption (ideal) = 0**
  - Actually DIBL (Drain-Induced Barrier Lowering), gate leakage, junction leakage are still present
- **Dynamic power consumption**

$$P_{avg} = \frac{1}{T} \int_0^T v(t) i(t) dt$$
$$P_{avg} = \frac{1}{T} \left[ \int_0^{T/2} V_{out} \left( -C_{load} \frac{dV_{out}}{dt} \right) dt + \int_{T/2}^T (V_{DD} - V_{out}) \left( C_{load} \frac{dV_{out}}{dt} \right) dt \right]$$
$$P_{avg} = \frac{1}{T} \left[ \left( -C_{load} \frac{V_{out}^2}{2} \right) \Big|_0^{T/2} + \left( V_{DD} V_{out} C_{load} - \frac{1}{2} C_{load} V_{out}^2 \right) \Big|_{T/2}^T \right]$$
$$P_{avg} = \frac{1}{T} C_{load} V_{DD}^2 = C_{load} V_{DD}^2 f$$
 
# Static CMOS


- Complementary pullup network (PUN) and pulldown network (PDN)
- Only one network is on at a time
- PUN: PMOS devices
  - Why?
- PDN: NMOS devices
  - Why?
- PUN and PDN are *dual* networks




 
# Dual Networks



- **Dual networks: parallel connection in PDN = series connection in PUN, vice-versa**
- **If CMOS gate implements logic function F:**
  - PUN implements function F
  - PDN implements function  $G = \overline{F}$


  
# NAND Gate

---

- **NAND function:  $F = \overline{A \cdot B}$**
- **PUN function:  $F = \overline{A \cdot B} = \overline{A} + \overline{B}$** 
  - “Or” function (+) → parallel connection
  - Inverted inputs  $\overline{A}, \overline{B}$  → PMOS transistors
- **PDN function:  $G = \overline{F} = A \cdot B$** 
  - “And” function (•) → series connection
  - Non-inverted inputs → NMOS transistors




# NOR Gate

---

- NOR gate operation:  $F = \overline{A+B}$

- PUN:  $F = \overline{A+B} = \overline{A} \cdot \overline{B}$

- PDN:  $G = \overline{F} = A+B$

 

# Analysis of CMOS Gates

---

- Represent “on” transistors as resistors




- Transistors in series  $\rightarrow$  resistances in series
  - Effective resistance =  $2R$
  - Effective length =  $2L$
 
# Analysis of CMOS Gates (cont.)

---

- Represent “on” transistors as resistors




- Transistors in parallel  $\rightarrow$  resistances in parallel
  - Effective resistance =  $\frac{1}{2} R$
  - Effective width =  $2W$
 
# CMOS Gates: Equivalent Inverter

---

- Represent complex gate as inverter for delay estimation
- Typically use worst-case delays
- Example: NAND gate
  - Worst-case (slowest) pull-up: only 1 PMOS “on”
  - Pull-down: both NMOS “on”



# Example: Complex Gate

---

Design CMOS gate for this truth table:

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$F = \overline{A \cdot (B + C)}$$

## Example: Complex Gate


---

Design CMOS gate for this logic function:

$$F = \overline{A \cdot (B + C)} = \overline{A} + \overline{B \cdot C}$$

1. Find NMOS pulldown network diagram:

$$G = \overline{F} = A \cdot (B + C)$$

 


Not a unique solution: can exchange order of series connection



## Example: Complex Gate

---

 
2. Find PMOS pullup network diagram:  $F = \overline{A} + (\overline{B} \cdot \overline{C})$




Not a unique solution: can exchange order of series connection (B and C inputs)

# Example: Complex Gate

Completed gate:

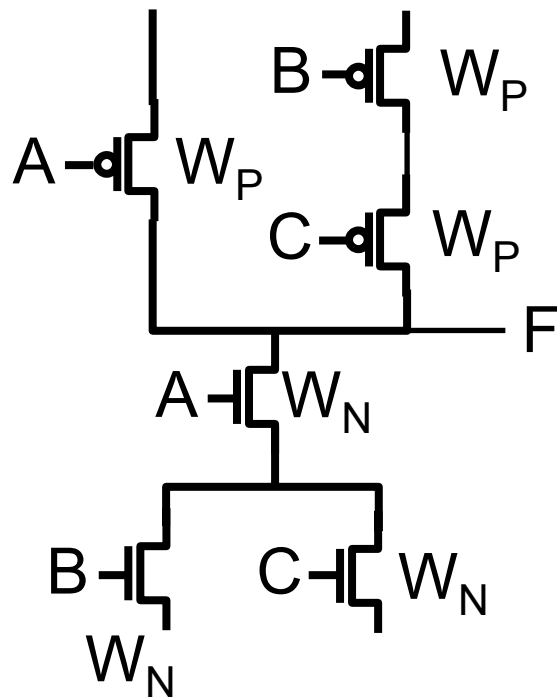

 - What is worse-case pullup delay?
- What is worse-case pulldown delay?
- Effective inverter for delay calculation:



# CMOS Gate Design

---

- **Designing a CMOS gate:**
  - Find pulldown NMOS network from logic function or by inspection
  - Find pullup PMOS network
    - By inspection
    - Using logic function
    - Using dual network approach
  - Size transistors using equivalent inverter
    - Find worst-case pullup and pulldown paths
    - Size to meet rise/fall or threshold requirements

# Analysis of CMOS gates

---

- Represent “on” transistors as resistors



- Transistors in series  $\rightarrow$  resistances in series
  - Effective resistance =  $2R$
  - Effective width =  $\frac{1}{2} W$  (equivalent to  $2L$ )
  - Typically use minimum length devices ( $L = L_{\min}$ )

# Analysis of CMOS Gates (cont.)

---

- Represent “on” transistors as resistors



- Transistors in parallel  $\rightarrow$  resistances in parallel
  - Effective resistance =  $\frac{1}{2} R$
  - Effective width =  $2W$
  - Typically use minimum length devices ( $L = L_{min}$ )

# Equivalent Inverter

---

- **CMOS gates: many paths to Vdd and Gnd**
  - Multiple values for  $V_M$ ,  $V_{IL}$ ,  $V_{IH}$ , etc
  - Different delays for each input combination
- **Equivalent inverter**
  - Represent each gate as an inverter with appropriate device width
  - Include only transistors which are on or switching
  - Calculate  $V_M$ , delays, etc using inverter equations

# Static CMOS Logic Characteristics

---

- **For  $V_M$ , the  $V_M$  of the equivalent inverter is used (assumes all inputs are tied together)**
  - For specific input patterns,  $V_M$  will be different
- **For  $V_{IL}$  and  $V_{IH}$ , only the worst case is interesting since circuits must be designed for worst-case noise margin**
- **For delays, both the maximum and minimum must be accounted for in race analysis**

# Equivalent Inverter: $V_M$

---


- **Example: NAND gate threshold  $V_M$**   
**Three possibilities:**
  - A & B switch together
  - A switches alone
  - B switches alone
  
- **What is equivalent inverter for each case?**


 
# Equivalent Inverter: Delay

---


- Represent complex gate as inverter for delay estimation
- Use worse-case delays
- Example: NAND gate
  - Worse-case (slowest) pull-up: only 1 PMOS “on”
  - Pull-down: both NMOS “on”


 
# Example: NOR gate


---

- Find threshold voltage  $V_M$  when both inputs switch simultaneously
- Two methods:
  - Transistor equations (complex)
  - Equivalent inverter
  - Should get same answer




# Example: Complex Gate

Completed gate:

 

 - What is worse-case pullup delay?
- What is worse-case pulldown delay?
- Effective inverter for delay calculation:



# Transistor Sizing

---

- **Sizing for switching threshold**
  - All inputs switch together
- **Sizing for delay**
  - Find worst-case input combination
- **Find equivalent inverter, use inverter analysis to set device sizes**

# Common CMOS Gate Topologies

---

- **And-Or-Invert (AOI)**
  - Sum of products boolean function
  - Parallel branches of series connected NMOS
- **Or-And-Invert (OAI)**
  - Product of sums boolean function
  - Series connection of sets of parallel NMOS

# Stick Diagrams


---

- **Dimensionless layout sketches**
- **Only topology is important**
- **Two primary uses**
  - Useful intermediate step
    - Transistor schematic is the first step
    - Layout is the last step
  - Final layout generated automatically by “compaction” program
    - Not widely used; a topic of research
- **Use colored pencils or pens whose colors match Cadence layer colors**




 
# Inverter Stick Diagram

- Diagram here uses magic standard color scheme
- Label all nodes
- Transistor widths ( $W$ ) often shown—with varying units
  - Often in  $\lambda$  in this class
  - Also nm or  $\mu\text{m}$
  - Sometimes as a unit-less ratio—this stick diagram could also say the PMOS is 1.5x wider than the NMOS (saying “1” and “1.5” instead of “ $6\lambda$ ” and “ $9\lambda$ ”)



 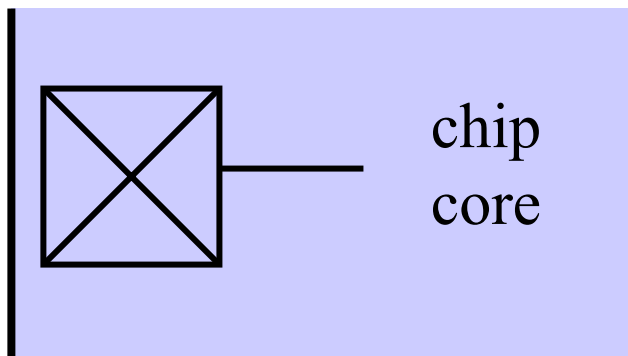
# Stick Diagrams

- Can also draw contacts with an “X”
- Do not confuse this “X” with the chip I/O and power pads on the edge of chip (shown with a box with an “X”) or any other markers





 
# Layout for the Inverter in the Stick Diagram


 
# Graph-Based Dual Network

---



- **Use graph theory to help design gates**
  - Mostly implemented in CAD tools
- **Draw network for PUN or PDN**
  - Circuit nodes are vertices
  - Transistors are edges


  
# Graph-Based Dual Network (2)


---

- **To derive dual network:**
  - Create new node in each enclosed region of graph
  - Draw new edge intersecting each original edge
  - Edge is controlled by inverted input




- Convert to layout using consistent Euler paths

 
# Propagation Delay Analysis - The Switch Model



(a) Inverter

 

(b) 2-input NAND

 

(c) 2-input NOR


$$t_p = 0.69 R_{on} C_L$$

(assuming that  $C_L$  dominates!)
 
# Switch Level Model

---

- **Model transistors as switches with series resistance**
- **Resistance  $R_{on}$  = average resistance for a transition**
- **Capacitance  $C_L$  = average load capacitance for a transition (same as we analyzed for transient inverter delays)**



# What is the Value of $R_{on}$ ?

---


- *Depends strongly on the operating region*
- *For hand analysis use a fixed value of  $R$  which is the average of the two end points of the transition*
- *Similar to the previous approach of averaging currents*

**EXAMPLE:** For  $t_{pHL}$  for an inverter, the  $R_{on}$  is:

$$\begin{aligned} R_{on} &= \frac{1}{2}(R_{NMOS}(V_{out} = V_{DD}) + R_{NMOS}(V_{out} = V_{DD}/2)) \\ &= \frac{1}{2}\left(\left(\frac{V_{DS}}{I_D}\right)_{V_{out} = V_{DD}} + \left(\frac{V_{DS}}{I_D}\right)_{V_{out} = V_{DD}/2}\right) \end{aligned}$$
 
# Switch Level Model Delays

Delay estimation using switch-level model (for general RC circuit):



$$I = C \frac{dV}{dt} \quad \rightarrow \quad dt = \frac{C}{I} dV$$

$$I = \frac{V}{R} \quad \rightarrow \quad dt = \frac{RC}{V} dV$$

$$t_1 - t_0 = t_p = \int_{V_0}^{V_1} \frac{RC}{V} dV$$

$$t_p = RC [\ln(V_1) - \ln(V_0)] = RC \ln \left( \frac{V_1}{V_0} \right)$$

# Switch Level Model RC Delays

---

- For fall delay  $t_{phl}$ ,  $V_0=V_{DD}$ ,  $V_1=V_{DD}/2$

$$t_p = RC \ln\left(\frac{V_1}{V_0}\right) = RC \ln\left(\frac{\frac{1}{2} V_{DD}}{V_{DD}}\right)$$

$$t_p = RC \ln(0.5)$$

$$t_{phl} = 0.69 R_n C_L$$

$$t_{plh} = 0.69 R_p C_L$$

← Standard RC-delay equations from literature



# Numerical Examples

---

- **Example resistances for 1.2  $\mu\text{m}$  CMOS**

$$V_{DD} = 5V, W/L_{eff}=1 \text{ (} W/L_{eff}=2 \text{ is a minimum sized device } 1.8\mu\text{m}/0.9\mu\text{m)}$$
$$L_{eff} = 1.2\mu\text{m} - 2(.15\mu\text{m}) = 0.9\mu\text{m}$$

$$R_n(W/L_{eff}=2) = (5 \text{ V} / 0.46 \text{ mA} + 2.5 \text{ V} / 0.29 \text{ mA}) / 2 = 9.7 \text{ k}\Omega \text{ (for } t_{pHL}\text{)}$$


$$R_n(W/L_{eff}=1) = 9.7 * 2 = 19.4 \text{ k}\Omega \text{ (for } t_{pHL}\text{)}$$

$$R_p(W/L_{eff}=6) = (5 \text{ V} / 0.57 \text{ mA} + 2.5 \text{ V} / 0.24 \text{ mA}) / 2 = 9.6 \text{ k}\Omega \text{ (for } t_{pLH}\text{)}$$

$$R_p(W/L_{eff}=1) = 9.6 * 6 = 57.6 \text{ k}\Omega \text{ (for } t_{pLH}\text{)}$$

**SOLVE RC NETWORK TO DETERMINE DELAYS**

# Analysis of Propagation Delay

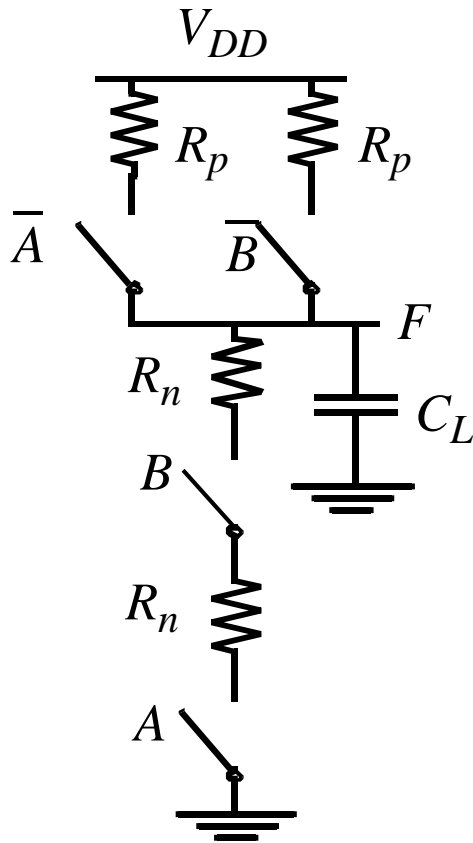

2-input NAND


1. Assume  $R_n = R_p =$  resistance of minimum sized NMOS inverter
2. Determine “Worst Case Input” transition (Delay depends on input values)
3. Example:  $t_{pLH}$  for 2input NAND
  - Worst case when only ONE PMOS Pulls up the output node
  - For 2 PMOS devices in parallel, the resistance is lower

$$t_{pLH} = 0.69 R_p C_L$$


4. Example:  $t_{pHL}$  for 2input NAND
  - Worst case : TWO NMOS in series

$$t_{pHL} = 0.69(2R_n)C_L$$

# Design for Worst Case

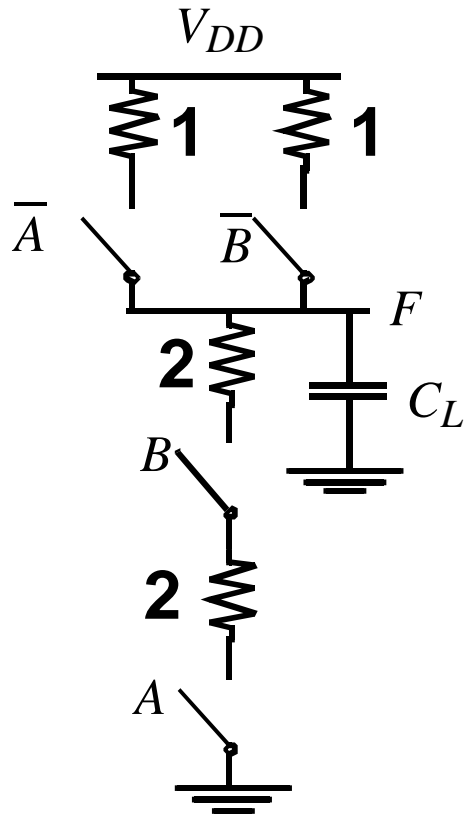


**NAND Gate**

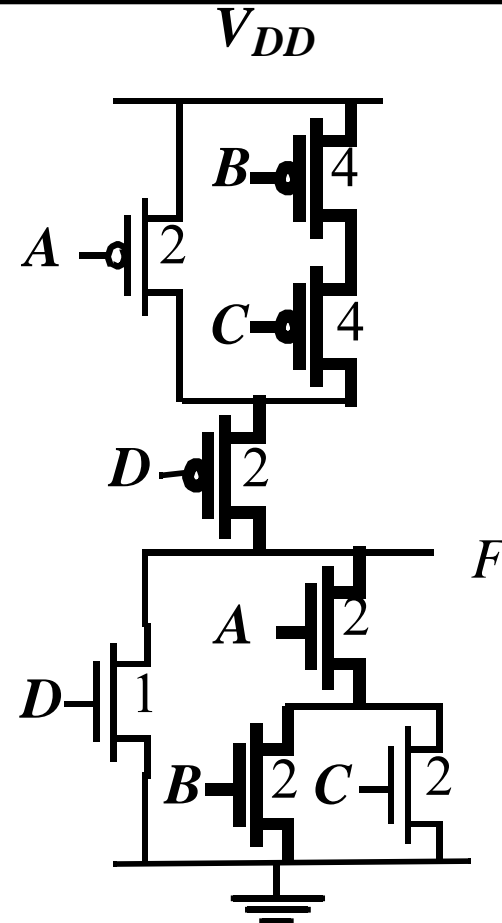

**Complex Gate**

Here it is assumed that  $R_p = R_n$

# Fan-In and Fan-Out

 

## Fan-Out

Number of logic gates connected to output  
(2 FET gate capacitances per fan-out)

## Fan-In

Number of logical inputs  
Quadratic delay term due to:  
1. Resistance increasing  
2. Capacitance increasing  
for  $t_{pHL}$  (series NMOS)


$$t_p \text{ proportional to } a_1 FI + a_2 FI^2 + a_3 FO$$

# Fast Complex Gates - Design Techniques

- **Increase Transistor Sizing:**

**Works as long as Fan-out capacitance dominates self capacitance (S/D cap increases with increased width)**

- **Progressive Sizing:**


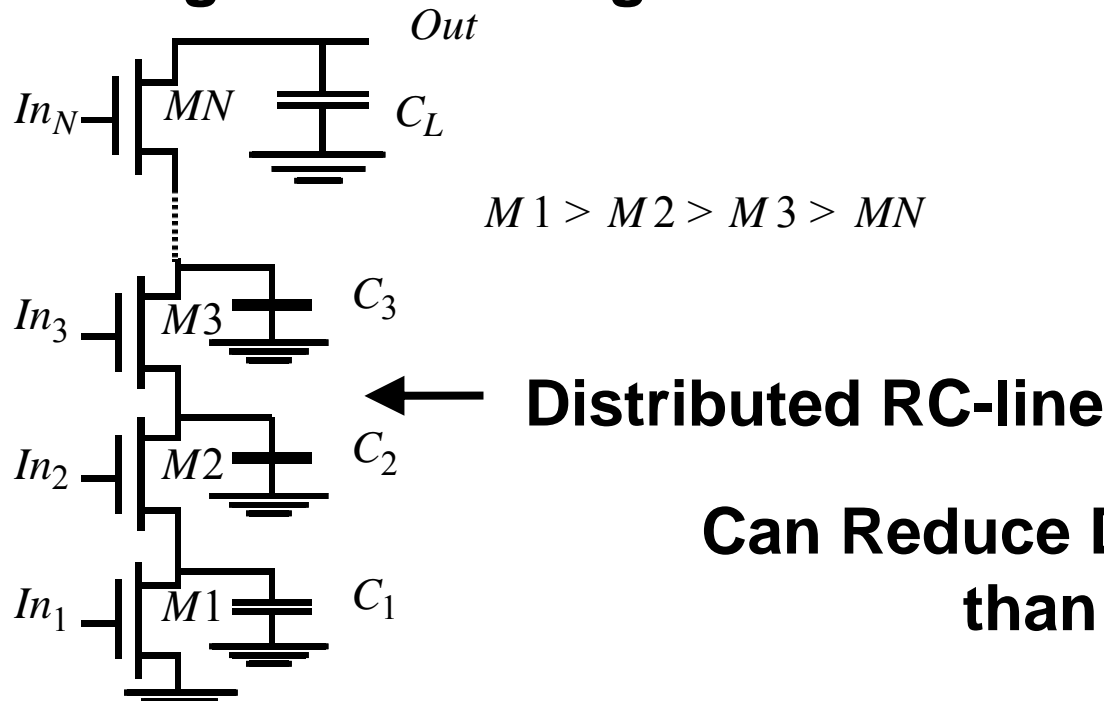


**Can Reduce Delay by more than 30%!**
  
# Fast Complex Gates - Design Techniques (2)

- Transistor Ordering


Place last arriving input closest to output node



# Fast Complex Gates - Design Techniques (3)

---


- Improved Logic Design

 

Note Fan-Out capacitance is the same, but Fan-In resistance lower for input gates (fewer series FETs)

# Fast Complex Gates - Design Techniques (4)



- Buffering: Isolate Fan-in from Fan-out

 


Keeps high fan-in resistance isolated from large capacitive load  $C_L$



# 4 Input NAND Gate

  

# Capacitances in a 4 input NAND Gate

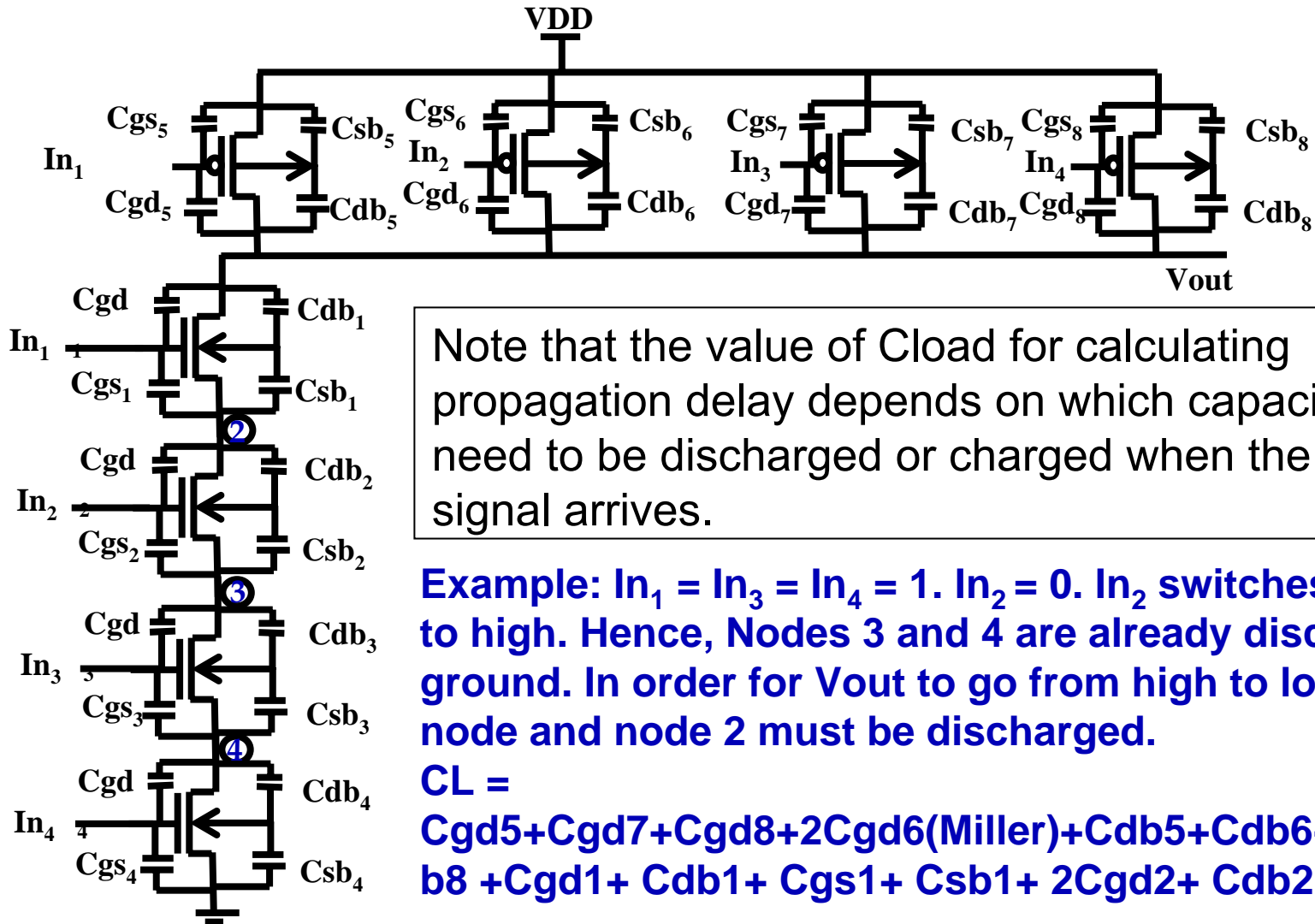

# Next Topic: Arithmetic

---

- **Computing arithmetic functions with CMOS logic**
  - Half adder and full adder circuits
  - Circuit architectures for addition
  - Array multipliers