

1. Single Transistor DRAM

Problem 1

a) Bitline $BL = V_{DD} = 5V$, Wordline $= V_{DD} = 5V$
 Final voltage $V_S = V_{DD} - V_{T,n}$, but $V_{SB} = V_S \Rightarrow$

$$V_S = V_{DD} - V_{T_0} - \gamma(\sqrt{|2\phi_F| + V_S} - \sqrt{|2\phi_F|})$$

$$= 5 - 1.0 - 0.3(\sqrt{0.6 + V_S} - \sqrt{0.6})$$

Solve by iteration (or graphically) $V_S = 3.62 V$

b) During a READ-1, $V_S = 3.62 V$ and $BL = V_{DD}/2$. Capacitors C_{BL} and C_S short together and share their charge.

$$Q_{BL} = C_{BL} \frac{V_{DD}}{2} = (450 \text{ fF})(2.5 V)$$

$$Q_S = C_S V_S = (50 \text{ fF})(3.62 V)$$

$$V_{BL}(\text{final}) = \frac{Q_{TOT}}{C_{TOT}} = \frac{Q_{BL} + Q_S}{C_{BL} + C_S} = \frac{(450 \text{ fF})(2.5 V) + (50 \text{ fF})(3.62 V)}{500 \text{ fF}}$$

$$V_{BL}(\text{final}) = 2.61 V$$


Note Using 10.1 in K+L p.420, $V_{BL}(\text{final}) = \frac{V_{DD}}{2} + \Delta V = 2.5 V + \frac{50 \text{ fF} \cdot 2.5 V}{500 \text{ fF}}$
 $= 2.75 V$ is incorrect!

The book equation assumed $V_S = V_{DD}$!

2. SRAM Cell Design

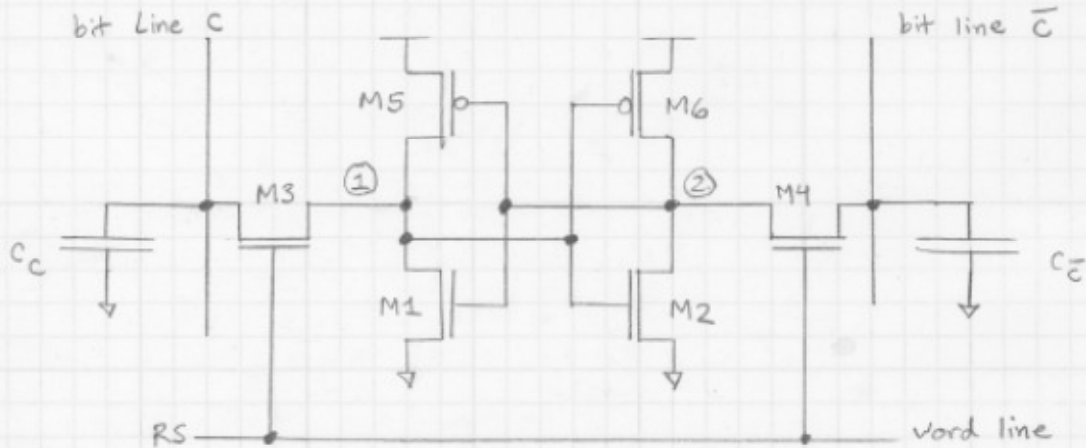Problem 2

To change the state of the cell for $V_C \leq 0.5V$, the voltage at node ① must be V_{DD} (if it were 0V then the cell wouldn't change state).



For M1, M2, $w/L = 4/4$ } must size M5, M6 assuming $(w/L)_5 = (w/L)_6$
 For M3, M4, $w/L = 2/4$ }

Suppose node ① is initially at V_{DD} . To switch the SRAM state, node ① voltage must go below the M6, M2 inverter switching threshold:

$$\text{Voltage @ node ①} = V_1 \leq V_{TH} = \frac{V_{T0,n} + \sqrt{\frac{1}{K_R}} (V_{DD} - V_{T0,p})}{1 + \sqrt{\frac{1}{K_R}}}$$

$$K_R = \frac{k_n}{k_p} = \frac{k_n' (w/L)_2}{k_p' (w/L)_6} = \frac{2 (4/4)}{(w/L)_6} = 2 \left(\frac{L}{w}\right)_6$$

If node ① initially at V_{DD} , node ② is initially 0V. Assuming $V_{TH} \approx V_{DD}/2$, then M5 and M3 are in linear region and M1 is cut off.

$$I_{DS, M3} = I_{DS, M5} \Rightarrow$$

$$\frac{k_n' (w/L)_3}{2} \left[2(V_{DD} - V_{T,n3})(V_1 - V_C) - (V_1 - V_C)^2 \right] = \frac{k_p' (w/L)_6}{2} \left[2(-V_{DD} - V_{T,p6})(V_1 - V_{DD}) - (V_1 - V_{DD})^2 \right]$$

Assume $V_{DD} = 5 \text{ V}$. $V_{T0,P} = -0.7 \text{ V}$


$$\text{For } V_{T,n3}: V_{SB} = 0.5 \text{ V} \Rightarrow V_{T,n3} = V_{T0} + \gamma (\sqrt{|2\phi_F| + V_{SB}} - \sqrt{|2\phi_F|}) \\ = 0.7 \text{ V} + 0.4 (\sqrt{0.6 + 0.5} - \sqrt{0.6}) \text{ V} = 0.810 \text{ V}$$

$$\text{Let } X = \left(\frac{W}{L}\right)_6, V_1 = V_{TH} = \frac{0.7 + \sqrt{X/2} (5 - 0.7)}{(1 + \sqrt{X/2})} = \frac{0.7 + \sqrt{X/2} (4.3)}{1 + \sqrt{X/2}}$$

Plug $V_1(x)$ into the current equations and solve numerically...

$$\left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_5 \cong \boxed{0.5} \quad V_{TH} = 1.9 \text{ V}, \text{ therefore linear assumption was good.}$$

3. Voltage Scaling

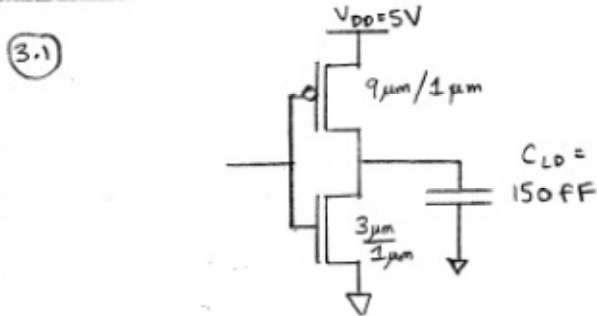

$t_{pLH} = t_{pHL}$ for balanced inverter.

$$\begin{aligned}
 t_{pHL} &= \frac{C\Delta V}{I_{avg}} = \frac{C_{LD}(V_{DD}/2)}{I_{avg}} = \frac{C_{LD}(V_{DD}/2)}{\frac{1}{2} \left(\underbrace{I_{D0S}}_{\text{sat}} \Big|_{\substack{V_{GS}=5V \\ V_{DS}=5V}} + \underbrace{I_{D0S}}_{\text{linear}} \Big|_{\substack{V_{GS}=5V \\ V_{DS}=2.5V}} \right)} \\
 &= \frac{(150\text{fF})(2.5V)}{\frac{1}{2} \left(\frac{300\mu\text{A}/V^2}{2} \left(\frac{3}{1} \right) (5V - 0.8V)^2 + 300\mu\text{A}/V^2 \left(\frac{3}{1} \right) [(5V - 0.8V)(2.5V) + (2.5V)^2/2] \right)} \\
 &= \frac{(150\text{fF})(2.5V)}{7.288\text{mA}} = \boxed{51.45\text{ps}}
 \end{aligned}$$

3.2 $P_{max} = C_{LD} V_{DD}^2 f_{max} = \frac{C_{LD} V_{DD}^2}{\frac{1}{2}(t_{pLH} + t_{pHL})} = \boxed{72.88\text{mW}}$

3.3 $V_{DD,min} = \boxed{1.5093V}$

$$P_{max} = C_{LD} V_{DD,min}^2 \left(\frac{1}{500\text{ps}} \right) = \boxed{683\mu\text{W}}$$