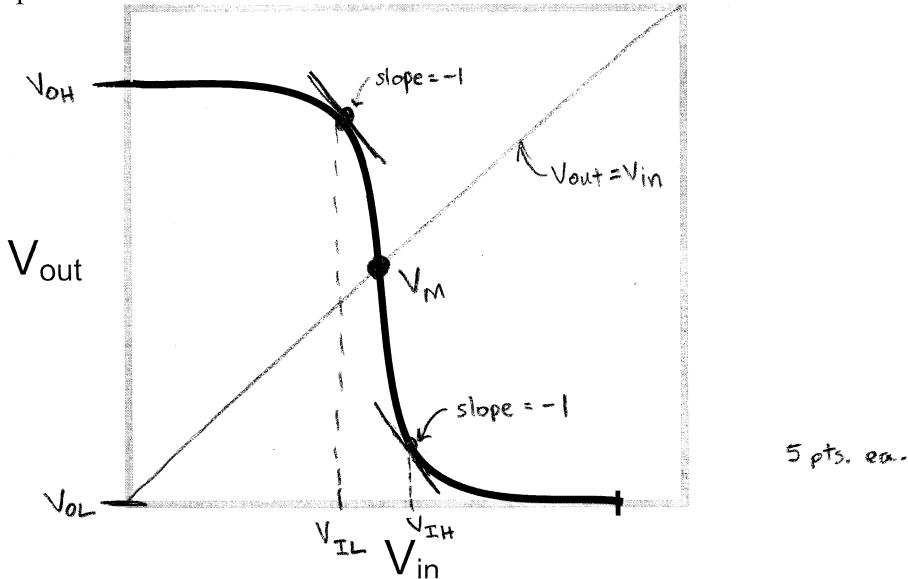



Name: Solutions

Lab Section: _____

Problem 1 (5 points) Label the following points on the Voltage Transfer Curve below: VOH, VOL, VIH, VIL, and VM. Indicate any other lines that are necessary to define the preceding voltage points.



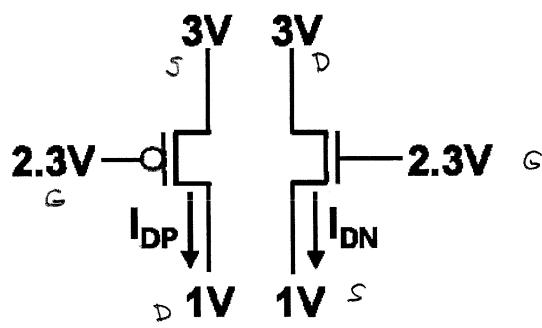Problem 2 (5 points) For the following circuit, find the value of W_p/L_p so that currents I_{DN} and I_{DP} are equal, given: $W_n/L_n = 1$, $V_{T,n} = 0.5V$, $\mu_n C_{ox} = 300 \times 10^{-6} A/V^2$, $V_{T,p} = -0.5V$, $\mu_p C_{ox} = 100 \times 10^{-6} A/V^2$, $\lambda = 0$, $\gamma = 0$, $V_{DD} = 3V$. Show all work to receive full credit.



$$\begin{aligned} V_{GS,N} &= 2.3V - 1V = 1.3V > V_{TN} = 0.5V && \text{NMOS sat} \\ V_{DS,N} &= 3V - 1V = 2V > V_{GS,N} - V_{TN} = 0.8V && \underline{\text{sat}} \\ V_{GS,P} &= 2.3V - 3V = -0.7V < V_{TP} = -0.5V \\ V_{DS,P} &= 1V - 3V = -2V < V_{GS,P} - V_{TN} = -0.7V - (-0.5V) \\ &= -0.2V && \text{PMOS sat} \end{aligned}$$

$$\begin{aligned} I_{DS,N} &= \frac{\mu_n C_{ox}}{2} \left(\frac{W_n}{L_n} \right) (V_{GS,n} - V_{TN})^2 \\ &= \frac{300 \mu A/V^2}{2} (1) (0.8V)^2 = 96 \mu A \end{aligned}$$

$$\begin{aligned} I_{DS,P} &= \frac{\mu_p C_{ox}}{2} \left(\frac{W_p}{L_p} \right) (V_{GS,p} - V_{TP})^2 \\ &= \frac{100 \mu A/V^2}{2} \left(\frac{W_p}{L_p} \right) (-0.2V)^2 = 2 \mu A \end{aligned}$$

$$\left(\frac{W_p}{L_p} \right) = \frac{I_{DS,N}}{I_{DS,P}} = 48$$