

Name: Solutions Lab Section: \_\_\_\_\_

**Problem 1 (3 points)** Suppose a 1μm wide wire in Metal 1 (M1) has resistance per unit length  $r = 100\text{m}\Omega/\text{mm}$  and capacitance per unit length  $c = 100\text{pF}/\text{mm}$  while a 1μm wide wire in Metal 2 (M2) has resistance per unit length  $r = 80\text{m}\Omega/\text{mm}$  and capacitance per unit length  $c = 120\text{pF}/\text{mm}$ . Using the Elmore delay approximation, what is the delay for the fastest of the two wires assuming length  $L=1.3\text{mm}$ ?

$$\tau_D = \frac{rcL^2}{2}$$

(1pt.)

$rc \text{ (M1)} = 10,000 \text{ m}\Omega \cdot \text{pF}/\text{mm}^2$       M2 fastest (1pt.)

$rc \text{ (M2)} = 9600 \text{ m}\Omega \cdot \text{pF}/\text{mm}^2$        $\tau_D \text{ (M2)} = \frac{9.6 \times 10^3 (1.3)^2}{2} = \boxed{8.112 \text{ ps}}$

(1pt.)

**Problem 2 (2 points)** Using the Elmore delay approximation, what is the maximum length of a 1μm wide wire in Metal 1 (M1) such that its delay is less than 25ps?

$$\frac{rcL^2}{2} \leq 25\text{ps} \Rightarrow L \leq \sqrt{\frac{2(25\text{ps})}{(100\text{m}\Omega/\text{mm})(100\text{pF}/\text{mm})}} = \boxed{2.24 \text{ mm}}$$


(1pt.)      (1pt.)

**Problem 3 (5 points)** For the inverter buffer chain below, assume the optimal fanout factor is  $f = 4.4$  and a minimum size inverter has  $W_n = 0.45\mu\text{m}$  and  $W_p = 1.35\mu\text{m}$ . How many stages  $N$  are required for a minimum delay through the chain and what are the transistor widths for the final inverter in the chain?

$N = \boxed{5 \text{ or } 6}$

$W_n \text{ (Nth inverter)} = \boxed{168.7 \text{ or } 742 \mu\text{m}}$

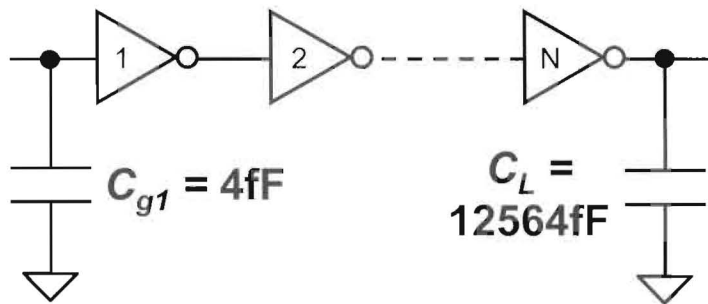$W_p \text{ (Nth inverter)} = \boxed{506 \mu\text{m} \text{ or } 2226 \mu\text{m}}$



$$F = \frac{C_L}{C_{g1}} = 3141, \quad f^N = F \quad (2\text{pt.})$$

$$N = \frac{\ln(F)}{\ln(f)} = \frac{\ln(3141)}{\ln(4.4)} \quad (1\text{pt.})$$

$$= 5.43$$

for  $N=5$ :  $W_n = (0.45\mu\text{m})(4.4)^{(5-1)} = 168.7\mu\text{m}$  (1pt.)

$W_p = (1.35\mu\text{m})(4.4)^{(5-1)} = 506\mu\text{m}$

for  $N=6$ :  $W_n = (0.45\mu\text{m})(4.4)^{(6-1)} = 742\mu\text{m}$  (1pt.)

$W_p = (1.35\mu\text{m})(4.4)^{(6-1)} = 2226\mu\text{m}$