 

Arithmetic Building Blocks


Chapter 11 Rabaey



Announcements

- Today: wrap up sequential circuits, start discussing arithmetic circuits

A Generic Digital Processor

 

Building Blocks for Digital Architectures

Datapath (Arithmetic Unit)

- Bit-sliced datapath (adder , multiplier, shifter, comparator, etc.)

Memory

- RAM, ROM, Buffers, Shift registers


Control

- Finite state machine (PLA, random logic.)
- Counters

Interconnect


- Switches
- Arbiters
- Bus

Bit-Sliced Design

 


Tile identical processing elements

Full Adder

 

A	B	C_i	S	C_o	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

The Binary Adder

 


$$S = A \oplus B \oplus C_i$$

$$= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i$$

$$C_o = AB + BC_i + AC_i$$

The Ripple-Carry Adder

 


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{\text{adder}} \approx (N - 1)t_{\text{carry}} + t_{\text{sum}}$$

Goal: Make the fastest possible carry path circuit

Complimentary Static CMOS Full Adder

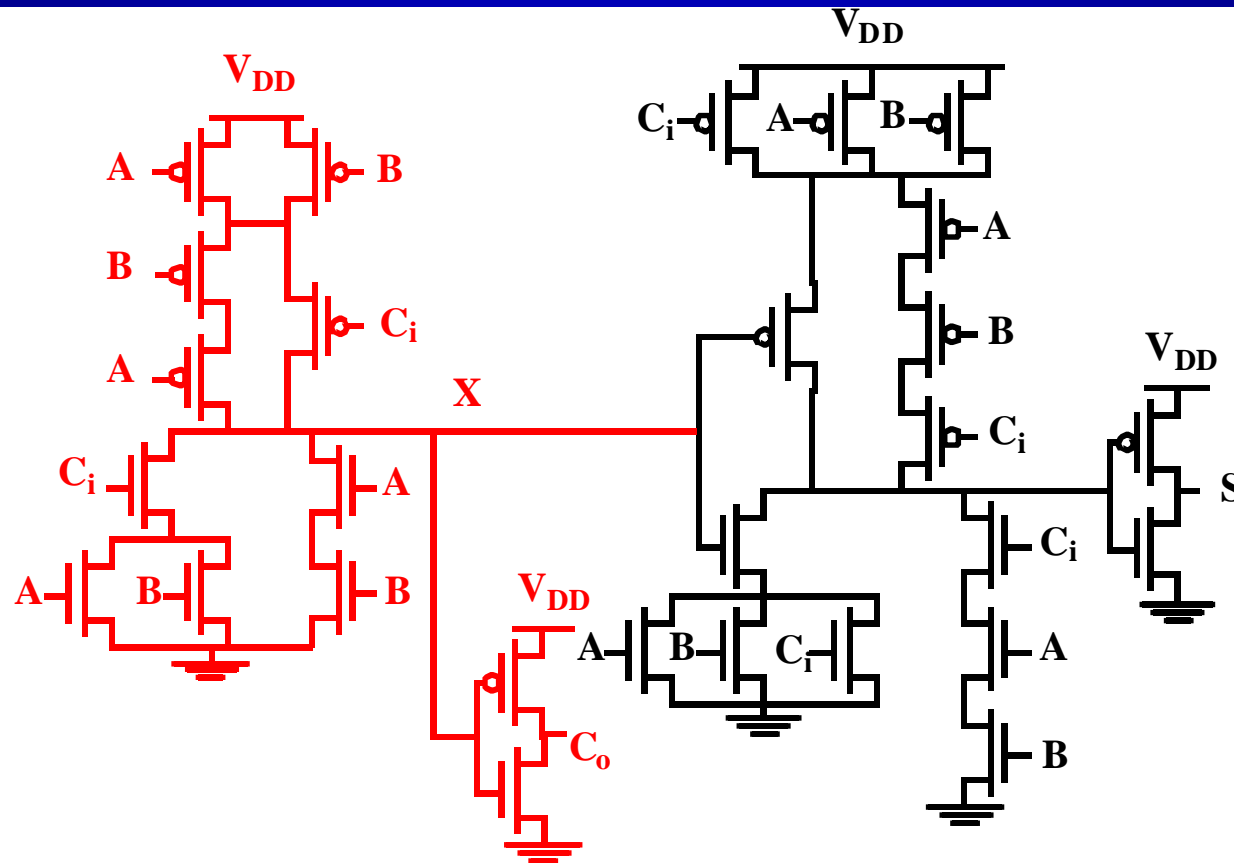


28 Transistors

Arithmetic

A Closer Look

- Drawbacks

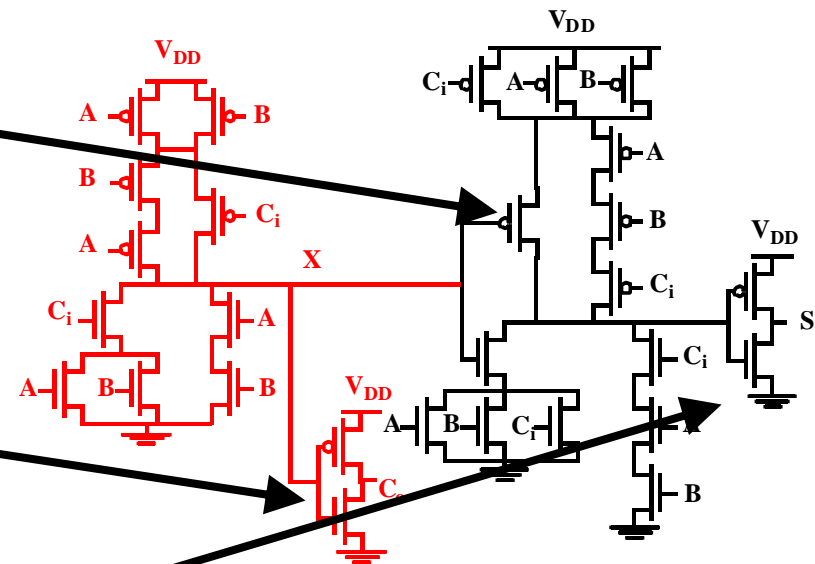- » Tall PMOS Stack
 - Slows down circuit
- » C_o load is 2 diffusion and 6 gate capacitances
- » C_i goes through the extra output inverter to C_o
 - Could optimize with next stage
- » Sum generation has extra inverter on output
 - Not the critical path




28 Transistors

- Positive

- » C_i closest to output node


Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

 
Minimize Critical Path by Reducing Inverting Stages



Exploit Inversion Property

Note: need 2 different types of cells

Applying Inversion Property

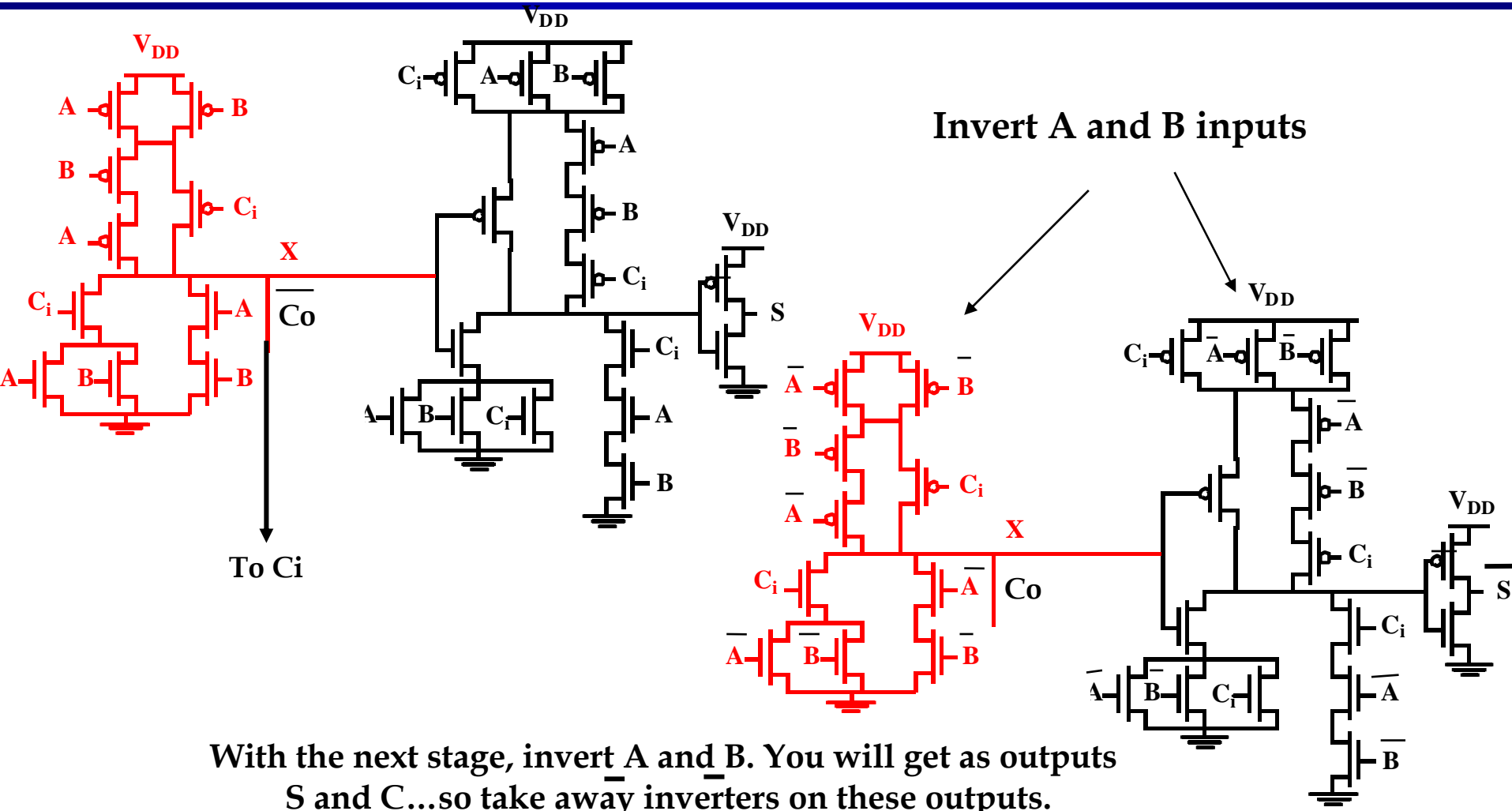

With the next stage, invert \bar{A} and \bar{B} . You will get as outputs S and C ...so take away inverters on these outputs.

Express Sum and Carry as Function of P, G, D

Define 3 new variable which ONLY depend on A, B

Generate (G) = AB $C_0 = 1$ if $G = 1$

Propagate (P) = A \oplus B $C_0 = C_i$ if $P = 1$

Delete = $\bar{A} \bar{B}$ $C_0 = 0$ if $D = 1$


$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

A	B	C_i	S	C_o	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

Can also derive expressions for S and C_o based on D and P

A Better Structure: the Mirror Adder

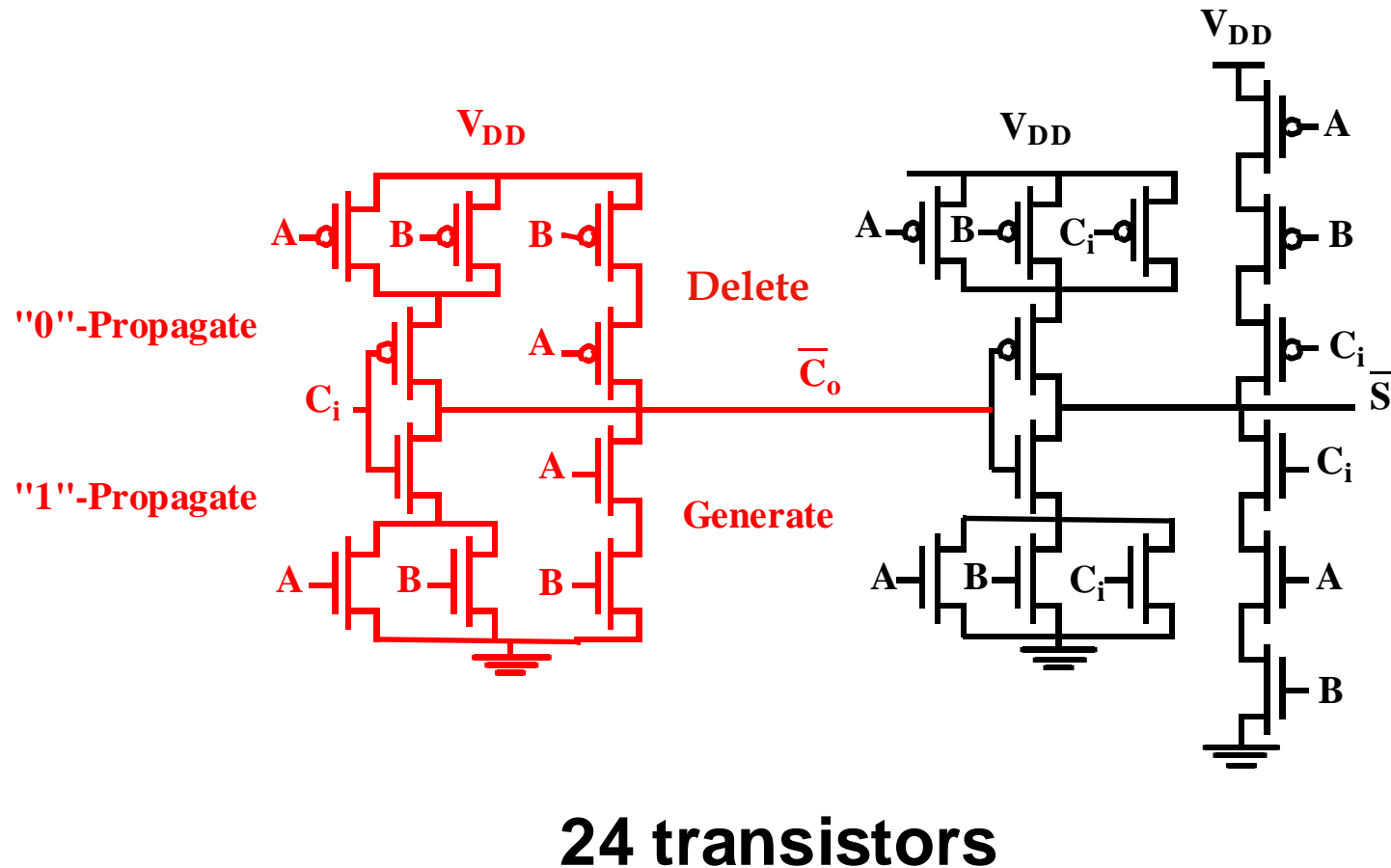

The Mirror Adder I

- The NMOS and PMOS chains are **completely symmetrical**. This guarantees identical rising and falling transitions if the NMOS and PMOS devices are properly sized. A maximum of two series transistors can be observed in the carry-generation circuitry.
- When laying out the cell, the most critical issue is the minimization of the capacitance at node C_o . The reduction of the diffusion capacitances is particularly important.
- The capacitance at node C_o is composed of four diffusion capacitances, two internal gate capacitances, and six gate capacitances in the connecting adder cell .


The Mirror Adder II

- The transistors connected to C_i are placed closest to the output.
 - Fastest for late arriving inputs, C_i tends to arrive late
- Only the transistors in the carry stage have to be optimized for optimal speed. All transistors in the sum stage can be minimal size.

Adder Architectures


- In addition to optimizing each full adder cell and exploiting inversion property, we can also reorganize the add computation to speed things up
- Basic idea is to overlap propagating the carry with computing the Propagate and Generate functions
- Discuss three basic architectures
 - Carry-Bypass
 - Carry-Select
 - Carry-Lookahead

Carry-Bypass Adder

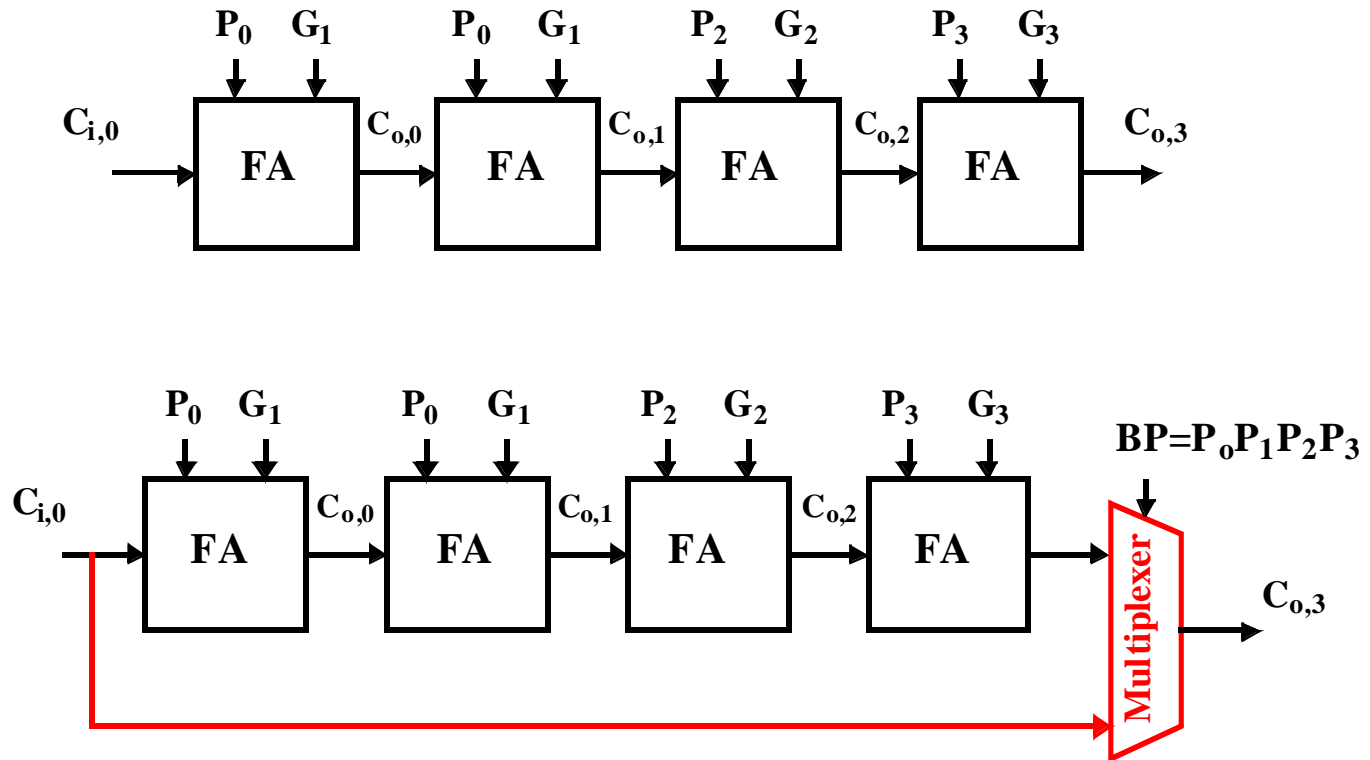


Idea: If (P_0 and P_1 and P_2 and $P_3 = 1$)
then $C_{o,3} = C_{i,0}$, else “kill” or “generate”.

Carry-Bypass Adder (cont.)

 


Note that this is done at the expense of a MUX in the carry delay path !!

Carry Ripple vs. Carry Bypass

 


Essentially greater than 4 bits is needed to overcome the overhead of the MUX


Carry-Select Adder

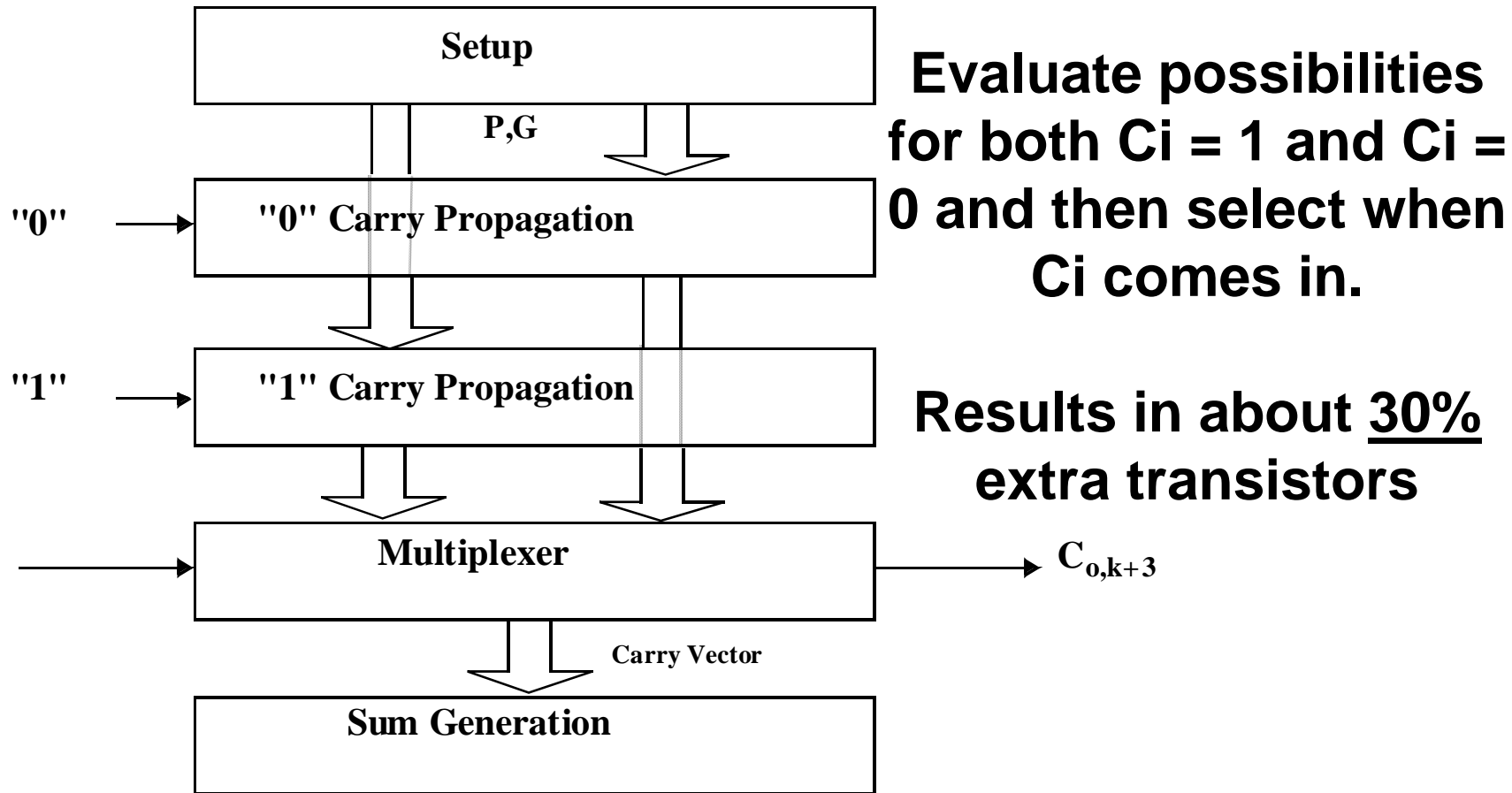

Carry Select Adder: Critical Path

 

Linear Carry Select

 


$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$

Carry-Select Adder Observations


- The inputs to the final multiplexer are steady long before the Mux select (C_i) arrives
 - » Path is the same as is the number of bits
- Would be helpful to try and even out the delays so that the critical path is balanced between inputs and Mux select.
 - » Make logic simpler with the least significant bits by reducing the number of bits handled in the FA or half adder (HA). HA is FA without C_i (2 ins, 2 outs)
 - » Add bits progressively as you move to the MSB

Square Root Carry Select

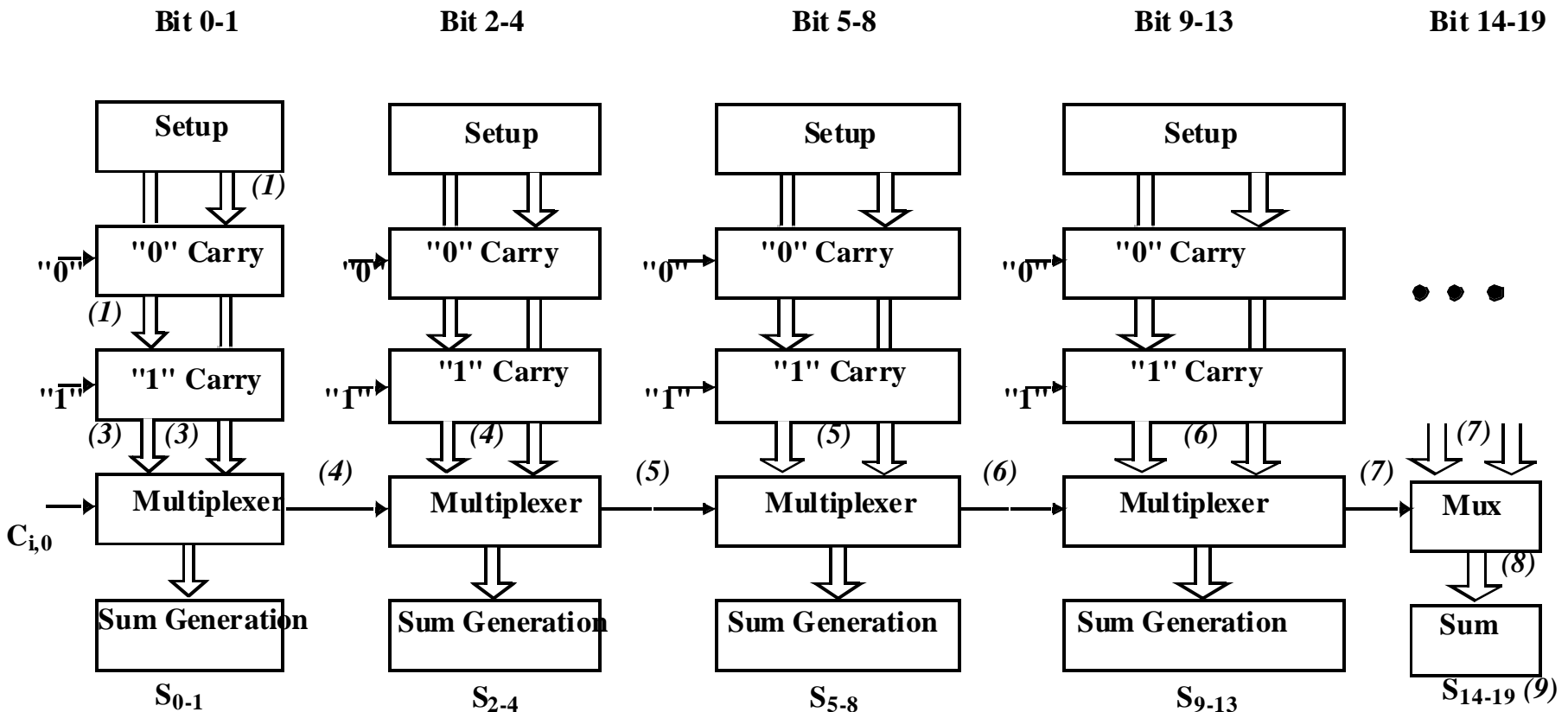


$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$


Adder Delays: Comparison

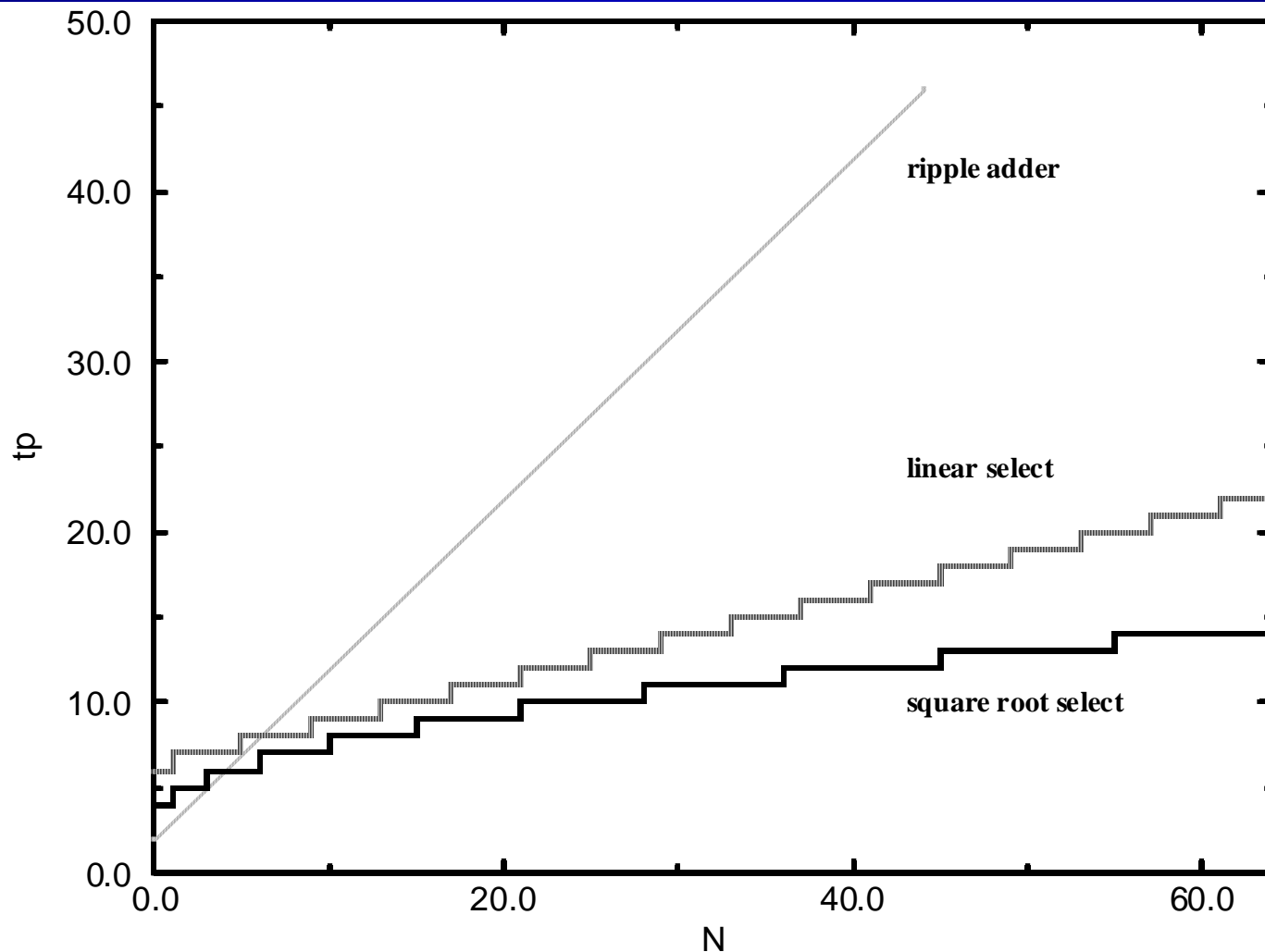

Carry Look Ahead: Basic Idea

 

Look-Ahead: Topology

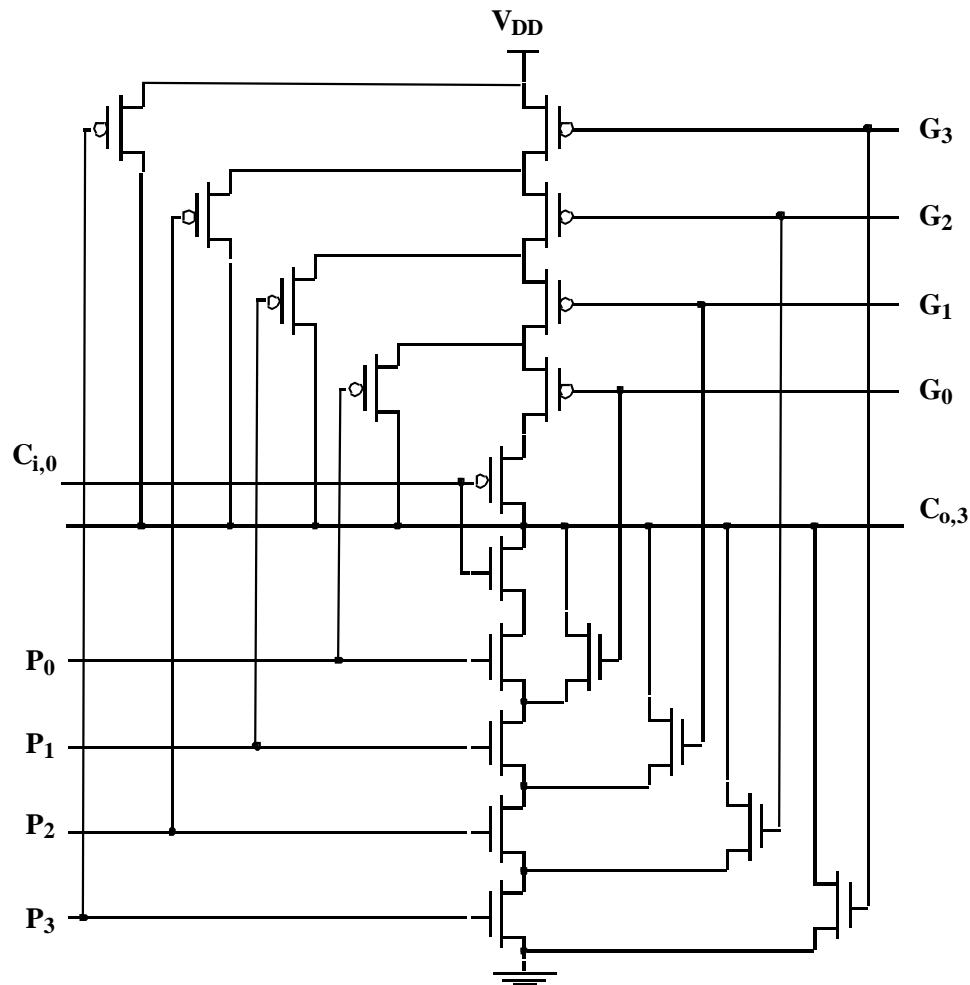

- **No more than $N = 4$ bits**
- **Delay still increases linearly with number of bits**
- **Capacitance, resistance too high for $N > 4$**

Binary Multiplication

$$\begin{aligned} Z &= \mathbf{X} \times \mathbf{Y} = \sum_{k=0}^{M+N-1} Z_k 2^k \\ &= \left(\sum_{i=0}^{M-1} X_i 2^i \right) \left(\sum_{j=0}^{N-1} Y_j 2^j \right) \\ &= \sum_{i=0}^{M-1} \left(\sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right) \end{aligned}$$

with

$$\begin{aligned} \mathbf{X} &= \sum_{i=0}^{M-1} X_i 2^i \\ \mathbf{Y} &= \sum_{j=0}^{N-1} Y_j 2^j \end{aligned}$$

Binary Multiplication


$$\begin{array}{r} 101010 \\ \times 1011 \\ \hline 101010 \\ 101010 \\ 000000 \\ 101010 \\ \hline 111001110 \end{array}$$

AND operation


Partial Products

The diagram illustrates the binary multiplication of 101010 and 1011. The first step is the AND operation, which produces four partial products: 101010, 101010, 000000, and 101010. These are then summed to produce the final product, 111001110. The partial products are highlighted with a grey background, and an arrow points from the label 'AND operation' to the first partial product.

The Array Multiplier



 


The MxN Array Multiplier: Critical Path

 


$$t_{mult} \approx [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + t_{and}$$

Adder Cells in Array Multiplier

   

Identical Delays for Carry and Sum


Multiplier Floorplan

 

Array Multiplier Reflections

- Many equal critical paths
 - » Very hard to optimize by transistor sizing
- We could pass the carry bits diagonally down instead of across
 - » Output does not change
 - » Need to add an extra stage to accommodate this

Carry Save Multiplier

 


Vector Merging Adder

$$t_{mult} = (N - 1)t_{carry} + [t_{and} + t_{merge}]$$

The Tree Multiplier

 
- Note that the partial products layout looks as follows:



- Note that we can rearrange and add the partial products differently
- Reduce number of adder circuits and logic depth
- FA compresses $3b$ to $2b$, HA has $2b$ in and $2b$ out


Tree Multiplier

- Re arranging

 


Tree Multiplier

- Re arranging

 


Tree Multiplier

- Re arranging

 


Tree Multiplier

- Re arranging

 


Tree Multiplier

- Re arranging

 

Wallace-Tree Multiplier

 

Multipliers: Summary

- Optimization goals different than Adder
 - » Identify critical path
 - » More system level optimization than individual cell optimization

Tree Multiplier

- Re arranging

