

(1.1)

$$\frac{W_n}{W_p} = ?$$

$$V_{th} = V_{in} = V_{out} = 2.2$$

$$\tau_{rise} = 5 \text{ ns}$$

$$V_{out} = V_{10\%} = 0.5 \text{ V}$$

$$V_{90\%} = 4.5 \text{ V}$$

$$I_{avg} = \frac{1}{2} \left[I(V_{in} = V_{th}, V_{out} = 0.5 \text{ V}) + I(V_{in} = V_{th}, V_{out} = 4.5 \text{ V}) \right]$$

$$|V_{ds}| \geq |V_{ds} - V_{th}|$$

$$4.5 > 5 - 1$$

sat for PMOS

$$|V_{ds}| \geq |V_{ds} - V_{th}|$$

$$0.5 > 5 - 1$$

linear region

$$I_{avg} = \frac{1}{2} \left[\frac{1}{2} k_p (V_{in} - V_{T,p})^2 + \frac{1}{2} k_p [2(V_{in} - V_{T,p})V_{out} - V_{out}^2] \right]$$

$$= \frac{1}{4} k_p [16 + 2(-5+1)(-0.5) - (-0.5)^2] = \frac{W_p}{L_p} \times 98.75 \mu\text{A}$$

$$\tau_{rise} = \frac{C \cdot \Delta V}{I_{avg}} \Rightarrow 5 \times 10^{-9} = \frac{2 \times 10^{-12} \times 4}{\frac{W_p}{L_p} \times 98.75 \times 10^6} \Rightarrow \frac{W_p}{L_p} \approx 16.2 \quad \underline{\underline{W_p \approx 16.2 \mu\text{m}}}$$

$$V_{th} = \frac{V_{T,n} + \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T,p})}{(1 + \sqrt{\frac{1}{k_R}})} \Rightarrow 2.2 = \frac{0.8 + \sqrt{\frac{1}{k_R}} (5 - 1)}{(1 + \sqrt{\frac{1}{k_R}})} \Rightarrow k_R = 1.65$$

$$\frac{W_n}{W_p} = 0.66 \Rightarrow W_n = 0.66 \times 16 \approx \underline{\underline{10.58 \mu\text{m}}}$$

(1.2)

$$\tau_p = ?$$

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{DD} - V_{T,n})} \left[\frac{2V_{T,n}}{V_{DD} - V_{T,n}} + \ln \left(\frac{4(V_{DD} - V_{T,n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH} = \frac{C_{load}}{k_p(V_{DD} - |V_{T,p}|)} \left[\frac{2|V_{T,p}|}{V_{DD} - |V_{T,p}|} + \ln \left(\frac{4(V_{DD} - |V_{T,p}|)}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PHL} = \frac{2 \times 10^{-12}}{50 \times 10^6 \times 10.58 \times 4.2} \left[\frac{1.6}{4.2} + \ln \left(\frac{4(5 - 0.8)}{5} - 1 \right) \right] = 1.115 \text{ ns}$$

$$\frac{2 \times 10^{-12}}{20 \times 10^6 \times 16.2 \times 4} \left[\frac{2}{4} + \ln \left(\frac{4 \times 4}{5} - 1 \right) \right] = \underline{\underline{1.988 \text{ ns}}}$$

$$\tau_p = \frac{\tau_{PHL} + \tau_{PLH}}{2} = \frac{1.115 + 1.988}{2} = \underline{\underline{1.551 \text{ ns}}}$$

(1.3)

If V_{DD} goes from 5V to 3.3V, then

τ_p will increase.

V_{th} will decrease.

$$V_{th} = 1.417V \text{ (Old one was 2.2V)}$$

$$\tau_{PLH} = 3.893ns$$

$$\tau_{PHL} = 2.038ns$$

$$\tau_p = \underline{2.965ns} \text{ } (\tau_{p,old} \text{ was } 1.551ns)$$

(2.1)

$$\tau_{PHL} < 0.825ns$$

$$C_{out} = 500fF + C_{db,n} + C_{db,p}$$

$$C_{db,n} = (100 + 9W_n)fF$$

$$C_{db,p} = (80 + 7W_p)fF$$

$$0.825 \times 10^{-9} = \frac{C_{out}}{W_n \times 50 \times 10^6 \times 4.2} \times 1.239 \Rightarrow \frac{C_{out}}{W_n} = 1.398 \times 10^{-13}$$

$$(680 + 9W_n + 7W_p) \times 10^{-15} = W_n \times 1.398 \times 10^{-13} \Rightarrow \boxed{680 + 9W_n + 7W_p = 139.8W_n}$$

$$2.4 = \frac{0.8 + \sqrt{1/k_R}(5-1)}{(1 + \sqrt{1/k_R})} \Rightarrow k_R = 1 \Rightarrow \frac{W_n}{W_p} = \frac{2}{5} \quad \boxed{W_p = \frac{5}{2}W_n}$$

$$680 + 9W_n + \frac{35}{2}W_n = 139.8W_n \Rightarrow \boxed{W_n = 6\mu m} \quad \boxed{W_p = 15\mu m}$$

(2.2)

$$\tau_{rise} = \frac{C \cdot \Delta V}{I_{avg1}} = \frac{250 \times 10^{-15} \times 4}{I_{avg1}}$$

$$\tau_{fall} = \frac{C \cdot \Delta V}{I_{avg2}} = \frac{250 \times 10^{-15} \times 4}{I_{avg2}}$$

$$I_{avg1} = \frac{1}{2} \left[\frac{1}{2} k_p (V_{in} - V_{Tp})^2 + \frac{1}{2} k_p [2(V_{in} - V_{Tp})V_{DSp} - V_{DSp}^2] \right] = \underline{1.481mA}$$

$$\tau_{rise} = \frac{250 \times 10^{-15} \times 4}{1.481 \times 10^{-3}} = \underline{0.675ns}$$

$$I_{avg2} = \frac{1}{2} \left[\frac{1}{2} k_n (V_{in} - V_{Tn})^2 + \frac{1}{2} k_n [2(V_{in} - V_{Tn})V_{out} - V_{out}^2] \right] = \underline{1.619mA}$$

$$\tau_{fall} = \underline{0.617ns}$$

3.10

a)

i) use exact method (diff. equations) for rise & fall time

τ_{fall}

$$C \frac{dV_{out}}{dt} = -\frac{1}{2} k_n (V_{in} - V_{Tn})^2$$

nMOS in sat. for $4V \leq V_{out} \leq 4.5V$

$$\frac{dV_{out}}{dt} = -2.4 \times 10^9 \text{ v/s}$$

$$\int_{t=0}^{t=t_{sat}} dt = -\frac{1}{2.4 \times 10^9} \int_{V_{out}=4.5}^4 dV_{out}$$

$$t_{sat} = \frac{0.5}{2.4 \times 10^9} = \underline{\underline{0.2083 \text{ ns}}}$$

nMOS in linear reg. for $0.5V \leq V_{out} \leq 4V$

$$C \frac{dV_{out}}{dt} = -\frac{1}{2} k_n [2(V_{in} - V_{Tn})V_{out} - V_{out}^2]$$

$$\int_{t=t_{sat}}^{t=t_{delay}} dt = -6.6 \times 10^{-9} \int_4^{0.5} \frac{dV_{out}}{8V_{out} - V_{out}^2}$$

$$t_{delay} - t_{sat} = \underline{\underline{2.23 \text{ ns}}}$$

$$t_{fall} = 2.23 + 0.2083 = \underline{\underline{2.4383 \text{ ns}}}$$

τ_{rise}

$$C \frac{dV_{out}}{dt} = \frac{1}{2} k_p (V_{in} - V_{DD} - V_{Tp})^2$$

pMOS in sat for $0.5V \leq V_{out} \leq 1.2V$

$$\frac{dV_{out}}{dt} = 2.406 \times 10^9 \text{ v/s}$$

$$\int_{t=0}^{t=t_{sat}} dt = \frac{1}{2.406 \times 10^9} \int_{V_{out}=0.5}^{1.2} dV_{out}$$

$$t_{sat} = \frac{0.7}{2.406 \times 10^9} = \underline{\underline{0.2908 \text{ ns}}}$$

pMOS in linear reg. for $1.2V \leq V_{out} \leq 4.5V$

$$C \frac{dV_{out}}{dt} = \frac{1}{2} k_p [2(V_{in} - V_{DD} - V_{Tp})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2]$$

$$\int_{t=t_{sat}}^{t=t_{delay}} dt = 5.9 \times 10^{-9} \int_{1.2}^{4.5} \frac{dV_{out}}{38 - 7.6V_{out} - (5 - V_{out})^2}$$

$$t_{delay} - t_{sat} = \underline{\underline{2.059 \text{ ns}}}$$

$$t_{rise} = 2.059 + 0.2908 = \underline{\underline{2.3498 \text{ ns}}}$$

ii) use average current method

$$\tau_{fall} = \frac{C \Delta V}{I_{avg}} = \frac{1.5 \times 10^{-12} \times 4}{I_{avg}}$$

$$I_{avg} = \frac{1}{2} \left[k_n (V_{in} - V_{Tn})^2 + \frac{1}{2} [2(V_{in} - V_{Tn})V_{out} - V_{out}^2] \right]$$

$$= 2.22 \text{ mA}$$

$$\tau_{fall} = \underline{\underline{2.7 \text{ ns}}}$$

$$\tau_{rise} = \frac{C \Delta V}{I_{avg}} = \frac{1.5 \times 10^{-12} \times 4}{I_{avg}}$$


$$I_{avg} = \frac{1}{2} \left[\frac{1}{2} k_p (V_{in} - V_{Tp})^2 + \frac{1}{2} k_p [2(V_{in} - V_{Tp})V_{out} - V_{out}^2] \right]$$

$$= 2.248 \text{ mA}$$

$$\tau_{rise} = \underline{\underline{2.668 \text{ ns}}}$$

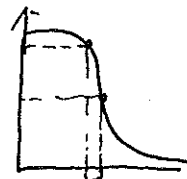3.2
b)

$$f = \frac{1}{2\tau_p} \Rightarrow \tau_p = \tau_{PHL} + \tau_{PLH} \quad \text{Notice:}$$



$$\tau_{PHL} = \frac{1.5 \times 10^{-12}}{45 \times 10^6 \times 10 \times (5-1)} \left[\frac{2}{4} + \ln \left(\frac{4 \times 4}{5} - 1 \right) \right] = 1.07 \text{ ns}$$

$$\tau_{PLH} = \frac{1.5 \times 10^{-12}}{25 \times 10^6 \times 20 \times 3.8} \left[\frac{2.4}{3.8} + \ln \left(\frac{4 \times 3.8}{5} - 1 \right) \right] = 2.11 \text{ ns}$$

$$\tau_p = 3.18 \text{ ns}$$

$$f = \frac{1}{6.36 \times 10^{-9}} \approx \underline{\underline{157 \text{ MHz}}}$$

τ_{PHL} only spans from $V_{DD} - V_{in}$ to $\frac{V_{DD}}{2}$.

But we asked for the time period for full logic swing.

$$\text{Thus } f = \frac{1}{\tau_{rise} + \tau_{fall}} = \frac{1}{2(\tau_{PHL} + \tau_{PLH})}$$

3.3

$$\text{Power} = C_{load} \cdot V_{DD}^2 \cdot f = 1.5 \times 10^{-12} \times 5^2 \times 157 \times 10^6 \approx \underline{\underline{5.91 \text{ mW}}}$$

3.4

$$\tau_{PHL} = \frac{m}{\frac{W_n}{L_n}} \Rightarrow 0.75 \tau_{PHL} = 0.75 \cdot \frac{m}{\frac{W_n}{L_n}} \Rightarrow 0.75 \tau_{PHL} = \frac{m}{\left[\frac{W_n}{L_n} \times \frac{1}{0.75} \right]}$$

$$\text{this means } \left(\frac{W_n}{L_n} \right)_{\text{new}} = \frac{10}{0.75} = \underline{\underline{13.3}}$$

$$\text{same procedure for } \left(\frac{W_p}{L_p} \right) \Rightarrow \left(\frac{W_p}{L_p} \right)_{\text{new}} = \frac{20}{0.75} = \underline{\underline{26.6}}$$

V_{TH} will not change because k_r does not change here.