

EEC 118 HOMEWORK #5

SOLUTIONS

1.1 $F = A \cdot C + B \cdot (D + E)$

1.2 Worst case combinations for V_{OL} : AC, BD, BE

1.3 Assume $V_{OL} \approx 0.05V_{DD} = 0.25V$

For NMOS load:

$$V_{T,n} = V_{T0,n} + \gamma \left(\sqrt{1 - 2\phi_F + V_{SB}} - \sqrt{1 - 2\phi_F} \right) = 1.0V + 0.4V^{1/2} (\sqrt{0.6V + 0.25V} - \sqrt{0.6V})$$

$$= 1.06V \approx 1V$$

$$V_{GS} = 7V - 0.25V > V_{Tn} = 1.06V \quad V_{DS} = 5V - 0.25V < V_{GS} - V_{T,n} \quad \text{linear}$$

$$I_{D,load} = \frac{\mu_n C_{ox}}{2} \left(\frac{5}{5} \right) \left[2(7 - V_{out} - 1)(5 - V_{out}) - (5 - V_{out})^2 \right]$$

$$= \frac{\mu_n C_{ox}}{2} [35 - 12V_{out} + V_{out}^2]$$

For NMOS pulldown, linear since $V_{DS} = 0.25V$ (assumed) and $V_{GS} = 5V$


$$I_{D,pulldown} = \frac{\mu_n C_{ox}}{2} \left(\frac{100}{5} \right) \frac{1}{2} [2(5 - 1)V_{out} - V_{out}^2] = I_{D,load}$$

$$\frac{\mu_n C_{ox}}{2} [35 - 12V_{out} + V_{out}^2] = \frac{\mu_n C_{ox}}{2} [80V_{out} - 10V_{out}^2]$$


$$9V_{out}^2 - 92V_{out} + 35 = 0 \Rightarrow V_{out} = 0.395V = V_{OL}$$

1.4 No, since pullup and pulldown are both NMOS, k_n cancels out when currents are equated.

2.1

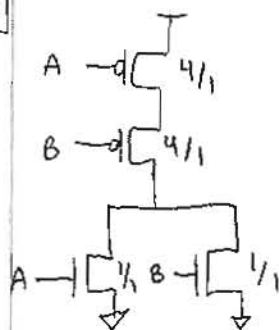

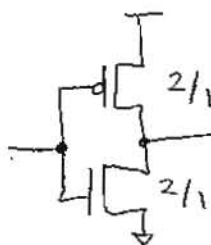Equivalent Inverter (all inputs switching)



$$K_p = \left(\frac{W}{L}\right)_p \mu_p C_{ox} = 2 \cdot 20 = 40 \mu A/V^2$$

$$K_n = \left(\frac{W}{L}\right)_n \mu_n C_{ox} = 2 \cdot 40 = 80 \mu A/V^2$$

$$K_R = \frac{K_n}{K_p} = \frac{80}{40} = 2$$

$$V_{OH} = V_{DD} = 5V$$

$$V_{OL} = 0V$$

$$V_{IL} = \frac{2V_{out} - V_{To,p} - V_{DD} + K_R V_{To,n}}{1 + K_R} \Rightarrow V_{IL} = \frac{2V_{out} + 0.7 - 5 + 1.4}{3}$$

$$\Rightarrow V_{out} = 1.5V_{IL} + 0.97 \quad (A)$$

$$\frac{K_n}{2} (V_{IL} - V_{To,n})^2 = \frac{K_p}{2} [2(V_{IL} - V_{DD} - V_{To,p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2]$$

$$40 (V_{IL} - 0.7)^2 = 20 [2(V_{IL} - 5 + 0.7)(V_{out} - 5) - (V_{out} - 5)^2]$$

$$\text{Plug in (A) for } V_{out} \Rightarrow 1.25 V_{IL}^2 + 6.07 V_{IL} - 17.43 = 0$$

$$V_{IL} = 2.02V$$

$$V_{IH} = \frac{V_{DD} + V_{To,p} + K_R (2V_{out} + V_{To,n})}{1 + K_R}$$

$$\frac{K_n}{2} [2(V_{IH} - V_{To,n})(V_{out}) - V_{out}^2] = \frac{K_p}{2} (V_{IH} - V_{DD} - V_{To,p})^2$$

$$V_{IH} = \frac{5 - 0.7 + 2(2V_{out} + 0.7)}{3} \Rightarrow 3V_{IH} = 5.7 + 4V_{out} \Rightarrow V_{out} = 0.75V_{IH} - 1.425 \quad (B)$$

$$40 [2(V_{IH} - 0.7)V_{out} - V_{out}^2] = 20 (V_{IH} - 5 + 0.7)^2$$

$$\text{Plug in (B) for } V_{out} \Rightarrow 0.88 V_{IH}^2 + 5.08 V_{IH} - 18.56 = 0$$


$$V_{IH} = 2.53V$$

2.1 (cont.)


$$NM_L = V_{IL} - V_{OL} = 2.02V$$

$$NM_H = V_{OH} - V_{IH} = 2.47V$$

3.1

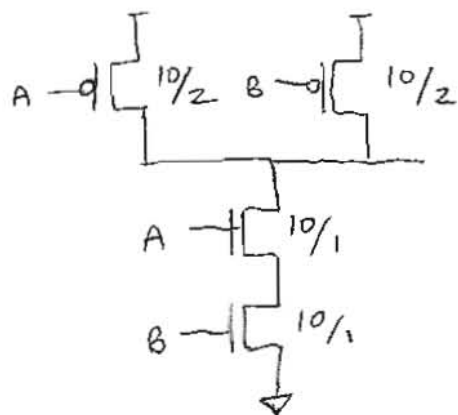

Equivalent inverter (worst case delays)

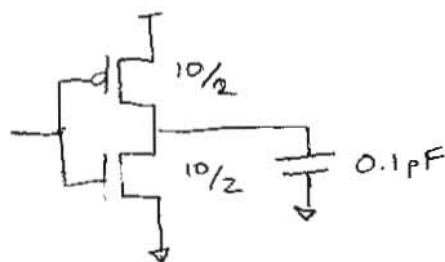

$$K_n = K'_n \left(\frac{W}{L} \right)_n = 20 \mu A/V^2 \left(\frac{10}{2} \right) = 100 \mu A/V^2$$

$$K_p = K'_p \left(\frac{W}{L} \right)_p = 10 \mu A/V^2 \left(\frac{10}{2} \right) = 50 \mu A/V^2$$

Can use several methods. Here, use formulas from lecture:

$$t_{pHL} = \frac{C_{load}}{K_n (V_{DD} - V_{T,n})} \left[\frac{2V_{T,n}}{V_{DD} - V_{T,n}} + \ln \left(\frac{4(V_{DD} - V_{T,n})}{V_{DD}} - 1 \right) \right]$$


$$t_{pLH} = \frac{C_{load}}{K_p (V_{DD} - |V_{T,p}|)} \left[\frac{2|V_{T,p}|}{V_{DD} - |V_{T,p}|} + \ln \left(\frac{4(V_{DD} - |V_{T,p}|)}{V_{DD}} - 1 \right) \right]$$

$$t_{pHL} = \frac{0.1 \times 10^{-12}}{100 \times 10^{-6} (4)} \left[\underbrace{\frac{2}{4} + \ln \left(\frac{4 \cdot 4}{5} - 1 \right)}_{2.7} \right] = \boxed{0.675 \text{ ns}}$$

$$t_{pLH} = 2t_{pHL} = \boxed{1.35 \text{ ns}}$$

4.1

$$F = A(B + C)$$

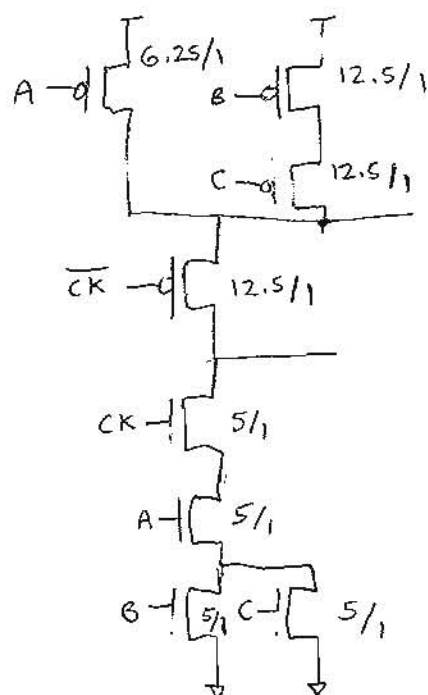

For $t_{\text{fall}} = t_{\text{rise}}$, $\mu_n W_n = \mu_p W_p$

$$\Rightarrow W_p = \frac{\mu_n}{\mu_p} W_n = 2.5 W_n$$

Other solutions possible...