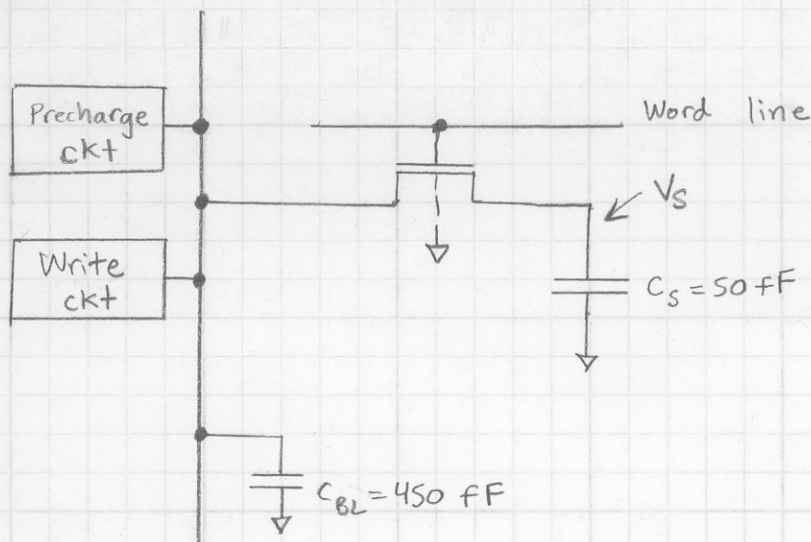


Problem 1



a.) Bitline $BL = V_{DD} = 5V$, Wordline $= V_{DD} = 5V$

Final voltage $V_S = V_{DD} - V_{T,n}$, but $V_{SB} = V_S \Rightarrow$

$$V_S = V_{DD} - V_{T_0} - \gamma(\sqrt{|2\phi_F| + V_S} - \sqrt{|2\phi_F|})$$

$$= 5 - 1.0 - 0.3(\sqrt{0.6 + V_S} - \sqrt{0.6})$$

Solve by iteration (or graphically) $V_s = 3.62 \text{ V}$

b.) During a READ-1, $V_s = 3.62 \text{ V}$ and $BL = V_{DD}/2$. Capacitors C_{BL} and C_s short together and share their charge.

$$Q_{BL} = C_{BL} \frac{V_{DD}}{2} = (450 \text{ fF}) (2.5 \text{ V})$$

$$Q_s = C_s V_s = (50 \text{ fF})(3.62 \text{ V})$$

$$V_{BL}(\text{final}) = \frac{Q_{\text{TOT}}}{C_{\text{TOT}}} = \frac{Q_{BL} + Q_S}{C_{BL} + C_S} = \frac{(450 \text{ fF})(2.5 \text{ V}) + (50 \text{ fF})(3.62 \text{ V})}{500 \text{ fF}}$$


$$V_{BL}(\text{final}) = 2.61 \text{ V}$$

Note Using 10.1 in K+L p.420, $V_{BL}(\text{final}) = \frac{V_{DD}}{2} + \Delta V = 2.5V + \frac{50\text{fF}}{500\text{fF}} 2.5V$
 $= 2.75V$ is incorrect!

The book equation assumed $V_S = V_{DD}$!

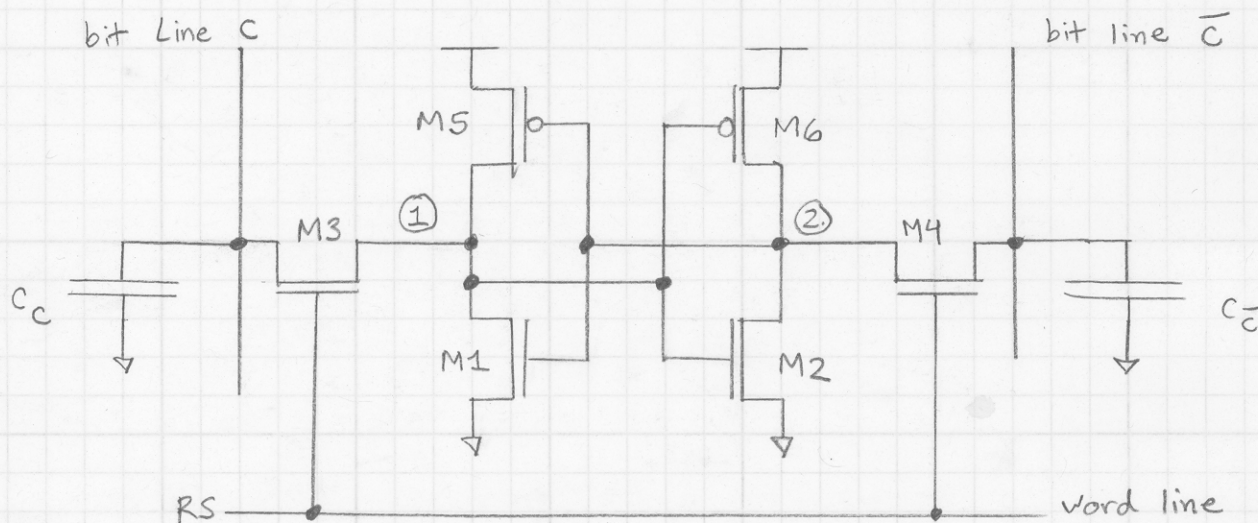Problem 2

To change the state of the cell for $V_c \leq 0.5V$, the voltage at node ① must be V_{DD} (if it were 0V then the cell wouldn't change state).



For M1, M2, $W/L = 4/4$ } must size M5, M6 assuming $(W/L)_5 = (W/L)_6$
 For M3, M4, $W/L = 2/4$

Suppose node ① is initially at V_{DD} . To switch the SRAM state, node ① voltage must go below the M6, M2 inverter switching threshold:

$$\text{Voltage @ node ①} = V_1 \leq V_{TH} = \frac{V_{T0,n} + \sqrt{\frac{1}{K_R}} (V_{DD} - |V_{T0,p}|)}{(1 + \sqrt{\frac{1}{K_R}})}$$

$$K_R = \frac{k_n}{k_p} = \frac{k'_n (W/L)_2}{k'_p (W/L)_6} = \frac{2(4/4)}{(W/L)_6} = 2 \left(\frac{L}{W} \right)_6$$

If node ① initially at V_{DD} , node ② is initially 0V. Assuming $V_{TH} \approx V_{DD}/2$, then M5 and M3 are in linear region and M1 is cut off.

$$I_{DS,M3} = I_{DS,M5} \Rightarrow$$

$$\frac{k'_n (W/L)_3}{2} [2(V_{DD} - V_{T,n3})(V_1 - V_c) - (V_1 - V_c)^2] = \frac{k'_p (W/L)_5}{2} [2(-V_{DD} - V_{T,p3})(V_1 - V_{DD}) - (V_1 - V_{DD})^2]$$

$$\left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_5 \approx \boxed{0.5} \quad V_{TH} = 1.9 \text{ V}, \text{ therefore linear assumption was good.}$$