

# Quiz #4


# EEEC118

# Spring 2010

Name: Solutions

Lab Section: \_\_\_\_\_

**Problem 1 (7 points)** Complete the following Domino-style dynamic logic three-input AND gate. Size the transistors such that the worst case precharge time (rise time for min. size inverter) equals the worst case evaluation time assuming  $V_{DD}=3.3V$ ,  $V_{TN}=|V_{TP}|=1V$ ,  $\mu_N=3\mu_P=300\mu A/V^2$ ,  $\gamma=0$ ,  $\lambda=0$ ,  $W_{min}=1\mu m$ ,  $L_{min}=1\mu m$ . Label the inputs A, B, C, clk, the dynamic node Xb, and the output X.

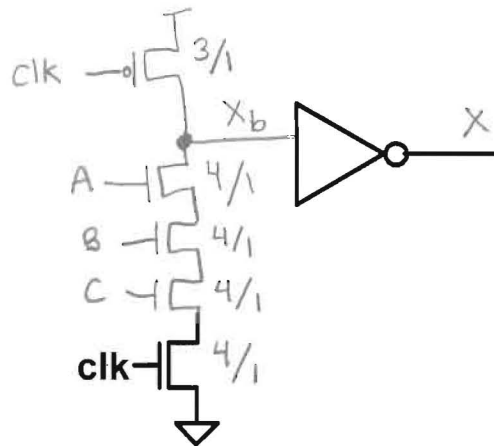

5pts. ckt + labels

2pts. Sizes

**Problem 2 (3 points)** For the following 1 transistor DRAM cell, fill in the boxes labeling the corresponding wires with the appropriate signal names:

Q: data storage bit

BL: bit line

WL: word line

