

# **EEC 118 Lecture #10: Dynamic Logic**

**Rajeevan Amirtharajah  
University of California, Davis**

**Jeff Parkhurst  
Intel Corporation**

# Announcements

---

- **Complete Lab 4 this week**


# Outline

---

- **Today: Alternative MOS Logic Styles**
- **Dynamic MOS Logic Circuits: Rabaey 6.3 (Kang & Leblebici, 9.4-9.6)**

# Review: Transmission Gate XOR


---

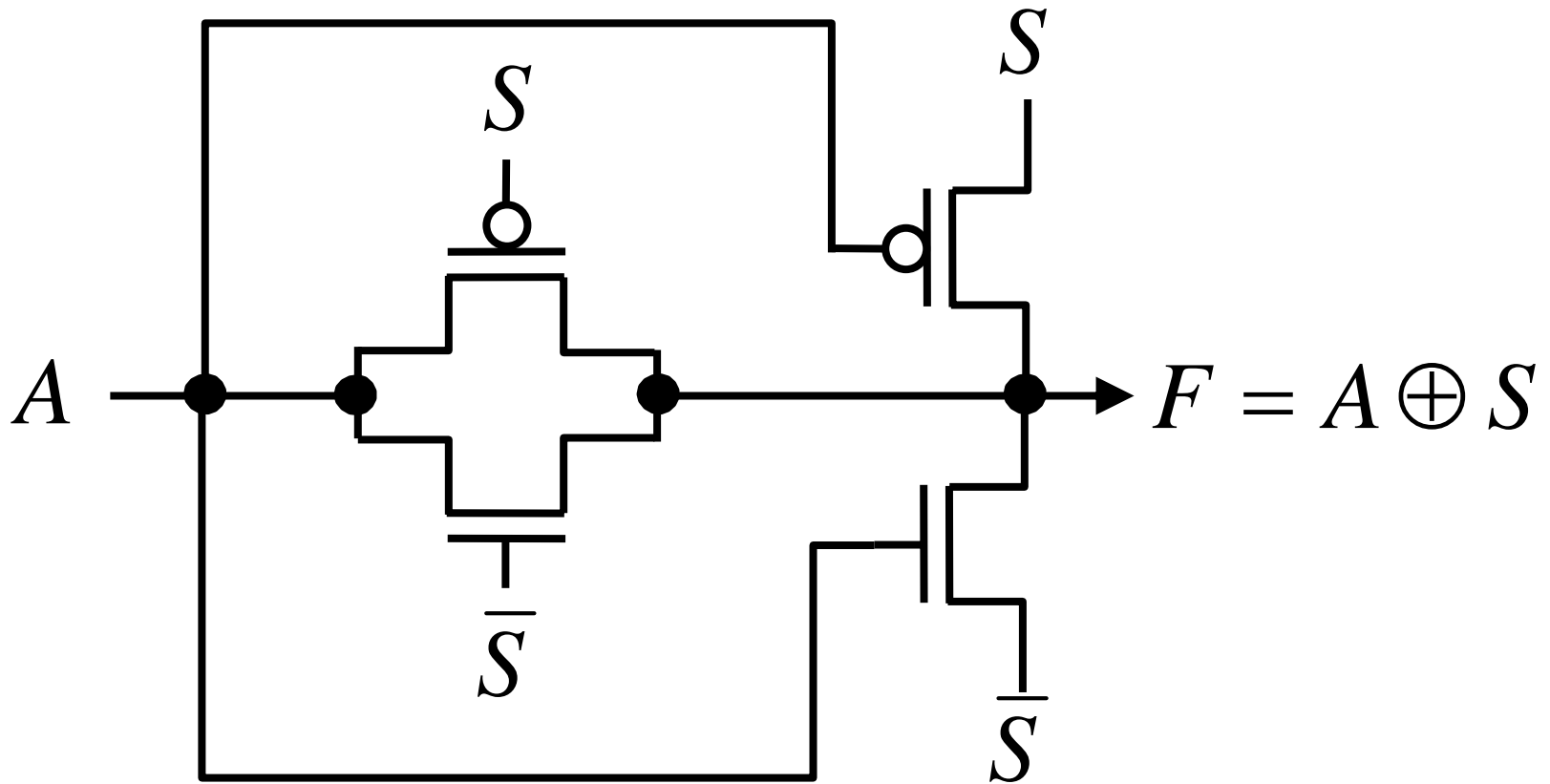

- If  $S = 0$ ,  $F = A$  and when  $S = 1$ ,  $F = \sim A$


# Review: Transmission Gate Multiplexer

---

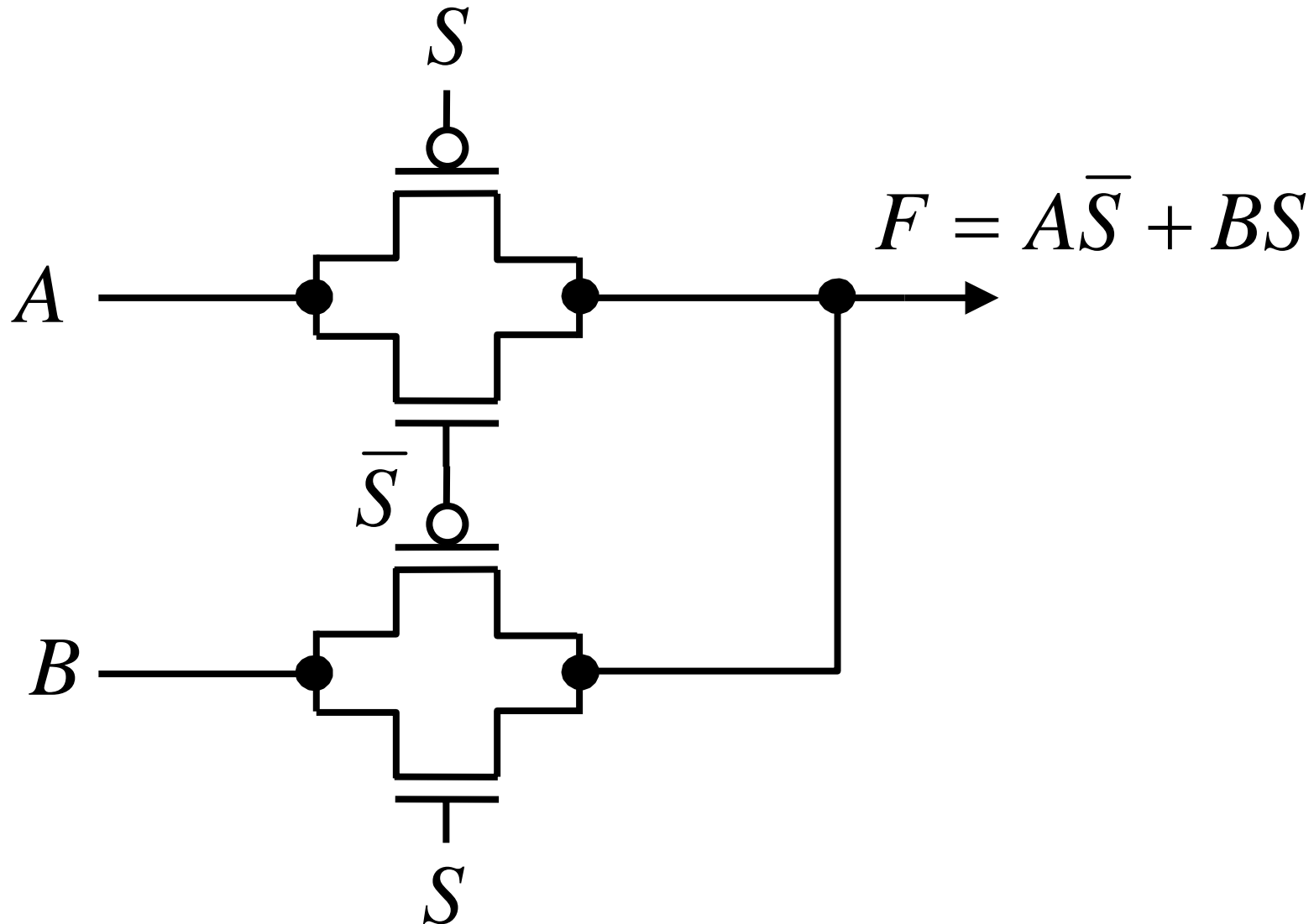
 
# Dynamic CMOS

- **Operation**
  - Clk low during Pre-charge
    - Mp is on while Mn is off
    - Output charged to Vdd
  - Clk high during evaluate
    - Mn is on while Mp is off
    - Output pulled down according to PDN function
- **PDN design same as static CMOS**




# Dynamic CMOS Tradeoffs

---

- **Advantages:**

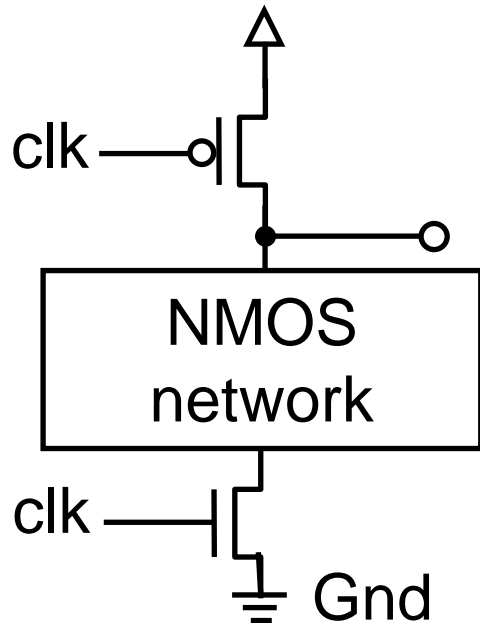
- Faster – why?
  - Reduced input load
  - No switching contention
- Less layout area



- **Disadvantages:**

- Multiple stage issues
- Charge leakage
- Charge sharing
- Capacitive coupling
- Cannot be cascaded
- Complicated timing/clocking
- Higher power
- Lower noise margins
- Does not scale well with process
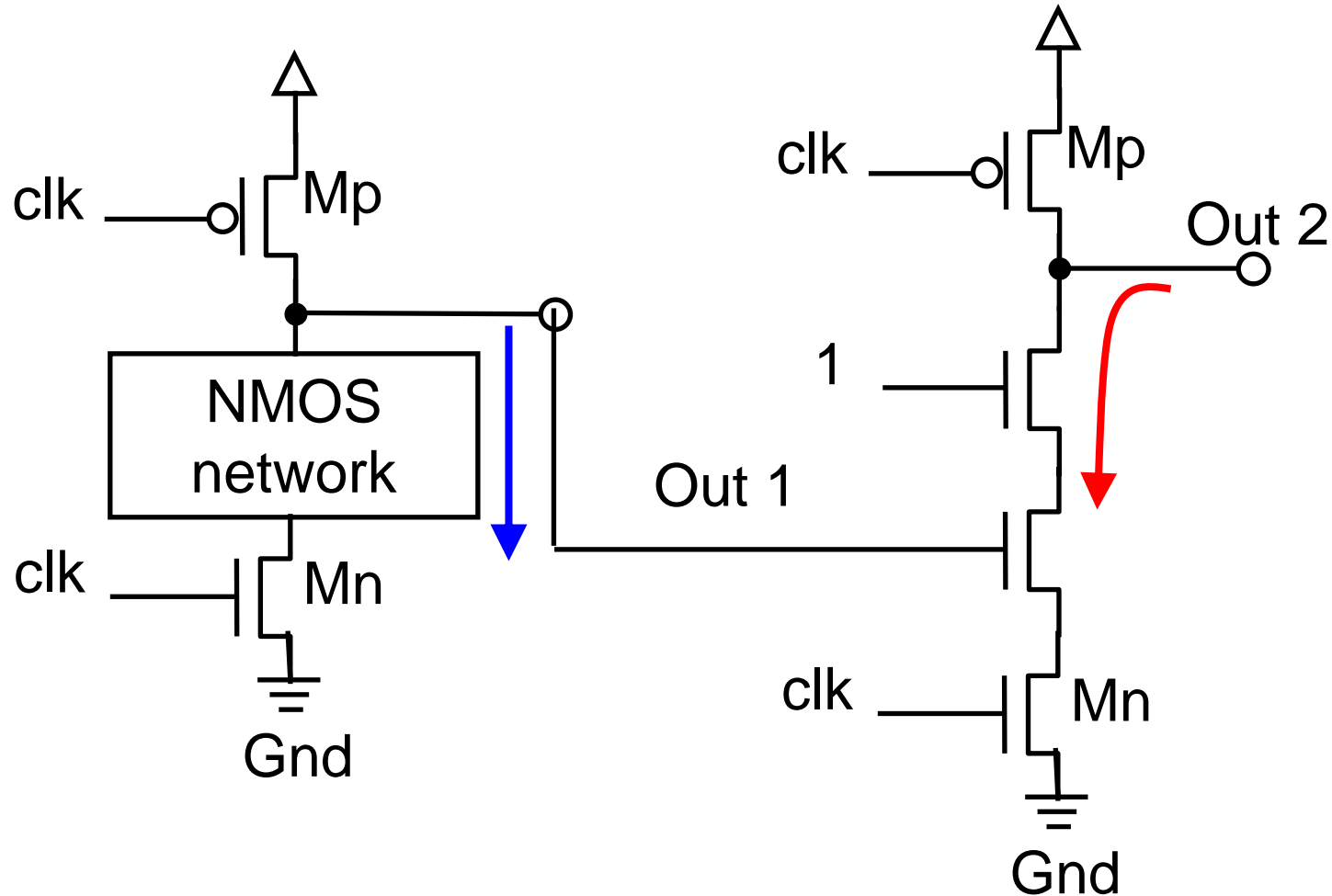
# Multiple Stage Issue: Output Discharge Race



- **During pre-charge stage, inputs to second gate are all high: Out 2 could discharge before Out 1 discharges**



# Cascading Multiple Stages

---


- **During pre-charge stage, inputs to second gate are all high**
  - At the beginning of evaluate stage, Out 2 is discharged.
  - Out 1 goes through its evaluation stage concurrently and goes low
    - Hence out 2 was supposed to be high, but already discharged.
    - Dynamic logic driven by the same clock cannot *be cascaded directly*

# Charge Sharing

---

- Output is floating after  $\text{clk} = '1'$  if inputs are  $'0'$
- If upper transistors in a stack switch, the intermediate and output node voltages will be equalized, possibly leading to a drop in the output voltage = noise
- Final output (initial charge distributed over both capacitors):
 
$$V = (C_1 V_1 + C_2 V_2) / (C_1 + C_2)$$



# Charge Leakage & Capacitive Coupling

---

- **Output is floating after  $\text{clk} = '1'$  if inputs are  $'0'$**
- **Since the current is not 0 when transistors are in cutoff, current can leak charge away from the output when all inputs are  $'0'$**
- **Changes in input signals couple to the output and intermediate nodes, also resulting in voltage drops**


# Noise Solutions

---

- **Charge sharing:**
  - Ensure the output capacitance is large enough such that the voltage drop is minimal
  - Precharge internal stack nodes to  $V_{DD}$
  - Pre-discharging internal stack nodes can increase performance, but worsens noise
- **Charge leakage/sharing and capacitive coupling:**
  - Add a keeper PMOS (weak P pullup) – increased evaluation contention

# Domino Logic

---

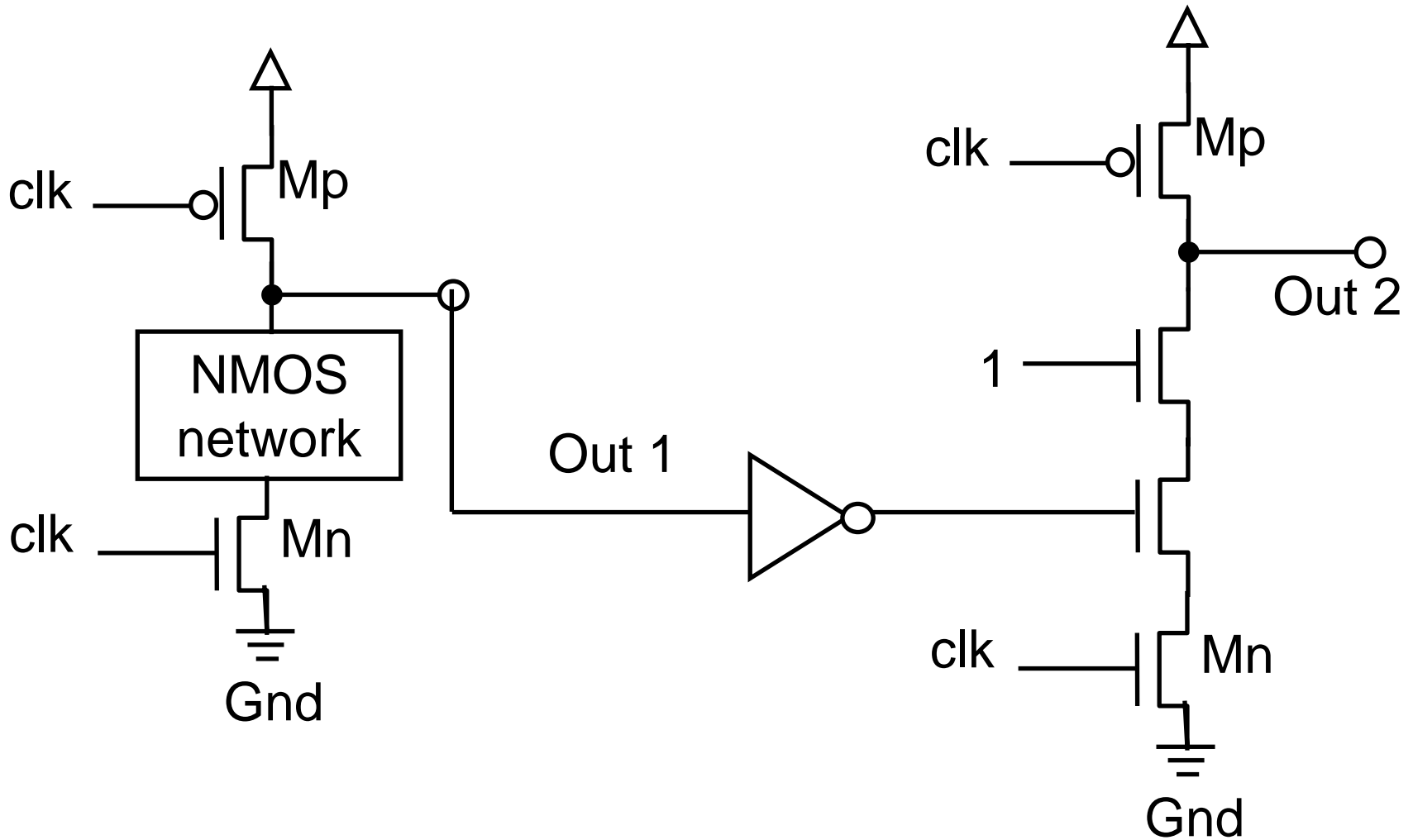

# Domino Logic

---

- **Add an inverter between dynamic gates**
  - Inverter drives the gate's fanout – increased performance
- **Sometimes the inverter is replaced with a more complex static CMOS gate**
  - Incorporates more logic per stage to improve speed
- **Static CMOS gate improves overall circuit dynamic noise margins**

# Cascading Domino

---

- **For gates with all inputs coming from other domino gates, the bottom NMOS transistor can be eliminated**
  - Why? All inputs will be '0' during precharge and can only transition from '0' to '1' during evaluate due to inverter between stages...
  - Results in increased performance due to decreased stack height
  - Precharge now depends on input precharge time

# Dynamic Logic Power

---

- **Power depends upon switching activity**

- Switching activity depends upon the probability of a ‘1’ input

$$P_{avg} = \frac{1}{T} C_{load} V_{DD}^2 = C_{load} V_{DD}^2 f$$

- Effective capacitance  $C_{load}$  is doubled when the gate evaluates because the gate must later precharge
- Frequency must be multiplied by the probability that an evaluation will occur

- **Power is usually higher for domino logic except when it replaces prior logic with very high activity factors**




# Bottom Line

---

- **Tradeoff between performance and power exists**
- **Many things can go wrong from a design standpoint (high risk)**
  - Charge sharing, noise, leakage currents, race conditions
- **Debugging challenge, especially in deep submicron**
  - Leakage currents put lower bound on clock frequency for testing
- **Best to use dynamic logic only when necessary**
  - High performance circuits such as microprocessor critical paths

# NORA Logic Gate

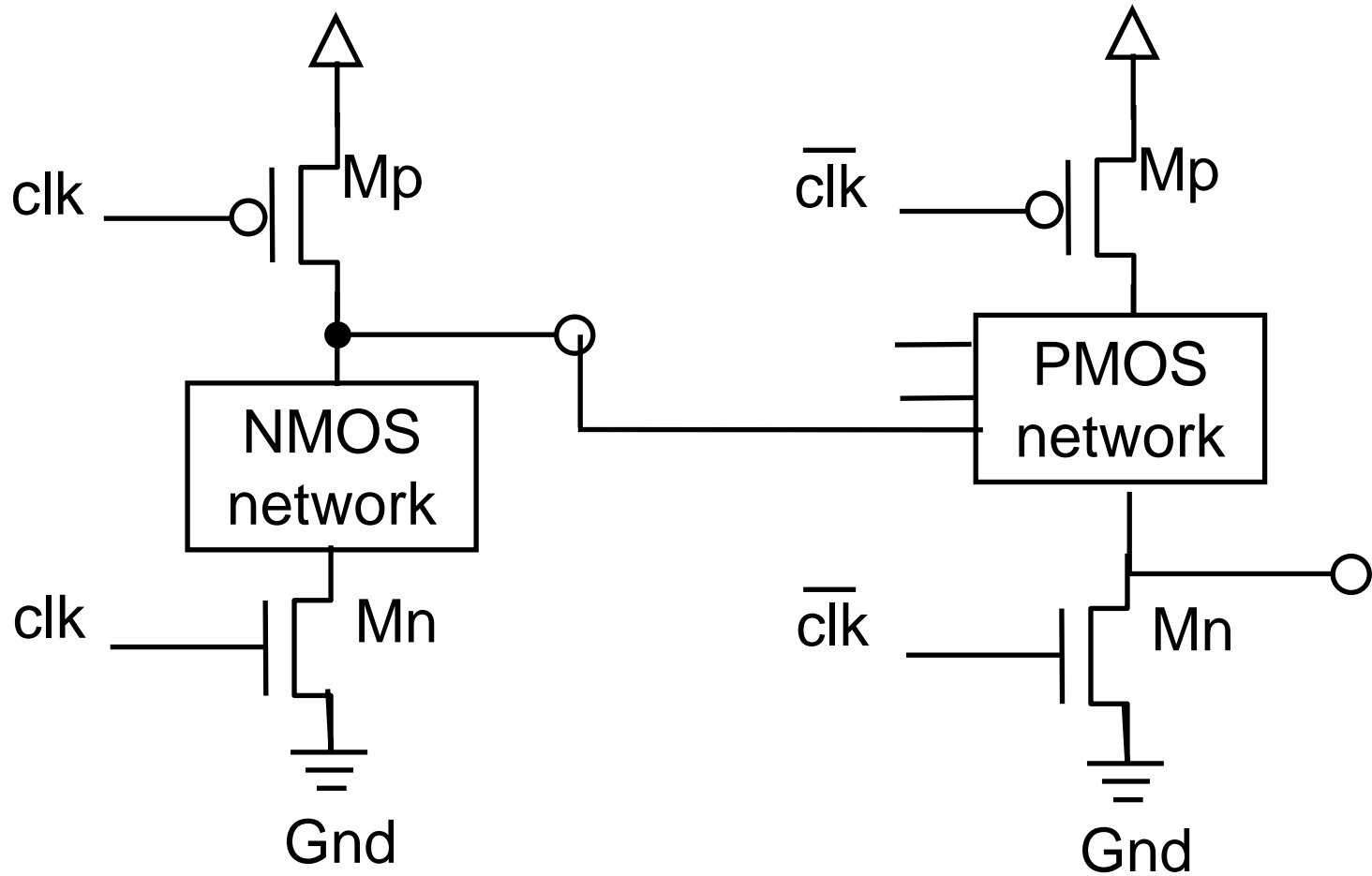

# NORA Logic

---

- **Solves problem of cascading dynamic gates, but is vulnerable to noise**
  - Alternate P-dynamic and N-dynamic stages
  - Both clk and  $\overline{\text{clk}}$  required
  - Lose some of the speed benefits due to added PUNs

# Zipper Logic

- **Like NORA logic...but,**
  - PMOS precharge and NMOS pre-discharge weakly on during evaluation stage...

# Variations on the Domino Theme

---


- **Multiple-Output Domino**

- Exploit situation when certain outputs are subsets of other outputs to reduce area
- Precharge intermediate nodes in PDN and follow with inverters to drive other N-block dynamic gates

- **Compound Domino**


- Use complex static CMOS gates (NANDs, NORs) on outputs of multiple dynamic gates in parallel
- Replaces large fanin domino gates with lower fanin gates
- Capacitive coupling from static gate outputs to dynamic gate outputs an issue

# Multiple Output Domino CMOS Logic

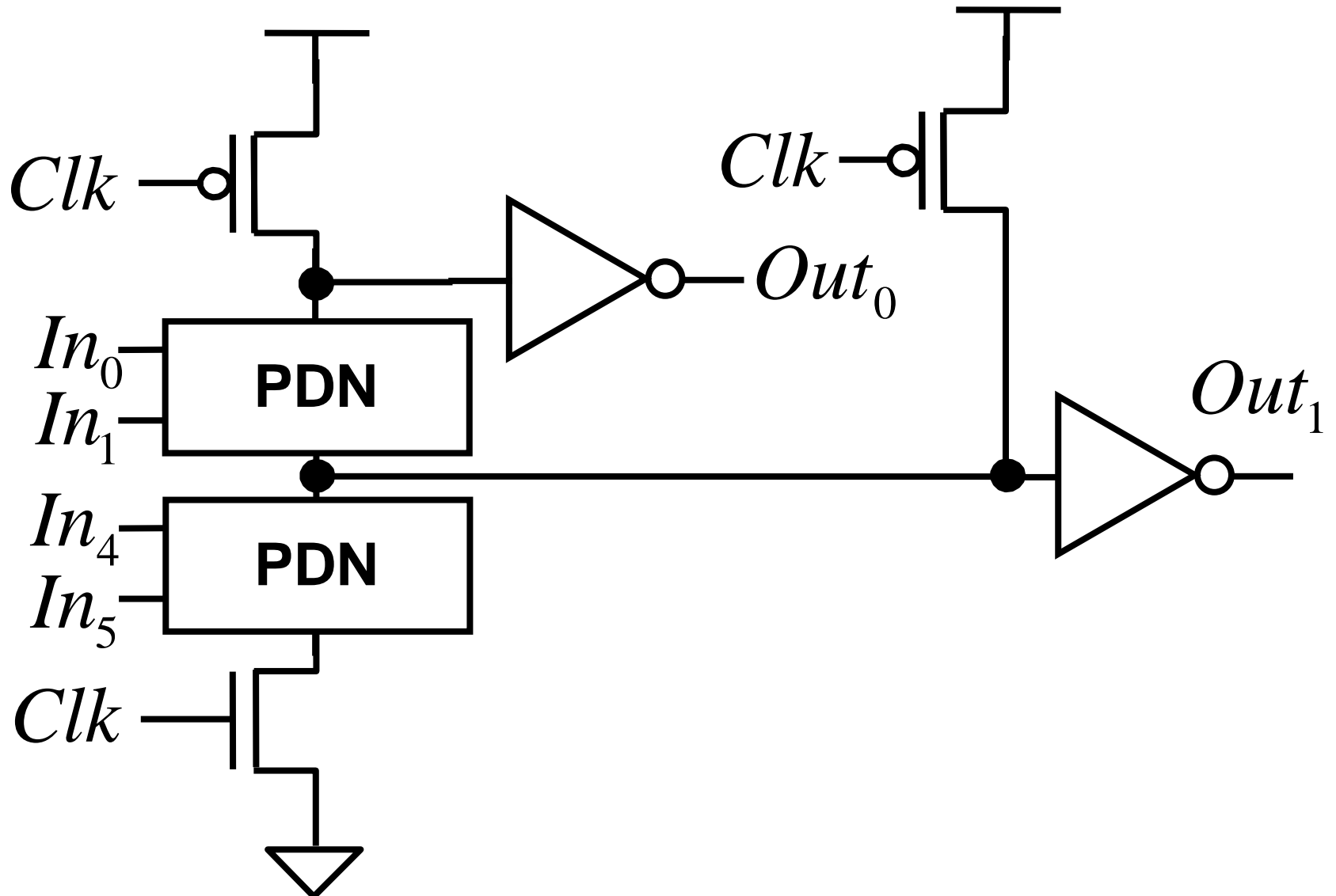

# Compound Domino CMOS Logic

---

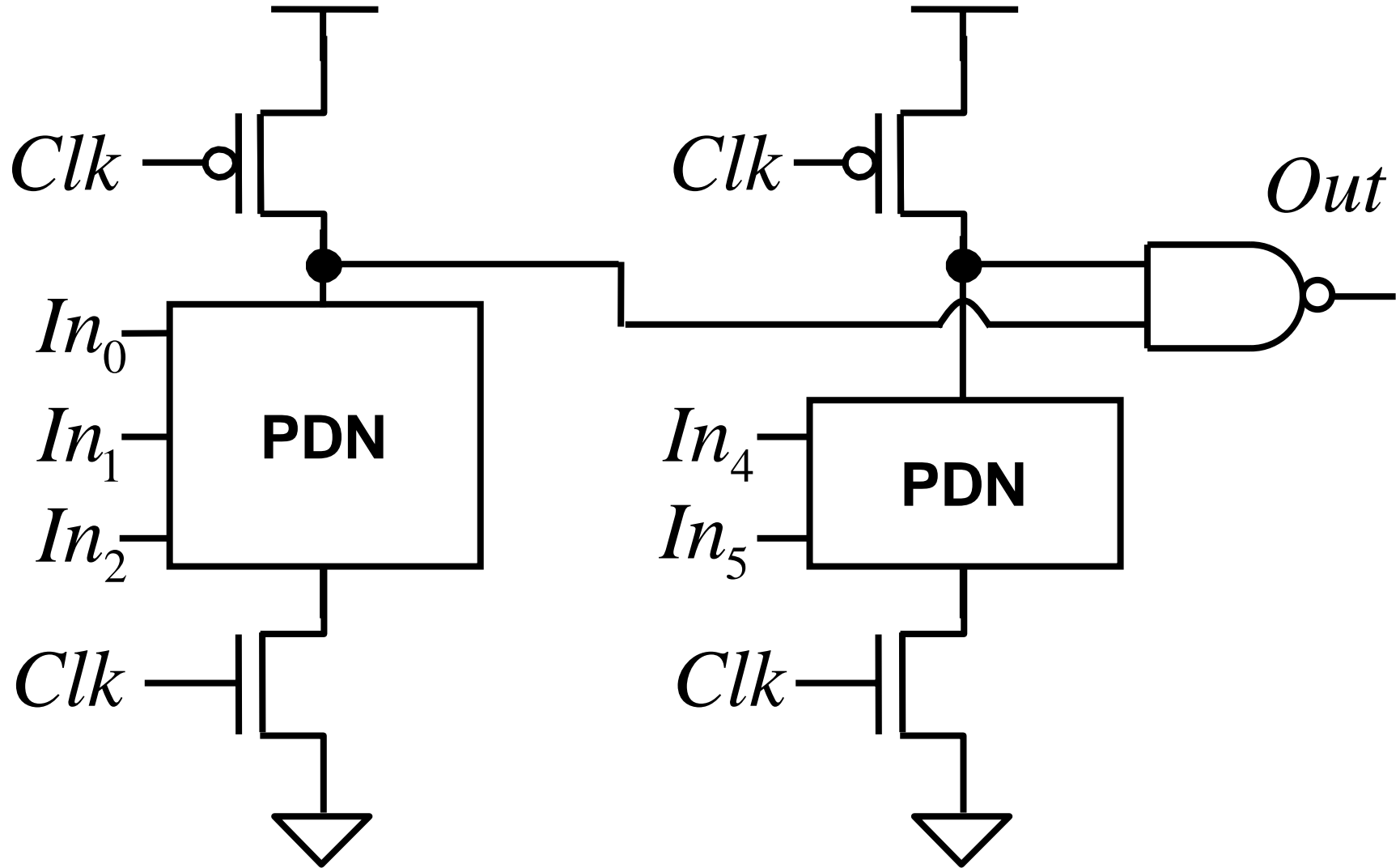

# Next Topic: Arithmetic

---

- **Computing arithmetic functions with CMOS logic**
  - Half adder and full adder circuits
  - Circuit architectures for addition
  - Array multipliers