

EEC 118 Lecture #15: Interconnect

**Rajeevan Amirtharajah
University of California, Davis**

Outline

- **Review and Finish: Low Power Design**
- **Interconnect Effects: Rabaey Ch. 4 and Ch. 9
(Kang & Leblebici, 6.5-6.6)**

Interconnect Modeling

- **Early days of CMOS, wires could be treated as ideal for most digital applications, not so anymore!**
- **On-chip wires have resistance, capacitance, and inductance**
 - Similar to MOSFET charging, energy depends solely on capacitance
 - Resistance might impact low power adiabatic charging, static current dissipation, speed
 - Ignore inductance for all but highest speed designs
- **Interconnect modeling is whole field of research itself!**

Interconnect Models: Regions of Applicability

- **For highest speed applications, wire must be treated as a transmission line**
 - Includes distributed series resistance, inductance, capacitance, and shunt conductance (*RLGC*)
- **Many applications it is sufficient to use lumped capacitance (*C*) or distributed series resistance-capacitance model (*RC*)**
- **Valid model depends on ratio of rise/fall times to time-of-flight along wire**
 - l : wire length
 - v : propagation velocity (speed of light)
 - l/v : time-of-flight on wire

Interconnect Models: Regions of Applicability

- **Transmission line modeling (inductance significant):**

$$t_{\text{rise}} (t_{\text{fall}}) < 2.5 \times (l / v)$$

- **Either transmission line or lumped modeling:**


$$2.5 \times (l / v) < t_{\text{rise}} (t_{\text{fall}}) < 5 \times (l / v)$$

- **Lumped modeling:**

$$t_{\text{rise}} (t_{\text{fall}}) > 5 \times (l / v)$$

Resistance

 
- Resistance proportional to length and inversely proportional to cross section
- Depends on material constant resistivity ρ ($\Omega\text{-m}$)



$$R = \frac{\rho L}{A} = \frac{\rho L}{tW} = R_{sq} \frac{L}{W} \quad R_{sq} = \frac{\rho}{t}$$

Parallel-Plate Capacitance

 
- **Width large compared to dielectric thickness, height small compared to width: E field lines orthogonal to substrate**



$$C = \frac{\epsilon_r}{h} WL$$


Fringing Field Capacitance

 - When height comparable to width, must account for fringing field component as well



Total Capacitance Model

 - When height comparable to width, must account for fringing field component as well
- Model as a cylindrical conductor above substrate



Total Capacitance Model

- **Total capacitance per unit length is parallel-plate (area) term plus fringing-field term:**

$$C = C_{pp} + C_{fringe} = \frac{\epsilon_r}{h} \left(W - \frac{t}{2} \right) + \frac{2\pi\epsilon_r}{\log(2h/t + 1)}$$

- **Model is simple and works fairly well (Rabaey, 2nd ed.)**
 - More sophisticated numerical models also available
- **Process models often give both area and fringing (also known as sidewall) capacitance numbers per unit length of wire for each interconnect layer**

Alternative Total Capacitance Models

- For wide lines ($w \geq t/2$) Kang & Leblebici Eq. 6.53:

$$C = \frac{\epsilon_r}{h} \left(W - \frac{t}{2} \right) + \frac{2\pi\epsilon_r}{\ln \left(1 + \frac{2h}{t} + \sqrt{\frac{2h}{t} \left(\frac{2h}{t} + 2 \right)} \right)}$$


- For narrow lines ($w \leq t/2$) Kang & Leblebici Eq. 6.54:

$$C = \frac{\epsilon_r W}{h} + \frac{\pi\epsilon_r \left(1 - 0.0543 \frac{t}{2h} \right)}{\ln \left(1 + \frac{2h}{t} + \sqrt{\frac{2h}{t} \left(\frac{2h}{t} + 2 \right)} \right)} + 1.47\epsilon_r$$

Capacitive Coupling


- Fringing fields can terminate on adjacent conductors as well as substrate
- Mutual capacitance between wires implies crosstalk, affects data dependency of power

dielectric

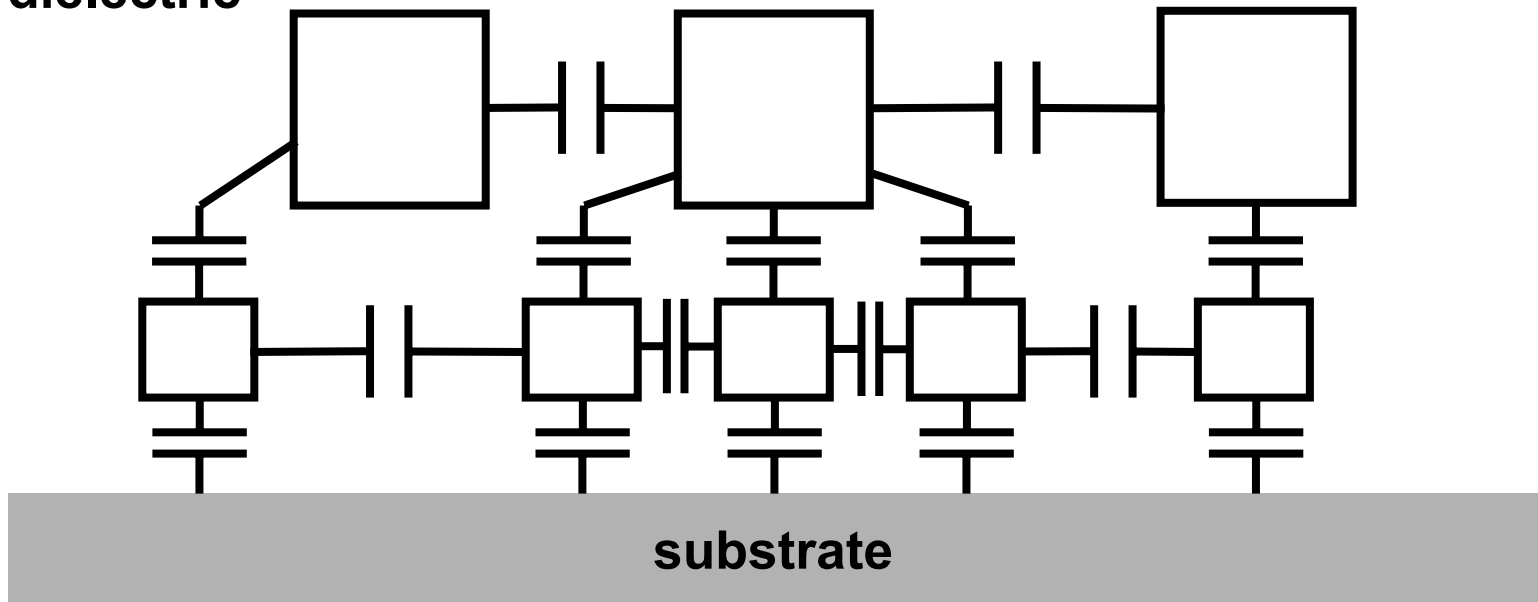

Miller Capacitance

 - Amount of charge moved onto mutual capacitance depends on switching of surrounding wires
- When adjacent wires move in opposite direction, capacitance is effectively doubled (Miller effect)



Data Dependent Switched Capacitance 1

- When adjacent wires move in same direction, mutual capacitance is effectively eliminated

$$A \uparrow B \uparrow C \uparrow \text{ OR } A \downarrow B \downarrow C \downarrow \quad C_{eff} = 0$$

$$A \downarrow B \uparrow C \downarrow \text{ OR } A \uparrow B \downarrow C \uparrow \quad C_{eff} = 4C_m$$

$$A \downarrow B \uparrow C \uparrow \text{ OR } A \downarrow B \downarrow C \uparrow$$
$$A \uparrow B \uparrow C \downarrow \text{ OR } A \uparrow B \downarrow C \downarrow \quad C_{eff} = 2C_m$$


Data Dependent Switched Capacitance 2

- When adjacent wires are static, mutual capacitance is effectively to ground

$$\begin{array}{l} 0 B \uparrow 0 \\ 1 B \uparrow 0 \\ 0 B \uparrow 1 \\ 1 B \uparrow 1 \end{array} \quad \text{OR} \quad \begin{array}{l} 1 B \downarrow 1 \\ 0 B \downarrow 1 \\ 1 B \downarrow 0 \\ 0 B \downarrow 0 \end{array} \quad C_{eff} = 2C_m$$

- Remember: it is the *charging* of capacitance where we account for energy from supply, not discharging


Lumped RC Model

 

- **Simplest model used to represent the resistive and capacitive interconnect parasitics**
- **Propagation delay (same as FET switch model):**


$$t_{PLH} \approx 0.69RC$$

RC T-Model

 

- **Significantly improves accuracy of transient behavior over the lumped RC model**
- **Useful if simulation time is a bottleneck, much simpler than fully distributed model**


Distributed RC Model

 

- Elmore delay approximation for RC ladder network:

$$t_{DN} = \frac{RC}{2} \quad \text{as } N \rightarrow \infty$$

Repeater Insertion to Reduce Wire Delay

 

- Insert inverters along long wires at regular intervals
- Breaks up resistance and capacitance, reducing delay dramatically

Inductance

- **Inductance can be determined by direct application of definition:**

$$\Delta V = L \frac{di}{dt}$$

- **Can compute inductance directly from wire geometry and surrounding environment using field solver**
- **Simpler approach relates capacitance per length c with inductance per length l :**

$$cl = \epsilon\mu$$

- Assumes uniform or “average” dielectric

Summary

- **Many important effects to consider in interconnect design**
 - Resistance, capacitance, inductance can all affect signal performance
 - Long rise/fall time signals, only resistance and capacitance needs to be considered
- **Several models useful for RC interconnect delay analysis**
 - Simple lumped (1 R, 1 C) model: easy to analyze and/or simulate, will be pessimistic
 - T-model ($2 R_{eq} = R/2$, 1 C): more accurate than lumped
 - Distributed model ($N R_{eq} = R/N$, $N C_{eq} = C/N$): most accurate, use Elmore delay approximation for hand analysis

Next Topic: Design for Manufacturability

- **Parameter variations in CMOS digital circuits**
- **Yield maximization and worst-case design**