

EEC 118 Lecture #3: Inverters

**Rajeevan Amirtharajah
University of California, Davis
Jeff Parkhurst
Intel Corporation**

Announcements

- **Lab 1 report due this week**
- **HW 2 due this Friday at 4 PM in box, Kemper 2131**


Outline

- **Review: MOSFET Regimes of Operation**
- **Lecture 2: Scaling, Parasitic Capacitances**
- **Inverter Operation: Rabaey 1.3.2, 5 (Kang & Leblebici, 5.1-5.3 and 6.1-6.2)**

Review: MOS Transistor Structure

- Important transistor physical characteristics

 - Channel length $L = L_D - 2x_d$ (K&L $L = L_{\text{gate}} - 2L_D$)
- Channel width W
- Thickness of oxide t_{ox}



MOSFET Drain Current Overview

Saturation:
$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Linear (Triode, Ohmic):


$$I_D = \mu C_{ox} \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

Cutoff:
$$I_D \approx 0$$


“Classical” MOSFET model, will discuss deep submicron modifications as necessary (Rabaey, Eqs. 3.25, 3.29)

MOS Transistor Symbols

NMOS

 


PMOS

 

Note on MOS Transistor Symbols

 
- **All symbols appear in literature**
 - Symbols with arrows are conventional in analog papers
 - PMOS with a bubble on the gate is conventional in digital circuits papers
- **Sometimes bulk terminal is ignored – implicitly connected to source or appropriate supply rail:**



- **Unlike physical bipolar devices, source and drain are usually symmetric**

Inverter Operation

 - **Inverter is simplest digital logic gate (1 input, 1 output)**




In	Out
0	1
1	0

- **Many different circuit styles possible**
 - Resistive-load
 - NMOS and Pseudo-NMOS
 - CMOS
- **Important static and dynamic characteristics**
 - Speed (delay through the gate)
 - Power consumption
 - Robustness (tolerance to noise)
 - Area and process cost

Inverter Model: Voltage Transfer Curve

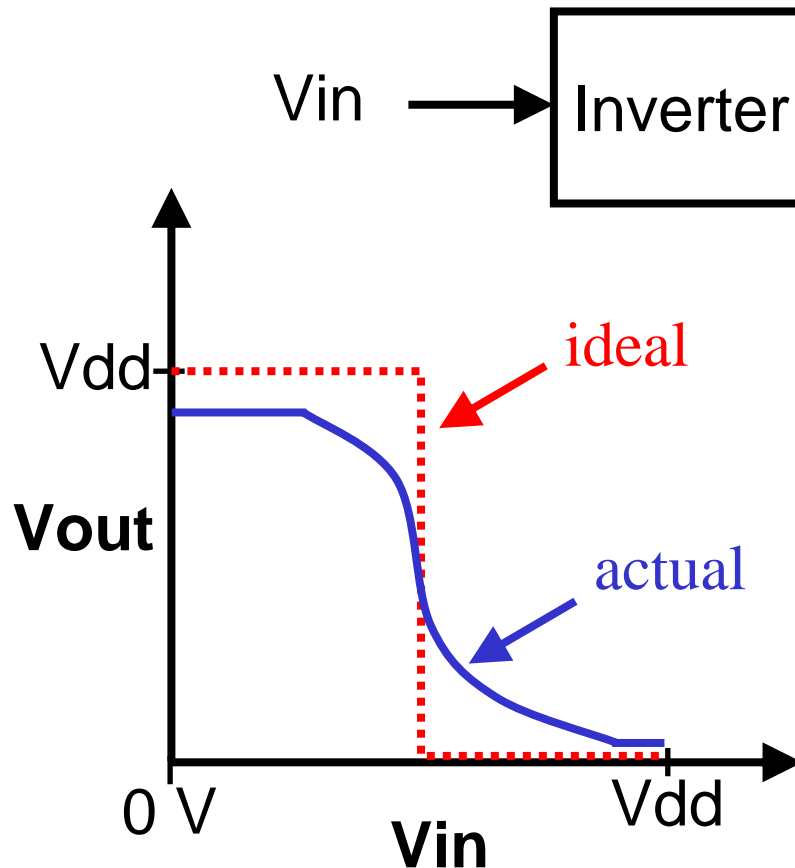
Voltage transfer curve (VTC): plot of output voltage V_{out} vs. input voltage V_{in}



Ideal digital inverter:


- When $V_{in}=0$, $V_{out}=V_{dd}$
- When $V_{in}=V_{dd}$, $V_{out}=0$
- Infinitely sharp transition region at inverter switching threshold

Actual Inverter: V_{OH} and V_{OL}

 

- V_{OH} and V_{OL} represent the “high” and “low” output voltages of the inverter
- V_{OH} = output voltage when $V_{in} = '0'$ (V Output High)
- V_{OL} = output voltage when $V_{in} = '1'$ (V Output Low)
- Ideally,
 - $V_{OH} = V_{dd}$
 - $V_{OL} = 0\text{ V}$

VOL and VOH

 

- In transfer function terms:

- $V_{OL} = f(V_{OH})$

- $V_{OH} = f(V_{OL})$


- f = inverter transfer function

- **Difference ($V_{OH} - V_{OL}$) is the *voltage swing* of the gate**

- *Full-swing logic* swings from ground to V_{DD}

- Other families with smaller swings


Inverter Switching Threshold

 

Inverter switching threshold:


- Point where voltage transfer curve intersects line $V_{out} = V_{in}$
- Represents the point at which the inverter switches state
- Normally, $V_M \approx V_{DD}/2$
- Sometimes other thresholds desirable

Noise Margins

 

- V_{IL} and V_{IH} measure effect of input voltage on inverter output
- V_{IL} = largest input voltage recognized as logic '0'
- V_{IH} = smallest input voltage recognized as logic '1'
- Defined as point on VTC where slope = -1

Noise Margins and Robustness

 

- Noise margin is a measure of the *robustness* of an inverter

$$- N_{ML} = V_{IL} - V_{OL}$$

$$- N_{MH} = V_{OH} - V_{IH}$$

- Models a chain of inverters.
Example:

- First inverter output is V_{OH}
- Second inverter recognizes input $> V_{IH}$ as logic '1'
- Difference $V_{OH} - V_{IH}$ is "safety zone" for noise

Noise Margin Motivation

- Why are V_{IL} , V_{IH} defined as unity-gain point on VTC curve?

– Assume there is noise on input voltage V_{in}


$$V_{out} = f(V_{in} + V_{noise})$$

– First-order Taylor series approximation:

$$V_{out} = f(V_{in}) + \frac{dV_{out}}{dV_{in}} V_{noise}$$


- If gain (dV_{out}/dV_{in}) > 1 , noise will be amplified.
- If gain < 1 , noise is filtered. Therefore V_{IL} , V_{IH} define regions where gain < 1

Inverter Time Response

 

- Propagation delay measured from 50% point of V_{in} to 50% point of V_{out}
- $t_{pHL} = t_1 - t_0$, $t_{pLH} = t_3 - t_2$, $t_p = \frac{1}{2}(t_{pHL} + t_{pLH})$



Rise and Fall Time

 

- **Fall time:** measured from 90% point to 10% point
 - $t_F = t_1 - t_0$
- **Rise time:** measured from 10% point to 90% point
 - $t_R = t_3 - t_2$
- **Alternately, can define 20%-80% rise/fall time**

Ring Oscillator

  
- **Ring oscillator circuit:** standard method of comparing delay from one process to another
- **Odd-number n of inverters connected in chain:** oscillates with period T (usually $n \gg 5$)



$$T = t_{plh1} + t_{phl1} + t_{plh2} + t_{phl2} + t_{plh3} + t_{phl3} + \dots$$


$$T = 2nt_p, \quad f = \frac{1}{T} = \frac{1}{2nt_p}, \quad t_p = \frac{1}{2nf}$$

Resistive Load Inverter

 


- Resistor pulls up to Vdd (V_{OH}), NMOS pulls down (V_{OL})

NMOS Inverter

 

- **Depletion NMOS always on, sourcing static current**

Inverter as Amplifier

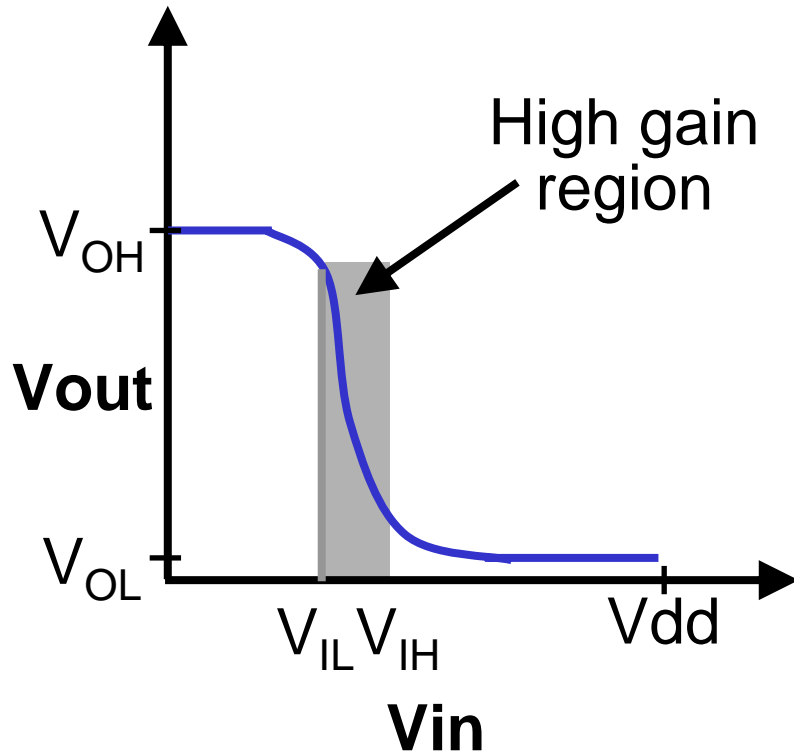

- For V_{in} between V_{IL} and V_{IH} , inverter gain > 1
- Acts as a linear amplifier (often very high gain)
- Logic levels '0' and '1' correspond to saturating amplifier output (output is pegged to high or low supply)
- Resistive load inverter same circuit as common source amplifier

Next Topic: CMOS Inverters

- **CMOS Inverters**
 - DC Characteristics: Sizing
 - AC Characteristics: Designing for speed