

# **EEC 118 Lecture #9: Sequential Logic**

**Rajeevan Amirtharajah  
University of California, Davis  
Jeff Parkhurst  
Intel Corporation**

# Announcements

---

- **Lab 4, Part 1 this week**
- **HW4 due Friday, 4PM in box, Kemper 2131**
- **Lab 3, Part 2 report due this week**

# Outline

---

- **Review: Static CMOS Logic**
- **Finish Static CMOS transient analysis**
- **Sequential MOS Logic Circuits: Rabaey, 7.1-7.3 (Kang & Leblebici, 8.1-8.5)**
- **Next Topic: Logical Effort**


# Sequential Logic Basic Definition

---

- **Combinational circuits' output is a function of the circuit inputs and a delay time**
  - Examples: NAND, NOR, XOR, adder, multiplier
- **Sequential circuits' output is a function of the circuit inputs, previous circuit state, and a delay time**
  - Examples: Latches, flip-flops, FSMs, pipelined adders and multipliers, microprocessors
  - Sequential elements are critical to implementing techniques such as feedback or blocks such as memory



# Sequential Logic Example: Mealy FSM

---

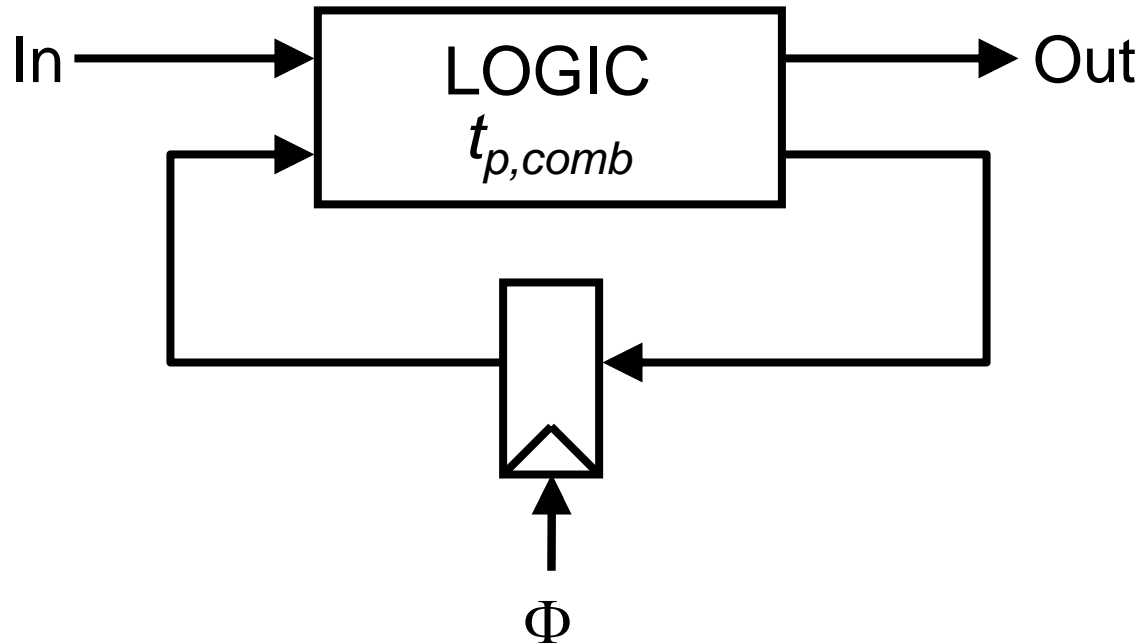


- **Two information storage mechanisms**
  - Positive feedback-based (static) circuits
  - Charge storage-based (dynamic) circuits
- **Clock signal  $\Phi$  controls timing of state (memory) updates**

# Positive Feedback: Bistability

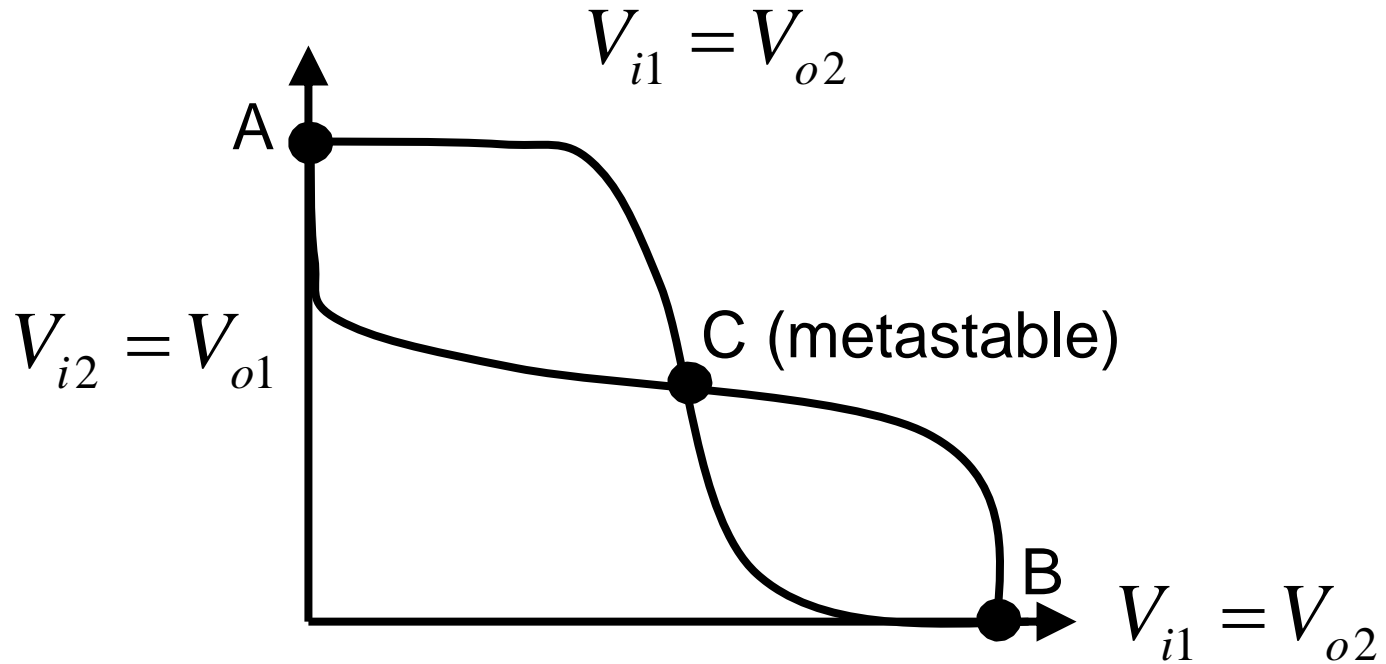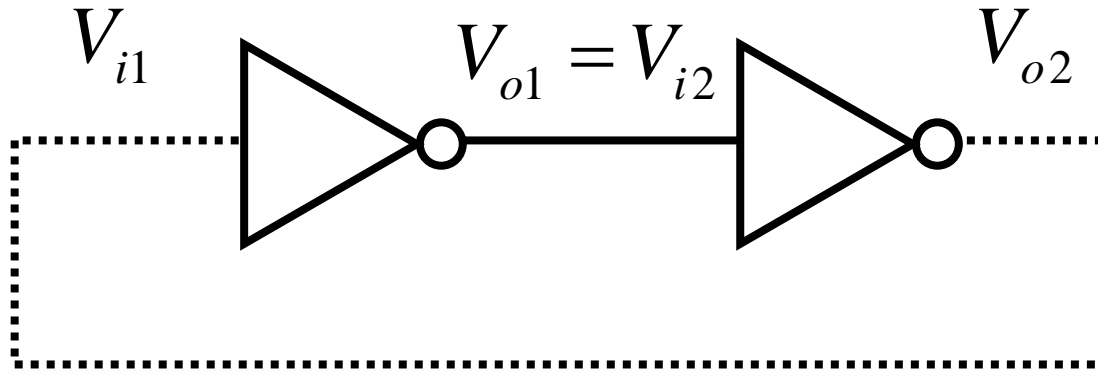

# Metastability

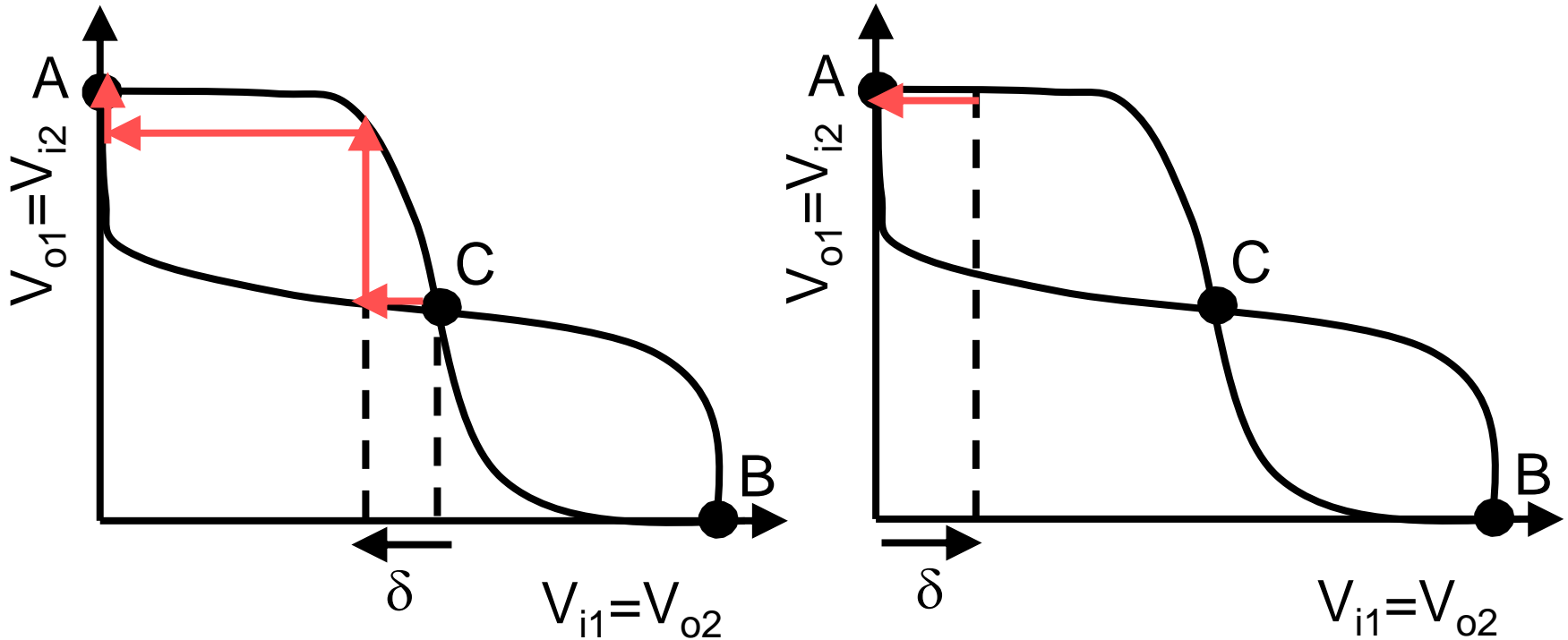

**Gain should be larger than 1 in the transition region**

# Bistable Elements

---


- **Bistable elements have two stable states or operation modes**
- **Cross-coupled inverters are the most basic bistable element**
  - Circuit forms the basis of latches and SRAM memory
  - Stable points on the VTC are those with the lowest energy
  - Points with high energy are unstable, perturbations are amplified


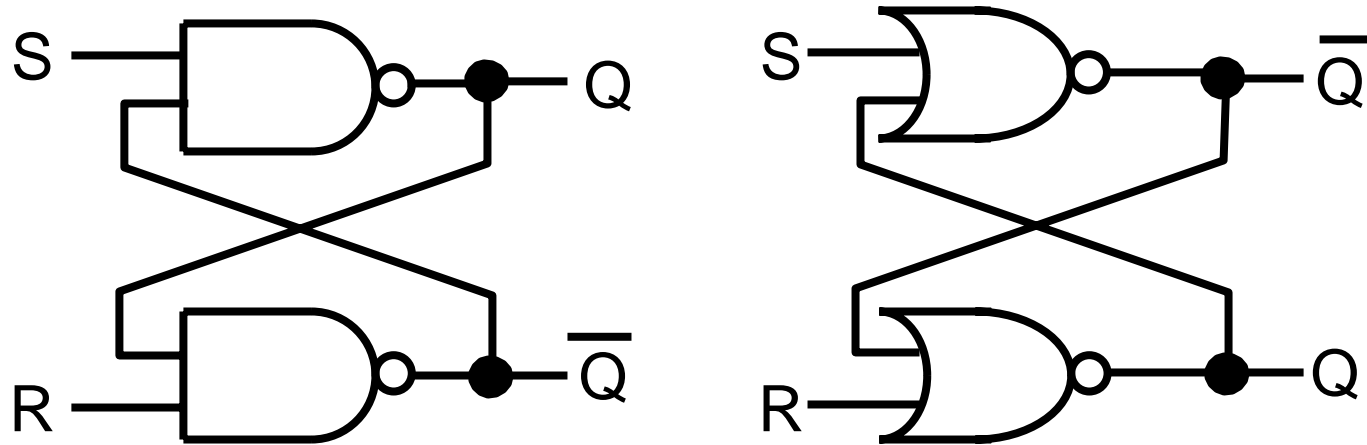
# Set-Reset (SR) Latch

---


- **Change inverters to NAND or NOR gates, with second inputs = S(set) and R(reset)**



- **Allows control of the state of the bistable element**
- **One input state is not allowed**
- **Gating S and R with the clock prevents the latch from responding except during one phase of the clock cycle**
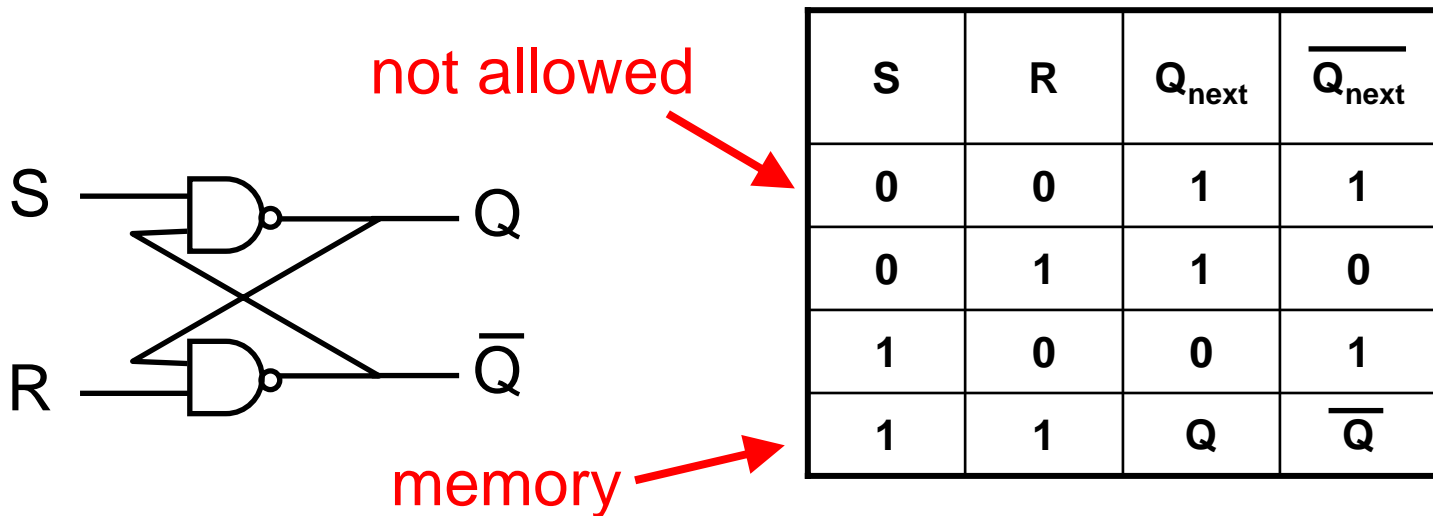
# SR Latch

- **Sequential circuits: circuits which “store state”:** circuits with memory elements
- **Latches: store previous output value for certain input combinations**
- **SR latch (NAND-based):**



# Other Latches


---

- **Clocked SR latch**
  - Adds clock input. Latch output can only be set/reset when  $\text{clk}=1$  (or  $\text{clk}=0$ )
- **Other latch types:**
  - JK latch: Removes “not allowed” state – e.g., toggles when inputs are both 1
  - T latch: Toggles when T input = 1
  - D latch: Output = D input
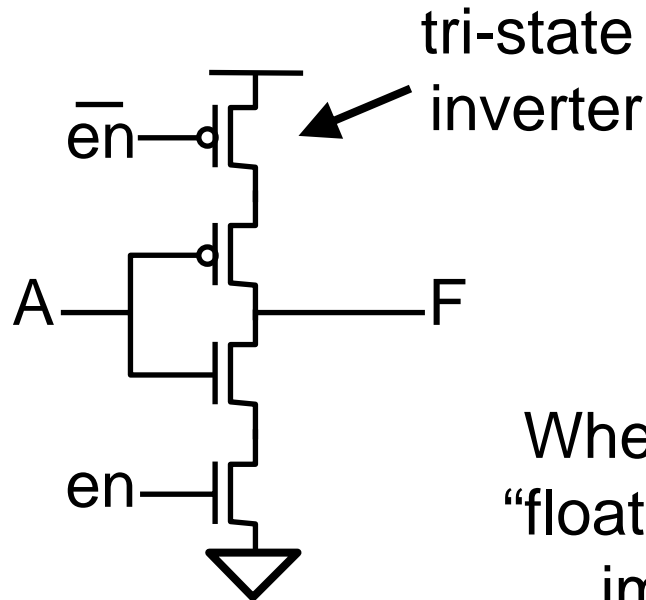
# Latch Circuits

---


- **Many methods for implementing latches**
  - Standard CMOS gates (cross-coupled NAND, etc)
  - Transmission gates
  - Tri-state inverters



When  $en=0$ ,  $F$  is “floating”, i.e. high impedance


# Positive Dynamic Transmission Gate Latch

---

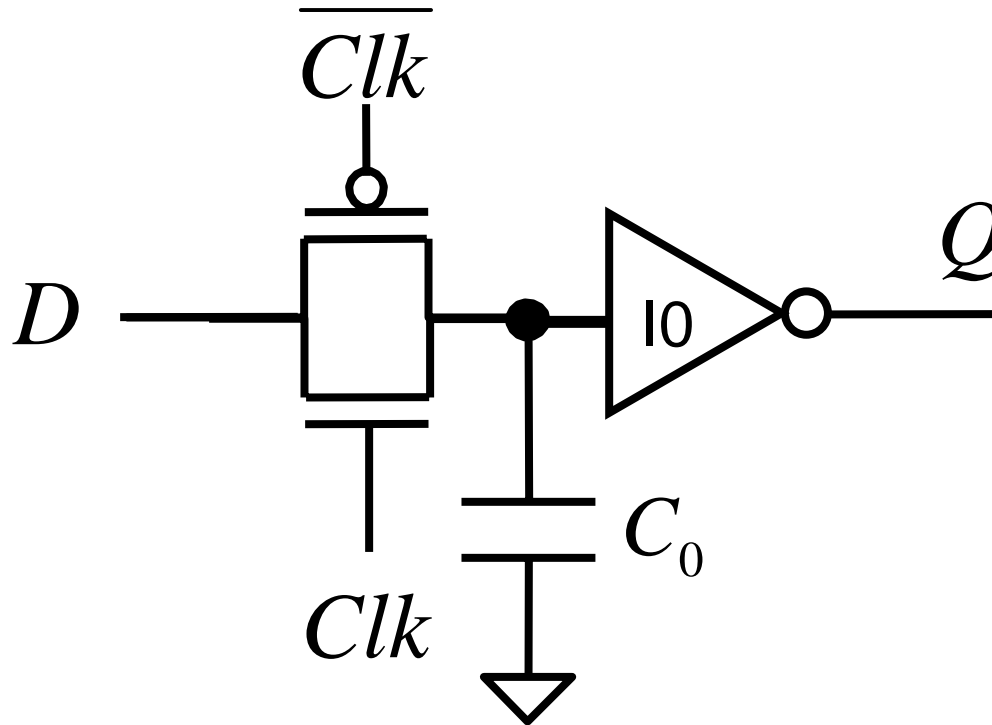


- No feedback devices
- Data stored on input capacitance of inverter  $I_0$
- Dynamic logic issues apply: leakage, capacitive coupling, charge sharing
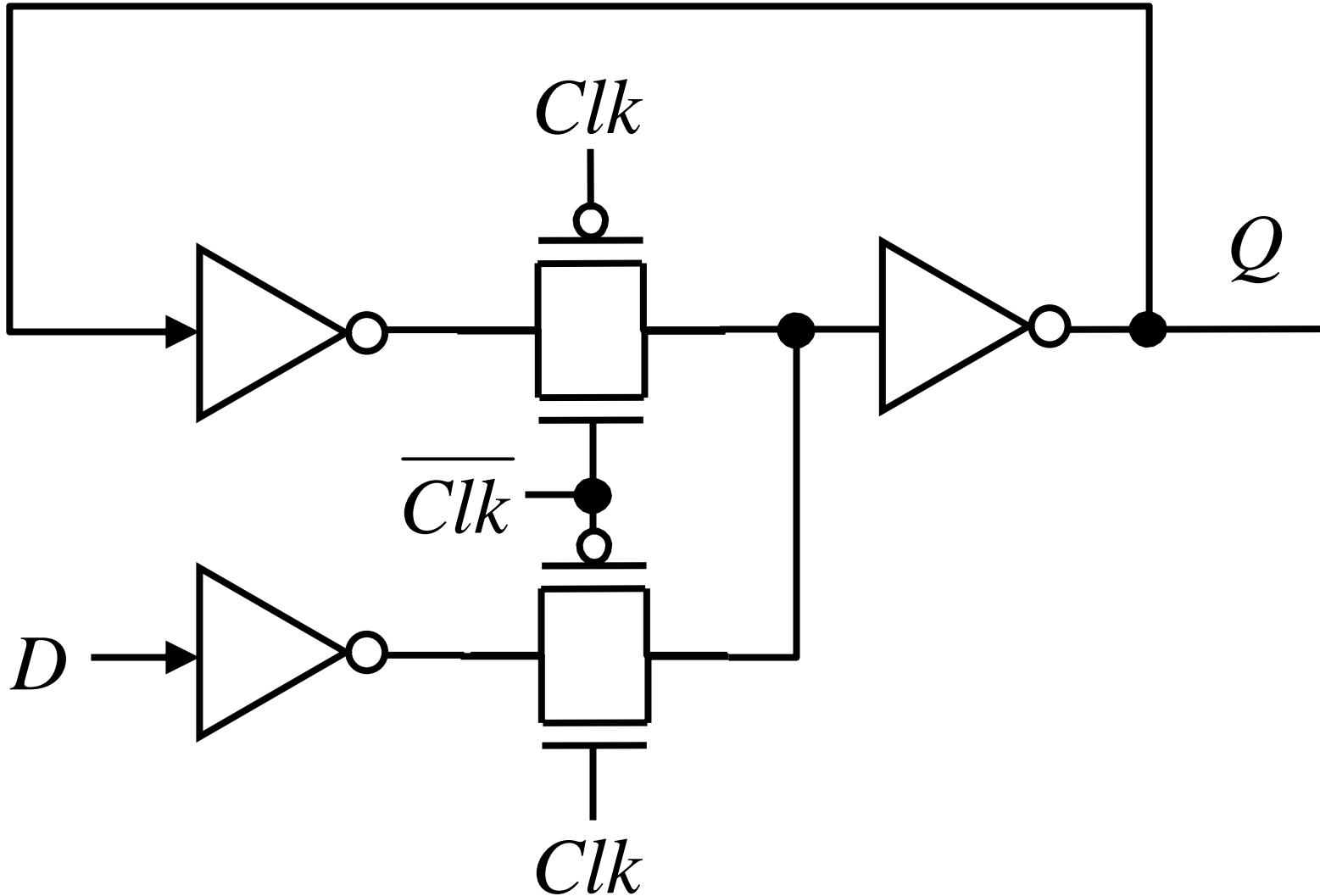
# Transmission Gate Positive Static Latch



# NMOS Pass Gate Positive Static Latch

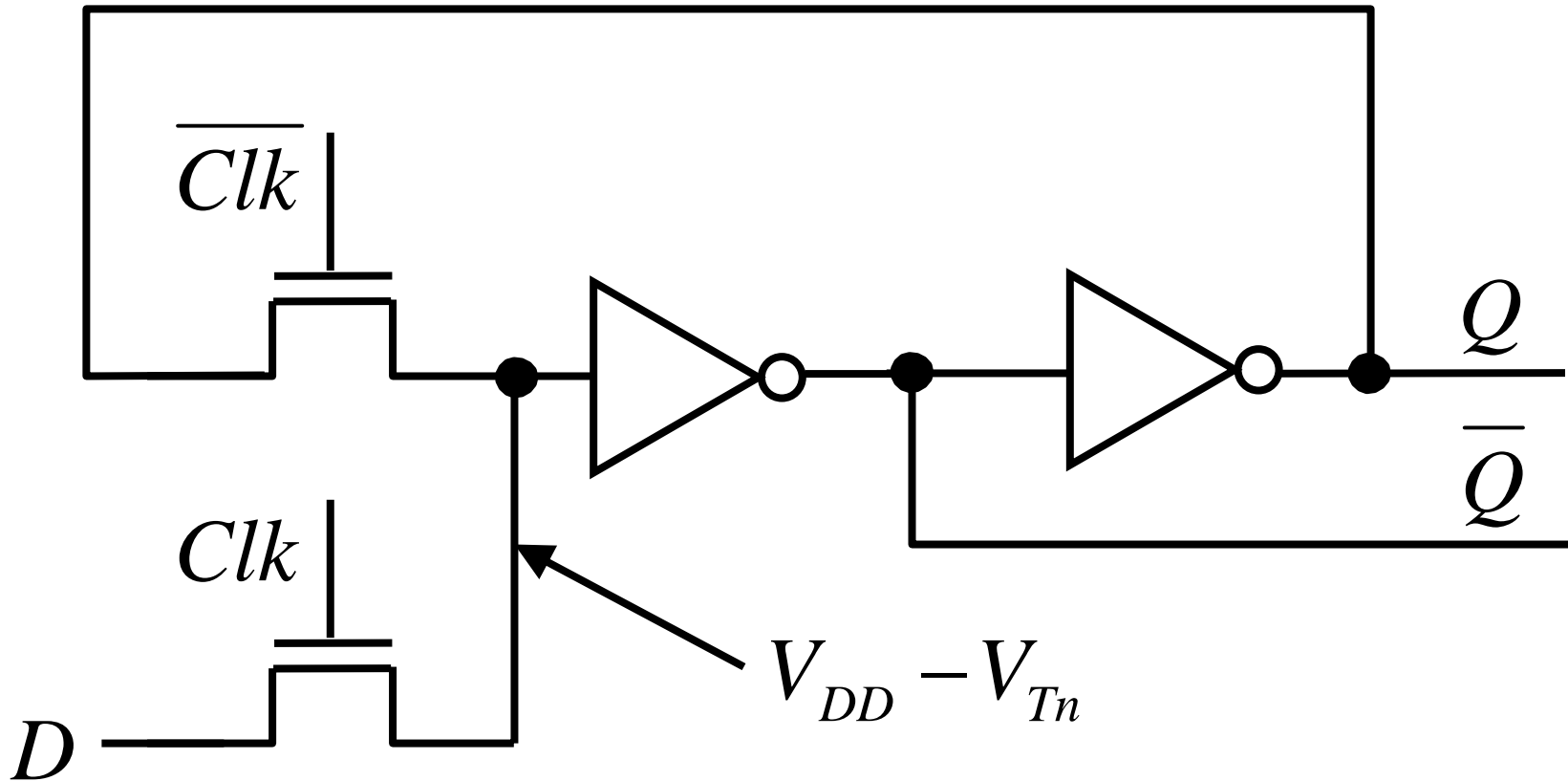

- Fewer devices, less area, lower clock load
- Threshold drop on internal nodes implies more static power, less noise margin

# Master-Slave Flip-Flop

---

- **By cascading two level-sensitive latches, one type of edge triggered flip-flop is created**
- **JK latch can be used for first stage so that no input combinations are invalid**
- **SR latch is then used for the second stage because inputs cannot be invalid**
- **Rather than using logic gate-based latches, can cascade latches such as above (e.g., transmission gate dynamic or static latches)**




# Edge-Triggered Flip-Flops

---

- **Types of latches/flip-flops:**
  - *Level-sensitive*: output is set when clock is a certain level (0 or 1)
  - *Edge-triggered*: output can only be set on a clock edge (rising or falling)
- **Advantages of edge-triggered flip-flops:**
  - Data only needs to be stable at clock edge
  - Reduces *race conditions*: potential errors where an input data change travels through multiple latches during their “transparent” phase

# Dynamic Positive Edge-Triggered FF

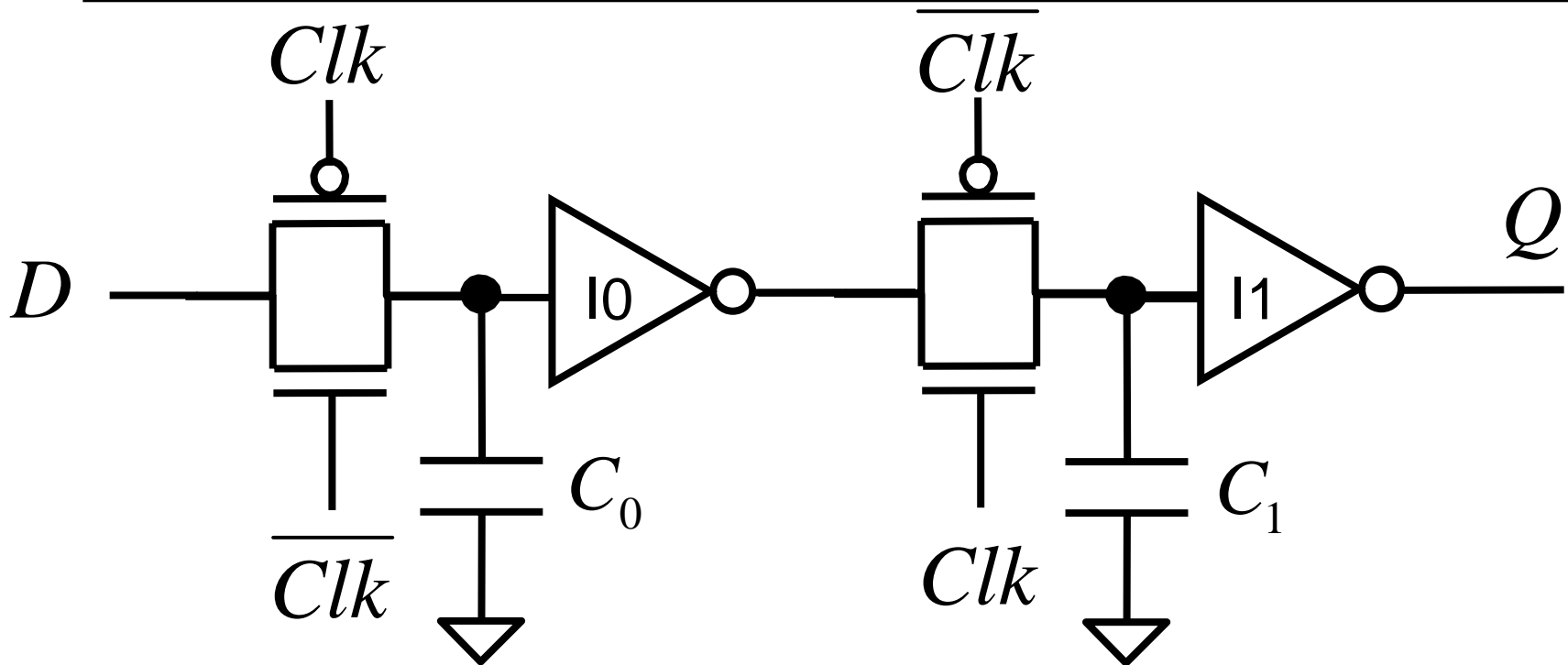


- No feedback devices
- Data stored on input capacitances of inverters I0 and I1
- Dynamic logic issues apply: leakage, capacitive coupling, charge sharing

# Clocked Circuit Timing

---

- **Timing definitions:**
  - Clock-to-Q or Propagation Delay ( $t_{clkQ}$ ): delay of flip-flop from clock edge to output Q
  - Setup Time ( $t_{setup}$ ): amount of time *before* clock edge that data has to be stable. If data arrives after this time, it will not be latched correctly.
  - Hold Time ( $t_{hold}$ ): amount of time *after* clock edge that data has to be stable.
- **It is possible to trade off setup and hold time with flip-flop circuit design**
  - Modify data and clock timing relationship by delaying one of the two signals


# Flip-Flop: Timing Definitions

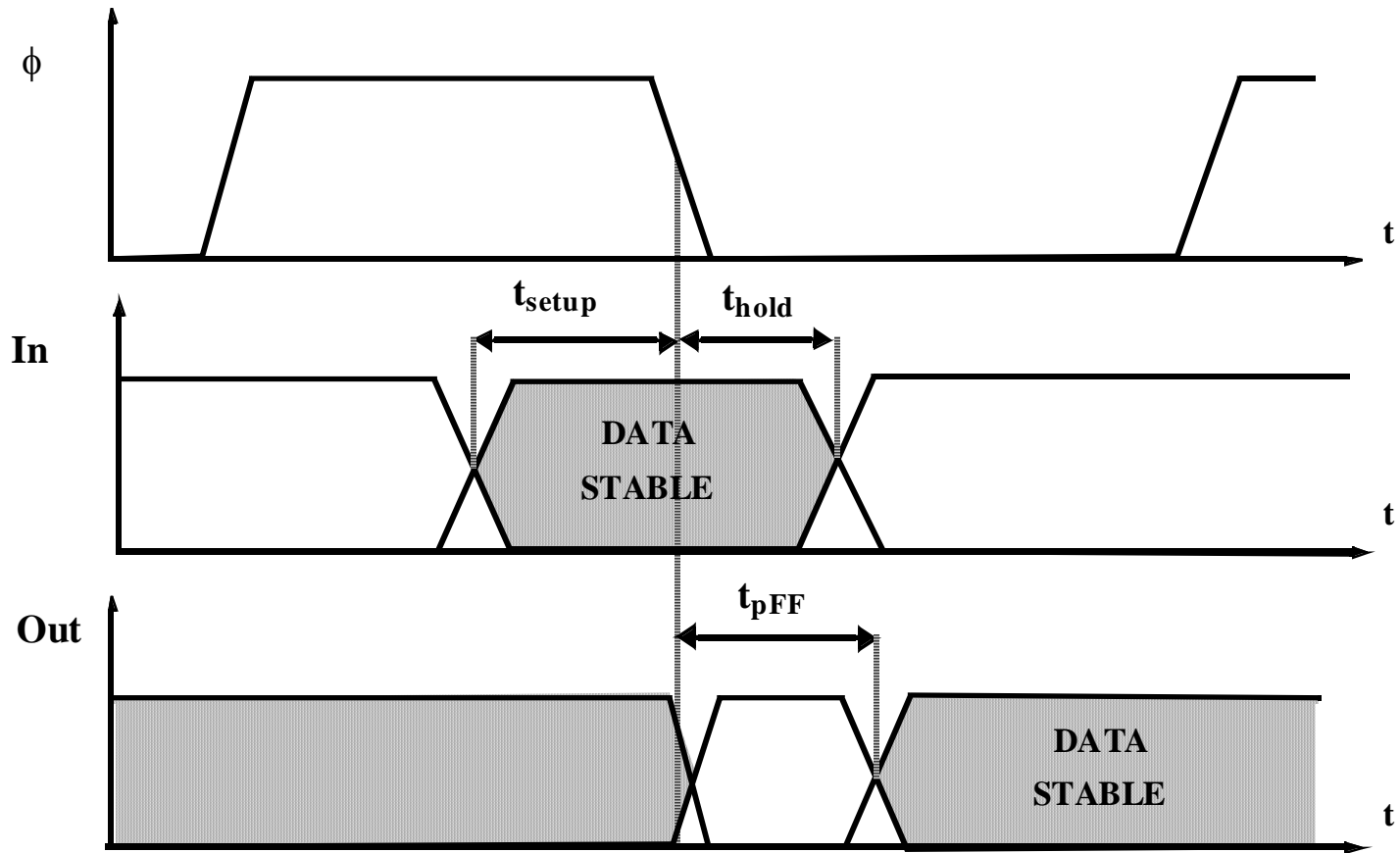

From Digital Integrated Circuits – Jan Rabaey Notes

# Maximum Clock Frequency

---

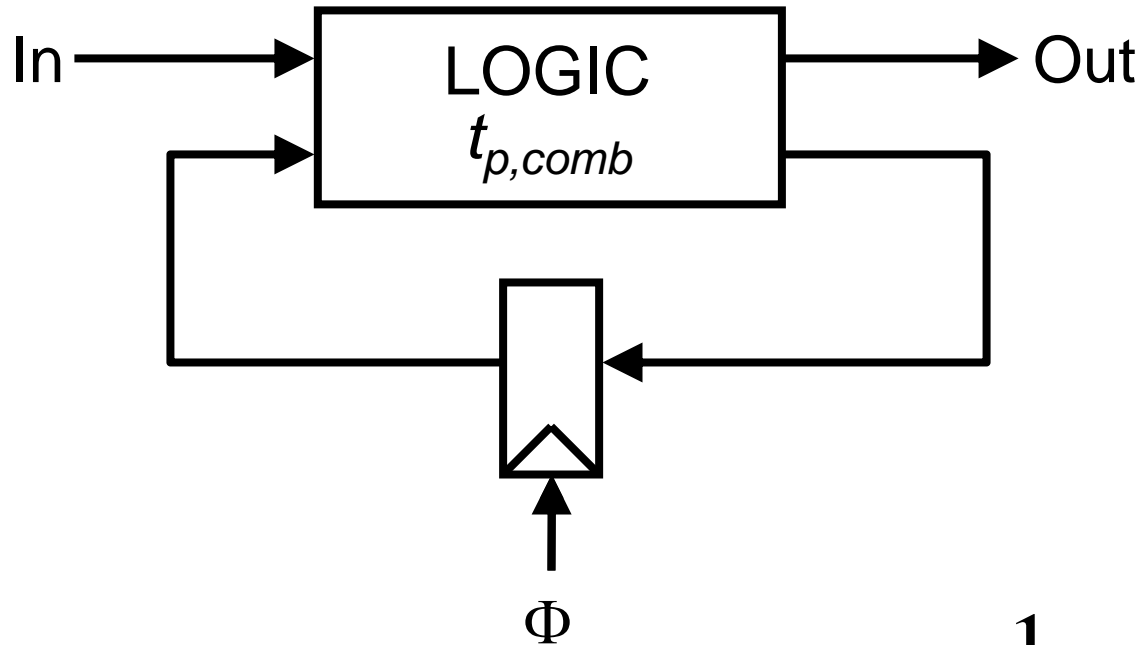


$$t_{pFF} + t_{p,comb} + t_{setup} < T = \frac{1}{f}$$

- **Signals must propagate out of flip-flop, through combinational logic, and be stable before next clock edge (clock period = T, clock frequency = f)**


# Staticized Dynamic Positive Edge-Triggered FF

---

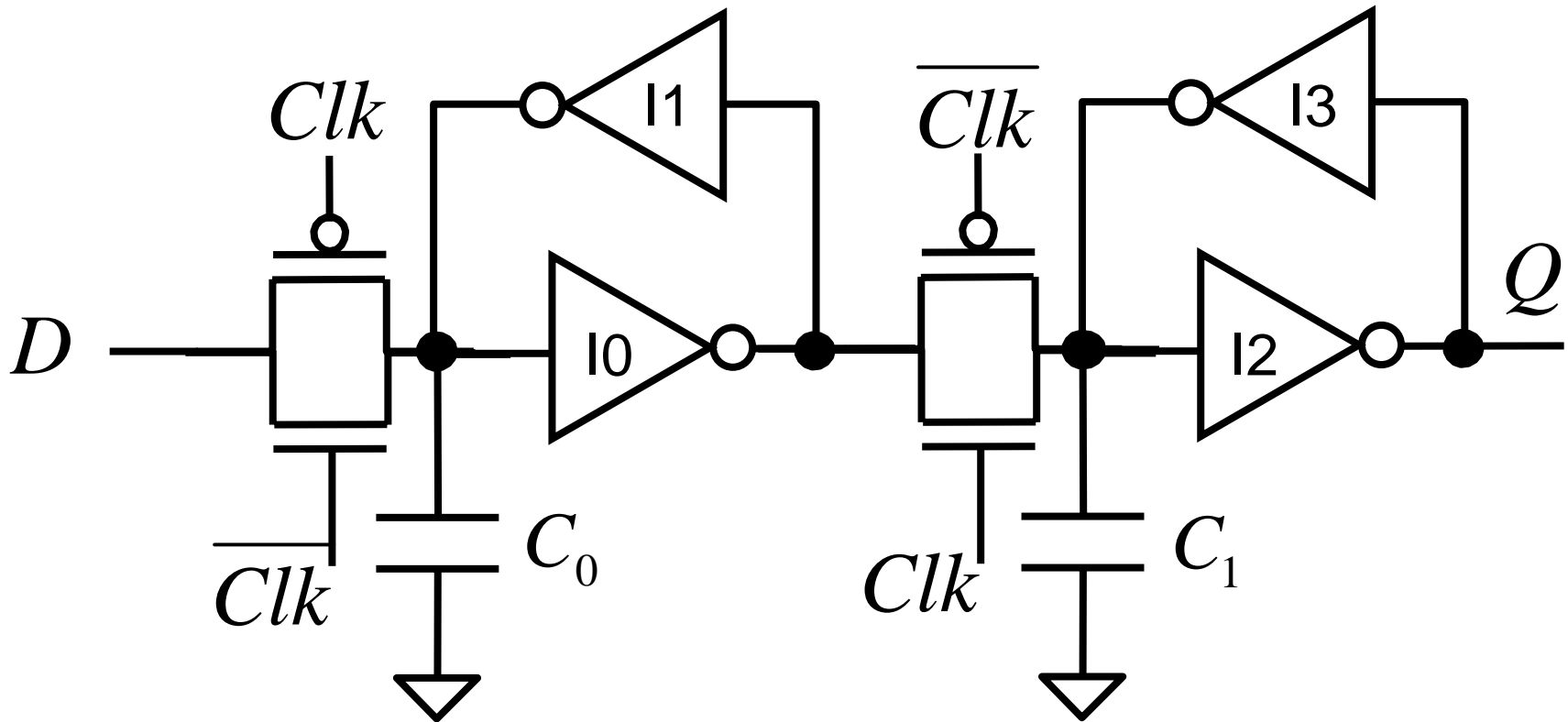


- Use weak feedback inverters to enhance robustness
- Returns to reduced clock load static flip-flop with same sizing issues

# Clock Overlap Failures

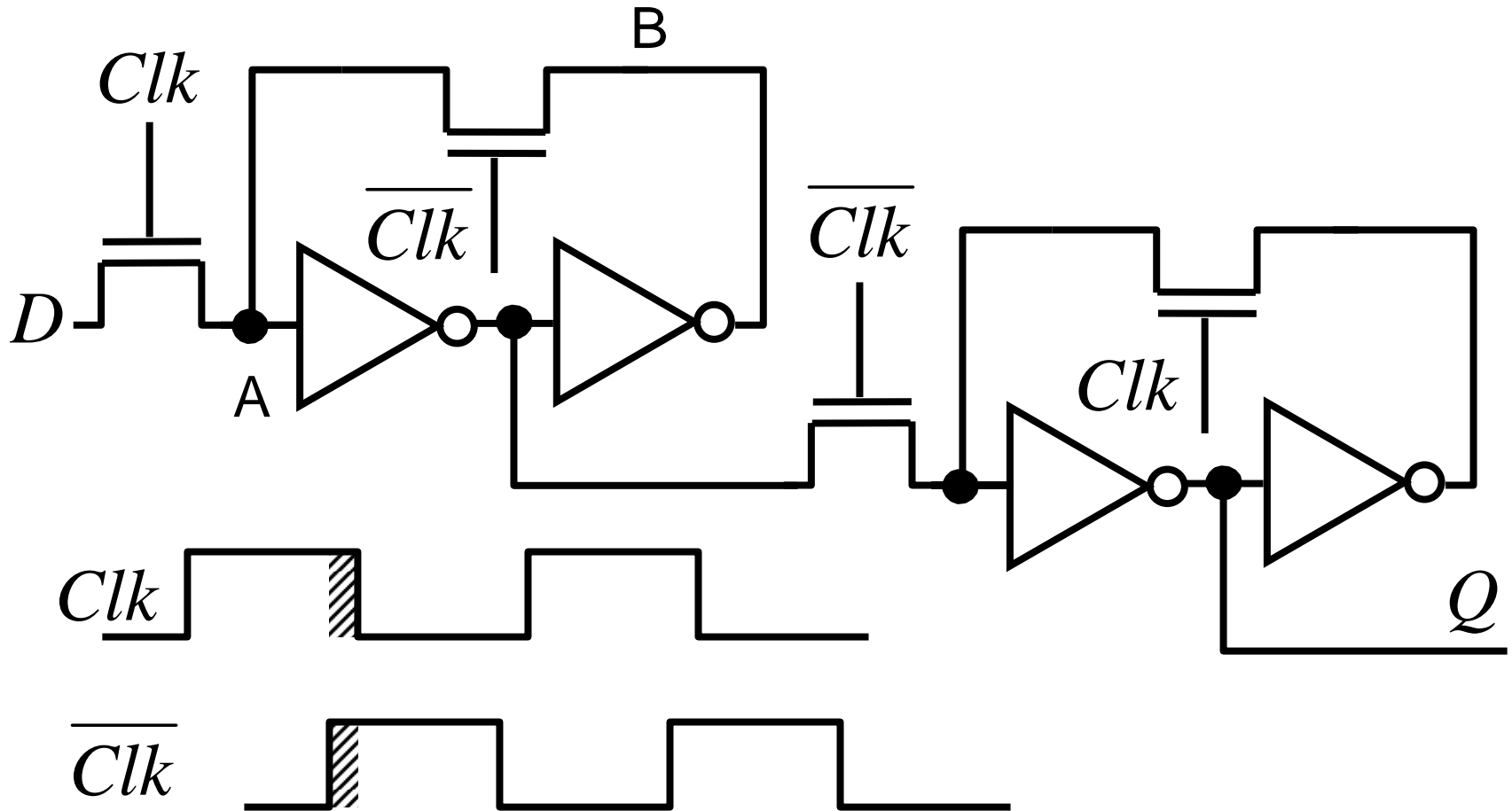

1. Both high simultaneously, race condition from  $D$  to  $Q$
2. Node  $A$  can be driven simultaneously by  $D$  and  $B$


# Race Through and Feedback Paths

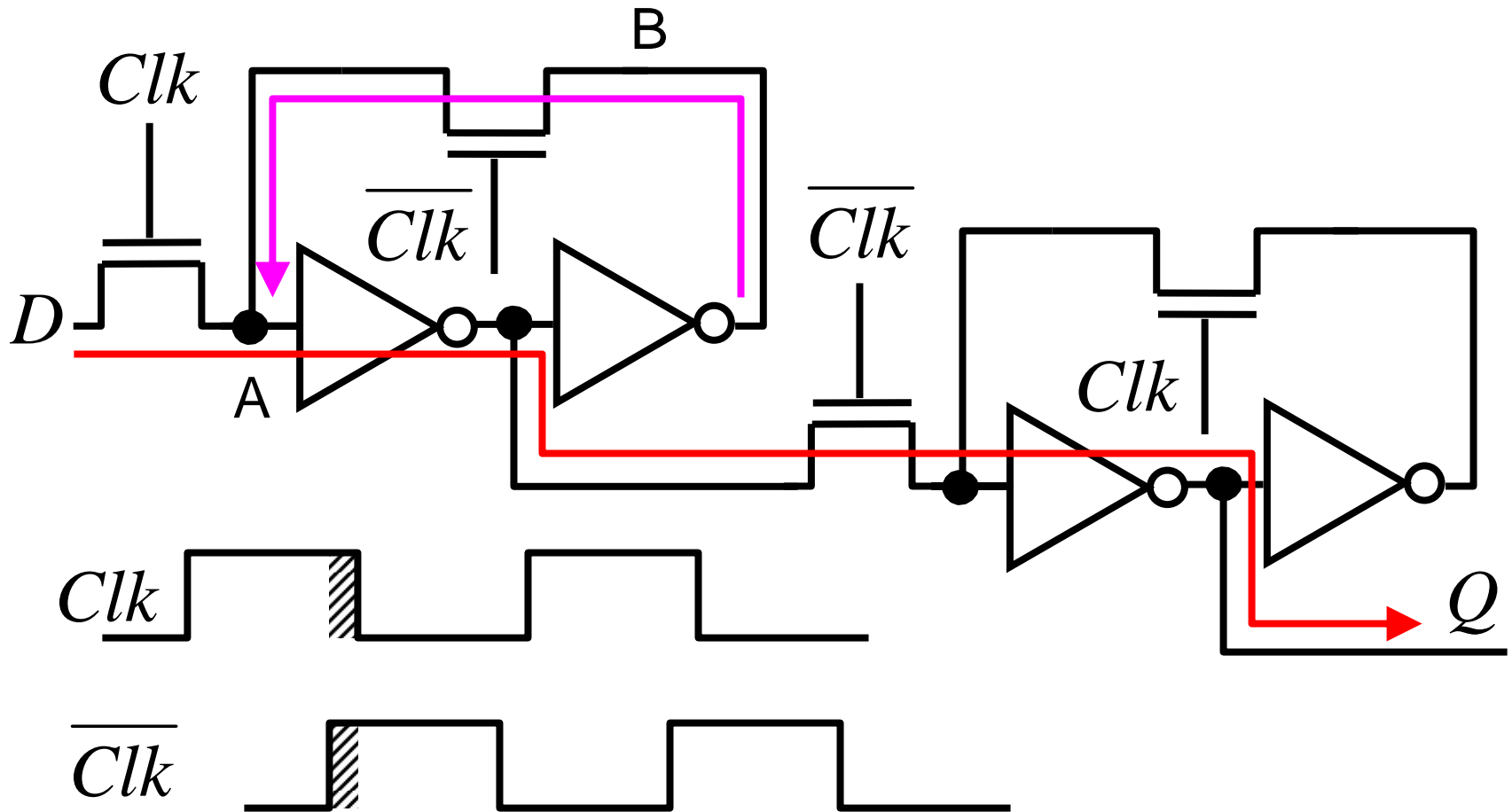

1. Both high simultaneously, race condition from  $D$  to  $Q$
2. Node  $A$  can be driven simultaneously by  $D$  and  $B$




# Nonoverlapping Clocks Methodology

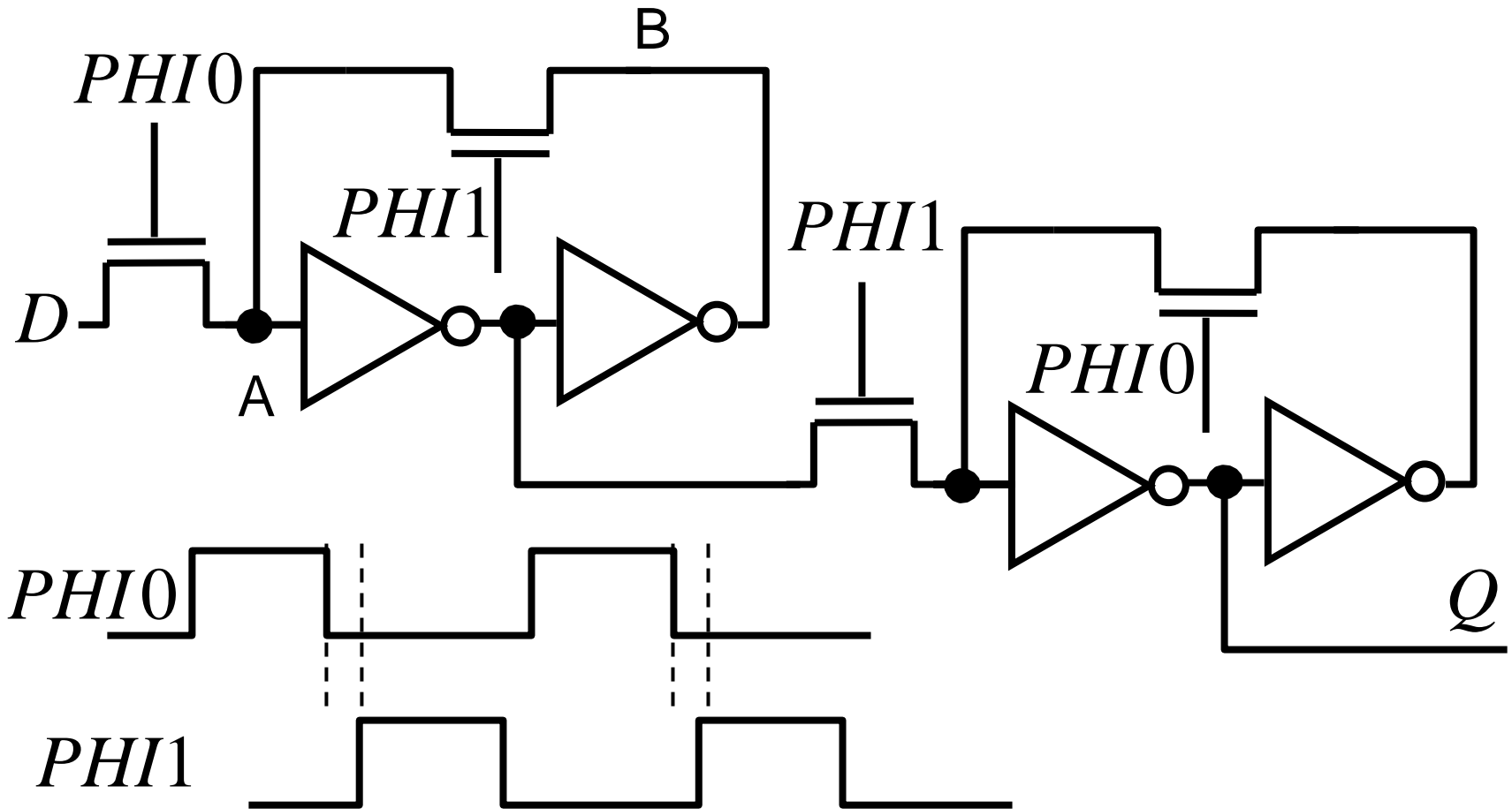


- **Guarantee nonoverlap period long enough**
- **Note: internal nodes left high Z during nonoverlap**
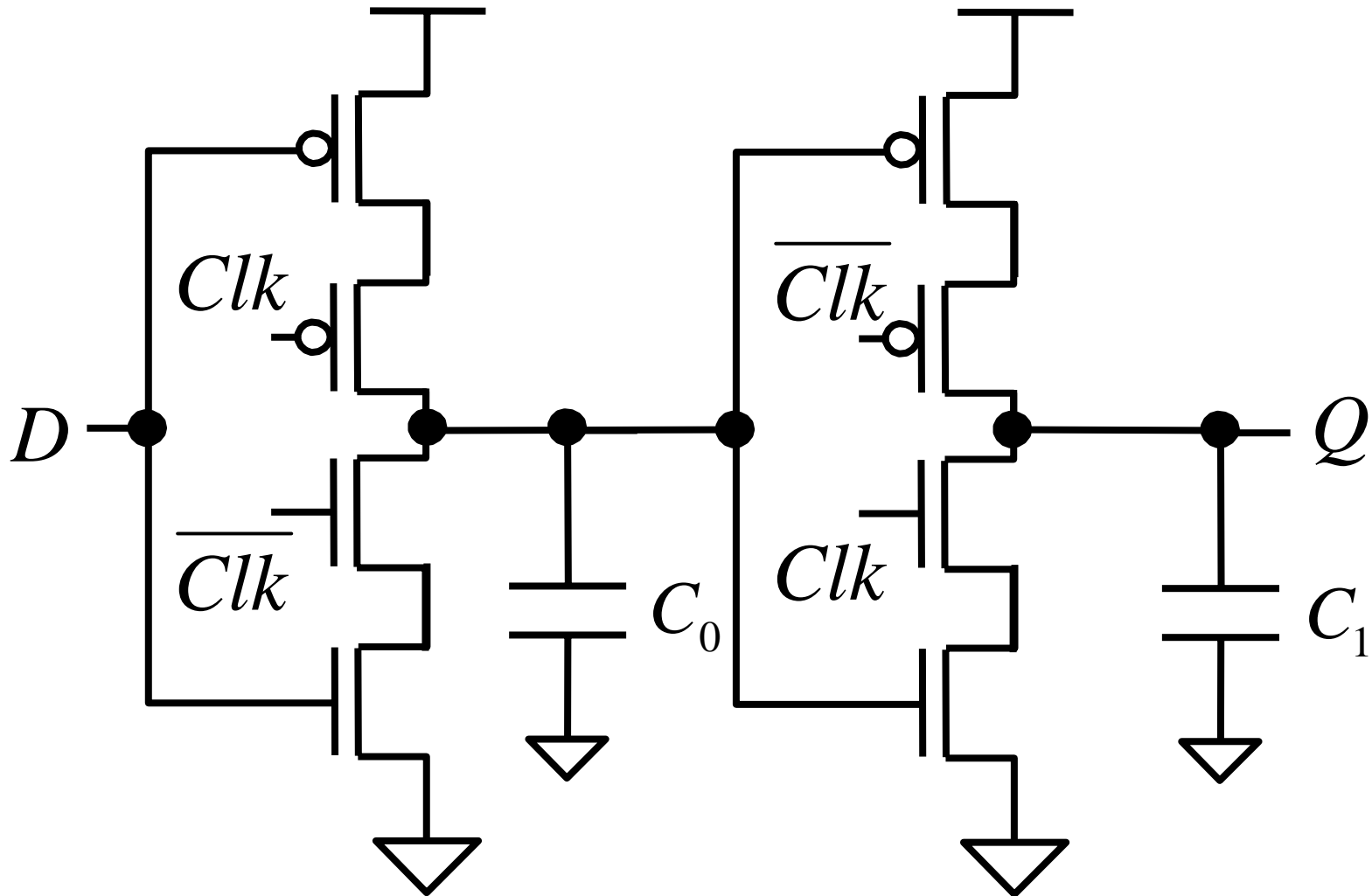
# C<sup>2</sup>MOS Edge Triggered Flip-Flop




- **Tristate inverters eliminate clock overlap race condition**

# Zero-Zero Overlap Condition

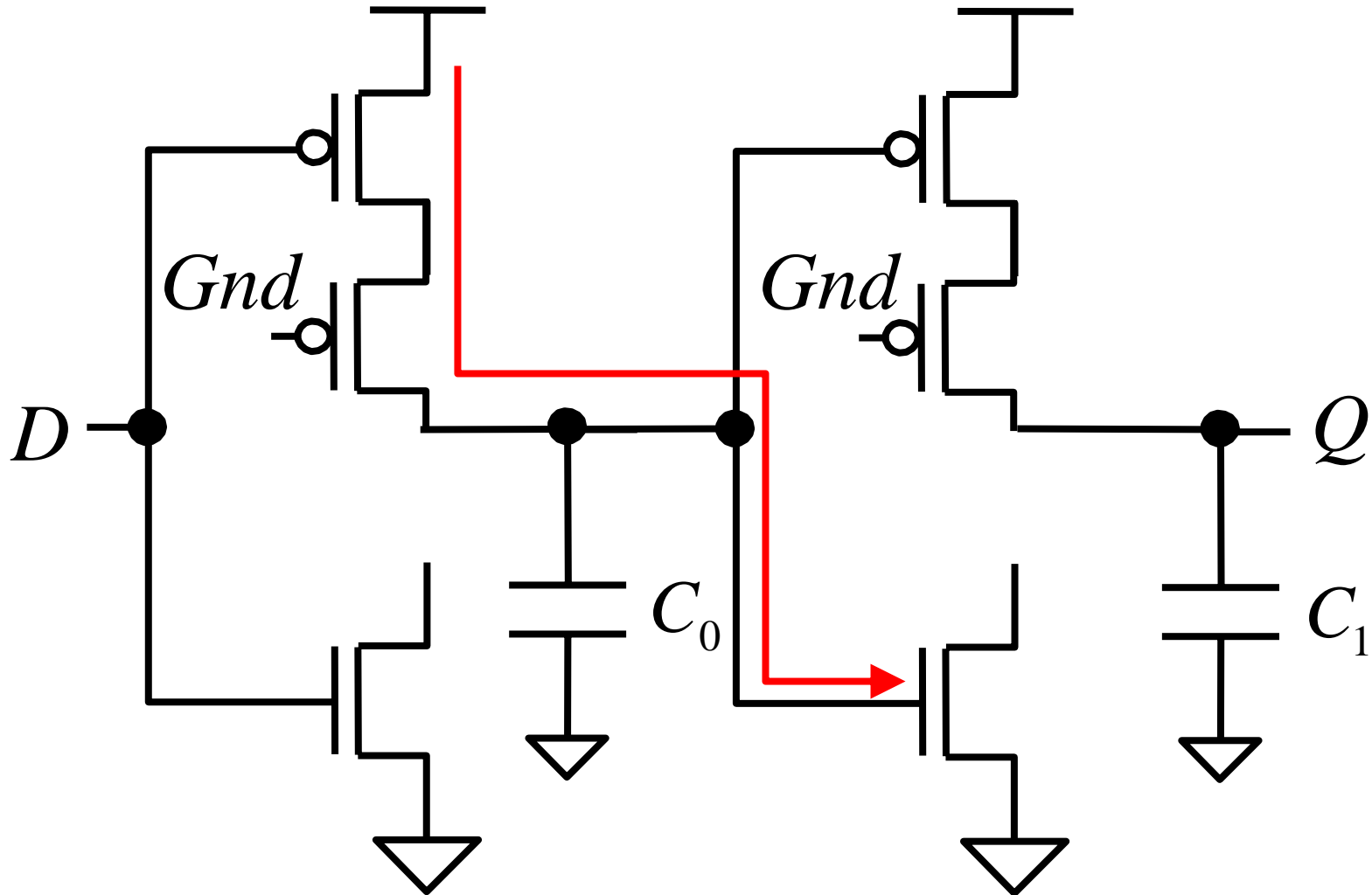

- **Both phases low simultaneously enables opposite nets**

# High-High Overlap Condition

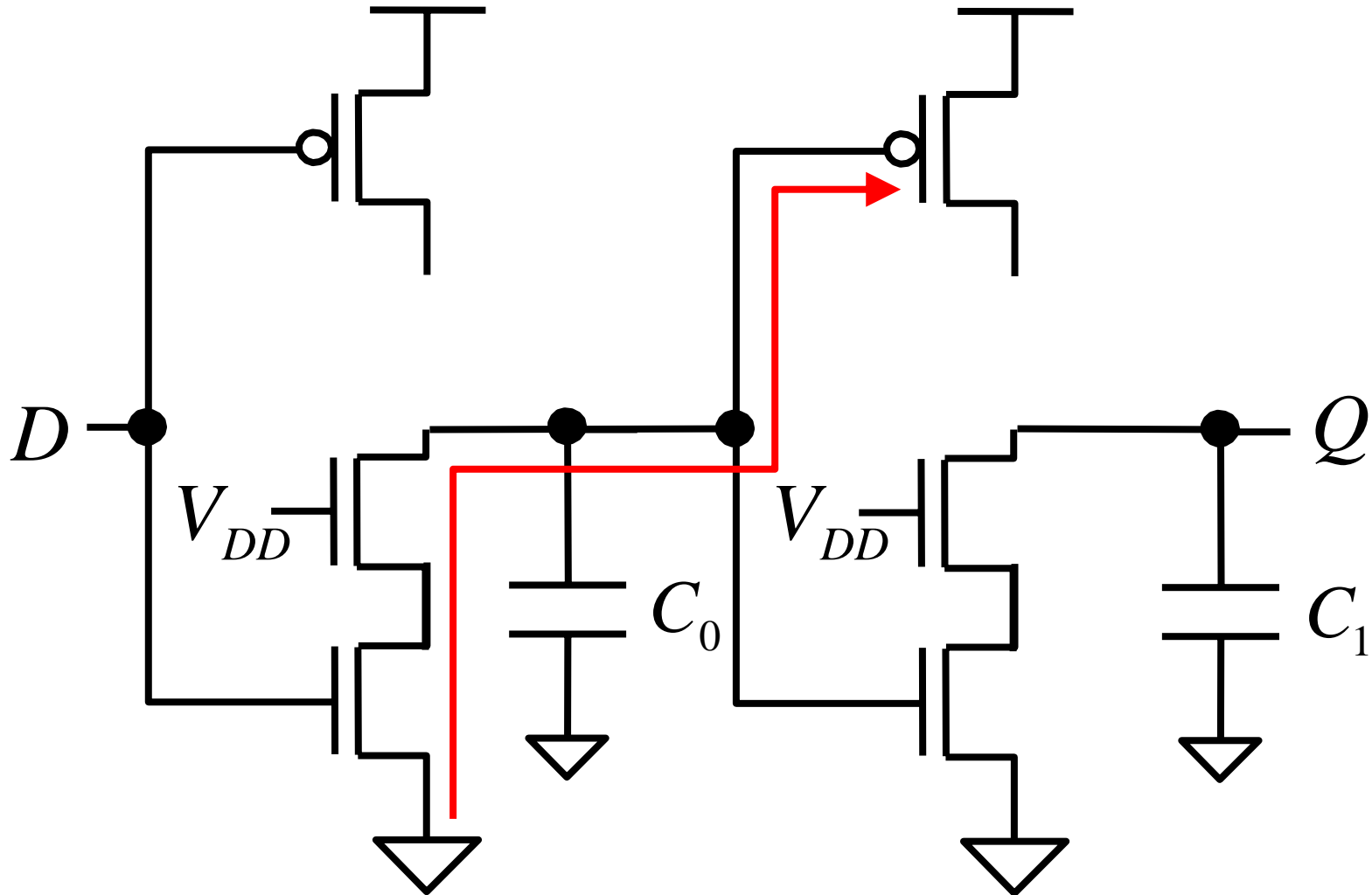


- **Both phases high simultaneously enables opposite nets**

# C<sup>2</sup>MOS Design

---

- **Clock overlap problems eliminated as long as rise and fall times remain fast**
  - Slow rise / fall times imply pullup and pulldown nets on simultaneously resulting in potential errors, static power
- **Dynamic flip-flop style leaves output high Z**
  - Must take care when using since output wire could be exposed to many more noise sources than internal nodes
- **Mix and match styles by using C<sup>2</sup>MOS as master and other types of latch as slave**
- **Clock load small, but potentially larger than transmission gate dynamic latches due to PMOS sizing**

# Pipelining

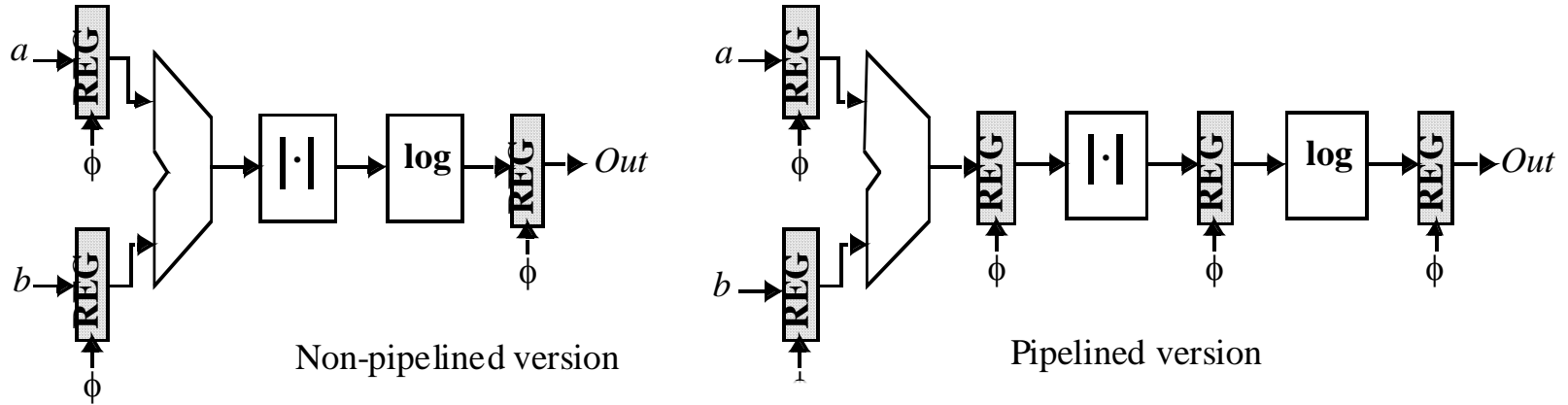

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log( a_2 + b_2 )$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log( a_3 + b_3 )$

From Digital Integrated Circuits – Jan Rabaey Notes

# Next Topic: Logical Effort

---

- **Systematic method for optimizing CMOS circuits for speed**
  - Balances gate delays and logic depth
  - Enables systematic method of finding minimum sizes to achieve delay specification
  - Implicitly assumes switch RC model for propagation delay