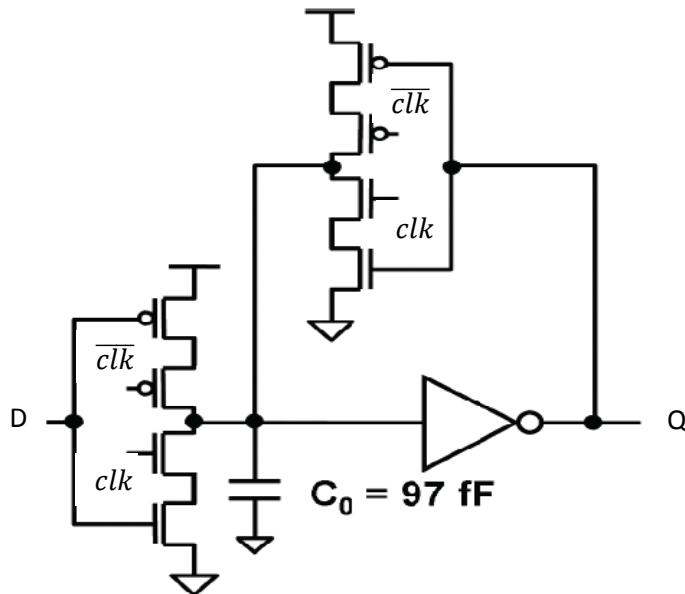


EEC 118 Solutions to Homework #5

Problem 1.1



We want the latch to be transparent when clk is positive, so we put clk at the gates of the NMOS's and clk_bar at the gates of the PMOS's. The feedback inverter makes it static instead of dynamic.

Problem 1.2

Since the output equals the input after some delay, we imagine the input D at V_{DD} and the output Q low before the clk signal goes high. We're given the t_{pLH} for the second inverter which is the delay for the output to go from GND to $0.5 V_{DD}$. Assuming that t_{pLH2} is the time from when the input changes to its 50% value till the output rises to the 50% value, the t_{pLH} from the input to the output is approximately $t_{HL1} + t_{pLH2}$ because we need the time it takes the voltage at the capacitor V_{C_0} or the input to the second inverter to become $0.5 V_{DD}$. We don't have to calculate the full fall time for the first inverter.

Using the average current method, $\tau_{pHL1} = \frac{C_{load}\Delta V}{I_{avg}}$ where ΔV is $0.5V_{DD}$.


$$I_{avg} = \frac{1}{2} [I(V_{in} = 1.8, V_{C_0} = 1.8) + I(V_{in} = 1.8, V_{C_0} = 0.9)]$$

Saturation since

$$V_{DS} \geq V_{GS} - V_{T,n}$$

Linear since

$$V_{DS} < V_{GS} - V_{T,n}$$

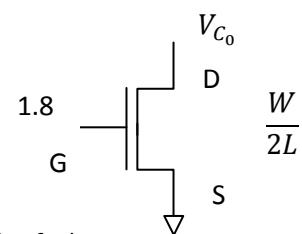

We can treat the two NMOS in series as one NMOS with an effective length of $2*L$.

$$I_{avg} = \frac{k_n}{4} \left[(V_{GS} - V_{T,n})^2 + 2(V_{GS} - V_{T,n})V_{DS} - V_{DS}^2 \right] = \frac{300\mu A}{4} \frac{0.45}{2 * 0.180} [1.2^2 + 2(1.2)(0.9) - 0.9^2] = 262 \mu A$$

$$\tau_{HL} = \frac{97 fF * 0.9 V}{262 \mu A} = 333 \text{ ps}$$

$$t_{pLH} = 333 \text{ ps} + 45 \text{ ps} = 378 \text{ ps}$$

You can also use the 2nd approximation using the saturation current, which gives $\tau_{HL} = 323 \text{ ps}$ and

$$t_{pLH} = 323 \text{ ps} + 45 \text{ ps} = 368 \text{ ps}.$$

Problem 1.3

The same can be done as in the previous problem, but for the output falling from high to low and the input low before clock goes high. Therefore, we will focus on the PMOS in the first inverter, and the second inverter has $t_{pHL} = 45 \text{ ps}$.


$$I_{avg} = \frac{1}{2} [I(V_{in} = 0, V_{C_0} = 0) + I(V_{in} = 0, V_{C_0} = 0.9)]$$

Saturation since

$$|V_{DS}| \geq |V_{GS}| - |V_{T,p}|$$

Linear since

$$|V_{DS}| < |V_{GS}| - |V_{T,p}|$$

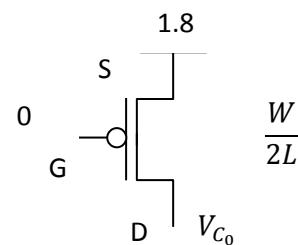

$$I_{avg} = \frac{k_p}{4} [(V_{GS} - V_{T,p})^2 + 2(V_{GS} - V_{T,p})V_{DS} - V_{DS}^2]$$

$$= \frac{100\mu A}{4} \frac{1.44}{2*0.180} [(-1.1)^2 + 2(-1.1)(-0.9) - (-0.9)^2] = 238 \mu A$$

$$\tau_{pLH1} = \frac{97 fF * 0.9 V}{238 \mu A} = 367 \text{ ps}$$

$$t_{pHL} = 367 \text{ ps} + 45 \text{ ps} = 412 \text{ ps}$$

Using the second average current approximation, $t_{pHL} = 360 \text{ ps} + 45 \text{ ps} = 405 \text{ ps}$


Problem 1.4

The Master stage latch in the flip-flop determines when a signal is “let in” or is the first of the two cascaded latches. In this case since the flip-flop is negative edge triggered, meaning that the output will hold the input value when the clock goes low, the master latch is active when the clock is high. The setup time is the time the input has to be stable before the active edge so that it can propagate to the input of the slave stage and be held. In this case, the longest possible propagation delay will determine the setup time. The longest propagation delay we see from the ideal clock pulse to the output changing to the 50% value is 412 ps. To be more conservative so that output reaches GND and since it’s an ideal clock, it would most likely take another 45 ps resulting in a setup time of 457 ps.

2.1

The Active low signal \overline{CLR} drives the gate of transistor P_7 . If \overline{CLR} is set to "0", transistor P_7 pulls the gates of $P_5 \& P_5$ up to V_{DD} . This sets Q low or clears Q and does not rely on the clock. Therefore it is Asynchronous.

2.2

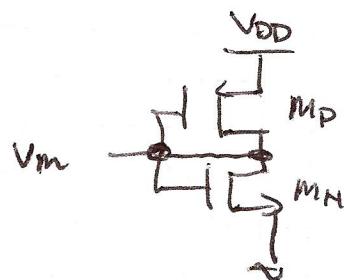

$$I_P = I_N \rightarrow \frac{K_N}{2} (V_m - V_{TN})^2 = \frac{K_D}{2} (V_{DD} - V_m - |V_{TP}|)^2$$

$$\frac{K_N}{K_D} (V_m - V_{TN})^2 = (V_{DD} - V_m - |V_{TP}|)^2$$

$$\sqrt{\frac{K_N}{K_D}} (V_m - V_{TN}) = (V_{DD} - V_m - |V_{TP}|) \Rightarrow \sqrt{\frac{K_N}{K_D}} V_m + V_m = V_{DD} + \sqrt{\frac{K_N}{K_D}} V_{TN} - |V_{TP}|$$

$$\text{Solve for } V_m = \frac{V_{DD} + \sqrt{\frac{K_N}{K_D}} V_{TN} - |V_{TP}|}{1 + \sqrt{\frac{K_N}{K_D}}}$$

The only difference between the C^2MOS stage and the inverter is the ratio of K_N/K_D .

For the inverter


$$\frac{K_N}{K_D} = \frac{300\mu A/V^2 \cdot 1.4/0.6}{100\mu A/V^2 \cdot 2.8/0.6} = \frac{800}{466} = 1.7$$

For the C^2MOS

$$\frac{K_N}{K_D} = \frac{300\mu A/V^2 \cdot 1.4/1.2}{100\mu A/V^2 \cdot 2.8/1.2} = \frac{400}{233} = 1.7$$

The Ratio of K_N/K_D is equal so the thresholds (V_m) are equal.

2.3

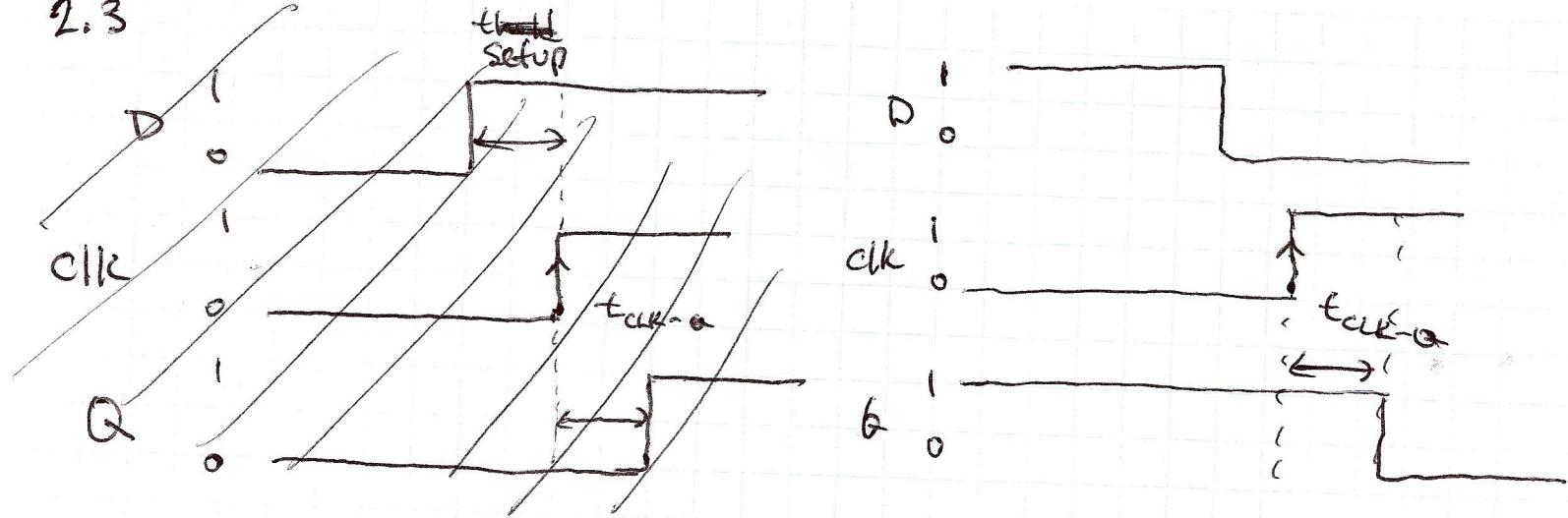

When the clock is low, the storage node formed by the gates of transistors $N_1 \& P_1$ is discharged when the signal D ~~rises~~ is low.

After the clock rises, the "0" stored on the gates of $N_1 \& P_1$ is passed to Q . When the clock signal is high the C²MOS stage drives the inverter formed by transistors $N_5 \& P_5$ to a logic "1".

This inverter then drives the output Q low.

From the we see that we need to compute the delay through the C²MOS stage & the inverter.

the total delay will be

$$t_{\text{tot}} = T_{PLH}^{C_{\text{mos}}} + T_{PHL}^{INV}$$

To find these we need to determine the load capacitance & the average current for both individually.

$$T_{PLH}^{C_{\text{mos}}} = \frac{C \Delta V}{I_{\text{AVG}}}$$

$$\Delta V = \cancel{\frac{V_{DD} - V_{SS}}{2}} \xrightarrow[10\% V_{DD}]{\quad} \cancel{10\% V_{DD}} \xrightarrow{5\% V_{DD}}$$

$$I_{\text{AVG}} = \frac{1}{2} (I_{\text{sat},P} + I_{\text{lin},P})$$

$$I_{\text{sat},P} = \frac{k_p}{2} (V_{DD} - |V_{TP}|)^2$$

$$k_p = \mu_p C_{ox} \cdot \frac{2 \cdot 8}{1.2} = 233 \text{ mA/V}^2$$

$$I_{\text{sat},P} = \frac{233 \cdot 3 \text{ mA}}{2} (1.8 - |-0.7|)^2 = 141 \text{ mA}$$

$$I_{\text{lin},P} = k_p \left[(V_{GS} - V_{TP}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Note: $2L$
is the effective length.

Linear when $V_{DS} < V_{GS} - V_{TP}$, $V_{GS} = V_{DD}$


$$\text{Assume mid point } V_{DS} = \cancel{\frac{V_{DD} - |V_{TP}|}{2}} = \frac{1.8 - |-0.7|}{2} = 0.65$$

$$I_{\text{lin},P} = 233 \text{ mA/V}^2 \left[(1.8 - |-0.7|) 0.65 - \frac{1}{2} 0.65^2 \right]$$

$$I_{\text{lin},P} = 233 \text{ mA/V}^2 \cdot 0.503 \text{ V}^2 = 117.5 \text{ mA}$$

$$I_{avg_P} = \frac{141\text{ nA} + 117.5\text{ nA}}{2} \approx 129.25\text{ nA}$$

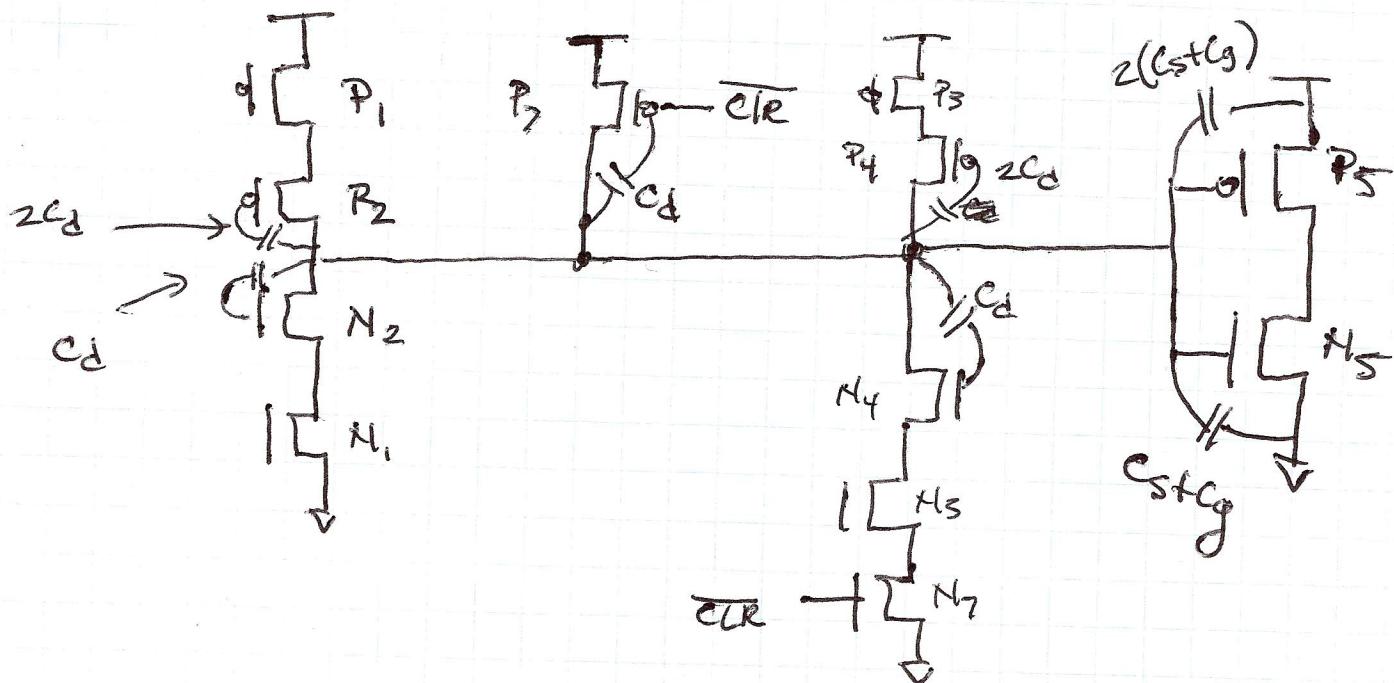Next we need to find the total capacitance connected to the output of the Z_{mos} stage.



All pMOS devices have capacitances which are 2x larger as they have twice the area.

$$C = 7C_d + 3C_s + 3C_g = 10C_s + 3C_g$$

$$C = 10 \cdot 10\text{ fF} + 3 \cdot 15\text{ fF} = 145\text{ fF}$$

$$T_{PLH, \text{Zmos}} = \frac{145\text{ fF} \cdot 0.9\text{ V}}{129.25\text{ nA}} = 1\text{ ns}$$

$$T_{PHL, INV} = \frac{C \Delta V}{I_{AVG}}$$

$$I_{AVG} = \frac{1}{2} (I_{SAT,N} + I_{INV,\mu})$$

$$I_{SAT,N} = \frac{k_N}{2} (V_{DS} - V_{TN})^2$$

$$k_N = m_N C_{ox} \frac{1.4}{0.6} = 700 \text{ mA/V}^2$$

$$I_{SAT,N} = \frac{k_N}{2} (1.3 - 0.6)^2 = 504 \text{ nA}$$

$$I_{INV,N} = k_N \left[(V_{GS} - V_{TN}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Assume mid point $V_{DS} = \frac{V_{DD} - V_{TM}}{2} = 0.6$

$$I_{INV,N} = 700 \text{ mA/V}^2 \left[(1.3 - 0.6) 0.6 - \frac{1}{2} 0.6^2 \right] = 378 \text{ nA}$$


$$I_{AVG,N} = \frac{504 \text{ nA} + 378 \text{ nA}}{2} = 441 \text{ nA}$$

$$2C_D + 2C_S + 2C_G$$

$$C = 6C_D + 3C_S + 3C_G$$

$$C = 9C_S + 3C_G$$

$$C = 135 \text{ fF}$$

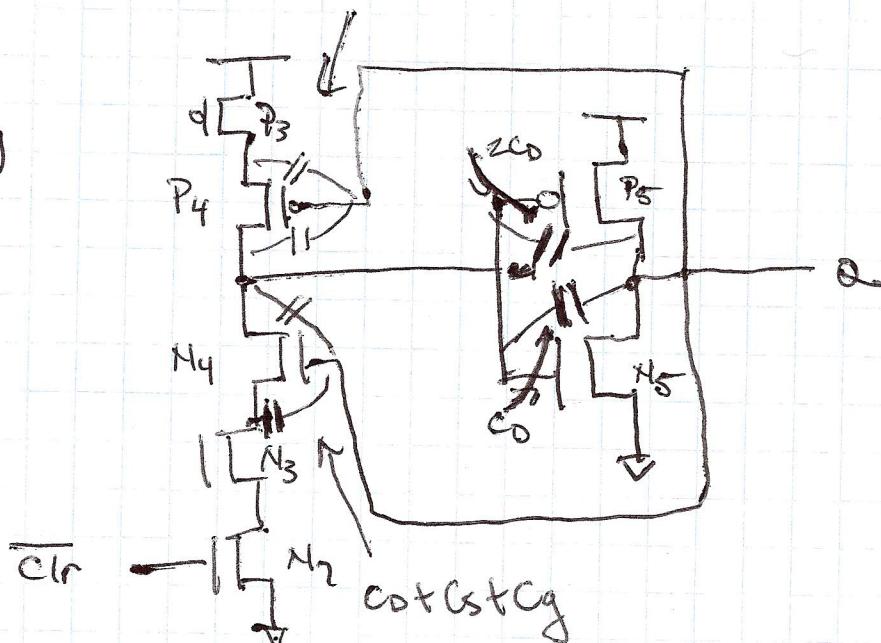

$$T_{PHL, INV} = \frac{135 \text{ fF} \cdot 0.4V}{441 \text{ nA}} = 0.276 \text{ ns}$$

$$T_{clk-Q} = 1.276 \text{ ns}$$