 


Computer Arithmetic

Multiplication & Shift

Chapter 3.4
EEC170 FQ 2005



Layout 8-bit Pipelined Multiplier

1

Multiply

- We will start with unsigned multiply and contrast how humans and computers multiply

2

How Humans Multiply

- We first generate all partial product terms

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
1010 ← Partial Product

```

3

How Humans Multiply

- We first generate all partial product terms

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
1010
0000 ← Partial Product

```

4

How Humans Multiply

- We first generate all partial product terms

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
1010
0000
1010 ← Partial Product

```

5

How Humans Multiply

- We first generate all partial product terms

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
1010
0000
1010
1010 ← Partial Product

```

6

How Humans Multiply

- ♦ Then add column by column, right to left

```

  1010
x 1101
=====
  1010
 0000
 1010
 1010
=====
  0 ← Product
  
```

7

How Humans Multiply

- ♦ Then add column by column, right to left

```

  1010
x 1101
=====
  1010
 0000
 1010
 1010
=====
 10 ← Product
  
```

8

How Humans Multiply

- ♦ Then add column by column, right to left

```

  1010
x 1101
=====
  1010
 0000
 1010
 1010
=====
 010 ← Product
  
```

9

How Humans Multiply

- ♦ Sometimes with one or more carry digits

```

  1010
x 1101
=====
  1 1010
  0000
 1010
 1010
=====
 0010 ← Product
  
```

10

How Humans Multiply

- ♦ Sometimes with one or more carry digits

```

  1010
x 1101
=====
 11 1010
  0000
 1010
 1010
=====
 00010 ← Product
  
```

11

How Humans Multiply

- ♦ Sometimes with one or more carry digits

```

  1010
x 1101
=====
 111 1010
  0000
 1010
 1010
=====
 000010 ← Product
  
```

12

How Humans Multiply

- ♦ Sometimes with one or more carry digits

```

    1010
  x 1101
  =====
1111
1010
0000
1010
1010
=====
0000010 ← Product

```

13

How Humans Multiply

- ♦ Sometimes with one or more carry digits

```

    1010
  x 1101
  =====
1111
1010
0000
1010
1010
=====
1000010 ← Product

```

14

How Humans Multiply

- ♦ Sometimes with one or more carry digits

```

    1010
  x 1101
  =====
1111
1010
0000
1010
1010
=====
1000010 ← Product

```

15

Human Method Not Best for Computers

- ♦ Each partial product must be stored ⇒ extra hardware
- ♦ Columns vary in size ⇒ complexity
- ♦ Multiple-digit carries ⇒ complexity
- ♦ Need a simpler method for low-cost multipliers

16

Shift & Add Multiply

- ♦ Simplest computer multiply is to shift Multiplicand left one bit per iteration to generate partial product
- ♦ Each iteration if corresponding Multiplier bit is 1:
 - Product = Product + Multiplicand
- ♦ NxN bit multiply takes N iterations (N clock cycles)

17

Shift & Add Multiply

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
00000000 ← Old Product
00001010 ← New Product

```

18

Shift & Add Multiply

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
00001010 ← Old Product
00001010 ← New Product

```

19

Shift & Add Multiply

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
00001010 ← Old Product
00110010 ← New Product

```

20

Shift & Add Multiply

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
00110010 ← Old Product
10000010 ← New Product

```

21

Shift & Add Multiply

- Computer multiply also shifts multiplier right so current multiplier bit is at a fixed position, the least significant bit (LSB)

22

Shift & Add Multiply

```

1010 ← Multiplicand
x 1101 ← Multiplier
=====
00000000 ← Old Product
00001010 ← New Product

```

23

Shift & Add Multiply

```

1010 ← Multiplicand
x 110 ← Multiplier
=====
00001010 ← Old Product
00001010 ← New Product

```

24

Shift & Add Multiply

```

1010 ← Multiplicand
x 11 ← Multiplier
=====
00001010 ← Old Product
00110010 ← New Product
    
```

25

Shift & Add Multiply

```

1010 ← Multiplicand
x 1 ← Multiplier
=====
00110010 ← Old Product
10000010 ← New Product
    
```

26

Software Multiple

- Very simple processors don't have hardware, implement shift & add in software

Multiply in C:

```

int product = 0;
for(int i = 0; i < 32; i++)
    if( ( multiplier >> i % 2 ) == 1)
        product = product + multiplicand << i;
    
```

27

MIPS Assembly Multiply


```

# multiplicand is in $a0, need not save
# multiplier is in $a1, need not save
#
move $v0, 0          # $v0 is the product
Loop: andi $t1, $a1, 1 # get multiplier bit
      beq $t1, $0, Next # test bit
      add $v0, $v0, $a0 # add partial product
Next: sll $a0, $a0, 1   # get next partial product
      slr $a1, $a1, 1   # position multiplier bit
      bne $a1, $0, Loop # got any bits left?
    
```

28


Simple Hardware Multiply

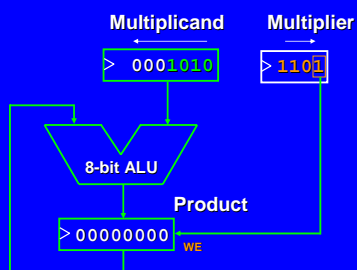- Like shift & add we have already seen
 - Multiplier LSB is write enable for Product latch




29

Simple Hardware Multiply

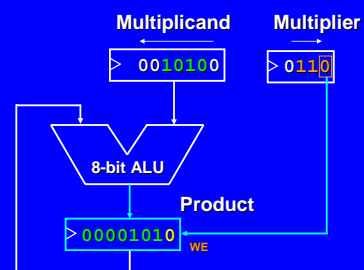


30

Simple Hardware Multiply

 


31

Simple Hardware Multiply

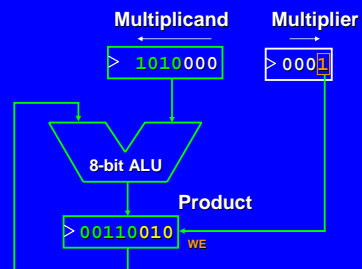

32

Simple Hardware Multiply

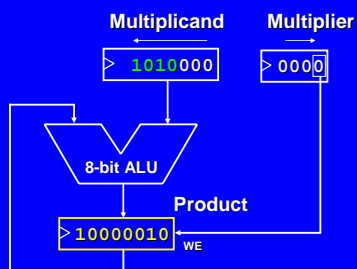

33

Refined Multiply Hardware


- Notice the following about the simple shift & add hardware:
 - Only N significant bits are being summed each cycle, but we are using a 2N-bit adder, a waste
 - Each cycle one new bit of the product is resolved, while one old bit of the multiplier is discarded
 - Simple multiply shifts Multiplicand left and keeps Product stationary. It is equivalent to keep Multiplicand stationary and shift Product right (same relative motion).

34

Refined Hardware Multiply

- ALU input is accept/not accept based on WE

Start of 1st Iteration

 


35

Refined Hardware Multiply

- When WE=0, shift but no ALU input


Start of 2nd Iteration

 

36

Refined Hardware Multiply


Start of 3rd Iteration

 

37

Refined Hardware Multiply


Start of 4th Iteration

 

38

Refined Hardware Multiply

Final Result: $10 \times 13 = 130$

 

39

Signed Multiplication

- Shift and Add only works for positive numbers
To include negative numbers must:

- Save XOR of sign bits to get product sign bit
- Convert multiplier/multiplicand to positive
- Do shift and add algorithm
- Negate result if product sign bit is 1

- Booth's Algorithm** handles positive /negative numbers uniformly

- Based on observation that

$$\begin{array}{r} \dots 011\dots 1110\dots = \\ \dots 100\dots 0000\dots = \\ + \dots 000\dots 0010\dots \end{array}$$

$$\text{E.g., } 01110_2 (14_{10}) = 10000_2 (16_{10}) - 00010_2 (2_{10}) \\ = 10000_2 - 00010_2$$

- I.e. convert string of 1s into leading +1 and a trailing -1

40

Booth's Algorithm

- Identify leading +1s and trailing -1s in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$\begin{bmatrix} i \\ i-1 \end{bmatrix}$

- 1 for 1 0
- +1 for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 00010 \Rightarrow 1$$

41

Booth's Algorithm

- Identify leading +1s and trailing -1s in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$\begin{bmatrix} i \\ i-1 \end{bmatrix}$

- 1 for 1 0
- +1 for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 00010 \Rightarrow 1$$

42

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$\begin{bmatrix} i & i-1 \end{bmatrix}$

- **-1** for 1 0
- **+1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 011$$

43

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$\begin{bmatrix} i & i-1 \end{bmatrix}$

- **-1** for 1 0
- **+1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

44

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$\begin{bmatrix} i & i-1 \end{bmatrix}$

- **-1** for 1 0
- **+1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

$$-1_{\text{ten}} = 1110 \Rightarrow 1$$

45

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$\begin{bmatrix} i & i-1 \end{bmatrix}$

- **-1** for 1 0
- **+1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

$$-1_{\text{ten}} = 1101 \Rightarrow 01$$

46

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$\begin{bmatrix} i & i-1 \end{bmatrix}$

- **-1** for 1 0
- **+1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

$$-1_{\text{ten}} = 1001 \Rightarrow 001$$

47

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$\begin{bmatrix} i & i-1 \end{bmatrix}$

- **-1** for 1 0
- **+1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

$$-1_{\text{ten}} = 1011 \Rightarrow 0001 = -1$$

48

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$i \quad i-1$

- 1** for 1 0
- +1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

$$-1_{\text{ten}} = 1111 \Rightarrow 0001 = -1$$

$$-6_{\text{ten}} = 101\boxed{0}\boxed{1} \Rightarrow 0$$

49

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$i \quad i-1$

- 1** for 1 0
- +1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

$$-1_{\text{ten}} = 1111 \Rightarrow 0001 = -1$$

$$-6_{\text{ten}} = 10\boxed{1}\boxed{0} \Rightarrow 10$$

50

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$i \quad i-1$

- 1** for 1 0
- +1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

$$-1_{\text{ten}} = 1111 \Rightarrow 0001 = -1$$

$$-6_{\text{ten}} = 1\boxed{0}\boxed{1}0 \Rightarrow 110$$

51

Booth's Algorithm

- Identify leading **+1s** and trailing **-1s** in Multiplier bit position i by looking at Multiplier bit i and bit $i-1$:

$i \quad i-1$

- 1** for 1 0
- +1** for 0 1
- 0 for 0 0
- 0 for 1 1

- Examples:

$$1_{\text{ten}} = 0001 \Rightarrow 0011 = 2-1 = 1$$

$$-1_{\text{ten}} = 1111 \Rightarrow 0001 = -1$$


$$-6_{\text{ten}} = \boxed{1}\boxed{0}10 \Rightarrow 1110 = -8+4-2 = -6$$

52

Booth Hardware Implementation

- Use ALU to **ADD** or **SUB** based on the trailing **-1s**, leading **1s** from the Multiplier

Start of 1st iteration

 


53

Booth Hardware Implementation

- Product shift is **arithmetic shift**, sign bit **does not change**


Start of 2nd iteration

 

54

Booth Hardware Implementation


Start of 3rd iteration

 

55

Booth Hardware Implementation


Start of 4th iteration

 

56

Booth Hardware Implementation

Final Result: $-6 \times -3 = 18$

 

57

Fast Multiply

- Shift & Add is slow: 32x slower than addition
- Fast processors have fast multiply hardware using more hardware than shift & add
- Basic example is a Wallace tree adder, which uses an array of full adder cells

58

Wallace Tree Stage 0


- Partial products produced sequentially (slow)

```

1010  Multiplicand
x 1101  Multiplier
=====
 1010
 0000
1010
1010
    
```

Partial Products

 - Partial products produced using array of AND gates (fast)



Partial Products

59

Wallace Tree Reducers

- Full adder cells used to reduce column segment of height 3 to row of width 2
 - sum and carry out
- Half adders used selectively for height-3 column that does not need full reduction

Full Adder




Half Adder



60

Wallace Tree Strategy

 
- ♦ In stages reduce column height from $\leq N$ to height 2, then use fast adder



61

Wallace Tree Multiplier: 4x4 Example


Stage 1

 

62

Wallace Tree Multiplier: 4x4 Example


Stage 1

 

63

Wallace Tree Multiplier: 4x4 Example


Stage 1

 

64

Wallace Tree Multiplier: 4x4 Example


Stage 1

 

65

Wallace Tree Multiplier: 4x4 Example


Stage 1

 

66

Wallace Tree Multiplier: 4x4 Example


Stage 1

 

67

Wallace Tree Multiplier: 4x4 Example

Stage 1

 


Stage 2

68

Wallace Tree Multiplier: 4x4 Example

Stage 1

 


Stage 2

69

Wallace Tree Multiplier: 4x4 Example

Stage 1

 


Stage 2

70

Wallace Tree Multiplier: 4x4 Example

Stage 1

 


Stage 2

71

Wallace Tree Multiplier: 4x4 Example


Stage 1

 

Stage 2


72

Wallace Tree Multiplier: 4x4 Example

 


73

Wallace Tree Multiplier: 4x4 Example

 

74

Wallace Tree Multiplier: 8x8 Example

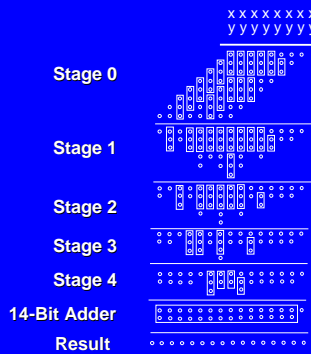

75

Wallace Tree Mult (cont.)

- Column height is reduced by about 2/3 during each level
- For NxN multiply, an estimate for number of levels:

$$N \times (2/3)^x = 2$$

$$(2/3)^x = 2/N$$

$$x \log_2(2/3) = \log_2(2/N)$$

$$x = \log_2(2/N) / \log_2(2/3)$$

$$x = [\log(2) - \log(N)] / -0.6$$

$$x = -1.7 \times [1 - \log_2(N)]$$


$$x = 1.7 \cdot \log_2(N) - 1.7$$

2 Levels for N=4, 4 Levels for N = 8, 7 levels for N = 32

76


Barrel Shifter

 - Want shifter that is fast, not shift one bit position at a time
- Can be done in $N-1=31$ shifts in $\log_2 N=5$ stages using an array of $N \log_2 N=160$ multiplexers



77

Barrel Shifter

 

78

