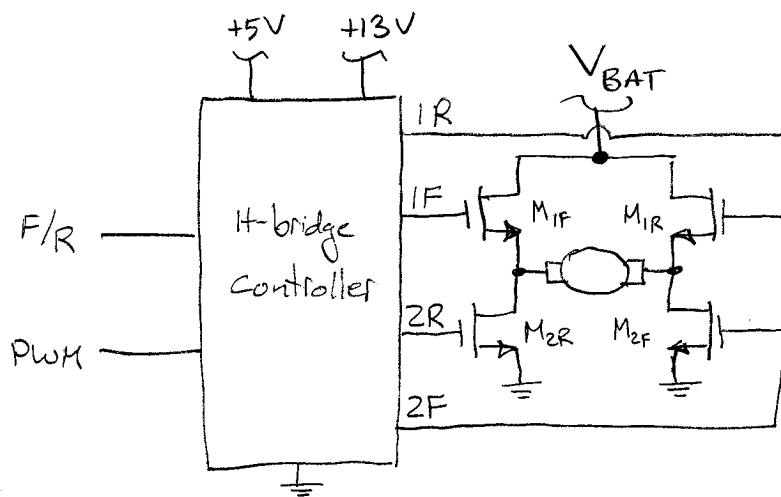


R. Spencer

The circuit uses two inputs;


- 1) PWM — the same PWM signal that you use for a single NMOS drive
- 2) F/R — (forward/reverse) a CMOS compatible logic signal, 1 $\Rightarrow$ forward, 0 $\Rightarrow$ reverse

The circuit has four outputs to connect to the bridge;



The schematic is on page 2. V_{OFF} should be set to about 1V, which causes the hysteretical comparators' thresholds to be about 0.52V & 1.12V. When the gates of all MOSFETs are $< 0.52V$, 'OFF' will be high, signifying that the bridge is off and it is safe to change directions if desired. The flip-flops are clocked at 1kHz and keep track of the present and previous states of F/R.

$U_8 = CD4009$

 

The two flip flops driven by F/R are used to

- 1) deglitch the F/R signal
- 2) ensure that $F \neq R$ are turned off and the PWM output is disabled until the H-bridge is off.

The four comparators with hysteresis are used to check whether the H bridge is off or not. If you switch from F to R (or vice versa) without ensuring the bridge is off, you may turn on M_{1F} and M_{2R} or M_{1R} and M_{2F} simultaneously, which destroys the bridge.

The open-drain buffers (U7) drive the bridge transistors. The top transistors are either off or on and the bottom ones are pulse-width modulated. You can't set the PWM frequency too high or the gates won't be able to switch fast enough. About 5-6 kHz is good.

The +13 V supply was chosen as a compromise between being sure $M_{1F} \neq M_{1R}$ can be fully on when V_{BAT} is high ($\sim 8V$) and not breaking down the gate oxides when the car is going slow and the back emf in the motor is low ($V_{a\max} = 10V$).