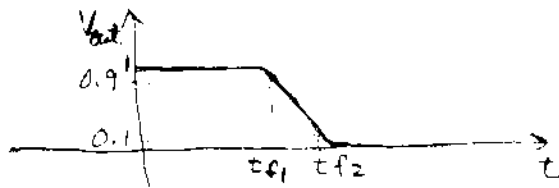


Quiz solution

fall time

KCL at output

$$C_L \frac{dV_{out}}{dt} + \frac{\beta_n}{2} (V_{GS} - V_{tn})^2 = 0, \quad \text{nMOS saturated} \\ V_{GS} = V_{DD}$$

$$t_{f1} = 2 \frac{C_L}{\beta_n (V_{DD} - V_{tn})^2} \int_{V_{DD} - V_{tn}}^{0.9V_{DD}} dV_{out} = \frac{2 C_L}{\beta_n (V_{DD} - V_{tn})^2} V_{out} \Big|_{V_{DD} - V_{tn}}^{0.9V_{DD}} = \\ \frac{2 C_L}{\beta_n (V_{DD} - V_{tn})^2} (0.9V_{DD} - (V_{DD} - V_{tn})) = \frac{2 C_L}{\beta_n (V_{DD} - V_{tn})^2} (V_{tn} - 0.1V_{DD})$$

KCL at outputnMOS linear

$$C_L \frac{dV_{out}}{dt} + \beta_n \left[(V_{GS} - V_{tn}) V_{DS} - \frac{V_{DS}^2}{2} \right] = 0, \quad V_{DD} = V_{GS}, \quad V_{DS} = V_{out}$$

$$t_{f2} = \frac{C_L}{\beta_n (V_{DD} - V_{tn})} \int_{0.1V_{DD}}^{V_{DD} - V_{tn}} \left[\frac{V_{out}^2}{2(V_{DD} - V_{tn})} - V_{out} \right]^{-1} dV_{out}$$

in order to solve this integral, need to use partial fraction expansion and let $2(V_{DD} - V_{tn}) = x$

$$\left[\frac{V_{out}^2}{x} - V_{out} \right]^{-1} = \frac{x}{V_{out}(V_{out} - x)}$$

$$\frac{x}{V_{out}(V_{out} - x)} = \frac{A}{V_{out} - x} + \frac{B}{V_{out}} \rightarrow \text{solve } \begin{matrix} A = 1 \\ B = -1 \end{matrix}$$

$$\int \frac{dV_{out}}{V_{out} - x} - \int \frac{dV_{out}}{V_{out}} = \ln(V_{out} - x) - \ln(V_{out})$$

$$\ln(V_{out} - x) - \ln(V_{out}) \Big|_{0.1V_{DD}}^{V_{DD} - V_{tn}} =$$

$$\ln(V_{DD} - V_{tn} - 2(V_{DD} - V_{tn})) - \ln(V_{DD} - V_{tn}) - [\ln(0.1V_{DD} - 2V_{DD} - V_{tn}) - \ln(0.1V_{DD})] =$$

$$\ln\left(\frac{19V_{DD} - 20V_{tn}}{V_{DD}}\right) \cdot \frac{C_L}{\beta_n (V_{DD} - V_{tn})}; \quad \text{constant term}$$

$$\text{Let } n = \frac{V_{tn}}{V_{DD}}$$

$$t_f = t_{f2} - t_{f1} = \frac{2 C_L}{\beta_n V_{DD} (1-n)} \left[\frac{(n-0.1)}{(1-n)} + \frac{1}{2} \ln(19-20n) \right]$$