
 


# Homework # 1 Solution

EECI18  
SPRING '03

Problem 1.1 4-input NAND gate,  $F = \overline{A \cdot B \cdot C \cdot D}$


 


Problem 1.2:  $F = \overline{AB + BC + AC}$

It's best to use Karnaugh map.

	B			
	1	1	0	1
A	1	0	0	0
	C			


- Logic for NMOS =  $AB + BC + AC$
- Logic for PMOS =  $\overline{AB} + \overline{BC} + \overline{AC}$

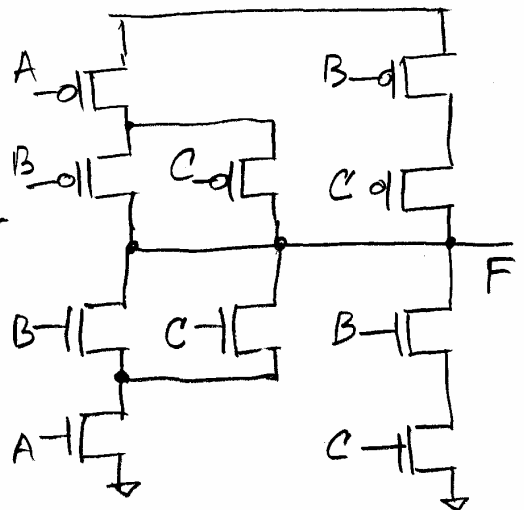 


Problem 1.3: 3-input OR gate.

$$F = A + B + C = \overline{\overline{A + B + C}} = \overline{\bar{A} \cdot \bar{B} \cdot \bar{C}}$$

Two possible implementations.

 



Straight-forward; bad high-PMOS stack

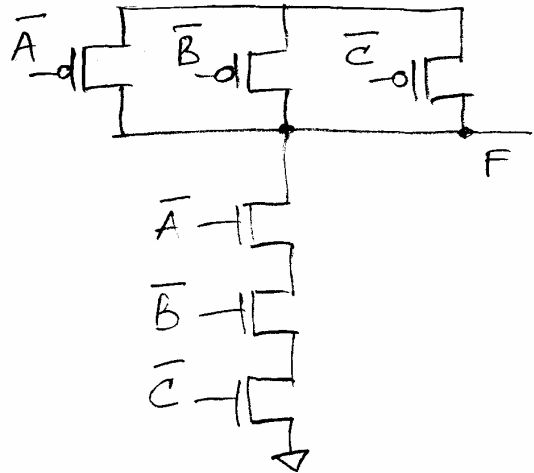

Simple circuit; need inverting input

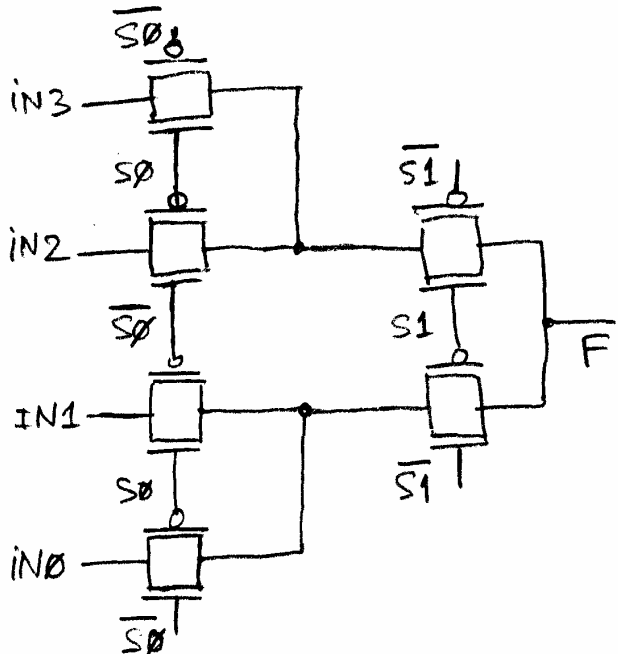 Problem 1.4: 4-input multiplexer

You can use one 4:1 MUX or three 2:1 MUX's.






Preferred, using less transistors

# Problem 1.5



In layout, lines of same material cannot cross. You will face that often in your layout. The common solution is to switch to a different material over the crossing to eliminate it.

 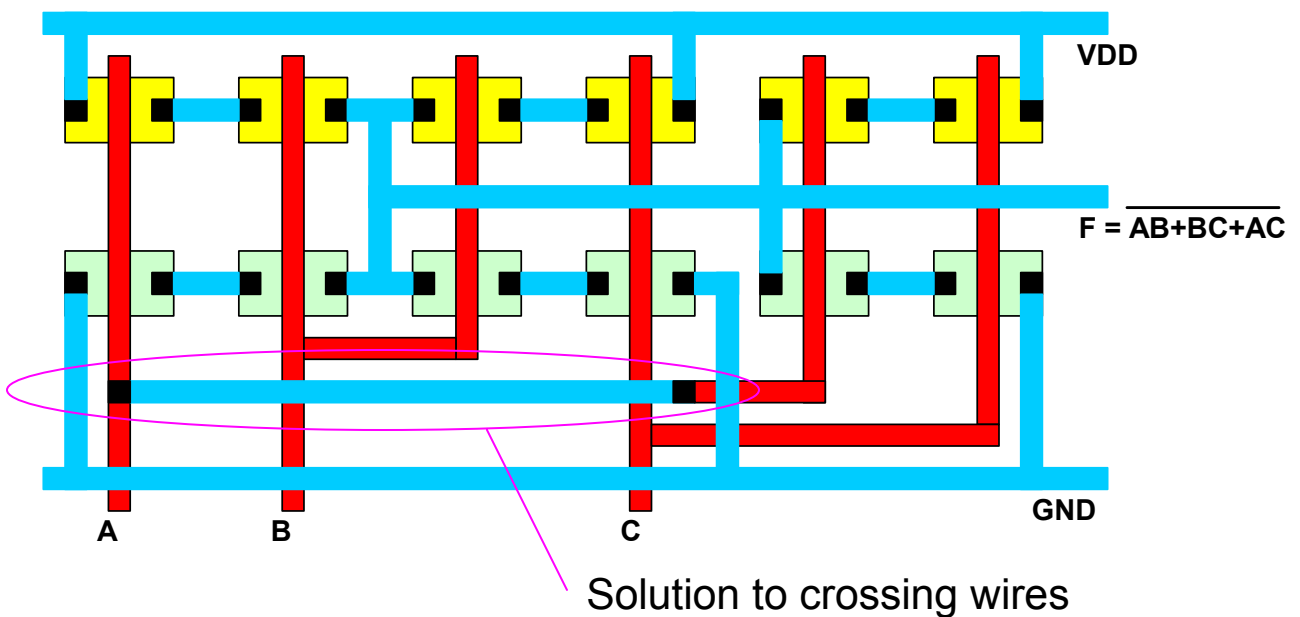 

Problem 1.6. S-R latch

