

Homework Solution # 2

Problem 2.1: Given  $K_p = \mu \frac{e}{t_{ox}} = \mu \cdot \frac{e}{1.0 \times 10^{-7}} = 10 \mu A/V^2$

$$\text{For new } t_{ox} = 800 \text{ Å, } K_p = \mu \cdot \frac{e}{8.0 \times 10^{-8}} = (\mu \cdot \frac{e}{1.0 \times 10^{-7}}) \cdot \left( \frac{1.0 \times 10^{-7}}{8.0 \times 10^{-8}} \right)$$

$$= 1.25 \times 10 \mu A/V^2 = 12.5 \mu A/V^2$$

Therefore, the drain current of n- and p-transistors is increased by 25%.

Problem 2.2: The effective width and length of the transistor

$$W = 20 + (0.5 + 0.5) = 21 \mu m$$

$$L = 5 - (1 + 1) - (0.5 + 0.5) = 2 \mu m$$

$$\text{Then, } \beta = K_p \cdot \left( \frac{W}{L} \right) = (15 \mu A/V^2) \times \left( \frac{21 \mu m}{2 \mu m} \right) = 0.16 mA/V^2$$

$\beta$  is increased by  $(\frac{21}{2}) / (\frac{20}{5}) \approx 2.6$  times

Problem 2.3:  $I_{d,sat} = \frac{1}{2} \beta (V_{gs} - V_t)^2 (1 + \lambda V_{ds})$

$$g_m(\text{sat}) = \left. \frac{\partial I_d}{\partial V_{gs}} \right|_{V_{ds}=\text{const.}} = \beta (V_{gs} - V_t) (1 + \lambda \cdot V_{ds})$$

Assume  $V_{gd} = 0$  or  $V_{gs} = V_{ds}$ ,


$$g_m(\text{sat}) = (40 \mu A/V^2)(5V - 1V)(1 + 0.03 \times 5)$$

$$= 184 \mu A/V$$

 Problem 2.4: Input switching voltages refer to  $V_{IL}$  and  $V_{IH}$

For inverters, these voltages can be found using equations (2.23) and (2.27) in textbook and  $\frac{dV_{out}}{dV_{in}} = -1$ . (Figure 2.17,) If no solution exists for a switching voltage, it can be found from equation (2.24).

For 2-input NOR gate, there are 2 possible switching scenarios.



Assume PMOS and NMOS are identically sized such that  $\beta_p = \beta_n$ . That is,  $K_p (\frac{W_p}{L_p}) = K_n (\frac{W_n}{L_n})$ .

(a)  $V_{IH}$ :

Using equation (2.27) and solving for  $\frac{dV_{out}}{dV_{in}} \Big|_{V_{in}=V_{IH}} = -1$ , you'll get

$$4 [(V_{IH} - V_{tn})^2 - \frac{1}{k} \cdot (V_{IH} - V_{DD} - V_{tp})^2] = \left[ (V_{IH} - V_{tn}) - \frac{1}{k} (V_{IH} - V_{DD} - V_{tp}) \right]^2$$

(b)  $V_{IL}$ :

Using equation (2.23) and solving for  $\frac{dV_{out}}{dV_{in}} \Big|_{V_{in}=V_{IL}} = -1$ , you'll get

$$4 [(V_{IL} - V_{tp})^2 - 2(V_{IL} - \frac{V_{DD}}{2} - V_{tp})V_{DD} - k(V_{IL} - V_{tn})^2] = \left[ (V_{IL} - V_{tp}) - V_{DD} - k(V_{IL} - V_{tn}) \right]^2$$

To illustrate the effect of switching scenarios on  $V_{IH}$  and  $V_{IL}$ , I'll assume  $V_{DD} = 5V$ ,  $V_{tn} = -V_{tp} = 1V$ .

- Case A:  $V_{IL} = 1.8V$ ;  $V_{IH} = 3.0V \Rightarrow NM_L = 1.8V$ ;  $NM_H = 2V$
- Case B:  $V_{IL} = 1.5V$ ;  $V_{IH} = 2.7V \Rightarrow NM_L = 1.5V$ ;  $NM_H = 2.3V$
- Worst case noise margins:  $NM_L = \min(1.8V, 1.5V) = 1.5V$   
 $NM_H = \min(2V, 2.3V) = 2V$

Noise margins are reduced in multi-input gates.