

**EEC 118 EXPERIMENT No. 2**  
**NMOS and PMOS TRANSISTOR PARAMETERS \***

**I. OBJECTIVE**

The objective of this experiment is to determine the electrical parameters of NMOS and PMOS transistors made with a standard metal-gate CMOS process. These parameters will be used for hand calculations of circuit characteristics in later experiments.

**II. PRELAB**

Before coming to the laboratory, study chapter 2 in textbook to learn the definitions of threshold voltage  $V_T$ , device transconductance parameter  $\kappa$ , body coefficient  $\gamma$ , and output conductance parameter  $\lambda$ . Also read “Input protection of MOS Gates” at the end of this lab.

Assumed Data:

$$\text{Gate Oxide Capacitance } C_{ox} = 35 \text{ nF/cm}^2$$

$$2|\phi_F| = 0.6\text{V}$$

$$\text{electron mobility } \mu_n = 580 \text{ cm}^2 / \text{V-s}$$

$$\text{hole mobility } \mu_p = 232 \text{ cm}^2 / \text{V-s}$$

source-drain pn junctions are abru\* pt junctions


**III. TRANSISTOR PARAMETERS-MEASUREMENT AND CALCULATION**

(1) Use the connections shown in Figure 1 to measure drain current  $I_D$  as a function of  $V_{DS} = V_{GS}$  for  $V_{DS} = 3, 3.5, 4, 4.5, 5, 5.5, 6,$  and  $6.5$  Volts for

---


\* Excerpt from Paul Hurst et al's EEC118 Lab Manual, Spring 2001 – printed with Prof Hurst's permission

NMOS devices. Make these measurements at  $V_{SB} = 0, 2, \text{ and } 5$  Volts, making sure that the body is *negative* with respect to the source.

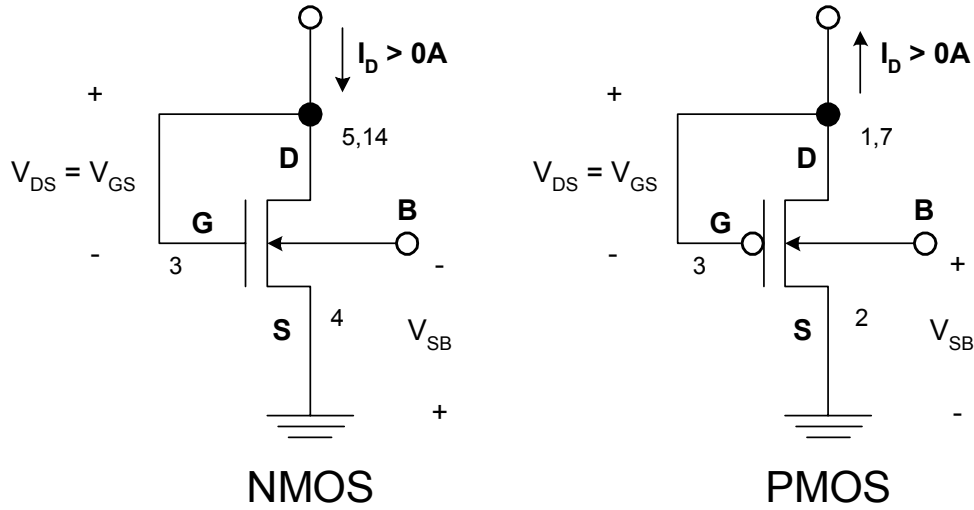


**Figure 1.**

- (2) Repeat Step (1) for a PMOS device. Note that all polarities are reversed! The body is positive with respect to the source. Therefore,  $V_{DS}$  should be negative for all measurements.
- (3) Plot  $\sqrt{I_D}$  vs.  $V_{GS} = V_{DS}$  for both devices at three values of body bias. Figure 2 shows sample plots. Draw the best-fit straight line through your data points. From intercepts, determine  $V_T$  for  $|V_{BS}| = 0, 2$  and  $5$  V for each device. From  $V_{BS} = 0$  V plot, determine the transconductance parameter  $\kappa = \kappa' W/L$ . Estimate  $W/L$  for both transistors.

 


**Figure 2.**

- (4) With  $V_{BS} = 0V$  and  $V_{GS} = 2.5V$ , measure drain current  $I_D$  at  $V_{DS} = 2, 2.5, 3, 3.5, 4, 4.5, 5, 5.5,$  and  $6$  Volts using the connections shown in Figure 3 for both NMOS and PMOS devices.

 


**Figure 3.**

- (5) Using the data from parts (1) and (2), plot  $V_T$  vs.  $\sqrt{|2\phi_F| + |V_{BS}|} - \sqrt{|2\phi_F|}$ . Assuming  $|2\phi_F| = 0.6V$  for both transistors, estimate  $\gamma_P$  and  $\gamma_N$ .
- (6) Using your data from part (4), plot  $I_D$  vs.  $V_{DS}$  with  $V_{BS} = 0V$  for both devices and determine the channel length modulation factor,  $\lambda$ , from the slopes as shown in Figure 4.

 

**Figure 4.**

- (7) Use the curve tracer to plot  $I_D$  vs.  $V_{DS}$  for the NMOS transistor with  $V_{BS} = 0$ . Sketch the curves in your lab notebook for the region  $0 \leq V_{GS} \leq 2.5V$  and  $0 \leq V_{DS} \leq 5V$ .
- (8) Use the curve tracer to plot  $I_D$  vs.  $V_{GS}$  for the “diode-connected” NMOS transistor as shown in Figure 5. Sketch the curve in your notebook for  $0 < V_{GS} < 10V$  with  $V_{BS} = 0V$ .

 

**Figure 5.**