

Quiz #1 Solution

Given are components of the flashlight. The front bulb is a 4.5V bulb and the rear one is 1.5V. Connect the flashlight so that when the switch is in the F position the front bulb lights, and when it is in the R position the rear one does it.

